The Lowdown on Tape Playback Equalization

NOVEMBER 1958

Radio-Electronics

TELEVISION • SERVICING • HIGH FIDELITY

HUGO GERNSBACK, Editor

Power Transistor Tester

Installing Community and Commercial Antennas

Simple Low-Frequency Oscillator

Relay Adjustments

Servicing Pleasure-Boat Radio Installations

(See page 44)

35c
U.S. and Canada

For superb hi-fi listening... **Jensen** presents . . . in modest space . . . at new low costs . . . performance challenging comparison with speakers of any size at any price!

Featuring the new Flexair* woofer and Bass-Superflex* enclosure principle that establish completely new standards of bass reproduction.

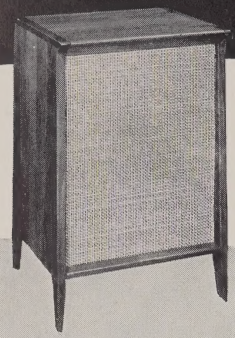

NEW JENSEN CN-100 3-WAY SYSTEM

WITH NEW "FLEXAIR" WOOFER

A new 12" 3-way system, the CN-100 reproducer gives a new small-scaled fine furniture look to the hi-fi speaker, ideally suited to small living spaces. The 12" Flexair superlow resonance woofer in Bass-Superflex enclosure gives full bass response to a low 20 cycles. Special 8-inch mid-channel and RP-103 h-f unit assure smooth clean response to 15,000 cycles. Crossover frequencies 600 and 4000 cycles. 32" H., 21" W., 18¼" D. Available in Walnut, Tawny Ash, and Mahogany. **Net Price.....149.50**

BF-100 ENCLOSURE FOR 12" SYSTEMS

In up-to-the-minute "Flair Line" styling, the BF-100 cabinet is ideal for all 12" speakers, and system kits including those with Flexair 12" woofers. Incorporates new acoustical design with tube-loaded port for unusual extension of the l-f range. Available in Walnut, Tawny Ash and Mahogany. **Net Price.....69.50**

JENSEN'S AMAZING TR-10 TRI-ETTE • Big Speaker Bass in Smallest Space Sophisticate's Choice In 3-Way Components

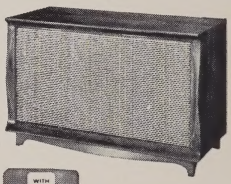

WITH NEW FLEXAIR WOOFER

Heart of the Tri-ette is the new Flexair 12" woofer with its superlow free-air resonance of 20 cycles and high damping. In conjunction with the new Bass-Superflex enclosure, useful response down to 25 cycles is attained with the lowest distortion ever measured on such a small reproducer. Cabinet is extra rigid with Fiberglass lining. Special 8-inch midchannel handles the range from 600 to 4,000 cycles, through L-C crossover network. RP-103 Tweeter carries the response from 4,000 to 15,000 cycles. 13⅞" H., 25" W., 11⅜" D. Choice of Walnut, Tawny Ash and Mahogany. **Net Price....114.50**

ST-944 Stand . For floor use. Places top of cabinet 28" above floor. **Net Price.....12.95**

ST-945 Base . For table or shelf. **Net Price..... 5.45**

ABOUT JENSEN'S NEW FLEXAIR WOOFER

The new Jensen Flexair Woofers are designed to extend bass response down to very low frequencies. They have highly-damped superlow resonance at the very bottom of the audio range—16 to 20 cycles. They have an exceptional degree of linearity and are capable of a total movement of 1". In even a relatively small Bass-Superflex enclosure, they deliver their extreme low-frequency performance with a new low in distortion.

WITH NEW "FLEXAIR" WOOFER

WITH NEW "FLEXAIR" WOOFER

KT-33 3-WAY SYSTEM KIT

Includes basic speaker components for 3-way system identical in performance with Jensen CN-100 and TR-10 reproducers. Includes Flexair 12-inch woofer, special 8 inch m-f unit, and RP-103 compression h-f unit. Complete with control, crossover network, wiring cable, and full instructions for building enclosure and installing speaker system. **Net Price $80.00**

WITH NEW "FLEXAIR" WOOFER

KT-34 TRI-PLEX II SPEAKER KIT

Components used in the TP-250 Tri-Plex II reproducer. 15-inch Flexair woofer, new compression driver m-f unit, and new phase correcting supertweeter. Response from 16 cycles to upper limits of audibility in Jensen Bass-Superflex enclosure (Jensen BF-200 suggested). Complete with 400 and 4,000 cycle networks, wiring cables and instructions for building enclosure. Impedance 16 ohms. **Net Price $179.50**

WITH NEW "FLEXAIR" WOOFER

NEW TP-250 TRI-PLEX II 3-WAY SYSTEM

This latest version of the Jensen Tri-Plex reproducer incorporates the extreme bass capability of the 15" Flexair woofer, in combination with advances in midchannel and supertweeter design. This beautiful unit outperforms any speaker system of comparable size or cost. Excellent for superb monophonic reproduction or as one side of a stereo system. Response range, 16 cycles to beyond audibility. Components available also in kit form (see KT-34). 30½" H., 34½" W., 18¾" D. **Net Price.....294.50**

BF-200 Cabinet only for 15" Systems, net price 129.75

Send for Bulletin JH-1

*Trademark

Jensen

Division of The Muter Company

MANUFACTURING COMPANY

6601 S. Laramie Ave., Chicago 38, Illinois

In Canada: J. R. Longstaffe Co., Ltd., Toronto

In Mexico: Radios Y Televisión, S.A., Mexico D.F.

Here's a NEW Way to Reach the Top in TV SERVICING

ALL PRACTICE METHOD— PROFESSIONAL TECHNIQUES

Includes 17" picture tube, all other tubes, components for TV receiver. Also 5 inch professional type Scope and highly accurate Signal Generator. Training low in cost; monthly terms.

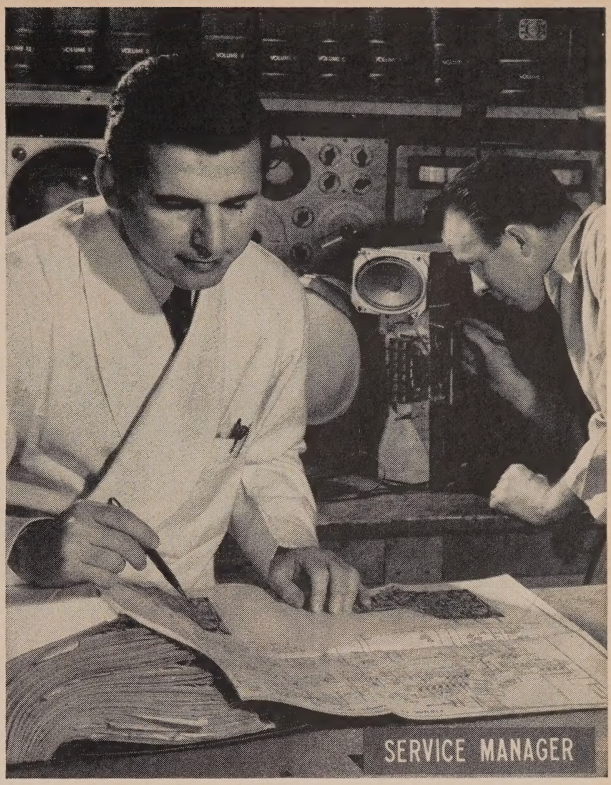

IF YOU HAVE some Television or Radio experience, or if you know basic Television-Radio principles but lack experience—NRI's Professional Television Servicing course can equip you to go places in TV servicing. This advertisement is your personal invitation to get a free copy of our booklet which describes this training in detail.

You Get Color-TV Textbooks Early

The day you enroll, N.R.I. sends you special Color-TV books to speed your knowledge and understanding of this vast, growing phase of Television. Many full color pictures and diagrams help you recognize defects and help you learn how to correct them quickly and properly. To cash in on the coming Color-TV boom you'll need the kind of knowledge and experience this N.R.I. training gives.

You Learn-By-Doing "All The Way"

This is 100% learn-by-doing, practical training. We supply all the components, all tubes, including a 17" picture tube, and comprehensive manuals covering a thoroughly planned program of practice. You learn how experts diagnose TV receiver defects quickly. You see how various defects affect the performance of a TV receiver—picture, sound and color; learn to know the causes of defects, accurately, easily, and how to fix them.

You do more than just build circuits. You get practice recognizing, isolating and fixing innumerable TV receiver troubles. You get actual experience aligning TV receivers, eliminating interference, using germanium crystals to rectify the TV picture signal, obtaining maximum brightness and definition by properly adjusting the ion trap and centering magnets, etc. There isn't room to list all the servicing experience you get.

Graduate C. Dority of Silver Spring, Md., says:
"Your course is so thorough that anyone interested in the challenge of servicing shouldn't miss this opportunity. I can find my way around a TV Chassis as easy as I can my own home as a result of your course."

James D. McIngvale of Lake Cormorant, Miss., says:
"I have serviced about 95% of common Television complaints. A year ago I would not have known where to start. I can now fix a TV receiver defect in minutes when it used to take hours."

Get Details Free—Mail Coupon

Once again—if you want to go places in TV servicing, we invite you to find out what you get, what you practice, what you learn from NRI's course in Professional Television Servicing. See pictures of equipment supplied, read what you practice. Judge for yourself whether this training will further your ambition to reach the top in TV servicing. We believe it will. We believe many of tomorrow's top TV servicemen . . . for black and white, UHF and Color-TV . . . will be graduates of this N.R.I. training. Mail the coupon now. There is no obligation. National Radio Institute, Dept. 8MFT, Washington 16, D.C.

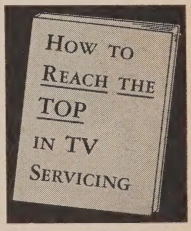

Oldest and Largest Home Study Radio-Television School

National Radio Institute, Dept. 8MFT
Washington 16, D.C.

Please send my FREE copy of "How to Reach the Top in TV Servicing." I understand no salesman will call.

Name_____ **Age**_____

Address_____

City_____ **Zone**_____ **State**_____

Accredited Member National Home Study Council

NOVEMBER, 1958

Radio-Electronics

Formerly RADIO-CRAFT ■ Incorporating SHORT WAVE CRAFT ■ TELEVISION NEWS ■ RADIO & TELEVISION

EDITORIAL

31 Opportunities in Electronics—Hugo Gernsback

ELECTRONICS

32 Satellite Measures Cloud Cover—Edward Rich, Jr.
35 The Backward Diode—Ed Bukstein
36 Get the Most Out of Your Relays—James A. McRoberts
39 Three-Way Timer—E. H. Leftwich
42 WESCON Visit—Tom Jaski

RADIO

44 Radio for Weekend Sailors, Part I—Leo G. Sands
48 Two Multiband Transistor Sets—Robert F. Scott
52 The QRM Dodger—Don M. Wherry, W6EUM

TEST INSTRUMENTS

54 Down Low With an Audio Oscillator—Tom Jaski
56 Dc-Ac Attenuator Has Many Uses—I. Queen
59 This Tester Checks Power Transistors—W. F. Jordan and H. C. Lin
61 A Low-Cost Frequency Standard—Paul S. Lederer

AUDIO—HIGH FIDELITY

78 Lowdown on Tape Playback Equalization—Herman Burstein and Henry C. Pollak
83 Stereo Phono Cartridges, Part III—Julian D. Hirsch
90 New Discs and Tapes, Stereo and Mono—Reviewed by Chester Santon
92 Ready for Stereo?, Part II—Donald C. Hoefler
96 Low-Cost Transistor Hearing Aid—Forrest H. Frantz, Sr.

TELEVISION

98 The TV Man Rides the Gravy Train—E. H. Leftwich
102 Try, Try Again—G. P. Oberto
103 Dipoles and Yagis—Engineering Staff, Scala Radio Co.
108 FM–TV Dx—Robert B. Cooper, Jr.
110 TV Service Clinic—Conducted by Robert G. Middleton

142 Books
137 Business and People
16 Correspondence
140 Literature
118 New Tubes and Semiconductors
6 News Briefs
132 Noteworthy Circuits
125 On the Market
135 Patents
115 Technicians' News
122 Technotes
130 Try This One
136 50 Years Ago

ON THE COVER

(See story on page 44)

Shooting trouble in a typical small-craft radio transmitter is James Lafferty of Charles Rogers & Sons, Manasquan, N.J., a leading marine radio service shop in what some call the small-boat capital of the country.

Color original by Hans Knopf

Hugo Gernsback ..... Editor and Publisher
M. Harvey Gernsback ..... Editorial Director
Fred Shunaman ..... Managing Editor
Robert F. Scott ..... W2PWG, Technical Editor
Larry Steckler ..... Associate Editor
David Lachenbruch ..... Associate Editor
I. Queen ..... Editorial Associate
Robert G. Middleton ..... Television Consultant
Elizabeth Stalcup ..... Production Manager
Cathy Coccozza ..... Advertising Production
Wm. Lyon McLaughlin ..... Tech. Illustration Director
Sol Ehrlich ..... Art Director
Fred Neinast ..... Staff Artist
Lee Robinson ..... General Manager
John J. Lamson ..... Sales Manager
G. Aliquo ..... Circulation Manager
Adam J. Smith ..... Director, Newsstand Sales
Robert Fallath ..... Promotion Manager

Average Paid Circulation
Over 199,000

RADIO-ELECTRONICS is indexed in *Applied Science & Technology Index* (Formerly *Industrial Arts Index*)

RADIO-ELECTRONICS, November, 1958, Vol XXIX, No. 11. Published monthly at Mt. Morris, Ill., by Gernsback Publications, Inc. Second-Class mail privileges authorized at Mt. Morris, Ill. Copyright 1958 by Gernsback Publications, Inc. All rights reserved under Universal, International and Pan-American Copyright Conventions.
SUBSCRIPTION RATES: U.S., U.S. possessions and Canada, $4.00 for one year; $7.00 for two years; $10.00 for three years; single copies 35c, Pan-American countries $4.50 for one year; $8.00 for two years; $11.50 for three years. All other countries $5.00 a year; $9.00 for two years; $13.00 for three years.
SUBSCRIPTIONS: Address correspondence to Radio-Electronics, Subscription Dept., 154 West 14th St., New York 11, N.Y. When requesting a change of address, please furnish an address label from a recent issue. Allow one month for change of address.
GERNSBACK PUBLICATIONS, INC. Executive, Editorial and Advertising Offices, 154 West 14th St., New York 11, N.Y. Telephone Algonquin 5-7755. **Hugo Gernsback,** Chairman of the Board; **M. Harvey Gernsback,** President; **G. Aliquo,** Secretary.
BRANCH ADVERTISING OFFICES and **FOREIGN AGENTS** listed on page 147.
POSTMASTER: If undeliverable, send Form 3579 to: RADIO-ELECTRONICS, 154 West 14th St., New York 11, N.Y.

*Trademark registered U. S. Pat. Office.

GREATEST ADVANCE IN SHOP-METHOD HOME TRAINING

EARN MORE MONEY... GET INTO TELEVISION ELECTRONICS – RADIO

Learn ALL 8 PHASES in ONE MODERN HOME-STUDY COURSE
At Home — In Spare Time

YOU GET ALL THIS NEWEST PRACTICAL EQUIPMENT

- Parts to build a modern TV set, including all tubes plus a large screen Picture Tube
- Parts to build a powerful Superhet Receiver, standard broadcast and short wave
- Parts to conduct many experiments and build Continuity Checker, RF Ocillator, TV Circuits, Audio Oscillator, TRF Receiver, Signal Generator
- A Valuable Professional Multitester

YOUR NATIONAL SCHOOLS TELERAMA COURSE COVERS ALL 8 PHASES

1. TELEVISION, INCLUDING COLOR TV
2. RADIO, FM AND AM
3. INDUSTRIAL ELECTRONICS
4. SOUND RECORDING AND HI FIDELITY
5. PREPARATION FOR FCC LICENSE
6. AUTOMATION
7. RADAR AND MICRO WAVES
8. COMMUNICATIONS

YOU ARE NEEDED IN THE TELEVISION-ELECTRONICS-RADIO INDUSTRY! You can build a secure future for yourself if you get into Electronics NOW! Today's shortage of trained technicians creates tremendous opportunities. National Schools Shop-Method trained technicians are in constant and growing demand for high-pay jobs in Broadcasting and Communications, Electronic Research, Servicing and Repair, and many other branches.

Let National Schools, a Resident Technical School for over 50 years train you for today's unlimited opportunities in electronics! Our Shop Method trains you to be a MASTER-TECHNICIAN. Completely up to date, developed by experienced instructors and engineers, your Telerama Course will teach you all phases of the industry quickly, clearly and correctly. You can master the most modern projects, such as Color TV, printed circuits — even prepare for FCC License without taking a special course. You can handle sales, servicing, manufacturing, or make good money in your own business. SEND FOR FACTS TODAY!

EARN AS YOU LEARN. Many of our students earn their entire tuition and more in Spare Time jobs we show them how to do while learning.

YOU GET EVERYTHING YOU NEED — Clear, profusely illustrated lessons, shop-tested manuals, modern circuit diagrams, practical job projects — all the valuable equipment shown above — many other materials and services — consultation privilege with our qualified staff, and Graduate Employment Service. EVERYTHING YOU NEED for outstanding success in Electronics

RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles, the world's TV capital, start NOW in our big, modern Shops, Labs and Radio-TV Studios. Here you work with latest Electronic equipment—professionally installed—finest, most complete facilities offered by any school. Expert, friendly instructors. Personal attention. Graduate Employment Service. Help in finding home near school—and part time job while you learn. Check box in coupon for full information.

MEMBER
NATIONAL HOME STUDY COUNCIL
NATIONAL COUNCIL OF TECHNICAL SCHOOLS 1944

FREE! Fully illustrated "Career" Book in TV-Radio-Electronics. PLUS actual sample lesson—yours at no cost, no obligation. CLIP COUPON NOW . . . MAIL IT TODAY!

APPROVED FOR G.I. TRAINING

NATIONAL SCHOOLS

4000 S. FIGUEROA ST., LOS ANGELES 37, CALIF.

NATIONAL SCHOOLS
TECHNICAL TRADE TRAINING SINCE 1905
LOS ANGELES 37, CALIFORNIA

GET FAST SERVICE – MAIL NOW TO
NATIONAL SCHOOLS, DEPT. RG-118
4000 S. FIGUEROA ST
LOS ANGELES 37, CALIF.

Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.

NAME _____ AGE _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____
☐ Check if interested ONLY in Resident School training at Los Angeles.
VETERANS: Give date of Discharge _____

FOR A brighter TV picture

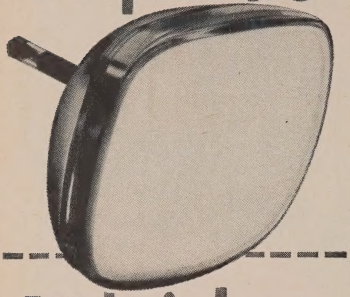

FOR A brighter profit picture

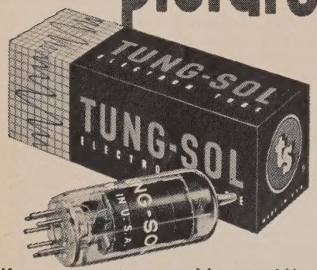

Keep your customers sold on *you!* Use the exact same tubes leading *independent* set makers specify. Tell your supplier you'd rather have Tung-Sol Tubes.

Tung-Sol Electric Inc., Newark 4, N. J.

TUNG-SOL®

MAGIC MIRROR ALUMINIZED

PICTURE TUBES

RECEIVING TUBES

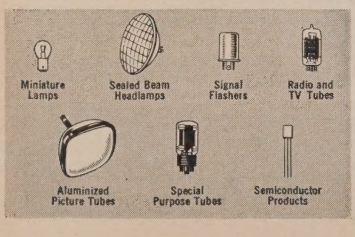

NEWS BRIEFS

STEREO MULTIPLEX adapters have been put on the market by several manufacturers, although the FCC hasn't yet decided which system of stereo multiplexing it will authorize.

The possibility of nationwide stereo FM broadcasting received a big boost when the National Broadcasting Co. asked the FCC for permission to broadcast stereo experimentally using a multiplexing system on WRCA-FM, New York. NBC is expected to test the so-called "compatible" or sum-and-difference system of stereo multiplexing developed by Crosby Laboratories, Syosset, N. Y.

In this method of multiplexing, the main FM channel carries the complete program (or sum of "left" and "right" signals). The multiplex subchannel contains the "difference" signals. A filter network in the receiver or converter separates the "left" and "right" signals and distributes them to the proper amplifiers. An FM receiver without a converter will receive only the main channel—or sum of both the "left" and "right"—providing monophonic reproduction of the full program.

Several FM stations are on the air with experimental multiplexed stereo. WBAI and WFUV, New York, are transmitting "compatible" stereocasts. WGHF, Brookfield, Conn., and others are using a "straight" multiplexing system in which one channel of the sound is carried on the main FM channel, the second on the multiplex subchannel.

ELECTRONICS will play a major role in the generation of atomic power by the fusion method—as much as 50% of the required equipment being electronic. A "test track" for nuclear fusion research will be built at Princeton University by the Allis-Chalmers Manufacturing Co. and RCA (model shown was displayed at the international conference on atomic energy in Geneva).

In the fusion method of generating power, a low-pressure gas or "plasma" (derived from deuterium) is heated to 100,000,000°F—10 times hotter than the sun—in a high vacuum. In the Princeton fusion installation, twenty 500-kw electron tubes, at frequencies near 100 mc, will do the heating. Dc power generators for the project will deliver about 200 megawatts peak power.

"MOON BOUNCE" SIGNALS have been received by at least 30 people, and possibly 60 or more, according to the US Army Signal Engineering Laboratory at Fort Monmouth, N.J., which is aiming radar signals at the moon with 1.2 megawatts of radiated power (RADIO-ELECTRONICS, August, 1958, page 6).

Responses to its Diana project have come from the US, Europe and Latin America, a laboratory spokesman said. The moon radar has been operating on frequencies of 108 and 151.11 mc, and the laboratory has been sending QSL cards to amateurs who report the conditions under which they have received the signal.

During November and December, the moon radar pulses will be on 413.25 mc. Readers who pick up the signals may send a listener's card to Diana, c/o RADIO-ELECTRONICS, 154 W. 14 St., New York 11, N. Y. The information will be forwarded to the Signal Corps and will be acknowledged with a moon radar QSL card.

TWO ELECTRONIC DEVICES to help solve the problem of headlight glare are being offered as extra equipment on all 1959 Chrysler-built cars.

A self-dimming inside rear-view mirror (see diagram page 10) automatically flips upward to deflect the glare of headlights from a car following closely behind. A small opening in

(*Continued on page* 10)

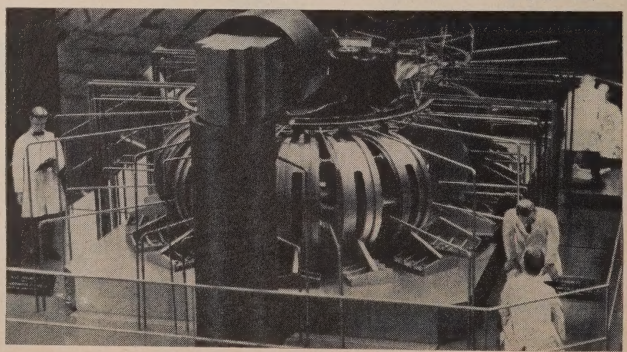

In Spare Time at Home—Prepare for a Better Job—or Your Own Business in One of the Many Branches of

ELECTRONICS

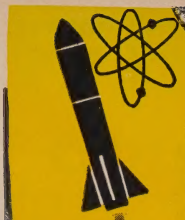

You build and keep this valuable Vacuum Tube VOLTMETER

You build and keep this 5-inch COLOR OSCILLOSCOPE — almost a "must" for TV servicing.

RADIO – TELEVISION – RADAR

If you are seeking a better job or a business of your own, the appealing field of Television-Radio-Electronics offers REAL PROMISE!

In this fast-growing field, trained Electronic technicians find many good-paying, interesting jobs in manufacturing, installing, operating, servicing. Equally important is the fact that these are GOOD JOBS—offering the kind of a future that an untrained man often dreams about.

No previous technical experience or advanced education needed. Prepare for this profitable field in your spare time at home, or in our modern Chicago or Toronto Laboratories. Nothing else like it! Send for FREE details.

HOME MOVIES . . .
. . . make important points crystal clear. Speeds your learning. It's almost like having an instructor at your side!

MILITARY SERVICE
If you are subject to military service, the information we have should prove very helpful. Mail coupon today.

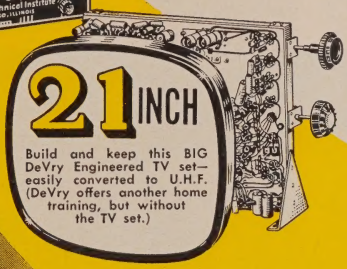

Build and keep this BIG DeVry Engineered TV set—easily converted to U.H.F. (DeVry offers another home training, but without the TV set.)

COLOR TV
DeVry Tech's program also includes training in Color Television

EARN WHILE YOU LEARN
After you get part of DeVry Tech's training with equipment at home, you may then in your spare time, begin to earn real money servicing Radio and Television sets.

Your GUIDE to Profitable Job Opportunities

TV-Radio Broadcast Technician
Color Television Specialist
Radar Operator • Laboratory Technician
Airline Radio Man • Computer Specialist
Quality Control Manager
Your Own Sales & Service Shop
. . . *PLUS MANY OTHERS*

Build over 300 practical projects from many shipments of Radio-Electronic parts. You build and operate TV-Radio circuits . . . wireless microphone . . . and many other major projects—all designed to provide outstanding practical experience at home.

YOU GET THE SAME **EMPLOYMENT SERVICE** that has helped thousands of our graduates toward fine careers in Electronics.

Send for *FREE* BOOKLET TODAY!

Accredited Member of National Home Study Council

"One of North America's Foremost Electronics Training Centers"

DeVRY TECHNICAL INSTITUTE
Formerly DeForest's Training, Inc.
CHICAGO 41, ILLINOIS

ACT NOW!

Get information-packed publication FREE! Mail coupon today.

DeVRY TECHNICAL INSTITUTE
4141 Belmont Ave., Chicago 41, Ill., Dept. RE-11-O

Please give me your FREE booklet, "Electronics and YOU," and tell me how I may prepare to enter one or more branches of Electronics.

Name _____ Age _____
PLEASE PRINT
Street _____ Apt. _____
City _____ Zone _____ State _____

Canadian residents address DeVry Tech of Canada, Ltd.
626 Roselawn Ave., Toronto 12, Ontario

2044

here's your convenient, economical way to buy dependable crystal diodes... at your CBS-Hytron distributor's now

More reliable products through Advanced-Engineering

CBS-HYTRON, Danvers, Massachusetts • A Division of Columbia Broadcasting System, Inc.

FREE... ANY 3

of these superb High-Fidelity

COLUMBIA and EPIC RECORDS

if you join the Columbia (LP) Record Club now—and agree to purchase 4 selections during the coming 12 months

1 The greatest of all piano concertos

JOHNNY'S
GREATEST HITS
JOHNNY MATHIS
CHANCES ARE · TWELFTH OF NEVER
NOT FOR ME TO SAY · WILD IS THE WIND
COME TO ME · WONDERFUL, WONDERFUL
PLUS 6 OTHERS

3 Sensational new Johnny Mathis album

8 Solitaire, Misty, Dreamy, 7 more

6 A "must" for any record collection

2 Moonglow, The Lamp is Low, 10 more

4 Original and best recording of this hit

16 Jealousy, High Noon, 10 more songs

7 Where or When, Be My Love, 10 more

ROSSINI: WILLIAM TELL AND BARBER OF SEVILLE OVERTURES
DONIZETTI: DAUGHTER OF THE REGIMENT OVERTURE
SCHUBERT: MARCHE MILITAIRE
TCHAIKOVSKY: MARCHE SLAV
STRAUSS: RADETZKY MARCH
VAN KEMPEN
CONCERTGEBOUW AND LAMOUREUX ORCHESTRAS

9 Six thrilling overtures and marches

19 Almost one hour of dance music

14 Complete score includes 16 numbers

5 Mean to Me, Blue Skies, 10 more

10 The Duke reaches new heights

17 Classic portrayal of the 4 seasons

12 Laura, Stella by Starlight, 10 more

22 Tony with a wonderful beat

15 Two truly virtuoso performances

13 2 lovely works—superbly performed

TCHAIKOVSKY: serenade in c major
BORODIN: nocturne BARBER: adagio
VAUGHAN WILLIAMS: greensleeves
Strings of The Philadelphia Orchestra—Ormandy

21 Four melodic works for strings

20 Suave arrangements of 14 numbers

11 Whiffenpoof Song, Aura Lee, etc.

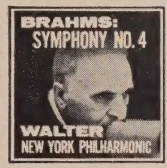

23 A great work—a grand performance

18 Duchin's 15 finest performances

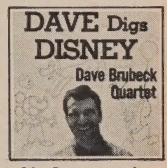

24 Dave works over six Disney tunes

. . . a convenient method of acquiring, systematically and with expert guidance, an outstanding record library of the music you enjoy most — at far less than the usual cost

★ You receive, at once, ANY 3 of the superb Columbia and Epic records shown here — FREE

★ Your only obligation as a member is to purchase four selections from the more than 100 Columbia and Epic records to be offered in the coming 12 months. Thus, you receive seven records for the price of four — a saving of as much as 42%

★ After purchasing only four records you receive a Columbia or Epic Bonus record of your choice free for every two additional selections you buy

★ You enroll in any of the four Club Divisions: Classical; Listening and Dancing; Broadway, Movies, Television and Musical Comedies; Jazz

★ Each month the Club's staff of musical experts selects outstanding recordings from every field of music . . music that deserves a place in any well-planned library. These selections are described in the Club Magazine, sent to you free each month

★ You may accept or reject the selection for your Division, take any of the other records offered, or take NO record in any particular month

★ You may discontinue membership at any time after purchasing four records from the Club

★ The records you want are mailed and billed to you at the regular list price, plus a small mailing charge

★ You must be delighted with membership or you may cancel by returning the free records within 10 days

COLUMBIA (LP) RECORD CLUB
Terre Haute, Indiana

FREE—ANY 3—MAIL ENTIRE COUPON NOW!

COLUMBIA (LP) RECORD CLUB, Dept. 245-1
TERRE HAUTE, INDIANA

Please send me as my FREE gift the 3 records whose numbers I have circled at the right—and enroll me in the following Division of the Club:

(check one box only)

☐ **Classical** ☐ **Listening and Dancing** ☐ **Jazz**
☐ **Broadway, Movies, Television and Musical Comedies**

I agree to purchase four selections from the more than 100 to be offered during the coming 12 months . . . at regular list price, plus small mailing charge. For every two *additional* selections I accept, I am to receive a 12" Columbia or Epic Bonus record of my choice FREE.

Name.....
(Please Print)

Address.....

City.....ZONE.....State.....

CANADA: Prices slightly higher, address 11-13 Soho St., Toronto 2B

If you wish to have this membership credited to an established Columbia or Epic record dealer, authorized to accept subscriptions, please fill in the following:

Dealer's Name.....

Dealer's Address.....109-C-2

CIRCLE 3 NUMBERS BELOW:

1. Beethoven: Emperor Concerto
2. Doris Day—Day By Night
3. Johnny Mathis' Greatest Hits
4. South Pacific—Orig. Broadway Cast
5. Frank Sinatra—That Old Feeling
6. Dvorak: New World Symphony
7. 'S Marvelous—Ray Conniff
8. Erroll Garner—Other Voices
9. Rossini: William Tell Overture, etc.
10. Ellington at Newport
11. Norman Luboff Choir—Just A Song
12. Andre Kostelanetz—Calendar Girl
13. Schubert: "Unfinished" Symphony; Mendelssohn: Midsummer Night's Dream
14. My Fair Lady—Orig. Broadway Cast
15. Paganini & Saint-Saens Violin Concertos
16. Frankie Laine—Command Performance
17. Vivaldi: The Seasons
18. Eddy Duchin Story
19. Lester Lanin at the Tiffany Ball
20. Percy Faith—Gershwin Hits
21. Strings of Philadelphia Orchestra
22. Tony Bennett—Beat of My Heart
23. Brahms: Symphony No. 4
24. Dave Brubeck Digs Disney

L-20

®"Columbia," (LP), "Epic," Marcas Reg.
© Columbia Records Sales Corp., 1958

Precision

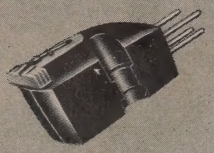

...precisely for music!

A pickup precisely designed for music! A stereo pickup with all the compliance, frequency response and distortion-free performance required for the highest quality music reproduction. This...is the STANTON Stereo-FLUXVALVE... where quality starts and the music begins!

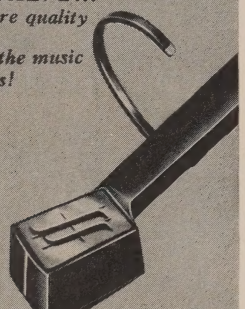

The STANTON Model 196 UNIPOISE Arm with integrated Stereo-FLUXVALVE Pickup—$59.85 with replaceable 0.7 mil diamond T-GUARD Stylus.

The STANTON Model 371 Stereo-FLUXVALVE Cartridge—$29.85 with replaceable 0.7 mil diamond T-GUARD Stylus.

Hermetically sealed for a lifetime of trouble-free use, the STANTON Stereo-FLUXVALVE performs in a way no other pickup can equal. Use it in automatic or manual record playing systems.

PHOTOGRAPHED BY MORT WELDON

"For those who can hear the difference"

FINE QUALITY HIGH FIDELITY PRODUCTS BY

PICKERING & COMPANY, INC.

Plainview, N. Y.

FLUXVALVE, T-GUARD, UNIPOISE are registered trademarks

Address Dept. G118 for a free copy of IT TAKES TWO TO STEREO by Walter O. Stanton.

NEWS BRIEFS *(Continued from p. 6)*

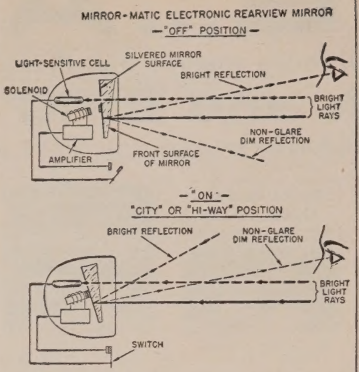

the surface of the mirror admits lights to a photo-cell mounted in the rear of the mirror housing. When light intensity reaches an objectionable level, current from the cell activates an amplifier tube which energizes a solenoid, pulling the mirror prism a few degrees upward to give a secondary dim image.

The mirror is wired through the headlight system so it works only while the lights are on. A two-way "city-highway" switch adjusts the sensitivity of the circuit so that the mirror won't dip in response to street lights in city driving.

The second anti-glare device is an improved headlight dimmer using a circuit of 2 transistors and one 12-volt tube. The principal innovation is a "red-sensitivity" circuit which dims the headlights in response to the taillights of a car being followed.

The dimmer's sensitivity is adjustable by a driver to a range of 900-1,200 feet for headlights of approaching cars and 200-500 feet for taillights. The dimmer may be overridden at any time by a foot switch.

SPUTNIK TV RELAY may now be under construction in Russia to extend Soviet television to 2.2 billion people in Europe, Asia, Africa and Australia. An article in the Soviet magazine *Knowledge Is Strength* states that the principle has been officially endorsed by the Government and that "this launching can be readied and carried out now."

The article says the relay satellite would be placed in orbit 22,350 miles high, where it would move at the same speed as the earth—in effect staying in one spot with relation to the ground beneath it. The authors say a 2-kw relay transmitter would be adequate, getting its power from solar batteries at first, and later from small nuclear reactors.

The cost would be far less than building thousands of TV transmitters and relay stations, even if each relay satellite lasted only a year.

FUNDAMENTAL ELECTRONICS course for hams will be broadcast weekly over the First US Army Military Affiliate Radio System (MARS) network. Beginning Wednesday, Nov. 5, the 25-week

(*Continued on page* 14)

you learn MORE from a SAMS BOOK

OVER 1,000,000 SAMS BOOKS bought to date

JUST OUT!

"Handbook of Electronic Circuits"

valuable reference book on important circuits, authored by RCA Service Company, Inc.

This practical handbook discusses the following circuits: 4 power supply circuits; 14 circuits used in radio stages; 8 circuits used in transmitter stages; 32 circuits used in TV receiver stages; 7 additional circuits having special applications. An analysis of the operation of each circuit is given; a schematic for each is included; a component failure analysis describes various troubles which could occur if particular components in the circuit should fail. Of real value to engineers, technicians, students. 80 pages; 8½ x 11".

☐ **Handbook of Electronic Circuits** Only.....**$2.00**

SAMS "BEST-SELLERS"

☐ **Servicing TV Sync Systems.** Covers theory function and variation of all types. Speeds sync system servicing. 320 pages, 5½ x 8¼". Only.....**$3.95**

☐ **TV Servicing Guide.** Picture tube screen photos show trouble symptoms; describes proper repair procedures. 132 pages, 8½ x 11". Only.....**$2.00**

☐ **Television Tube Location Guide.** Vol. 7 in this invaluable series. Covers 1956-57 sets. Only.....**$2.00**

☐ **Tape Recorder Manual.** Vol. 1; covers recorders produced in 1956-57. Only...**$2.95**

☐ **Auto Radio Service Manual.** Vol. 7; covers auto radios produced in 1956-57. Only **$3.75**

☐ **How To Understand and Use TV Test Instruments.** Revised to include data on Color TV Servicing. Only.....**$3.50**

☐ **Recording & Reproduction of Sound.** Oliver Read's best-selling volume on all aspects of audio. 810 pages. Only.....**$7.95**

☐ **Color TV Training Manual.** Trains you practically for Color servicing; 260 pages; includes many color illustrations. Only...**$6.95**

☐ **Hi-Fi Handbook.** Invaluable data on hi-fi theory, design, selection, installation, components. Only.....**$3.00**

☐ **Servicing Transistor Radios.** Complete analysis of 70 popular transistor radio models, including basic pointers on servicing transistorized sets. 152 pages. Only.....**$2.95**

HOWARD W. SAMS & CO., INC.

Order from your Parts Jobber, or mail to Howard W. Sams & Co., Inc., Dept. 2-L8 2201 E. 46th St., Indianapolis 6, Ind.

Send books checked above. My (check) (money order) for $.....is enclosed.

Name_____

Address_____

City_____ Zone____ State_____

(outside U.S.A. priced slightly higher)

6 months from today

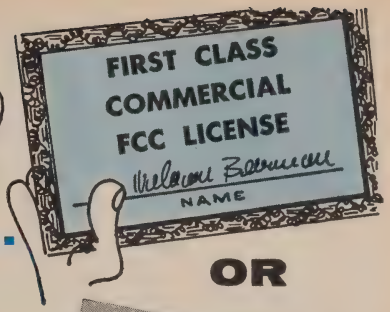

WHICH WILL YOU HOLD . . .

OR

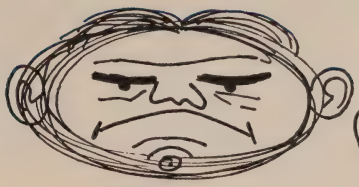

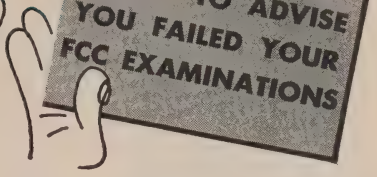

add technical training to your practical experience. Get your FCC license quickly!

then use our effective

Job Finding Service!

Get your FCC Commercial License

or your money back

The Master Course in Electronics will provide you with the mental tools of the electronics technician and prepare you for a First Class FCC License (Commercial) with a radar endorsement. When you successfully complete the Master Course, if you fail to pass the FCC examination, you will receive a full refund of all tuition payments.

Employers Make Offers Like These

to Our Graduates Every Month

Broadcast Station in Illinois: "We are in need of an engineer with a first class phone license, preferably a student of Cleveland Institute of Radio Electronics; 40 hour week plus 8 hours overtime."

West Coast Manufacturer: "We are currently in need of men with electronics training or experience in radar maintenance. We would appreciate your referral of interested persons to us."

Our Trainees Get Jobs Like These Every Month

CHIEF ENGINEER

"Since enrolling with Cleveland Institute I have received my 1st class license, served as a transmitter engineer and am now Chief Engineer of Station WAIN. I also have a Motorola 2-Way Service Station. Thanks to the Institute for making this possible."

Lewis M. Owen, Columbia, Ky.

TEST ENGINEER

"I am pleased to inform you that I recently secured a position as Test Engineer with Melpar, Inc. (Subsidiary of Westinghouse). A substantial salary increase was involved. My Cleveland Institute training played a major role in qualifying me for this position."

Boyd Daugherty, Falls Church, Va.

Names of Trainees in Your Area Provided on Request

Carl E. Smith, E.E., President

CLEVELAND INSTITUTE OF RADIO ELECTRONICS

Dept. RE-23, 4900 Euclid Bldg., Cleveland 3, Ohio

Get these valuable Booklets

FREE!

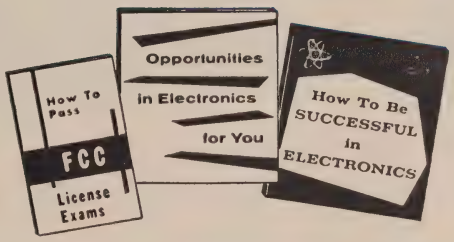

Accredited by National Home Study Council

Cleveland Institute of Radio Electronics

Dept. RE-23, 4900 Euclid Bldg., Cleveland, Ohio

Please send Free Booklets prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below:

- ☐ Millitary
- ☐ Radio-TV Servicing
- ☐ Manufacturing
- ☐ Amateur Radio
- ☐ Broadcasting
- ☐ Home Experimenting
- ☐ Telephone Company
- ☐ Other .....

In what kind of work are you now engaged? .....

In what branch of Electronics are you interested?.....

Name .....Age .....

Address .....

City ..... Zone.....State .....

RE-23

USE ZENITH

QUALITY CIRCUIT TUBES FOR

Maximum Performance

AND

Zenith Dependability

Zenith's quality reputation with your customers is an asset to you when you use Zenith parts to service Zenith TV

HERE'S WHY:

At Zenith, *quality* is the keynote . . . in circuit tubes, this means uniform, long-life performance!

To insure the highest standard of performance, Zenith circuit tubes are tested under all operating conditions, using the most modern laboratory equipment and techniques.

Rigid manufacturing specifications, production quality controls and performance tests *insure* dependability and customer satisfaction. That's why you should—

USE ZENITH QUALITY CIRCUIT TUBES FOR ALL YOUR SERVICE WORK

SEE YOUR ZENITH DISTRIBUTOR

You can safely guarantee Zenith repairs when you use dependable Zenith components.

Buy circuit tubes by Zenith . . .

backed by 40 years of leadership in radionics exclusively. The quality goes in before the Zenith names goes on.

ZENITH® MEANS QUALITY

ZENITH RADIO CORPORATION • PARTS AND ACCESSORIES DIVISION 6001 W. Dickens, Chicago 39, Illinois

TAKE A LOOK AT YOUR FUTURE IN RADIO-TV-ELECTRONICS—FREE!

I.C.S. Career Kit tells you where the big-pay jobs are . . . who are the industry's most wanted men . . . how you can "cash in" in a big way on your own future.

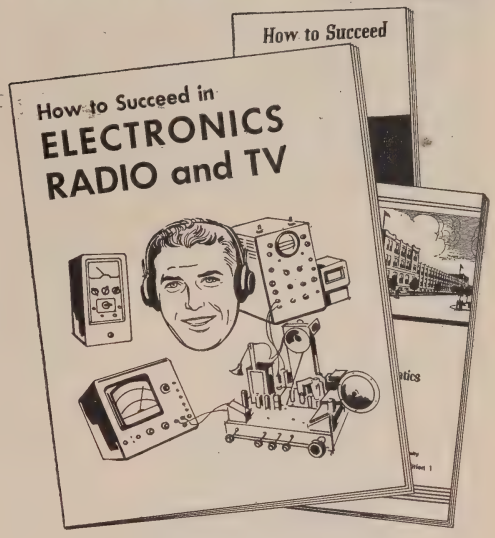

Here's your chance to find out where you're going—fast! And it won't cost you a thing except the time it takes to clip and mail the coupon at the bottom of this page.

Radio-TV-Electronics is the fastest growing industry of all time. Opportunity for men in this field is almost unlimited. The rewards are great.

But to "cash in" you must be properly trained. You must know more than simply wires and tubes. You must be able to understand and apply the principles of Radio-TV-Electronics.

That's where I. C. S. comes in . . . the world's oldest and largest technical training school. Here are the people who know—who can tell you—what you need to go places in Radio-TV-Electronics.

You get the full story with your free I. C. S. Career Kit.

So take a minute now to get a look at your future in Radio-TV-Electronics. Send for your free I. C. S. Career Kit. You have nothing to lose. You can gain an exciting, well-paid career in a vital industry.

Send the coupon below for your *free* I. C. S. Career Kit!

1 "How to Succeed," 36-page guide to advancement

2 Electronics, Radio and TV handbook or the field of your choice

3 Sample lesson (Math) to demonstrate I. C. S. Method

For Real Job Security—Get an I.C.S. Diploma! **I.C.S., Scranton 15, Penna.**

Accredited Member, National Home Study Council

INTERNATIONAL CORRESPONDENCE SCHOOLS

ICS

BOX 91225K, SCRANTON 15, PENNA. (Partial list of 259 courses)

Without cost or obligation, send me "How to Succeed" and the opportunity booklet about the field BEFORE which I have marked X (plus sample lesson):

RADIO TELEVISION ELECTRONICS
- ☐ General Electronics Tech.
- ☐ Industrial Electronics
- ☐ Practical Radio-TV Eng'r'g
- ☐ Practical Telephony
- ☐ Radio-TV Servicing

BUSINESS
- ☐ Cost Accounting
- ☐ Managing a Small Business
- ☐ Purchasing Agent

DRAFTING
- ☐ Electrical Drafting

HIGH SCHOOL
- ☐ High School Diploma
- ☐ Good English
- ☐ High School Mathematics

ELECTRICAL
- ☐ Electrical Engineering
- ☐ Elec. Engr. Technician
- ☐ Elec. Light and Power
- ☐ Practical Electrician
- ☐ Professional Engineer (Elec.)

LEADERSHIP
- ☐ Industrial Foremanship
- ☐ Industrial Supervision
- ☐ Personnel-Labor Relations
- ☐ Supervision

Name_____ Age____ Home Address_____

City_____ Zone____ State_____ Working Hours____ A.M. to____ P.M.____

Occupation_____

Canadian residents send coupon to International Correspondence Schools, Canadian, Ltd., Montreal, Canada. . . . Special tuition rates to members of the U. S. Armed Forces.

Mr. Dealer
PHILCO
offers you a Complete and Universal line of
FULL FIDELITY NEEDLES
• DIAMOND
• SAPPHIRE
• OSMIUM

Now, one complete line of precision-engineered and custom-designed needles to fit every make and model phonograph and High Fidelity receiver. Every Philco needle measures up to the highest quality and life test standards. All Philco needles are individually packaged for absolute protection.

FREE! NEEDLE COUNTER DISPLAY!
Ask your Philco Distributor how you can get this sparkling, jewel case needle dispenser free. It's a sales-maker for you right on your counter at the point of sale.

COMPLETE PHILCO NEEDLE CATALOG
The most accurate, up-to-date, easy-to-read needle catalog in the industry. Cross references are complete . . . Illustrations are big . . . Makes selling easy.

PHILCO FIDELITAPE
will bring new customers into your store. Unequalled in uniformity of output. Guaranteed splice free. Extra strength and extra length.

See Your Philco Distributor Today!

PHILCO® Accessory Division

World-Wide Distribution

Service Parts • Power-Packed Batteries • Universal Components • Long-Life Tubes • Heavy-Duty Rotors • Star-Bright 20/20 Picture Tubes • Long-Distance Antennas • Appliance Parts • Laundry Parts • Universal Parts and Accessories

series will be heard every Wednesday, 8–9 p.m., EST, on 4.03 mc.

The course is sponsored by the US Army Signal School at Fort Monmouth, N. J. A complete schedule may be obtained by writing Chief Warrant Officer Herbert M. Huffman, MARS Director, Signal Section Headquarters, First US Army, Governors Island, New York 4, N. Y.

Calendar of Events

Hi-Fi Show, Oct. 29–Nov. 1, Windsor Hotel, Montreal, Canada.
Electron Devices Meeting, Oct. 30–Nov. 1, Shoreham Hotel, Washington, D. C.
International Hi-Fi Show, Nov. 7–9, Detroit Leland Hotel, Detroit, Mich.
Hi-Fi Musical Show, Nov. 7–9, Hotel Paxton, Omaha, Neb.
Conference on Electrical Techniques in Medicine and Biology, Nov. 12–14, Nicollet Hotel, Minneapolis, Minn.
Hi-Fi Fair—Nov. 14–16, Hotel Carter, Cleveland, Ohio.
Northeast Electronics Research and Engineering Meetings, Nov. 19–20, Mechanics Hall, Boston, Mass.
Hi-Fi Show, Nov. 21–23, New Washington Hotel, Seattle, Wash.
Electronic Computer Exhibition, Nov. 28–Dec. 4, Olympia, London, England.
1958 Mid-America IRE Electronics Convention, Dec. 9–11, Kansas City Municipal Auditorium, Kansas City, Mo.
2nd National Symposium on Global Communications, Dec. 3–5, Colonial Inn, St. Petersburg, Fla.

FIVE NEW TV STATIONS have begun telecasting since we last reported:

WFPK-TV, Louisville, Ky..... 5
WJCT, Jacksonville, Fla..... 7
KAYS-TV, Hays, Kans..... 2
WTAE, Pittsburgh, Pa..... 4
KWGB-TV, Goodland, Kans.....10

The same number went off the air:

WBLN, Bloomington, Ill.....15
KFSA-TV, Fort Smith, Ark.....22
WNOW-TV, York, Pa.....49
WVUE, Philadelphia, Pa.....12
WILK-TV, Wilkes-Barre, Pa.....34

The following call letters changed:

WJXT, Jacksonville, Fla..... 4 (formerly WMBR-TV)
WMTW-TV, Poland Springs, Me. 8 (formerly WMTW)
KXMC-TV, Minot, N. D.....13 (formerly KCBJ-TV)
WNEW-TV, New York, N. Y..... 5 (formerly WABD)

Although the count remains the same for the US, 538, there are now 451 vhf and 87 uhf stations, including 32 noncommercial.

With the addition of:

CKBL-TV, Matane, Que..... 9

Canada has increased its total to 54.

DR. ERNEST O. LAWRENCE, Nobel Prize-winning developer of the cyclotron and the inventor of the Lawrence one-gun color TV picture tube, died in Palo Alto, Calif., following surgery. He was 57. At the time of his death he was director of the University of California Radiation Laboratory. His color tube, which promised a less expensive approach to color television, has never been produced in quantity, but Allen B. DuMont Laboratories currently is doing further development work on the Lawrence tube and an associated color receiver. END

Learn Electronics

PREPARE FOR YOUR F. C. C. LICENSE—YOUR TICKET TO A BETTER JOB AND HIGHER PAY!

F.C.C. LICENSE—THE KEY TO BETTER JOBS

An F.C.C. *commercial* (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire *licensed* technicians.

WHICH LICENSE FOR WHICH JOB?

The THIRD CLASS radiotelephone license is of value primarily in that it qualifies you to take the second class examination. The scope of authority covered by a third class license is extremely limited.

The SECOND CLASS radiotelephone license qualifies you to install, maintain and operate most all radiotelephone equipment except commercial broadcast station equipment.

The FIRST CLASS radiotelephone license qualifies you to install, maintain and operate every type of radiotelephone equipment (except amateur) including all radio and television stations in the United States, its territories and possessions. This is the highest class of radiotelephone license available.

GRANTHAM TRAINING PREPARES YOU

The Grantham Communications Electronics Course prepares you for a *FIRST CLASS* F.C.C. license, and it does this by TEACHING you electronics. Each point is covered simply and in detail, with emphasis on making the subject easy to understand. The organization of the subject matter is such that you progress, step-by-step, to your specific objective—a first class F.C.C. license.

CORRESPONDENCE OR RESIDENCE CLASSES

Grantham training is available by correspondence or in resident classes. Either way (residence or correspondence), we train you quickly and well—NO previous training required. A beginner may qualify for his first class license in as little as 12 weeks.

THREE COMPLETE SCHOOLS: *To better serve our many students throughout the entire country, Grantham School of Electronics maintains three complete schools—one in Washington, D.C., one in Hollywood, Calif., and one in Seattle, Wash. All schools offer the same rapid courses in F.C.C. license preparation, either home study or resident classes.*

This booklet **FREE!**

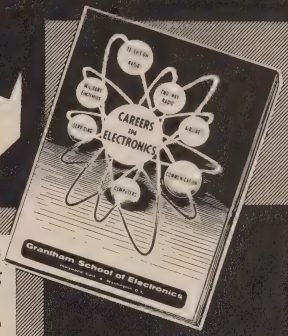

This free booklet gives details of our training and explains what an F.C.C. license can do for your future.

GET YOUR FIRST CLASS COMMERCIAL F.C.C. License in 12 Weeks!

HERE'S PROOF...

that Grantham students prepare for F.C.C. examinations in a minimum of time. Here is a list of a few of our recent graduates, the class of license they got, and how long it took them:

	License	Weeks
Donald E. Mason, 2659 Centinella, Santa Monica, Calif.	1st	12
Everett T. Bozard, 411 N. Wash. St., Alexandria, Va.	1st	12
Henry M. Best, 1003 Vermont St., Fremont, N. C.	1st	11
Harold V. Jones, P.O. Box 705, Alamogordo, N. M.	1st	13
Michael F. Aperio, 916 Townsend St., Chester, Pa.	1st	12
Earl A. Stewart, 3918 Modesto Dr., San Bernardino, Calif.	1st	14
Donald L. Leeburg, Box 1075, Anchorage, Alaska	1st	12
J. Milton Condit, 1312 N. 78th Street, Seattle, Wash.	1st	8
John R. Bahrs, 72 Hazelton St., Ridgefield Park, N. J.	1st	12
Richard Baden, 4226-37th St., N.W., Washington, D.C.	1st	12
James F. Stewart, 2618½ Prospect Ave., La Crescenta, Calif.	1st	12
Norman R. Cook, 130 Olive Street, Neodeska, Kans.	1st	12

GRANTHAM SCHOOL OF ELECTRONICS

WASHINGTON D.C.	821 - 19th Street, N.W. Washington, D.C.	(ST 3-3614)
HOLLYWOOD CALIF.	1505 N. Western Ave. Hollywood, Calif.	(HO 7-7727)
SEATTLE WASH.	408 Marion Street Seattle, Wash.	(MA 2-7227)

MAIL COUPON TO SCHOOL NEAREST YOU

(Mail in envelope or paste on postal card)

To: GRANTHAM SCHOOL OF ELECTRONICS
Washington • Hollywood • Seattle

Gentlemen:
Please send me your free booklet telling how I can get my commercial F.C.C. license quickly. I understand there is no obligation and no salesman will call.

Name_____ Age_____

Address_____

City_____ State_____

I am interested in: ☐ Home Study, ☐ Resident Classes 84 S

BETTER BUSINESS is in the cards

with the

Centralab®

FR-22A

FASTATCH® Control Kit

It's like playing with a stacked deck! The odds are 80 to 1 that you can draw the dual-concentric control you need from this kit. Avoid delays—avoid extra trips to your distributor. Over 120 different combinations can be assembled from this small stock!

You'll be flush with new profits when you pair these units . . . so ante up $30.73 (Your resale price totals $49.55!)—keep a full house always—and you can bet you'll end up a big winner.

Every control factory assembled and tested—all you do is snap them together.

Catalog 30 listing the full line of Centralab products is available free from your distributor, or write us for it.

Centralab products are listed in COUNTERFACTS and PHOTOFACTS.

Centralab B-5804 ®

A DIVISION OF GLOBE-UNION, INC.
922L E. KEEFE Ave. • MILWAUKEE 1, Wis.
In Canada: 804 Mt. Pleasant Rd. • Toronto, Ontario

CONTROLS • SWITCHES • PACKAGED ELECTRONIC CIRCUITS
CERAMIC CAPACITORS • SEMI-CONDUCTOR PRODUCTS

Correspondence

HARMONIC CANCELLATION

Dear Editor:

In his article "Special Amplifier Circuits" (August, page 40), Herbert Ravenswood states that "curvature in the 12AU7 . . . introduces second-harmonic distortion, which will ultimately cancel in the output stage."

Doesn't a push-pull amplifier cancel only even-order harmonics generated within that stage? A distorted input should still give a distorted output.

Mr. Ravenswood is further concerned with second harmonics of second harmonics. Since these are also even-order harmonics, why would they not also be canceled?

GEORGE REIS

Milwaukee, Wis.

(Mr. Reis' letter was referred to Mr. Ravenswood for comment.—*Editor*)

Dear Editor:

Mr. Reis is not the only one to question these points, so I am glad of this opportunity to set things straight for the record.

The first statement he questions depends to some extent on the way the push-pull amplifier functions. In its simplest form, each "side" of the amplifier operates as a separate amplifier unit, using a common power supply. The signal paths are almost completely separate from the phase inverter through to the output transformer, where they are recombined. In this arrangement, my original statement stands true: recombination will cancel equal quantities of second harmonic, wherever along each amplifier they are generated.

In some amplifiers, larger-than-usual common impedances are included in the coupling, along with deliberate large amounts of feedback for the spurious in-phase components. This arrangement helps maintain balance very closely at all stages and does, to some extent, reduce second-harmonic components being generated along the way. But recombination at the output will still cancel any second-harmonic components, so long as they are equal and opposite in phase.

So curvature introducing second-harmonic distortion anywhere along a push-pull amplifier will ultimately cancel at the output. But other distortions may creep in which do not cancel.

On this second point a little further elaboration seems necessary. Curvature can be expressed in terms of a power law. A curve that will add simple second harmonic could be written

$$y = A(x + ax^2)$$

where x is input, y output, A amplification of the stage, and a is the second-harmonic distortion coefficient.

free! ALLIED'S 1959

value-packed 452-page ELECTRONIC SUPPLY CATALOG

the only COMPLETE guide to everything in electronics

WORLD'S LARGEST STOCKS

- Latest Stereo Hi-Fi Systems—Everything in Hi-Fi Components
- Money-Saving, Build-Your-Own KNIGHT-KITS—Latest Models
- Values in Recorders and Supplies
- Latest Public Address Systems, Paging and Intercom Equipment
- Amateur Receivers, Transmitters and Station Gear
- Test & Laboratory Instruments
- Specialized Electronic Equipment for Industrial Application
- TV Tubes, Antennas, Accessories
- Huge Listings of Parts, Tubes, Transistors, Tools, Books

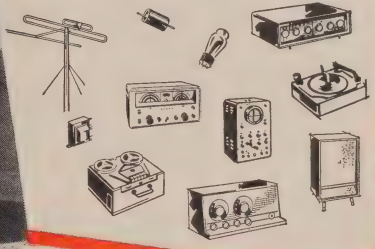

featuring:

MONEY-SAVING knight-kits: Finest electronic equipment in money-saving kit form. Complete selection of latest Hi-Fi amplifier, tuner and speaker kits (new Stereo units); Hobbyist kits; Test Instruments and Amateur kits. KNIGHT-KITS are an exclusive ALLIED product.

HI-FI! STEREO! See the world's largest selection of quality Hi-Fi music systems and famous name components. First with the latest in STEREO! Save on ALLIED-recommended complete systems. Own the best in Hi-Fi for less!

Send for ALLIED's 1959 Catalog—it's the leading supply guide—452 pages packed with the world's largest selection of quality electronic equipment at lowest, money-saving prices. Get *every* buying advantage at ALLIED: fastest shipment, expert personal help, lowest prices, guaranteed satisfaction...

send for the leading electronic supply guide

FREE!

EASY PAY TERMS: Only 10% down; available on orders of $20 or more. Fast handling—no red tape.

ALLIED RADIO

our 38th year

World's Largest Electronic Supply House

ALLIED RADIO CORP., Dept. 2-L8
100 N. Western Ave., Chicago 80, Ill.

☐ Send FREE 452-Page 1959 ALLIED Catalog

*Name*_____

*Address*_____

*City*_____ *Zone*____ *State*_____

Now! The Most Important Product Announcement in the History of H. H. Scott!

Here are the exciting details on

The Stereo Amplifier that sets the Standards for the Next Decade!

The H. H. Scott engineering laboratories proudly introduce the new Model 299 40 watt stereophonic amplifier and control center. It contains many advance features that not only meet the needs of today's stereophonic program sources, but anticipate the requirements of the future. Check the details of this new amplifier, and see for yourself why the new 299 is superior to any other amplifier available.

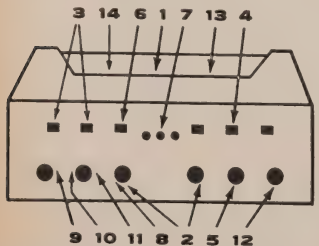

1 40 watt power stage consisting of dual 20 watt power amplifiers. You need this much power to meet the requirements of today's speaker systems. 2 Completely separate Bass and Treble controls on each channel so that different speakers may be matched. 3 Provision for connecting both a stereo phono cartridge and stereo tape heads. 4 Phase reverse switch to compensate for improperly phased tape recordings or loudspeakers. 5 Special balancing circuit for quick and accurate volume balancing of both channels. 6 Separate record scratch and rumble filters. 7 Unique visual signal light control panel. Instantly indicates mode of operation. 8 Can be used as an electronic crossover (bi-amplifier). 9 Special compensation for direct connection of tape playback heads without external preamp. 10 Special switching lets you use your stereo pickup on monaural records. 11 You can play a monaural source such as an FM tuner through both channels simultaneously effectively doubling power. 12 Loudness compensation. 13 Stereo tape recorder output. 14 D.C. filament supply for preamp to virtually eliminate hum (80 db below full power output). 15 Distortion (first order difference tone) less than 0.3%.

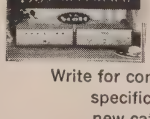

Size in accessory walnut case: 15½w x 5h x 12½d. Price $199.95. (*West of Rockies $204.95*)

Write for complete technical specifications and new catalog RE-11.

h.h. Scott

H. H. SCOTT, INC.
111 POWDERMILL RD., MAYNARD, MASS.
EXPORT: TELESCO INTERNATIONAL CORP.
36 W. 40TH ST., N. Y. C.

Passing this through a second stage, also producing second-harmonic distortion in opposite phase, can be written

$$z = B(y - by^2)$$

where z is the final output and B, b have similar significance to A, a in the first expression.

Now, writing the final output in terms of the original input, we get by substitution:

$$z = AB\ (x + ax^2) - ABb\ (x + ax^2)^2$$
$$= AB[x + (a - b)x^2 - 2abx^3 - a^2bx^4]$$

Notice that this has terms *up to* the fourth. The term in x^2 will produce the usual dc and second harmonic. The term in x^3 produces a fundamental component and third harmonic. The term in x^4 produces dc, second and fourth harmonics. For small orders of distortion, the second harmonic disappears when a = b. This leaves the major component as *third*, with a smaller component of fourth.

Consequently, my original statement would better read that second harmonics of second harmonics will produce components *up to* the fourth. While fourth may be canceled in the output recombination, the third definitely cannot be.

To illustrate with numbers: if a and b are both 5%, the analysis works out as follows: second, .00625%; third, 0.125%; fourth, .0015625%. Thus third is quite obviously the most serious remaining component.

A further interesting point is that compounding curvatures in this way, using terms in x^3 that yield third harmonic individually, produces an expression with terms *up to ninth*, including only odd orders.

HERBERT RAVENSWOOD
New York, N. Y.

STAND UP AND BE COUNTED

Dear Editor:

The TV service industry is a paradox:

On the one hand you have many individuals who are dedicated to their profession, studying to keep abreast of latest developments in their field, always striving to have the latest and most up-to-date equipment, maintaining the highest standards of integrity, and occasionally losing money on "tough dogs" for the personal satisfaction of a job well done.

On the other hand you have some nontechnical shop owners, some appliance store owners and (so-called) cut-rate service operators whose only purpose is to peddle their wares or services without assuming the responsibility of maintaining a high-quality and high-integrity service operation.

The latter TV shop gives the entire service industry a black eye because of its inability to fix a set in the shortest possible time and without using unnecessary parts (or its dishonest practices). Many sets are not fixed properly, but still the customer invariably winds up with a large repair bill.

Now you may say that this type of operation drives service business to the better shops; well, to a small degree

Learn TELEVISION-RADIO

Servicing or Communications

by Practicing at Home in Spare Time

NRI gives you kits to build these and other equipment

Electronic Technicians Have High Pay, Prestige Jobs

People look up to and depend on the Technician, more than ever before. His opportunities are great, and are increasing. Become a Radio-Television-Electronic Technician. At home, and in your spare time, you can learn to do this interesting, satisfying work—qualify for important pay. A stream of new Electronics products is increasing the job and promotion opportunities for Television-Radio-Electronic Technicians. Right now, a solid, proven field of opportunity for good pay is servicing the millions of Television and Radio sets now in use. The hundreds of Television and Radio stations on the air offer interesting jobs for Operators and Technicians. The military services reward qualified Technicians with higher rank and pay. Police, Aviation, Mobile Two-Way Radio are expanding. To ambitious men everywhere: here is rich promise of fascinating jobs, satisfaction and prestige, increasing personal prosperity.

Make Extra Money Soon, $10 to $15 a Week in Your Spare Time

NRI students find it practical and profitable to start fixing sets for friends and neighbors a few months after enrolling. Picking up $10, $15 and more a week gives substantial extra spending money. Use the Tester built with parts NRI furnishes, to locate and correct Radio-TV receiver troubles. Many who start in spare time, soon build full time Television-Radio sales and service businesses; others enjoy profitable spare time businesses and the security of a source of income to fall back on in case of layoffs, hard times or other changes in regular job. Postage free card will bring you complete facts about the NRI tested way to better pay.

ACT NOW FIND OUT WHAT NRI OFFERS YOU

NRI Has Trained Thousands for Successful Careers in TV-Radio

Studio Engr., Station KATV
"I am now Studio Engineer at Television Station KATV. Before enrolling for the NRI Course, I was held back by limitation of a sixth grade education." BILLY SANCHEZ, Pine Bluff, Ark.

Has All the Work He Can Do
"Since finishing NRI Course I have repaired more than 2,000 TV and Radio sets a year. NRI training certainly proved to be a good foundation." H. R. GORDON, Milledgeville, Ga.

Has Good Part Time Business
"Quite early in my training I started servicing sets. Now have completely equipped shop. My NRI training is the backbone of my progress." E. A. BREDA, Tacoma, Wash.

Cut Out and Mail Postage-Free Card NOW

Sample Lesson and Catalog Both FREE

SEE OTHER SIDE

OLDEST & LARGEST HOME STUDY RADIO-TV SCHOOL

National Radio Institute

Dept. C , Washington 16, D.C.

Please send me sample lesson of your Radio-Television Training and Catalog FREE. (No salesman will call.)

Name..... Age.....

Address.....

City..... Zone..... State.....

ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

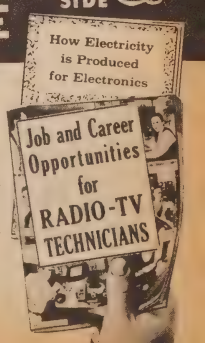

NRI SUPPLIES LEARN-BY-DOING KITS WITHOUT EXTRA CHARGE

Technical Know-How Pays Off in Interesting, Important Work

YOU BUILD AC-DC Superhet Receiver

NRI Servicing Course includes all needed parts. By introducing defects you get actual servicing experience practicing with this modern receiver. Learn-by-doing.

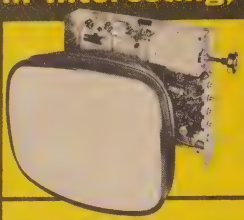

YOU BUILD This 17 Inch Television Receiver

As part of your NRI course you can get all components, tubes, including 17" picture tube, to build this latest style Television receiver; get actual practice on TV circuits.

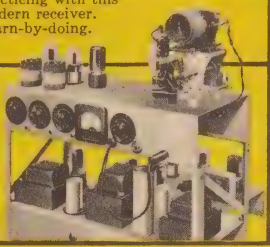

YOU BUILD Broadcasting Transmitter

As part of NRI Communications Course you build this low power Transmitter, learn commercial broadcasting operators' methods, procedures. Train for your FCC Commercial Operator's License.

YOU BUILD Vacuum Tube Voltmeter

Use it to earn extra cash fixing neighbors' sets; bring to life theory you learn from NRI's easy-to-understand texts.

For Higher Pay, Better Jobs Be a TV-Radio-Electronic Technician

Servicing Needs More Trained Men

Portable TV, Hi-Fi, Transistor Radios, Color TV are making new demands for trained Technicians. Good opportunities for spare time earnings or a business of your own.

Broadcasting Offers Satisfying Careers

4000 TV and Radio stations offer interesting positions. Govt. Radio, Aviation, Police, Two-Way Communications are growing fields. Trained Radio-TV Operators have a bright future.

J. E. Smith, Founder

Train at Home the NRI Way Famous for Over 40 Years

NRI is America's oldest and largest home study Television-Radio school. The more than 40 years' experience training men for success, the outstanding record and reputation of this school—benefits you in many ways. NRI methods are tested, proven. Successful graduates are everywhere, from coast to coast, in small towns and big cities. You train in your own home, keep your present job while learning. Many successful NRI men did not finish high school. Let us send you an actual lesson, judge for yourself how easy it is to learn.

No Experience Necessary—NRI Sends Many Kits for Practical Experience

You don't have to know anything about electricity or Radio to understand and succeed with N R I Course. Clearly written, well-illustrated NRI lessons teach TV-Radio-Electronic principles. You get NRI kits for actual experience. All equipment is yours to keep. You learn-by-doing. Mailing the postage-free card may be one of the most important acts of your life. Do it now. Reasonable tuition. Low monthly payments available. Address: **NATIONAL RADIO INSTITUTE, Washington 16, D. C.**

NRI Graduates Do Important Work

Now Quality Control Chief
"Had no other training in Radio before enrolling, obtained job working on TV amplifiers before finishing course. Now Quality Control Chief." T. R. Pavaloro, Norwich, N. Y.

NRI Course Easy to Understand
"I opened my own shop before receiving my diploma. I have had to hire extra help. I am independent in my own business." D. P. Cressey, Stockton, Cal.

Works on Color-TV
"NRI changed my whole life. If I had not taken the course, probably would still be a fireman, struggling along. Now Control Supervisor at WRCA - TV." J. F. Meline, NewYork, N.Y.

FIRST CLASS
Permit No. 20-R
(Sec. 34.9, P. L. & R.)
Washington, D.C.

BUSINESS REPLY CARD
No Postage Stamp Necessary if Mailed in the United States

POSTAGE WILL BE PAID BY
NATIONAL RADIO INSTITUTE
3939 Wisconsin Avenue
Washington 16, D.C.

SAMPLE LESSON
64-page CATALOG
both FREE

SEE OTHER SIDE

you are correct. But since the layman is not able to distinguish a qualified shop from a makeshift one, he is not in a position to switch to a better shop.

Therefore, what usually happens is this: People are scared away from service shops in general because of the incompetence of a few. Good service potential is lost as the incompetent shop informs its customer that the set cannot be fixed, or that it is cheaper to buy a new one.

Since my article, "The Facts About the Cost of TV Repairs," appeared in the June 28 *TV Guide*, I have been swamped with mail from TV owners. The majority of the letters were concerned with the problem of how to tell a qualified shop from a makeshift one. This avalanche of mail drove home to me the point that the real backbone of our industry, the dedicated technician, can never obtain the respect and economic standing that he so sorely deserves—unless we make a concentrated effort to accredit all qualified shops on a national basis.

Now that we are in the era of color TV, I think it is a fitting time for a national fellowship of qualified technicians to work toward this objective. I shall be most happy to cooperate with sincere service organizations and individuals willing to work for this objective. Stand up and be counted!

We should also work with state and municipal law enforcement agencies to help expose known dishonest operators.

As individuals we must bring the Ten Commandments into the marketplace for world peace—yes, world peace starts at home. We must not be satisfied with just what is legally right, but must insist on what is *morally* right.

Hudson Falls, N. Y. MELVIN COHEN

TV SERVICE BLUES

Dear Editor:

When I broke the vhf fine tuner dial cord on my 1957 RCA 21D744, I called a "basement repair man" who put on a new one. It lasted long enough for me to tune in two stations. A recall resulted in a second repair which lasted about the same length of time. Charge: $3.

I then called on my dealer. He pulled the set into the shop and installed a new cord. It slipped from the time I touched the dial. After a heated session, he returned the set to the shop and soldered a bronze cable in. It broke the first evening. Charge: $15.

I then called in a second dealer. He took the set in and cleaned off the solder and added an idler pulley—the cloth type—which lasted an evening. After a recall he put some "gook" on the belt and gave it more tension. Charge: $16.

It is still slipping. I will have to put one on myself to get it right. Thirty-four dollars and six service calls is just a little too much for me!

Rochester, N.Y. ROBERT Z. BARNEY

END

The features that have long made JBL loudspeakers the most wanted in the world for monaural systems are doubly important for stereo reproduction:

BEST

HIGH EFFICIENCY is synonymous with JBL. The JBL 15″ Model D130 with 4″ voice coil is the most efficient extended range loudspeaker made. The high efficiency of all JBL precision transducers is largely responsible for their smooth, accurate response and unequalled transient reproduction. Now it is found to have great practical significance when you consider the power requirements for your stereo system.

FOR

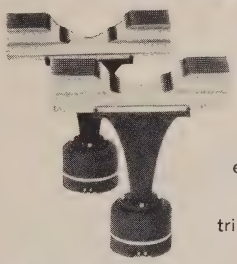

WIDE ANGLE DISTRIBUTION with smooth coverage of equal intensity regardless of frequency is best achieved with a JBL acoustical lens. A pair of model 375 high frequency drivers fitted with exponential horns and serpentine lenses, the kind used in the JBL Hartsfield, will distribute "the stereo frequencies" evenly over a broad area.

STEREO

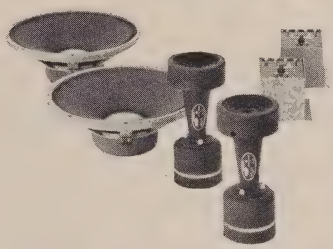

PROGRESSIVE PURCHASE extended range unit first, high frequency unit and dividing network later—makes it possible to build in logical steps to the ultimate in high fidelity sound—a JBL Signature two-way divided network system for each channel in your stereo system.

TOO!

And fundamentally, since you must in any case use twice the number of speakers as before, you will prefer JBL speakers for their clean, precision response. Write for your free copy of the complete JBL catalog and the name of the authorized JBL audio specialist in your community.

JBL

JAMES B. LANSING SOUND, INC. / 3249 CASITAS AVE., LOS ANGELES 39, CALIFORNIA

MAKE SURE YOUR NEW PICTURE TUBE IS A
SILVER SCREEN 85
IMPORTANT NOTICE
THERE'S A BIG DIFFERENCE IN TELEVISION PICTURE TUBES

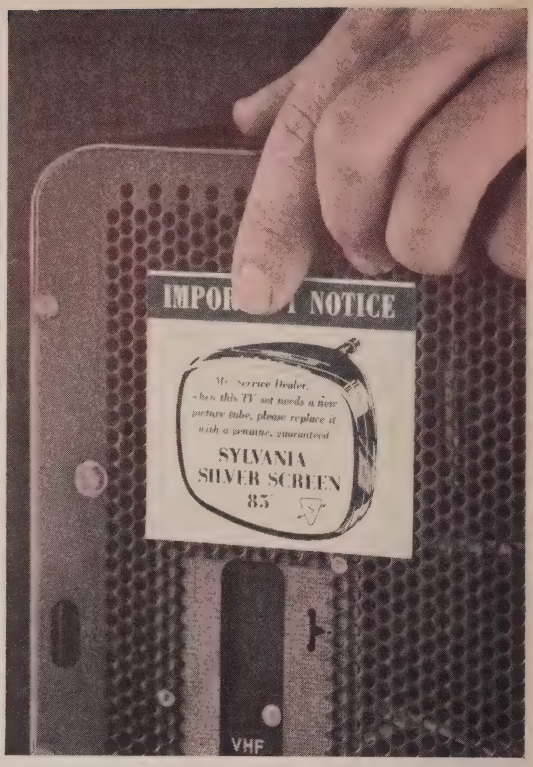

This label is your signal that a value-minded customer has been sold up to Silver Screen 85.

New consumer booklet from Sylvania helps you

SELL UP TO SILVER SCREEN 85

Free booklet tells the story of Silver Screen 85's superior performance—detachable sticker lets the consumer tell you he's *presold* on Silver Screen 85

Leave a copy on every service call or make a complete mailing to your customers and prospects. Either way, Sylvania's new booklet, "There's A Big Difference In Television Picture Tubes," can help you sell up to more profits through more Silver Screen 85 sales.

In layman's language, this booklet details the difference between Silver Screen 85 and cut-rate off-brand tubes. It's chock-full of facts as they were revealed in Sylvania's recent test of a nationwide sample. What's more, there's a handy sticker on the back of each booklet for the customer to attach to the back of his TV set. This is your signal that he's *presold up* to Silver Screen 85.

Get on the bandwagon. Let Sylvania help you sell up. Give each of your customers and prospects a copy of this new booklet. It's available free, complete with mailing envelope, from your Sylvania Distributor. Or write for a sample copy.

Bill Shipley's your No. 1 Salesman in the industry's biggest consumer advertising campaign.

SYLVANIA

SYLVANIA ELECTRIC PRODUCTS INC.
1740 Broadway, New York 19, N. Y.
In Canada: Sylvania Electric (Canada) Ltd.
University Tower Bldg., Montreal

LIGHTING • TELEVISION • RADIO • ELECTRONICS • PHOTOGRAPHY • ATOMIC ENERGY • CHEMISTRY-METALLURGY

WE'RE MAKING IT EASIER THAN EVER TO BECOME A WELL PAID

RADIO-TELEVISION SERVICE TECHNICIAN

NOW – Just $6 Starts You Training in RADIO-TELEVISION

the SPRAYBERRY "Learn-by-Doing" Way . . .

25 BIG, COMPLETE KITS of PARTS & EQUIPMENT

To help you learn *fast* the practical side of Radio-Television, we send you expertly engineered training kits to test and assemble for interesting, valuable shop-bench practice!

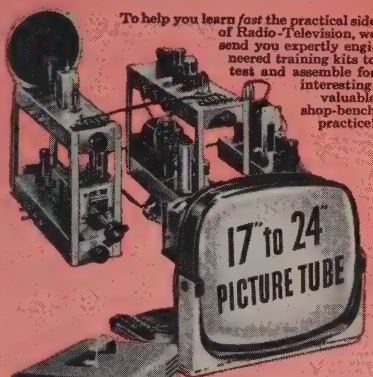

- The new Sprayberry Training Television Receiver, built and tested in 5 sections.
- Now offered . . . this fine modern oscilloscope.
- You build this powerful two-band superheterodyne radio receiver.

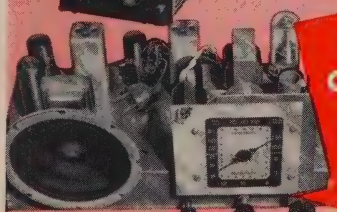

Big New CATALOG AND Sample Lesson FREE!

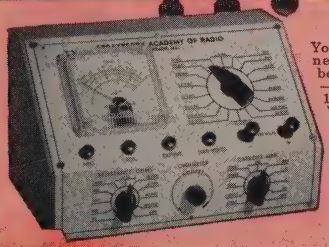

You build the new Sprayberry tester—a complete 18-range Volt-Ohm-Milliammeter test meter.

★ ★ ★ ★ **This great industry is begging for trained men . . . to step into good paying jobs or a profitable business of their own! Our new plan opens the doors of Radio-Television wide to every ambitious man who is ready to act at once!**

Men by the thousands... trained Radio-Television Service Technicians...are needed at once! Perhaps you've thought about entering this interesting, top paying field, but lack of ready money held you back. Now—*just $6 enrolls you* for America's finest, most up to date home study training in Radio-Television! Unbelievable? No, the explanation is simple! We believe Radio-Television *must* have the additional men it needs as quickly as possible. We are willing to do our part by making Sprayberry Training available for less money down and on easier terms than ever before. This is your big opportunity to get the training you need...to step into a fine job or your own Radio-Television Service Business.

Complete Facts Free—Act Now; Offer Limited

Only a limited number of students may be accepted on this liberal and unusual basis. We urge you to act at once...mail the coupon below and get complete details plus our big new catalog and an actual sample lesson—*all free.* No obligation...no salesman will bother you.

HOME STUDY TRAINING IN SPARE TIME

Under world-famous 27-year old Sprayberry Plan, you learn entirely at home in spare time. You keep on with your present job and income. You train as fast or as slowly as you wish. You get valuable kits of parts and equipment for priceless shop-bench practice. And everything you receive, lessons and equipment alike, is all yours to keep.

LET US PROVE HOW EASILY YOU CAN LEARN!

Radio-Television needs YOU! And Sprayberry is ready to train you on better, easier terms, that any ambitious man can afford. *Just $6 starts you!* Mail coupon today... let the facts speak for themselves. You have everything to gain. Let us prove the kind of opportunity that's in store for you!

SPRAYBERRY Academy of Radio-Television
1512 Jarvis Avenue, Dept. 20-N, Chicago 26, Illinois

Mail This Coupon Now—No Salesman Will Call

Sprayberry Academy of Radio-Television
Dept. 20-N, 1512 W. Jarvis Ave., Chicago 26, Ill.

Please rush all information on your ALL-NEW Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me. Include New Catalog and Sample Lesson FREE.

NAME..... Age.....

ADDRESS.....

CITY..... ZONE ..... STATE.....

New amplifier battles "noise"

Four-stage junction diode amplifier was developed at Bell Telephone Laboratories by Rudolf Engelbrecht for military applications. Operates on the "varactor" principle, utilizing the variable capacitance of diodes. With 400-mc. signal, the gain is 10 db. over the 100-mc. band.

The tremendous possibilities of semiconductor science are again illustrated by a recent development from Bell Telephone Laboratories. The development began with research which Bell Laboratories scientists were conducting for the U. S. Army Signal Corps. The objective was to reduce the "noise" in UHF and microwave receivers and thus increase their ability to pick up weak signals.

The scientists attacked the problem by conducting a thorough study of the capabilities of semiconductor junction diodes. These studies led to the conclusion that junction diodes could be made to amplify efficiently at UHF and microwave frequencies. This was something that had never been done before. The theory indicated that such an amplifier would be exceptionally free of noise.

At Bell Laboratories, development engineers proved the point by developing a new kind of amplifier in which the active elements are junction diodes. As predicted, it is extremely low in noise and efficiently amplifies over a wide band of frequencies.

The new amplifier is now being developed for U. S. Army Ordnance radar equipment. But it has numerous other possibilities. In radio astronomy, for example, it could be used to detect weaker signals from outer space. In telephony, it offers a way to increase the distance between relay stations in line-of-sight or over-the-horizon communications.

BELL TELEPHONE LABORATORIES

WORLD CENTER OF COMMUNICATIONS RESEARCH AND DEVELOPMENT

ownership of a complete and currently maintained

PHOTOFACT SERVICE DATA LIBRARY SPELLS SUCCESS FOR SERVICE TECHNICIANS

here's actual proof from the men who know!

"Sams PHOTOFACT is a must in my shop and I place it in highest regard. It is my most reliable service instrument if I may call it that, in the entire shop... makes for much faster servicing..."

—Gordon La Vier
La Vier Television
Midland, Mich.

"PHOTOFACT cuts our bench work to a minimum. Gives us a chance to realize a profit instead of a loss."

—Lee P. Shumavon
Shumavon Service
Dorchester, Mass.

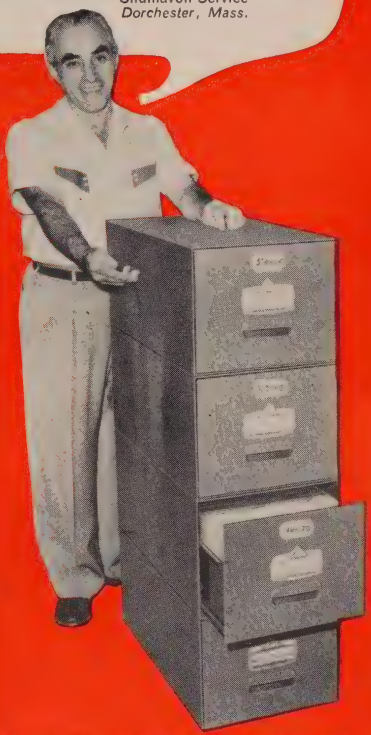

"I spend less time in diagnosis and repair of all bench jobs... would hate to think of Service without a good service library such as Sams PHOTOFACT."

—Gerry Brown
Brown Electronic Service
Ottumwa, Iowa

These are just a few of the hundreds of "Success with PHOTOFACT" letters in our files. From coast-to-coast, Service Technicians everywhere are enjoying the profit-making advantages of a complete PHOTOFACT Library. If you're not yet among them, see your Sams Distributor today, or write to Howard W. Sams for full details.

NEW! EASY-BUY PLAN

—the money-saving way to build your complete profit-making PHOTOFACT Library!

NO INTEREST—NO CARRYING CHARGE—AS LITTLE AS $10 DOWN

FREE! VALUABLE STEEL FILE CABINETS FOR REGULAR PHOTOFACT SUBSCRIBERS AND PHOTOFACT LIBRARY PURCHASERS

GET THE FULL DETAILS

HOWARD W. SAMS & CO., INC.
2205 E. 46th St., Indianapolis 6, Ind.

☐ Send details on PHOTOFACT Easy-Buy Plan and FREE File Cabinet offer.
☐ I'm a Service Technician: ☐ full-time; ☐ part time

My Distributor is: _____

Shop name _____

Attn. _____

Address _____

City _____ Zone ____ State _____

see what's new in electronic kits..

SEE THEM IN ALLIED'S 1959 CATALOG . . . THE WORLD'S

FREE send for it!

typical **knight-kit** values . . . see these and dozens of

knight-kit Stereo Adapter Control Kit..... Model Y-778 **$9.95**

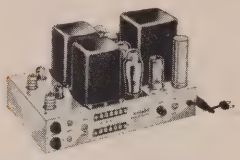

knight-kit 60-Watt Stereo Hi-Fi Amplifier Kit.... Model Y-777 **$84.50**

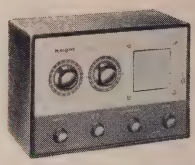

knight-kit "Space Spanner" 2-Band Receiver Kit..... Model Y-259 **$18.95**

knight-kit Stereo Deluxe Preamp Kit..... Model Y-776 **$62.50**

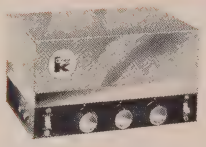

knight-kit 12-Watt Hi-Fi Amplifier Kit..... Model Y-784 **$19.95**
(less case)

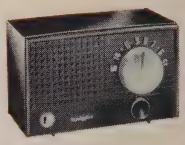

knight-kit "Ranger III" AC-DC Radio Kit..... Model Y-736 **$16.95**

knight-kit "Span-Master" 4-Band Receiver Kit..... Model Y-258 **$24.95**

knight-kit "Ranger" Clock-Radio Kit..... Model Y-737 **$24.95**

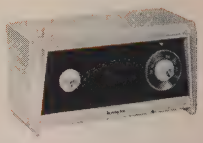

knight-kit "Ranger" Radio-Intercom Kit..... Model Y-739 **$27.50**

EASY TERMS AVAILABLE ON knight-kit ORDERS AS LOW AS $20

there's a money-saving knight-kit

SEE PAGE AFTER PAGE OF FASCINATING KITS, INCLUDING:

HI-FI KITS
18-Watt Amplifier
30-Watt Amplifier
FM-AM Tuner
FM Tuner
Hi-Fi Preamplifier
25-Watt Basic Amplifier
2-Way Speaker Systems
3-Way Speaker Systems

HOBBY KITS
Printed Circuit Radio
"Ocean-Hopper" Radio
5-Transistor Portable
2-Transistor Pocket Set
Transistor Lab Kit
1-Transistor Radio
2-Way Intercom
Photoelectronic System
Crystal Receiver
Wireless Broadcaster
Electronic Photoflash

INSTRUMENT KITS
5" Oscilloscopes
Vacuum Tube Voltmeter
Tube Testers
Volt-Ohm-Milliammeters
RF Signal Generator
Signal Tracer
Audio Generator
Sweep Generator
Capacitor Checker
R/C Tester
(cont'd. on next page)

ALLIED RADIO

see the outstanding 1959 knight®-kits

AN **ALLIED RADIO** PRODUCT

LEADING ELECTRONIC SUPPLY GUIDE

DO-IT-YOURSELF
WITH QUALITY
knight-kits
SAVE UP TO 50%

LOWEST IN COST: ALLIED'S giant buying power passes biggest savings on to you—you do the easy assembly yourself and your finished equipment equals the performance, appearance and quality of factory-built units selling for several times the low KNIGHT-KIT price. You save most with KNIGHT-KITS.

EASIEST TO BUILD: KNIGHT-KIT "Step-and-Check" instruction manuals with wall-sized picture diagrams are marvels of clarity—it's like having a good instructor at your side, guiding you every step of the way. You don't have to be an "expert" to enjoy building a KNIGHT-KIT; all parts are clearly marked and identified; wires are pre-cut to size, stripped and colored for easy proper use; printed circuitry and printed-circuit switches eliminate complex wiring. You'll have only the highest praise for KNIGHT-KIT ease of assembly. You'll be proud of your work.

LATEST DESIGN: We design the latest circuitry into our KNIGHT-KITS to achieve top-quality performance. We field-test each kit to assure perfection. We apply quality control standards to every step of our kit manufacturing process. Tried and proved professional design, precise manufacturing skill and premium quality parts help to insure your building success.

THE KITS WITH THE MONEY-BACK GUARANTEE

EASY TERMS ON ORDERS OF $20 OR MORE

other EASY-TO-BUILD kits

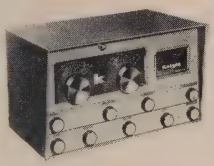

knight-kit Amateur Communications Receiver... Model Y-726 **$104.50**

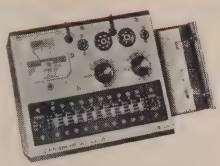

knight-kit "400" Tube Checker Kit..... Model Y-707 **$19.95**

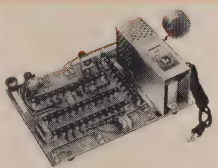

knight-kit 12-in-1 Electronic Lab Kit..... Model Y-272 **$14.95**

for every need

Transistor Checker
Flyback Checker
R/C Substitution Boxes
Voltage Calibrator
Battery Eliminator

AMATEUR KITS

50-Watt Transmitter
Self-Powered VFO
100 kc Crystal Calibrator
RF "Z" Bridge
Code Practice Oscillator

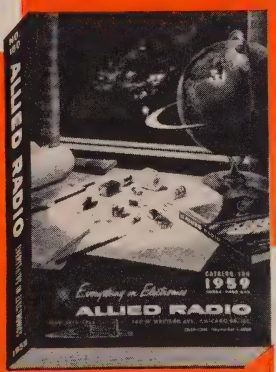

the world's largest electronic supply house

Our 38th Year

FREE send for the 452-page
1959 ALLIED CATALOG

Send for the value-packed 1959 ALLIED Catalog featuring the complete KNIGHT-KIT line. See this leading Buying Guide for everything in Electronics. Write for your FREE copy today.

ALLIED RADIO CORP., Dept. 132-L8
100 N. Western Ave., Chicago 80, Ill.

☐ Send FREE ALLIED 452-Page 1959 Catalog

Name_____

Address_____

City_____ Zone____ State_____

ROHN Designs Amazing No. 25 Tower to reach new heights in tower engineering

NEW GENERAL-PURPOSE COMMUNICATION OR HEAVY-DUTY TV TOWER

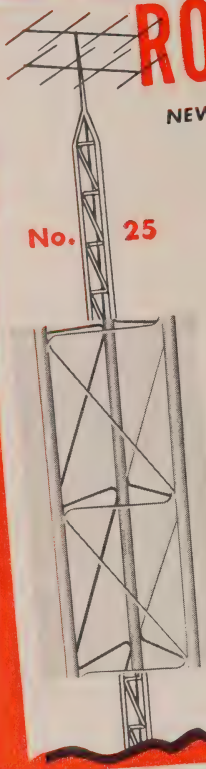

ROHN now offers a tower a full 33% stronger and more durable than similar sized and similar type towers that are found on the market today!

These amazing results are achieved through using **heavier-duty** side rail tubing, **quality** steel that is of the **highest** grade and a new "zig-zag" cross bracing **design.**

The strength of this tower allows it to be self-supporting under most conditions to 50′ and under guyed conditions up to 150′. The tower has been built to fit a tremendously wide range of needs in communications, amateur use and as a heavy-duty TV tower.

FLASH! The "RohnKote" enameling plant is in operation and ROHN products are available not only in **HOT-DIPPED GALVANIZING** but also in a specially developed 6-step enameling process known as "RohnKote".

NOW! 10 Different Lines of ROHN TOWERS, Including:

No. 6

Widely used for home TV, this tower features "magic triangle" cross bracing construction.

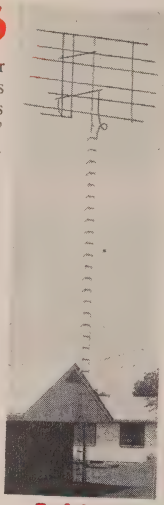

Packaged Towers in which the sections nestle inside each other.

No. 40

Heavy-duty communications tower suitable self-supporting at heights up to 60′ or guyed as high as 300′. Ideal for communications uses of all types, microwave, radio telephone, etc.

No. 20 & 30

Heavy-duty communications towers in RohnKote enamel.

Fold-Over Towers

Ideal for amateurs and experimenters inasmuch as the tower folds over for convenient antenna changing, etc. Supplied in both medium and heavy-duty sizes to handle practically any size beam.

Look to ROHN for these requirements, too:

A wide line of all types of accessories for towers is available but in addition, ROHN produces a complete line of:

MASTS

ROHN masts are outstanding in design and have special features that make them the best in the field and in addition, are as low or lower in cost than any other.

TUBING

Complete line of tubing, either plain or with 6" expanded end; in 10′ and 5′ length; 16 or 18 gauge; and in either hot-dipped galvanized or "RohnKote" enameling.

ROOF TOWERS

Specially designed roof towers have received tremendously wide acceptance and are available from heights of 2½′ to 10′.

BASES

A wide selection for mast and other type installations; wall mounts—for inexpensive installations; gable mounts; special mounts for antennas; drive-in ground mounts; and dozens of other specially designed items.

Make sure you have full details, catalog and prices on the entire ROHN line. Contact the ROHN representative in your area, or distributor, or contact:

ROHN *Manufacturing Company*

116 LIMESTONE, BELLEVUE

PEORIA, ILLINOIS PHONE 4-9156

STEREO AND MONAURAL

the experts say... in HI-FI the best buys are

EICO®

World-famous EICO advantages guarantee your complete satisfaction:

- Advanced engineering • Finest quality components
- "Beginner-Tested," easy step-by-step instructions
- LIFETIME service & calibration guarantee
- IN STOCK — Compare, then take home any EICO equipment—right "off the shelf"—from 1900 neighborhood EICO dealers.

Stereo Preamplifier HF85
FM Tuner HFT90
Stereo Amplifier-Preamp HF81
Monaural Integrated Amplifiers: 50, 30, 20, and 12-Watt (use 2 for Stereo)
Bookshelf Speaker System HFS1
Speaker System HFS2 36" H x 15¼" W x 11½" D
Monaural Preamplifiers: HF65, HF61 (stack 2 for Stereo)
Monaural Power Amplifiers: 60, 50, 35, 30, 22 and 14-Watt (use 2 for Stereo)
MEMBER INSTITUTE OF HIGH FIDELITY MANUFACTURERS INC.

Over 1 MILLION EICO instruments in use throughout the world.

NEW STEREOPHONIC EQUIPMENT

HF85: Stereo Dual Preamplifier is a complete stereo control system in "low silhouette" design adaptable to any type of installation. Selects, preamplifies, controls any stereo source—tape, discs, broadcasts. Superb variable crossover, feedback tone controls driven by feedback amplifier pairs in each channel. Distortion borders on unmeasurable even at high output levels. Separate lo-level input in each channel for mag. phono, tape head, mike. Separate hi-level inputs for AM & FM tuners & FM Multiplex. One each auxiliary A & B input in each channel. Independent level, bass & treble controls in each channel may be operated together with built-in clutch. Switched-in loudness compensator. Function Selector permits hearing each stereo channel individually, and reversing them; also use of unit for stereo or monophonic play. Full-wave rectifier tube power supply. 5-12AX7/ECC83, 1-6X4. Works with any 2 high-quality power amplifiers such as EICO, HF14, HF22, HF30, HF35, HF50, HF60. Kit **$39.95.** Wired **$64.95.** Includes cover.

HF81: Stereo Dual Amplifier-Preamplifier selects, amplifies & controls any stereo source—tape, discs, broadcasts—& feeds it thru self-contained dual 14W amplifiers to a pair of speakers. Monophonically: 28 watts for your speakers; complete stereo preamp. Ganged level controls, separate focus (balance) control, independent full-range bass & treble controls for each channel. Identical Williamson-type, push-pull EL84 power amplifiers, excellent output transformers. "Service Selector" switch permits one preamp-control section to drive the internal power amplifiers while other preamp-control section is left free to drive your existing external amplifier. Kit **$69.95.** Wired **$109.95.** Incl. cover.

MONAURAL PREAMPLIFIERS (stack 2 for Stereo)

NEW HF65: superb new design, Inputs for tape head, microphone, mag-phono cartridge & hi-level sources. IM distortion 0.04% @ 2V out. Attractive "low silhouette" design. **HF65A** Kit **$29.95,** Wired **$44.95. HF65** (with power supply) Kit **$33.95.** Wired **$49.95.**

HF61: "Rivals the most expensive preamps" — Marshall, AUDIOCRAFT. **HF61A** Kit **$24.95,** Wired **$37.95, HF61** (with power supply) Kit **$29.95.** Wired **$44.95.**

MONAURAL POWER AMPLIFIERS (use 2 for STEREO)

HF60: 60-Watt Ultra Linear Power Amplifier with Acro TO-330 Output Xfmr.; **"One of the best-performing amplifiers extant; an excellent buy."** AUDIOCRAFT Kit Report. Kit **$72.95.** Wired **$99.95.** Cover E-2 $4.50.

HF50: 50-Watt Ultra Linear Power Amplifier with extremely high quality Chicago Standard Output Transformer. Identical in every other respect to HF60, same specs at 50W. Kit **$57.95.** Wired **$87.95.** Cover E-2 $4.50.

NEW HF35: 35-Watt Ultra-Linear Power Amplifier. Kit **$47.95.** Wired **$72.95.** Cover E-2 $4.50.

HF30: 30-Watt Power Amplifier. Kit **$39.95.** Wired **$62.95.** Cover E-3 $3.95.

NEW HF22: 22-Watt Power Amplifier. Kit **$38.95.** Wired **$61.95.** Cover E-2 $4.50.

NEW HF14: 14-Watt Power Amplifier. Kit **$23.50.** Wired **$41.50.** Cover E-6 $4.50.

MONAURAL INTEGRATED AMPLIFIERS (use 2 for STEREO)

HF52: 50-Watt Integrated Amplifier with complete "front end" facilities & Chicago Standard Output Transformer. **"Excellent value"**—Hirsch-Houck Labs. Kit **$69.95.** Wired **$109.95.** Cover E-1 $4.50.

HF32: 30-Watt Integrated Amplifier. Kit **$57.95.** Wired **$89.95.** Both include cover.

HF20: 20-Watt Integrated Amplifier. "Well-engineered" — Stocklin, RADIO TV NEWS. Kit **$49.95.** Wired **$79.95.** Cover E-1 $4.50.

HF12: 12-Watt Integrated Amplifier. "Packs a wallop"—POP. ELECTRONICS. Kit **$34.95.** Wired **$57.95.**

SPEAKER SYSTEMS (use 2 for STEREO)

HFS2: Natural bass 30-200 cps via slot-loaded 12-ft. split conical bass horn. Middles & lower highs: front radiation from 8½" edge-damped cone. Distortionless spike-shaped super-tweeter radiates omni-directionally. Flat 45-20,000 cps, useful 30-40,000 cps. 16 ohms. HWD 36", 15¼", 11½". **"Eminently musical; would suggest unusual suitability for stereo."**—Holt, HIGH FIDELITY. Completely factory-built: Walnut or Mahogany. **$139.95;** Blonde, **$144.95.**

HFS1: Bookshelf Speaker System, complete with factory-built cabinet. Jensen 8" woofer, matching Jensen compression-driver exponential horn tweeter. Smooth clean bass; crisp extended highs. 70-12,000 cps range. Capacity 25 w. 8 ohms. HWD: 11" x 23" x 9". Wiring time 15 min. Price **$39.95.**

FM TUNER

HFT90: surpasses wired tuners up to 3X its cost. Prewired, pre-aligned, temperature-compensated "front end" — drift-free. Precision "eye-tronic" tuning. Sensitivity 1.5 uv for 20 db quieting — 6X that of other kit tuners. Response 20-20,000 cps ±1 db. K-follower & multiplex outputs. **"One of the best buys you can get in high fidelity kits."** — AUDIOCRAFT KIT REPORT. Kit **$39.95***. Wired **$65.95***. Cover $3.95.

* LESS COVER, F.E.T. INCL.

BEFORE YOU BUY, COMPARE:

You may examine the complete EICO line at any of 1900 neigborhood EICO distributors coast to coast. Compare critically with equipment several times the EICO cost — then you judge. You'll see why the experts recommend EICO, kit or wired, as your best buy.

EICO, 33-00 NORTHERN BLVD., L.I.C. 1, N.Y.
Fill out coupon on other side for FREE CATALOG

Add 5% in the West.

Copyright 1958 by Electronic Instr. Co., Inc. 33-00 N. Blvd., L.I.C. 1, N.Y.

the specs prove it . . your BEST BUY is EICO®

for COLOR & Monochrome TV servicing

FREE CATALOG

shows you HOW TO SAVE 50% on 50 models of top quality professional test equipment.

MAIL COUPON NOW!

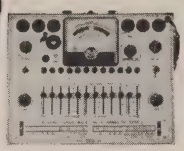

NEW! DYNAMIC CONDUCTANCE TUBE & TRANSISTOR TESTER #666

KIT $69.95 WIRED $109.95

COMPLETE with steel cover and handle.

SPEED, ease, unexcelled accuracy & thoroughness. **Tests all receiving tubes** (and picture tubes with adapter). **Composite indication of Gm, Gp & peak emission. Simultaneous** set of any 1 of 4 combinations of 3 plate voltages, 3 screen voltages, 3 ranges of continuously variable grid voltage (with 5% accurate pot). **New series-string voltages:** for 600, 450, 300 ma types. **Sensitive** 200 ua meter. **5 ranges meter sensitivity** (1% shunts & 5% pot). **10 SIX-position lever switches:** freepoint connection of each tube pin. **10 pushbuttons: rapid** insert of any tube element in leakage test circuit & speedy sel. of individual sections of multi-section tubes in merit tests. **Direct-reading** of inter-element leakage **in ohms. New gear-driven rollchart. Checks n-p-n & p-n-p transistors:** separate meter readings of **collector leakage current & Beta** using internal dc power supply. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet. **CRA Adapter $4.50**

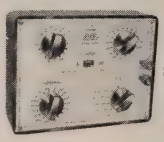

New!

Series/Parallel **R-C COMBINATION BOX #1140**

KIT $13.95 WIRED $19.95

TUBE TESTER #625

KIT $34.95 Wired $49.95

- tests 600 mil series string type tubes
- illuminated roll-chart

Pix Tube Test Adapter $4.50

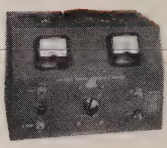

6V & 12V BATTERY ELIMINATOR & CHARGER #1050

KIT $29.95 WIRED $38.95

Extra-filtered for transistor equipt. **#1060 KIT $38.95 WIRED $47.95**

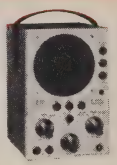

New!

Miniaturized **MULTI-SIGNAL TRACER #145A**

KIT $19.95 WIRED $28.95

20,000 Ohms/Volt V-O-M #666

KIT 24.95 Wired $29.95

1000 Ohms/Volt V-O-M #536

KIT $12.90 Wired $14.90

Reads 0.5 ohms —500 megs, 10 mmfd—5000 mfd, power factor-

KIT $19.95 Wired $29.95

R-C BRIDGE & R-C-L COMPARATOR #950B

NEW! TV-FM SWEEP GENERATOR & MARKER #368

KIT $69.95 WIRED $119.95

Entirely electronic sweep circuit (no mechanical devices) with accurately-biased **incereductor** for excellent linearity. **Extremely flat** RF output; **new AGC circuit** automatically adjusts osc. for max. output on each band with min. ampl. variations. **Exceptional tuning accuracy:** edge-lit hairlines **eliminate** parallax. **Swept Osc. Range 3-216 mc in 5 fund. bands. Variable Marker Range 2-75 mc in 3 fund. bands;** 60-225 mc on harmonic band. **4.5 mc Xtal Marker Osc., xtal supplied.** Ext. Marker provision. Sweep Width 0-3 mc lowest max. deviation to 0-30 mc highest max. dev; 2-way blanking. Narrow range phasing. Attenuators: Marker Size, RF Fine, RF Coarse (4-step decade). Cables: output, 'scope horiz., 'scope vertical. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet.

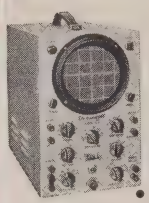

COLOR and Monochrome DC to 5 MC LAB & TV 5" OSCILLOSCOPE #460

KIT $79.95 WIRED $129.50

- **Features DC Amplifiers!**

Flat from DC-4.5 mc, usable to 10 mc. **VERT. AMPL.:** sens. 25 rms mv/in; input Z 3 megs; direct-coupled & push-pull **thruout;** K-follower coupling bet. stages; 4-step freq-compensated attenuator up to 1000:1. **SWEEP:** perfectly linear 10 cps-100 kc (ext. cap. for range to 1 cps); **preset TV V & H positions;** auto. sync. ampl. & lim. **PLUS:** direct or cap. coupling; bal. or unbal. inputs; edge-lit engraved lucite screen; dimmer; filter; bezel fits std photo equipt. High intensity trace CRT. 0.06 usec rise time. Push-pull hor. ampl., flat to 400 kc, sens. 0.6 rms mv/in. Built-in volt. calib. Z-axis mod. Sawtooth & 60 cps outputs. Astig. control. Retrace blanking. Phasing control.

5" PUSH-PULL Oscilloscope =425: Kit $44.95, Wired $79.95.
7" PUSH-PULL Oscilloscope =470: Kit $79.95, Wired $129.50.

NEW! RF SIGNAL GENERATOR #324

KIT $26.95 WIRED $39.95

150 kc to 435 mc with ONE generator! Better value than generators selling at 2 or 3 times its cost! Ideal for IF-RF alignment, signal tracing & trouble-shooting of TV, FM, AM sets; marker gen.; 400 cps audio testing; lab. work. **6 fund. ranges: 150-400 kc, 400-1200 kc, 1.2-3.5 mc, 3.5-11 mc, 11-37 mc, 37-145 mc; 1 harmonic band 111-435 mc. Freq. accurate to ±1.5%;** 6:1 vernier tuning & excellent spread at most important alignment freqs. **Etched tuning dial,** plexiglass windows, **edge-lit hairlines.** Colpitts RF osc. **directly plate-modulated by K-follower** for improved mod. **Variable depth of int. mod. 0-50%** by 400 cps Colpitts osc. **Variable gain ext. amplifier:** only 3.0 v needed for 30% mod. **Turret-mounted coils slug-tuned** for max. accuracy. Fine & Coarse (3-step) RF attenuators. RF output 100,000 uv; AF sine wave output to 10 v. 50-ohm output Z. 5-way jack-top binding posts for AF in/out; coaxial connector & shielded cable for RF out. 12AU7, 12AV7, selenium rectifier; xmfr-operated. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet.

NEW! PEAK-to-PEAK VTVM #232 & UNI-PROBE (pat. pend.)

KIT $29.95 WIRED $49.95

Half-turn of probe tip selects DC or AC-Ohms.

Uni-Probe — exclusive with EICO — only 1 probe performs all functions!

Latest circuitry, high sensitivity & precision, wide ranges & versatility. **Calibration without removing from cabinet.** New balanced bridge circuit. High Z input for negligible loading. 4½" meter, can't burn-out circuit. 7 **non-skip ranges on every function.** 4 functions: +DC Volts, −DC Volts, AC Volts, Ohms. Uniform 3 to 1 scale ratio for extreme wide-range accuracy. **Zero center.** One zero-adj. for all functions & ranges. **1% precision** ceramic multiplier resistors. Measure **directly** peak-to-peak voltage of complex & sine waves: 0-4, 14, 42, 140, 420, 1400, 4200. DC/RMS sine volts: 0-1.5, 5, 15, 50, 150, 500, 1500 (up to 30,000 v with HVP probe & 250 mc with PRF probe). Ohms: 0.2 ohms to 1000 megs. 12AU7, 6AL5, selenium rectifier; xfmr-operated. Deep-etched satin aluminum panel, rugged grey wrinkle steel cabinet.

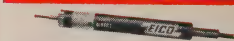

VTVM PROBES	KIT	Wired
Peak-to-Peak	$4.95	$6.95
RF	$3.75	$4.95
High Voltage Probe-1		$6.95
High Voltage Probe-2		$4.95
SCOPE PROBES		
Demodulator	$3.75	$5.75
Direct	$2.75	$3.95
Low Capacity	$3.75	$5.75

TURN PAGE FOR MORE EICO VALUES

Prices 5% higher on West Const.

EICO® Send for FREE CATALOG now

33-00 Northern Blvd., Long Island City 1, N.Y.

EICO, 33-00 Northern Blvd. Long Island City 1, N. Y. C-11

Show me HOW TO SAVE 50% on ☐ Test Instruments ☐ Hi-Fi ☐ Ham Gear. Send me FREE Catalog and name of neighborhood dealer.

Name.....

Address.....

City.....Zone.....State.....

OPPORTUNITIES IN ELECTRONICS

. . . Enterprise and Imagination the Keys to Electronics Fortune . . .

READERS frequently query the editor on opportunities in electronics today. They wish to go into the electronics business but do not know how to proceed. It is always difficult for an outsider to advise young men who wish to embark on a new undertaking in a new field. There are many requirements: education, ingenuity, enterprise and imagination, not to forget what is known in the vernacular as "guts." Even more important is the requirement of a nucleus—a *central idea.* Upon this a plan of action can then be evolved readily. Incidentally, no two persons will proceed exactly alike—the final how-to-do-it changes with each individual.

What about capital? Many successful beginners had little or none, but they were able to convince others of their integrity and ability and usually had little difficulty securing the money required. It is felt that rather than editorialize further on the subject, we should give some concrete examples of how others embarked into electronic enterprises. The factual thumbnail sketches of several outstanding men who made good might serve as a valuable guide to those who are seriously thinking of entering on an electronic business career.

MILTON JERROLD SHAPP, of Philadelphia, Pa., was a 34-year-old manufacturers' representative and a graduate engineer. At a "bull session" between technical discussions at the 1947 IRE show, Shapp conceived the Jerrold Electronics Corp., a firm which now does a business of over $5,000,000 a year. He discussed the idea of building a master antenna for use with a number of TV sets. After a year of discussion and study, Shapp formed the Jerrold Corp. with $500 in capital, and then designed and developed a multiset coupler. Today, he probably sells more master antenna systems than all other companies combined. Not only did he build master antennas—Shapp and his group proceeded to build community TV antennas to bring television to those in "shadowed" towns, in a similar manner that people receive telephone and power service. Today, more that 2,000,000 viewers in more than 600 communities receive their television service via community antennas, and Shapp claims that more than 85% of these systems use Jerrold Electronics Corp. equipment.

ALEXANDER M. PONIATOFF, of Redwood City, Calif., was a Russian political emigré who lived in Shanghai until 1927. A veteran of the Imperial Russian Navy, he emigrated to San Francisco where he became a General Electric development engineer and later worked for Dalmo Victor. He founded the Ampex Corp. in 1944 and manufactured precision electric motors for the Armed Forces. The first three letters in the name Ampex are his initials.

At the end of World War II, his concern was left without customers, and Poniatoff looked around for a new civilian product. He knew of the German successes with tape recording and, after scientific study, he turned his scientists and engineers to tape development. While his tape recorder was not the first in the US, it was one of the first to achieve the necessary fidelity for radio broadcasting. Bing Crosby tried it and decided to tape his shows prior to broadcasting. Thus began the tape revolution that changed radio broadcasting and phonograph recording methods almost overnight. Next, Ampex, despite its success and growth in the audio field, under Poniatoff's guidance determined to apply the same techniques to TV. They developed the first video tape recorder to be put to practical use. It was announced in 1956. Today, over 100 of these $45,000 machines are in use, yet Poniatoff looks to still further uses of these wide-band magnetic recorders in TV, motion pictures, instrumentation, the military and space. Ampex today is a $19,000,000 company.

BEN ADLER, of New Rochelle, N.Y., having worked with RCA and risen to manager of its test and measuring department, founded Adler Communications Laboratory in small rented headquarters in an unused shipyard in 1947. Convinced there was a need for a low-powered TV repeater for sparsely settled areas, he coined the word "translator," subsequently adopted by the FCC in its standards. To date he has produced 160 uhf and vhf translators now in use in the US, Canada, Mexico, Cuba, Brazil and Guam. His company is still the sole manufacturer of TV translators.

Adler Communications Laboratory now occupies a modern 4-acre research and development and manufacturing facility and has produced such diverse items as missile testers for the Navy, a complete 50-kw broadcast station on wheels for Radio Free Europe, a mobile communications system for use by the Atomic Energy Commission at the Nevada Proving Grounds. The company's willingness to attack tough problems has resulted in the addition of a half-dozen new products to the company's line in the past year.

MARTIN M. DECKER, Philadelphia, Pa., had no formal scientific training, but his experience in the Air Force convinced him there was going to be "unlimited opportunity for the development of electronics in many different directions." In 1951, in a small room in Philadelphia, he founded the Decker Aviation Corp., now the Decker Corp. which occupies a 9-acre site at Bala-Cynwyd, Pa., with more than 100 employees. The company's first business was modifying aircraft instruments for the US and Canadian Air Forces. In 1956, Decker refused a $5,000,000 offer for his company.

Among the devices developed by the Decker Corp. is the T-42 ionization transducer, a tiny glass tube which converts a mechanical change into a proportional electrical signal which can be recorded or used to open or close circuits. Then the company developed instruments utilizing the transducer for use in the Navy's IGY Aerobee-Hi rocket for measurements of outer-space atmospheric pressure, and for use in a rocket-borne capsule to record cosmic-ray data, 2,000 miles out in space. It is the heart of a flight simulator for intercontinental ballistic missiles, and, in medical electronics, it is used in the Decker Cardiodynameter, for body measurements in diagnosing heart and circulatory ailments. In addition to this, the CAA is considering equipping planes with a Decker system to help prevent mid-air collisions. Decker's work is in research and development only; manufacturing is done by others under subcontract. Last year's sales were more than $1,500,000.

DAVID F. SANDERS, of Plainfield, N.J., was one of three former Western Electric engineers who, shortly after World War II, founded Stavid Engineering Co. with a small research project for the Navy, which subsequently developed into a $200,000 design contract. Starting with a total of $10,000, which represented the savings of all three, this year the company, specializing in military electronics, is expected to realize $14,000,000 in sales. Stavid, under the leadership of Sanders, pioneered the "team system" of military contracting, and last year the Air Force's first major contract awarded on a team bid went to a group

(*Continued on page* 144)

Measuring cloud cover makes long-range weather reports possible, but it takes a lot of electronic gear crammed into a 20-inch sphere to do it

SATELLITE MEASURES CLOUD COVER

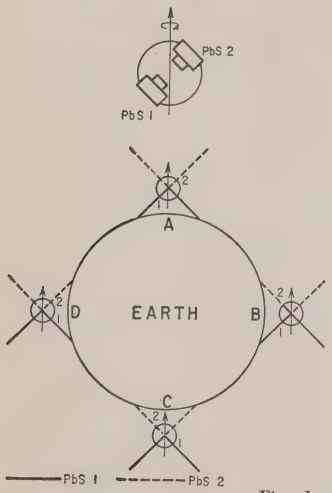

Fig. 1 — Photocell orientation at various points of the satellite's orbit.

By EDWARD RICH, JR. *

MANY contributions to the field of meteorology are being made in the IGY program. With the rapid advances of civilization, the need for reliable long-range weather predictions has increased. It is extremely important to know of impending major storms, hurricanes and typhoons, and their origin, speed and direction.

An electronic package has been designed at the US Army Signal Engineering Laboratory, Fort Monmouth, N. J., which will furnish sufficient cloud structure detail to enable meteorologists to plot the formation and movement of such storms. The package will be installed in a 20-inch sphere weighing 21 pounds. This *cloud-cover satellite* is designed to be launched in a Vanguard rocket.

The sphere is gold-plated both inside and out to reduce heat radiation losses from the internal package. But if the finish were 100% reflective, instrument temperatures would be too low for reliable operation. To adjust the amount of solar heat absorbed by the sphere, keeping instruments at operating temperatures, a dull film of silicon monoxide is deposited on the outside.

The basic operation of the cloud-cover instrumentation is not complicated. Light-sensitive lead sulphide cells in

* US Army Signal Research & Development Laboratory, Fort Monmouth, N. J.

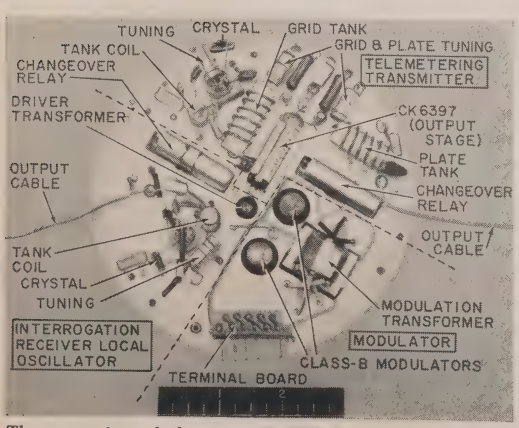

The transmitter deck.

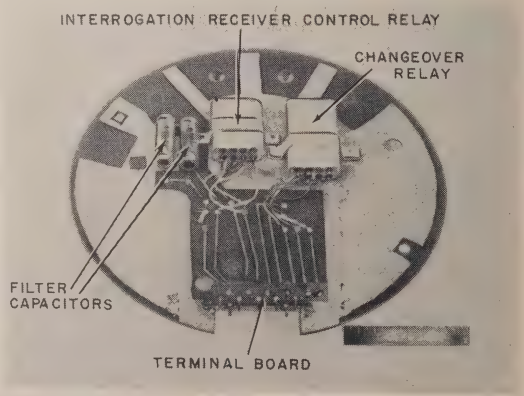

The relay control deck.

Ready to launch, the polished satellite is handled with soft gloves to avoid marring its finish.

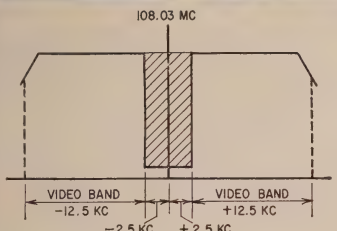

Fig. 2 — Transmitted signal response showing CW portion used for tracking.

the optical system convert the reflected light from the earth's cloud cover into electrical signals. The optical system consists of a pair of photosensitive detecting elements, which rotate around the sphere's axis (the vertical arrow running through the sphere) as it orbits. When the satellite is in position A, PbS 1 (1 in Fig. 1) scans the earth while PbS 2 (represented at 2) scans space. In position B, PbS 1 and 2 alternately scan the earth and space. When the satellite reaches C, PbS 2 scans the earth and PbS 1 space. At D, both cells again alternately scan the earth and space. So each of the detecting elements scans the earth, space, or earth and space, depending on the satellite's orbital position. The reflectivity, or *video* as it is called, of the surface scanned is translated into electrical signals. These can be interpreted in terms of the amount of cloud coverage over the area scanned. The signals are recorded on magnetic tape. When the satellite passes over a ground receiving station, the tape is played back and the information telemetered to the ground. A record–playback ratio of 1 to 50 compresses 50 minutes of daylight recording into the 1-minute period when the satellite is within receiving distance of a ground station.

Tracking and telemetering

The Minitrack system has been described before (see "Electronics and the IGY, Part II," RADIO-ELECTRONICS, March, 1958, page 82). The satellite is tracked by the interferometer method of measuring the phase angles of arrival at two separate antennas. To facilitate accurate fixes, a CW carrier must be used (see Fig. 2). This carrier, within a spread of ±2,500 cycles, must be free of modulation. Since the signal-to-noise ratio for a given power determines the usable bandwidth, the power available limits the bandwidth to 15 kc. Thus, for data transmission the net bandwidth is limited to 12.5 kc.

Because of the 1-to-50 speed ratio in the tape recorder, the actual frequency deviation allowed in the recording process can vary only between 50 and 290 cycles to satisfy the conditions of modulation. For this reason a subcarrier (290 cycles) is introduced and amplitude-modulated so the 50–290-cycle signal band will be recorded. This is done by modulating the 290-cycle subcarrier with the 0–240-cycle signal band available at the photocell. The variation in amplitude becomes proportional to the amount of reflected light gathered. Essentially, only one of the subcarrier sidebands is transmitted on the upper and lower side of the carrier frequency since attenuation is high above 15 kc.

Recording (see Fig. 3): The 290-cycle subcarrier is modulated by lead sulphide cells PbS 1 and PbS 2. The resulting video information is fed through the recording amplifier and is recorded directly on magnetic tape. The recording head is also used for playback purposes as in many conventional tape recorders. A 5-kc erase oscillator presents a clean tape to the record head for each recording cycle. The tape is an endless loop and is used over and over.

The last portion of the recording system is called a day–night switch. This is an all-important power-saving circuit that switches off all unneeded circuitry while the satellite is on the dark side of the earth. This cuts power consumption almost in half and effectively doubles the life of the battery supply. The day–night switch is triggered by a bias voltage supplied by a series of solar cells mounted in the optical system. When reflected light is available, recording takes place. In its absence, the recorder and associated circuitry are on standby.

Playback (see Fig. 4): Playback is started when the satellite receives a coded pulse from a ground-station transmitter. This pulse, picked up by the interrogation receiver, triggers a relay which energizes all the control-

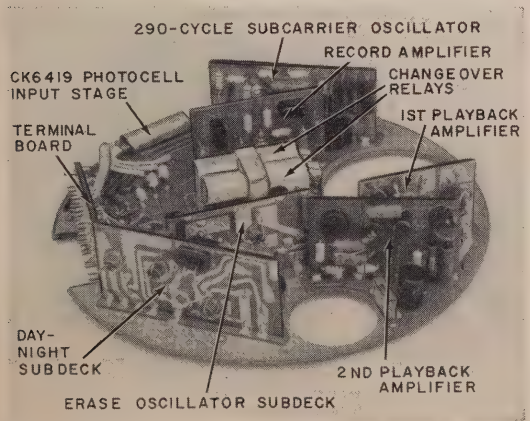

The main electronics deck.

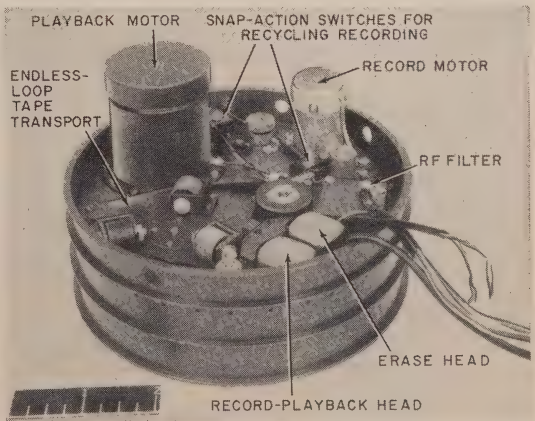

The miniature tape-recorder deck.

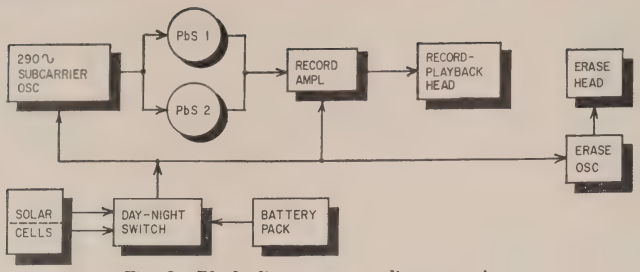

Fig. 3—Block diagram—recording operation.

ling relays. In this fashion the package is switched from record or standby to playback. The signal produced in the playback head is fed to a high-gain amplifier at the 50× speed and frequency ratio. The audio amplifier in turn excites the class-B modulator stage which produces over 1 watt of audio power. Combination plate and screen modulation is applied to the high-power telemetry transmitter. The transmitter's output, ranging from 1.0 to 1.25 watts, is capacitance-coupled to the special antenna phasing system, required to feed the four quarter-wave antenna stubs 90° out of phase with respect to each other. This results in two circularly polarized signals.

Deck assembly and function

Most of the satellite experiments being conducted for the IGY have certain features in common. Modular construction has become an accepted method of "building" the package. For this application a series of 5½-inch-diameter discs containing electronic circuitry is stacked, drawn together with bolts, and fitted to the instrumentation cylinder. Several of the satellites also carry an independent deck complete with battery supply containing a 10-mw tracking oscillator, commonly called Minitrack.

The assembled package is shown in Fig. 5. The decks are described below and illustrated in the photos.

Transmitter deck: This deck contains the high-power telemetry transmitter, push-pull class-B modulator, local oscillator for the interrogation receiver, and the relays that turn the transmitter on. The actual telemetry transmitter is a tube–transistor hybrid. A low-power transistor crystal oscillator drives two tubes (6397's) in parallel.

Interrogation receiver and relay deck: The interrogation receiver is an all-transistor, crystal-controlled, dual-conversion superhet. Local-oscillator injection is furnished by the transmitter deck. A relay deck is interfitted so relays mounted on the underside of a disc occupy waste space in the receiver deck. In this manner a set of relays is added to the package, yet its length is extended only 1/16 inch.

Main electronics deck: The main deck contains most of the electronics necessary for the experiment. Miniature subdecks are mounted vertically. Each contains a block of circuitry—the subcarrier oscillator, recording amplifiers, playback amplifiers, day–night switch and erase oscillator. The subdecks are arranged on the main deck to provide clearance holes for the tape recorder's recording and playback motors. When the two units are fitted together, the thickness of the main deck is included in the overall height of the tape recorder.

Tape recorder deck: The magnetic tape recorder was designed specifically for the instrumentation. It is one of the smallest recorders ever developed in regard to weight, size, frequency response and power consumption. On this deck is a 1-hour recorder—an endless loop, 75 feet of ¼-inch instrumentation-quality tape is used. Mechanical provisions have been made to record and erase with separate heads, record and playback with separate governor-controlled motors and automatically reset the relay system for recording at the end of a playback cycle.

Minitrack transmitter: This deck provides a 10-mw signal for tracking. Circuitry is very similar to the local oscillator and driver oscillator on the transmitter deck.

Battery deck: The last and bottom section of the instrumentation holds a number of mercury cells arranged in series and parallel combinations to supply the necessary power to operate the instrumentation for approximately 2 weeks.

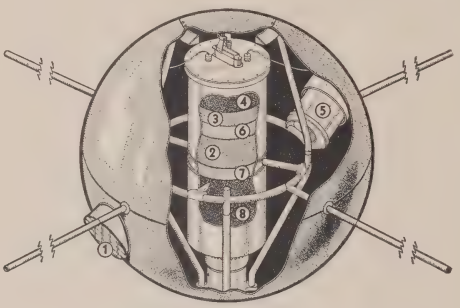

Fig. 5 — Component layout inside the cloud-cover satellite: 1. optic light baffle; 2. magnetic tape recorder; 3. interrogation receiver; 4. data transmitter; 5. photocell; 6. main deck; 7. tracking transmitter; 8. battery pack.

Construction details

All wiring, with the exception of interconnecting cables, is printed. The discs are glass-fiber epoxy laminate, copper-clad with a .00135-inch foil. A photographic process preserves the copper lines and areas needed for construction while the remainder of the material is etched away with ferric chloride. Printed lines, rf coils, tube shields and copper areas are silver-plated. The completed decks are coated with silicon lacquer prior to potting.

Damage to the foil-to-laminate bond by excessive soldering heat was eliminated by using silver-base solder with a low melting point. Dip soldering could not be used since components are mounted on both sides of the printed-circuit boards in almost every instance.

Heat distribution is an ever-present problem in all fields of electronics. It is a serious problem for builders of subminiature instruments. To dissipate and

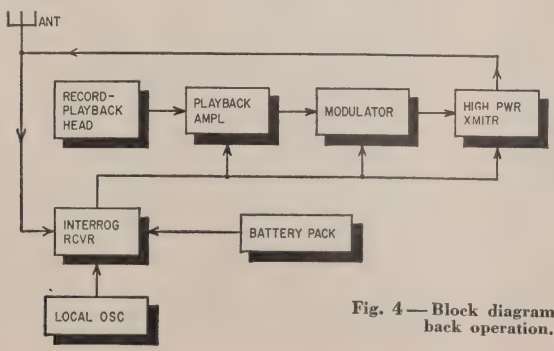

Fig. 4 — Block diagram — playback operation.

distribute the heat generated in the cloud-cover package, two basic methods were used. The first and more conventional is straight conduction from the hot element, the tape recorder, to the cylinder by multiple conduction paths. The second method, described below, is new and may find favor in other applications.

Normally, in power transistors the collector is connected to the case to facilitate good heat conduction. For this reason a metallic heat-conduction path to ground is not feasible. All the transistors, however, that generate an appreciable amount of heat do so during the 1-minute transmission period. Therefore a heat-storage system was devised. Heat sinks with sufficient thermal capacity and relatively long time constants are installed on each of the hot units. During playback, the sinks absorb the heat and slowly dissipate it into the foam potting material over the 90-minute cooling period. Using this system, temperature rise is limited to 5°C.

The potting material mentioned is technically known as "foamed-in-place plastic." Each of the decks, with the exception of the tape recorder, is potted in this material. It has a density of 12 to 15 pounds per cubic foot. Potting is performed in molds that are carefully polished and waxed to obtain a high dimensional stability along with a glazed skin finish. This potting process is fairly common in the missile field, although the potting material may differ. It eliminates failures of components due to shock, vibration and acceleration. In the 1-watt transmitter, however, the high-density material lowered the Q of the tank circuits to such an extent that output power was reduced some 20%. This loss was cut down to 1% by forming glass fiber inside the coils and prepotting the sensitive areas with 2-pound-per-cubic-foot material.

Aluminum rods hold the individual decks to the can cover. Terminal boards on each of the decks are arranged to form an intercabling channel down the side of the package. Two output connections are provided on the can cover to feed the low-power 108.00-mc and high-power 108.03-mc outputs to the antenna system. The input signal for the interrogation receiver picked up by the antenna is fed through proper filters, which are part of the Minitrack deck, to the receiver input.

A multipin connector is located in the center of the can cover to provide a way of disconnecting the batteries from the system and to allow for applying external power during a check of the instrumentation. A shorting plug is inserted into this connector and secured before launching, connecting the internal battery to the electronic circuits.

The overall package is 5½ inches in diameter, approximately 11 inches long, and weighs approximately 12 pounds. As a system it must operate over a temperature range of 0° to 60°C, and voltage variations of ±20% nominal. END

The Backward Diode

Zener diodes have applications in voltage regulation and wave clipping

By ED BUKSTEIN

MOST technicians have resigned themselves to the fact that the arrowlike symbol used to represent nonthermionic diodes does not point in the direction of electron flow. Now, to augment the confusion caused by this unfortunate choice of symbol, comes a new application for the silicon diode. In this application, the diode is intentionally connected with reverse polarity in a dc circuit.

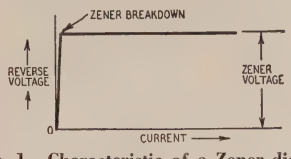

Fig. 1—Characteristic of a Zener diode when a reverse voltage is applied.

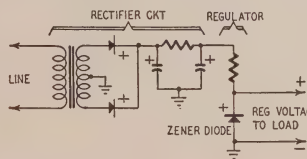

Fig. 2—Voltage drop across Zener diode remains constant even though current may vary over wide limits.

It is well known that a silicon diode has a low forward resistance and a high back resistance. Not so well known is that the back resistance suddenly decreases at a certain value of reverse voltage. The voltage required to produce this breakdown of back resistance is known as the Zener voltage. As shown by the characteristic curve in Fig. 1, the current is practically zero for all values of reverse voltage up to the Zener value. When the Zener breakdown occurs, the reverse current suddenly increases. As the characteristic curve shows, in this region the voltage across the diode is nearly independent of the current flow through it. This ability of the diode to maintain a constant voltage makes it useful in voltage reference and regulating circuits.

Fig. 2 shows how the Zener diode is connected to maintain a constant voltage across a load. Although current flow through the diode may vary, due to line voltage or load changes, the voltage across the diode remains constant. The Zener diode offers many advantages over other voltage regulating elements such as gas-filled tubes. It is smaller, lighter, mechanically rugged and has a long life. The Zener diode can be manufactured for any value of regulated voltage from a few volts to several hundred and for operating currents from a few milliamperes to over an ampere.

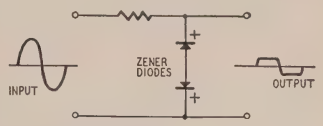

Fig. 3 — Connected in opposite directions, Zener diodes clip extremes of input waveform.

In general, it is better to use several low-voltage diodes connected in series rather than a single diode of higher Zener voltage. The advantage of the series arrangement is that the total power dissipation is divided among several diodes. For this reason, temperature change in each diode is relatively small and stability is improved.

Fig. 3 illustrates the possibility of using two Zener diodes in a squaring or clipping circuit. The two diodes are connected in opposing directions so that they break down on opposite alternations and prevent the output from rising above the Zener value. The Zener diode is a relatively recent development and many other uses for it will be forthcoming.

[Numerous Zener (voltage-reference) silicon diodes are made by National Semiconductor Products, Raytheon, Texas Instruments and other manufacturers of semiconductor products and sold through distributors and mail-order radio and electronic parts supply houses. Among the silicon diodes listed specifically for voltage-regulator and reference applications are the Raytheon 1N437 and 1N438, and Texas Instruments 650C-653C and 650C0-653C9.—*Editor*] END

Get the MOST out of your relays

By JAMES A. McROBERTS

There are many ways of adjusting relays. The best methods and their effects are detailed for the technician and experimenter

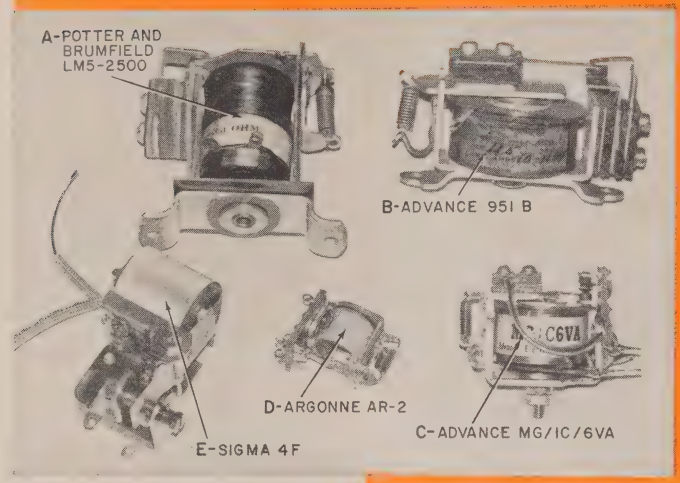

A group of five typical relays.

A spiral spring is used in this relay.

RELAYS were once confined to control and automation but now you can find them in auto radios and TV sets. Although relatively rugged and troublefree, occasionally they do need adjusting. Considerable know-how is necessary despite the apparent simplicity of the device and its circuit (see Fig. 1). Even new units should be checked for proper pull-in and dropout points.

Relay theory

Some knowledge of relay theory is needed if you are to adjust them properly. The why of adjustments becomes understandable. All relays reduce to the basic model of Fig. 1 no matter what shape or size they may take. For example, some relays have a spiral spring supplanting the helical spring found in others. The theory remains the same even when multiple contacts or complicated stops are used.

Let's start with the relay at rest in its unenergized position. Fig. 2-a shows the relay at rest and Fig. 2-b is a force diagram of this condition. We are concerned with the spring force F_S and force F_{NC} at the normally closed contact or rather the *moments* of these forces. (The *moment* is the force times the distance from the pivot or hinge.) Con-

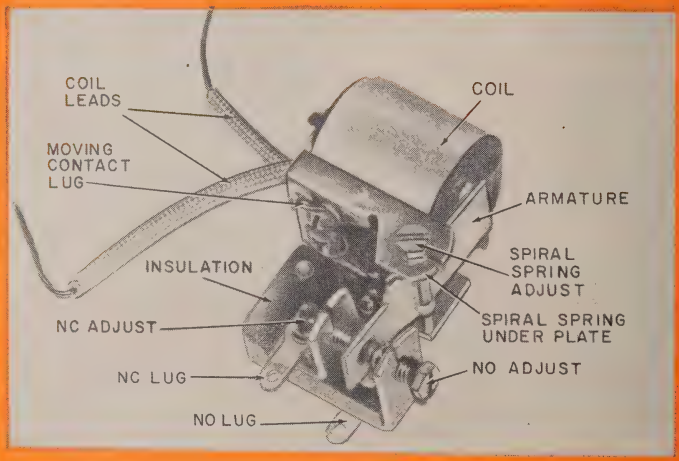

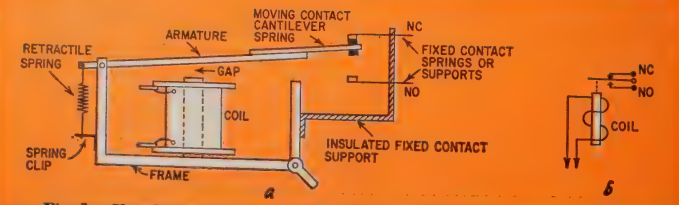

Fig. 1—Sketch of typical relay shows principal mechanical components.

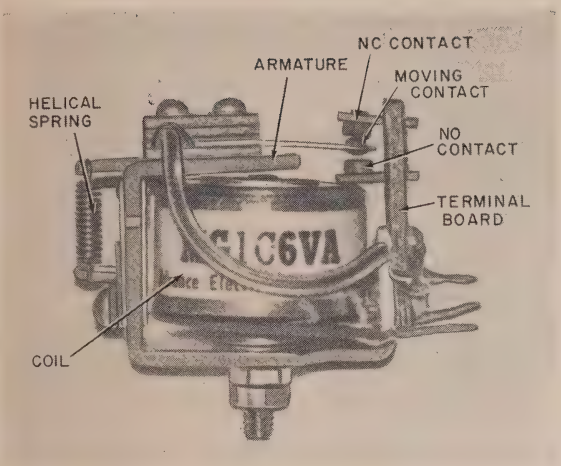

Closeup shows the helical spring usually used in relays.

tact (NC) moment counterbalances the spring (F_S) moment—disregard the equal and opposite forces on the fulcrum hinge or pivot and the residual core magnetism force F_M for now.

Current flowing through the relay coil applies a magnetizing force to the magnetic structure. It tries to force a magnetic flux through the core, armature and gap (sometimes several gaps, but always including one at the hinge). The flux across the armature gap produces a mechanical pull (F_A) at the same point as F_M (see Figs. 2-c, 2-d). The moment of this force tends to rotate the armature. When force F_A is large enough (due to increasing current) to overcome F_S with the aid of F_{NC} (contact pressure) the armature starts to move. Stage 1 of the operate cycle now ends.

Armature motion narrows the gap and the flux increases, producing a greater mechanical pull (F_A). (Total reluctance decreases because of narrowing gap.) Pull increases even if current remains constant. This is stage 2.

Stage 3 of operate is a buildup of contact pressure against the NO (normally open) contact as F_A continues to increase. Some force may be expended in flexing contact springs if the contacts are so mounted. Force of spring F_S has increased during both stage 2 and stage 3.

Stage 1 of the release cycle begins with a decrease of coil current. Force F_A and its moment decrease, too. When the other forces are overcome, the armature starts moving toward the rest position. This ends stage 1.

Note that if F_M is appreciable because of a small gap or residual magnetization, the armature may not release. The armature touching the pole piece can also keep it from releasing. This causes sticking, which is covered later.

Stage 2 is motion with the gap widening. Decrease in flux for dropping coil current lessens F_A.

Stage 3 is the buildup of contact pressure against the NC contact or flexing of its springs. Stage 3 ends with current at a minimum or zero, which is back where we started.

Testing a relay

Relays, both old and new, should be tested for the pull-in and dropout points. To do this use either of the two methods shown in Fig. 3. In dc relays the current is proportional to the voltage since coil resistance is fixed. Hence, wattage is often specified for pull-in and dropout (stage 2 current in operate and release cycles). Either method can be used to test the relay in its circuit (ammeter in series or voltmeter in shunt). For accuracy, use an ammeter whose resistance is less than 5% of the coil resistance or a voltmeter with an input impedance 20 times the coil resistance.

Using Ohm's law you can convert opening and closing currents to voltages across the coil or to wattage input.

The battery used in Fig. 3 should have more than twice the anticipated pull-in voltage. The rheostat (R) drops battery voltage to coil voltage—use about double the coil resistance for R. Finally, equip the working circuit with some sort of visual indicator like the lamp and battery shown or an ohmmeter to indicate relay action, either pull-in or dropout.

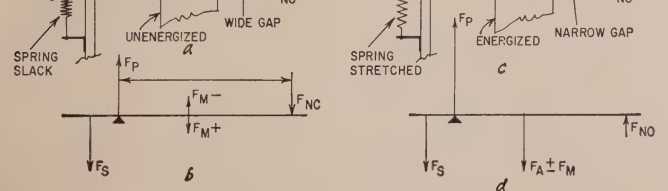

Fig. 2-a—Mechanical position of contacts and armature in rest position. b—Force diagram for Fig. 2-a. c—Contacts and armature in operate position. d—Force diagram for Fig. 2-c.

Range adjustment

Spring tension controls the range of the relay's critical points. Operate and release points may be doubled or halved in most relays by adjusting the spring tension. A Sigma 4F relay can be made to pull in at 3.0 ma and release at 1.5 ma or at an operate of 0.75 and dropout of about 0.3 (not exactly half due to residual magnetism).

Helical spring types may have the spring-tension adjusting nut sealed with wax. Unseal, adjust slightly, and test.

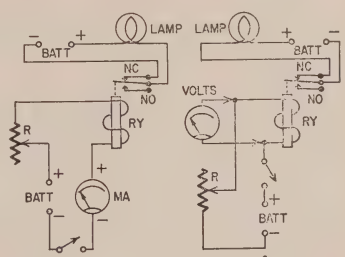

Fig. 3—Test circuits for dc relays: a—ammeter method; b—voltmeter method.

Continue to adjust and test until you are satisfied, then reseal. Spiral spring types have a similar adjustment.

Sometimes, the spring clip holding the spring to the frame may have to be bent—use a pair of needle-nose pliers. Adjust a little at a time, testing after each adjustment. Some flat springs have adjusting screws and locknuts. Others have to be formed (bent) to increase or decrease spring tension.

If spring tension is increased, more armature pull and coil current are needed to start the operate cycle. With the relay energized—armature pulled in—a high coil current is needed to hold it in at the start of stage 2 in the release cycle. Conversely, with less spring tension, pull-in and dropout occur at lower coil currents. If too little spring tension is used, the armature may not drop out at all and will stick, assuming that the armature is touching the coil core.

Fig. 4-a shows another range adjustment found on some units. A screw with locknut is provided to alter the gap between armature and pole piece. Narrowing the gap increases the flux and the pull by decreasing total reluctance

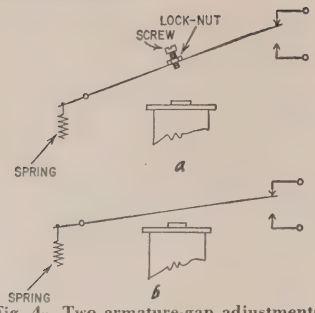

Fig. 4—Two armature-gap adjustments. See text for details.

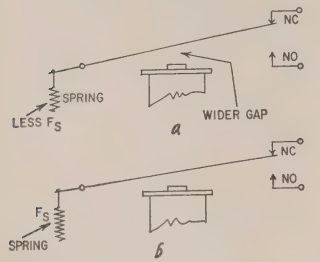

Fig. 5—How varying the position of the NC contact affects the operate point.

due to any fixed value of coil current. (Action is like decreasing resistance in an electrical circuit.) So, dropout occurs at lower current values if the gap is narrowed. Widening the gap has the opposite effect and makes this critical point higher.

Spring tension can be adjusted to supplement this action when making range adjustments. A test as indicated in Fig. 3 or in the operating circuit should always be made to define the operating points.

Fig. 4-b is still another kind of range adjustment. It can be used with or in place of preceding methods. Both fixed contacts are shifted relative to the frame while maintaining their original separation. The effect is a shift in the width of the armature to core gap as just described.

Changing the pull-in point

You may want to shift only the pull-in point. Fig. 5 gives you the general idea. In Fig. 5-a the fixed NC contact has been moved away from the NO contact. The NC contacts on some relays —such as Sigma 4F—can be adjusted with a screwdriver. To make the same adjustment on other relays, such as Potter & Brumfield LM5, the NC contact arm must be re-formed to move the stationary contact (use needle-nose pliers). The armature gap is widened for the operate cycle only, since the NO contact is not moved—compare with Fig. 5-b, the original adjustment.

When this is done, be sure that the NC contacts mate with the required pressure if they are part of the controlled circuit. Some adjustment of spring tension may be needed if a great increase in pull-in current value is desired. (The spring tension is lessened when the NC contact is moved away from the NO contact.) A readjustment of the NO contact may then be needed to maintain the same dropout value.

Moving the NC fixed contact closer to the NO contact narrows the gap, reducing pull-in current. A limit is imposed because the moving contact must be able to move sufficiently to create a contact gap large enough to break the circuit controlled by the relay. In the Sigma 4F example, the pull-in can be decreased from a factory adjustment of 1.5 ma to 0.9 ma without altering the dropout at 0.75 ma as a case in point. This adjustment, however, causes a decrease in the contact gap and to see that the contact gap is not reduced below the minimum requirement for breaking the circuit being controlled.

Dropout variation

Fig. 6 shows the effect of changing the position of the NO contact or a stop, if provided. Moving this contact (the NO one) away from the NC contact or stop lowers the dropout current value. The armature pull (relay energized) is increased, so a lower current holds the armature in position against the NO contact. A limit is reached due

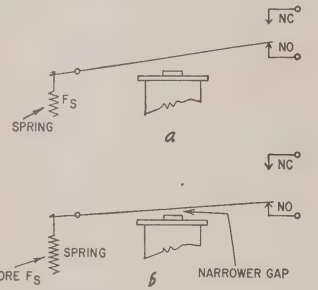

Fig. 6—Changing the position of the NO contact points varies the dropout point

to armature sticking, although this may be desirable in some instances (in burglar alarms, for instance, where you may want to cut off the power to unlatch the relay or reset it without triggering the alarm).

Some rise in the release point is obtained by moving the NO contact closer to the NC contact. As a result, dropout occurs at a higher current.

Differential adjustment

Relay differential is the current or voltage range between the pull-in and the dropout points. In the Sigma 4F example we have the differential as the difference between 0.75 and 1.5 ma or 0.75 ma for the factory settings.

Spreading the fixed contacts apart increases the differential or the spread between operate and release values. Pushing them together narrows this range. A similar action is obtained by setting the pull-in to one current value

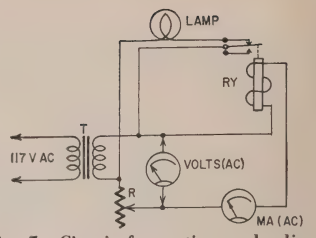

Fig. 7—Circuit for testing and adjusting ac relays.

and the dropout to another. The range adjustment may have been made previously or performed simultaneously with a change of the differential. Usually the range adjustment is made before setting the fixed contacts for a different range of values.

Ac relays

Test ac relays like the dc variety. Use an ac voltmeter and ammeter with a transformer as in Fig. 7. The transformer can power the indicating lamp or device if one is not provided by the circuit.

Ac relays are often specified in terms of coil voltage at pull-in such as 6, 12 or 110 volts. This means rms values. Or the coil pull-in volt-amperes may be specified with a given value of coil resistance. (Inductance is often neglected.) Allowable safe dissipation is often specified in volt-amperes, hence any calculation is similar to the dc relay. Thus a coil may operate at 6 volts with 1 ampere or 6 volt-amperes and have a safe dissipation of 9 va. So, 9 volts at 1 ampere is the maximum that should be applied.

New relays

New relays may exhibit a rather high range of critical points. Check to see that the helical spring seats in the grooves in the clip and the armature end. It may have shifted out of one or both grooves with a consequent increase in tension and range of operating values. Put the spring ends back in the slots or grooves and check again!

If a new relay has a high differential, it may be due to friction. Some friction is always present at the hinge or pivot of most relays. (The Advance type in the photo does not have a hinge, but a spring that flexes. Exclude such designs from this treatment.) If pivot or hinge friction is large, it will tend to prevent the relay from operating or releasing at the points (current values) it should. Correct by loosening the pivot bearings' adjustment screws slightly, where possible. Or apply a minute amount of penetrating and non-gumming oil to the hinge or pivot.

One word of warning, any bending or forming of contacts should be followed by a visual check for mating. Moving contact points must make parallel (flat) contact with both sets of fixed contacts. Otherwise you end up with rapid wear and a faulty adjustment.

END

THREE-WAY TIMER

Agitation timer, conventional timer and counter circuits are built into this photographer's electronic right hand

By E. H. LEFTWICH

THIS versatile unit is definitely *not* just another phototimer. It was designed to take the guesswork and headaches out of agitation timing for both color and monochrome photographic film processing. It is also an excellent conventional timer for enlarging and printing and has several other useful functions. It has definitely proved to be the most useful of the electronic controls in my darkroom.

The block diagram (Fig. 1) gives a good overall idea of the timer's operation. **In agitation timing, it:**

1. Accurately indicates a 1-minute interval.
2. Signals with a warning buzzer or pilot light the instant the 1-minute interval is reached.
3. Immediately following the signal,

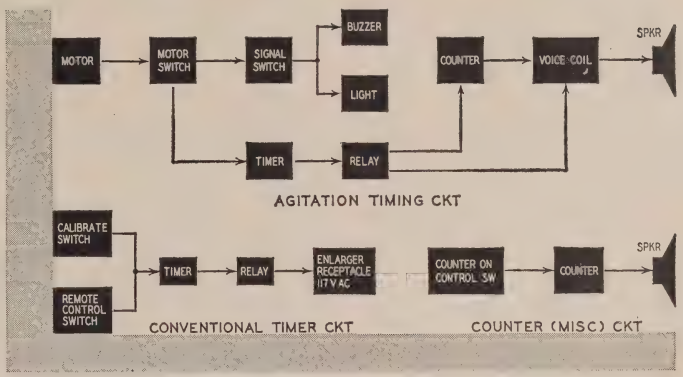

Fig. 1—Block diagram of the three-way timer.

R1—2,200 ohms
R2—pot, 10,000 ohms, wirewound
R3—15 megohms
R4, 12—270,000 ohms
R5—470,000 ohms
R6—470 ohms, 2 watts, wirewound
R7, 8—100,000 ohms
R9—3.3 megohms
R10—pot, 10 megohms
R11—22,000 ohms
R13—3,300 ohms
R14—1,000 ohms, 1 watt
R15—33 ohms, 1 watt
All fixed resistors ½ watt 10% unless noted, see text.
C1—2 μf, paper, 400 volts
C2—.05 μf, 400 volts
C3—0.22 μf, 400 volts
C4, 5—0.1 μf, 400 volts
C6—.005 μf, 600 volts
C7—25 μf, 50 volts, electrolytic
C8—8 μf, 250 volts, electrolytic
C9—12 μf, 250 volts, electrolytic
C10—16 μf, 250 volts, electrolytic
F—0.1 amp, 8AG
J1, 2—sockets, female (Amphenol 61-F1 or equivalent)
RECT—selenium 130 volts, 5 ma
RY—3-pole double-throw, 5000-ohm coil (Guardian 200-5000D) with contact assembly (Guardian 200-1) and contact switch parts (Guardian 200-3)
S1, 6, 7—spst, toggle
S2—spdt, center off, toggle (Cutler-Hammer 8816-K5 or equivalent)
S3, 4—switch contacts (see text)
S5—spst, momentary contact, pushbutton
T1—filament transformer: primary, 117 volts; secondary, 6.3 volts, 1 amp (Knight 62G030 or equivalent)
T2—output transformer: primary, 2,500 ohms; secondary, 3.2 ohms (Knight 62G063 or equivalent)
V1, 3—12AU7
V2—2050
Buzzer, high-frequency (Johnson 114-400 or equivalent)
Fuse holder for 8AG fuse
Motor, Telechron clock

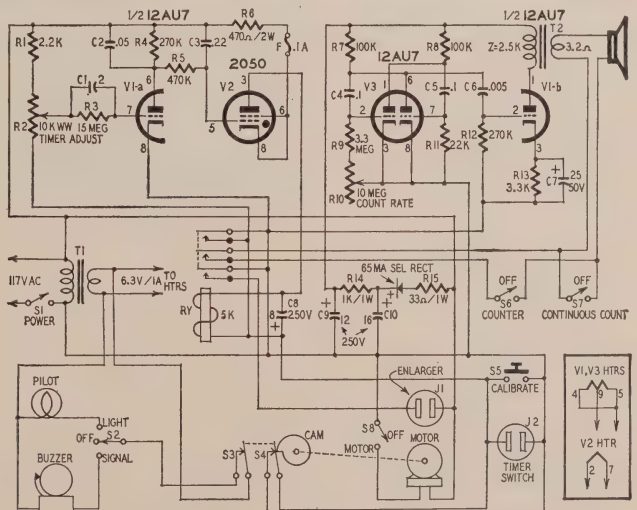

Sockets, 9-pin miniature (2)
Socket, octal
Pilot-light assembly, with 6-volt pilot lamp
Loudspeaker, 3-inch, PM
Terminal strips, 4 lugs (4)
Cabinet, 6 x 9 x 5 inches
Chassis, 1 x 6 x 4 inches
Dial plates, 1–24 (Mallory 394 or equivalent)
Miscellaneous hardware

Note: Since the ac line connects to several points in the circuit all wiring must be insulated and all components mounted so they cannot contact the chassis.

Fig. 2—Circuit of the versatile unit.

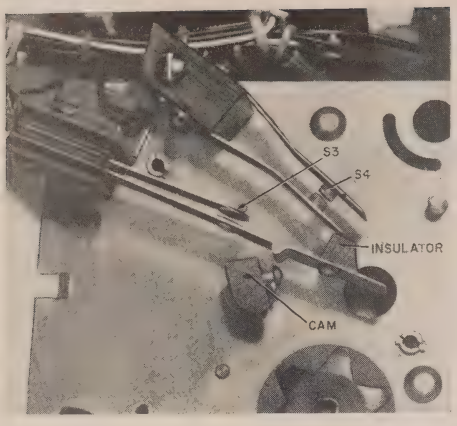

Fig. 3—Detailed look at switches S3 and S4.

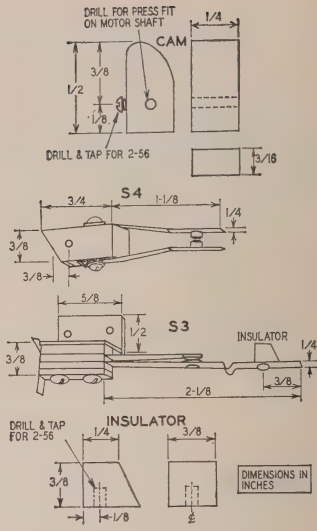

Fig. 5—Construction details for S3 and S4.

it automatically begins to count off 15 seconds audibly at the rate of 1 pulse a second. The counter then cuts off. The timer motor, which remains on, automatically *repeats* this cycle for as long as desired.

4. Triggers manually (tests) and adjusts counter rate through a range of 10 pulses per second to 1 pulse every 2 seconds.

In conventional timing it:

1. Switches enlarger or printer lamp on and off at preset intervals of 1–80 seconds.

2. Provides remote control or panel triggering of timer circuit.

3. Contains timer circuit calibration adjustment.

In counter (miscellaneous timing):

1. Counts audibly, by seconds, for checking elapsed time of enlarger exposures. The operator can check remaining time for a particular exposure and dodge, burn in, etc.

Three circuits

Fig. 2 shows the unit's circuitry. There are actually three circuits. These are standard types with some slight modifications.

1. Timer circuit: Uses V1-a, half of a 12AU7 twin triode, with V2, a 2050 thyratron, to actuate relay RY and supply plate voltage. Potentiometer R2, in V1's grid circuit, regulates the length of time that RY stays closed after S4 is closed. The switch circuit may also be closed manually with CALIBRATE switch S5 or by a remote switch plugged into TIMER SWITCH receptacle J2. There is a 1-second delay in the relay's operation, so all switches in the timer circuit must be held closed momentarily to start the timer. A 0.1-amp fuse protects V2's cathode against possible line surges.

2. Counter (multivibrator) circuit: The counter circuits uses both triode sections of V3, another 12AU7. It is normally on when the unit is in operation with S6 closed. Its pulses become audible when one pair of RY's contacts is closed to complete the voice coil circuit. A continuous count is obtained when switch S7 is closed. MOTOR switch S8 is opened only when a continuous count is desired or when the unit is not being used for agitation.

Frequency of counter pulses is varied by adjusting COUNT RATE potentiometer R10. Counter output is coupled to the grid of V1-b, thus providing an audio stage.

3. Motor–switch circuit: The motor–switch circuit consists of a standard Telechron electric-clock motor assembly and two sets of spst cam-actuated contacts. (S3 and S4 in Fig. 3) This assembly, which is the heart of the unit, provides the 1-minute *continuous* timing for agitation. This is how it works:

The cam mounted on the motor's second-hand shaft closes the two sets of contacts (S3 and S4) once each minute. The contacts remain closed for 1 second. S4 triggers the timer circuit and closes the counter voice coil circuit (through contacts of relay RY). At the same time S3 momentarily closes the signal circuit to the buzzer or light.

All parts are standard except for the motor-contact assemblies, spacers and clock motor. (I used 5% resistors but 10% units should be satisfactory.) *Even though all wiring is insulated from the chassis, it is suspended in the cabinet on insulating spacers to minimize shock hazard if a short circuit should occur (see Fig. 4).*

Fig. 3 is an enlarged view of the clock's front plate and Fig. 5 shows details of the cam and contact assemblies. Contacts with springs and fiber-block mountings can generally be found in surplus stores. As the motor has little power, contact springs must be made from thin stock and should be about the same length as those shown in Fig. 5.

Make the cam and insulator from small fiber blocks. Saw out and cut to shape. Drill the cam to fit the center (second-hand) shaft of motor. Drill and tap a 2-56 hole in the side of the cam

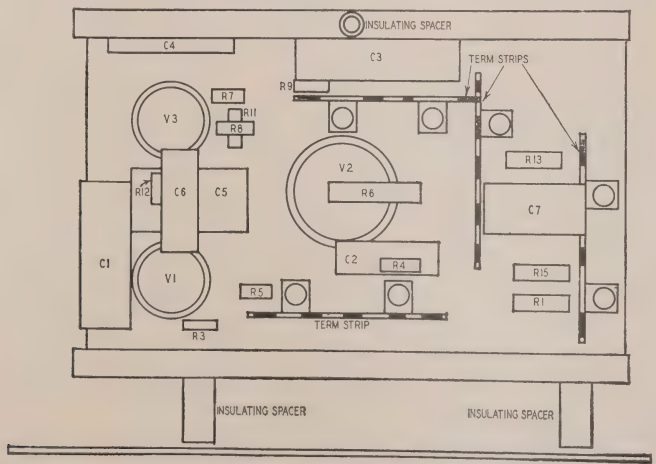

Fig. 4—Component layout under the chassis.

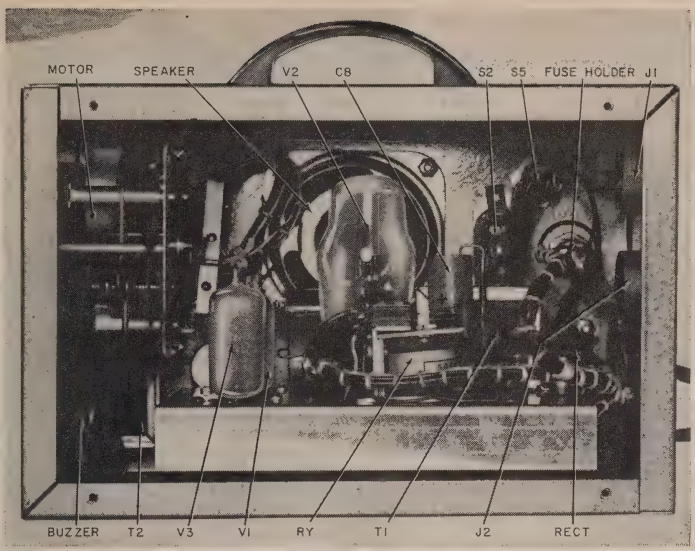

A look inside the case. Note the motor and buzzer mounted on the left.

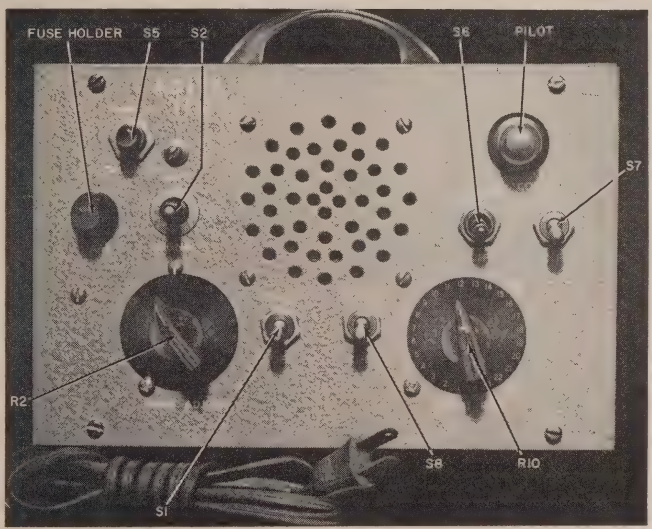

Front view of the completed timer. Jacks J1 and J2 are mounted on the left side of the case.

block, to take a 2-56 setscrew. To gain enough length to mount the cam on the shaft, carefully file off part of the flanges on which the minute and hour hands were originally mounted. Drill and tap the insulator for 2-56 and mount on the spring as shown in Fig. 3.

Adjust the contact springs (made from .012–.015-inch spring brass stock) so that the cam holds contact assembly S3 closed for at least 1 second and at the same time momentarily closes contact assembly S4. (Location of the contact assemblies will vary, depending on length and type of contact springs used.

Operating instructions

To use as an agitation timer: Place all switches in OFF position. Turn POWER switch on and allow 3 minutes for tubes to warm up. Set the TIMER ADJUST knob to about half of full clockwise position. Now push CALIBRATE switch and hold down for 1 second. Relay will close with an audible click and remain closed for the desired agitation time (usually 15 seconds) determined by the setting of the TIMER ADJUST switch. When the relay opens, a second click is heard. Use the second hand of your watch or an electric clock to check for 15 seconds.

Turn the COUNTER and CONTINUOUS COUNT switches on. With COUNT RATE knob at full counterclockwise position, counter pulses will start and are audible. Check the timing of pulses and slowly advance the COUNT RATE knob until a 1-pulse-per-second rate is obtained. Then turn off the CONTINUOUS COUNT switch and turn the SIGNAL–LIGHT switch on. Next turn the MOTOR switch on.

Hold a finger on the lever of the MOTOR switch and turn it off as soon as signal (buzzer or light) stops. When ready to start agitation, turn MOTOR switch on. Counter will audibly tick off 15 seconds and stop. After 45 seconds, light or buzzer will again signal and 15-second count will be repeated. The entire cycle repeats until POWER switch is turned off.

Enlarging or printing timer: Turn all switches off. Turn POWER switch on and wait 3 minutes for tubes to warm up. Calibrate the TIMER ADJUST control and make up a calibration chart.

To do this set the TIMER ADJUST control at its extreme counterclockwise position. Push the CALIBRATE switch and hold closed for 1 second. RY will close with an audible click and quickly open with a second click. Check the elapsed time between each click (in seconds) and note the dial setting on your chart. Slowly advance the TIMER ADJUST knob, one division at a time and note elapsed time (in seconds) for each setting. Continue until full clockwise position is reached. Your complete chart will give you a timing range of 1–80 seconds.

Use of an external timer (remote) switch is optional but is provided for by ENLARGER receptacle J1. The timer is normally triggered by pushing the CALIBRATE switch on the panel.

Set TIMER ADJUST control for the desired exposure. Plug the enlarger or printer ac line cord into receptacle J1 and, if remote control is desired, plus a spst pushbutton switch into J2. Push the CALIBRATE or remote switch and hold down for 1 second. The enlarger or printer light will come on and remain on for the interval selected. The cycle repeats only when the CALIBRATE or remote switch is again closed.

In addition, the COUNTER switch may be turned on and the counter will operate, counting off the seconds while the enlarger or printer lamp is on.

The CONTINUOUS COUNT switch may be turned on any time the power switch is on. This provides a continuous count of seconds.

For ventilation, use a perforated Masonite sheet for the back cover unit. If the timer is carefully wired and checked, there is little possibility of trouble. However, a few items may require minor correction.

POSSIBLE TROUBLE:	*REMEDY:*
Excessive (ac) hum.	Reverse leads to primary of output transformer.
TIMER ADJUST control operates backward.	Reverse outside leads on R2.
COUNT RATE control operates backward.	Reverse leads in R10

END

WESCON VISIT

Touring the 1958 West Coast electronics show

By TOM JASKI

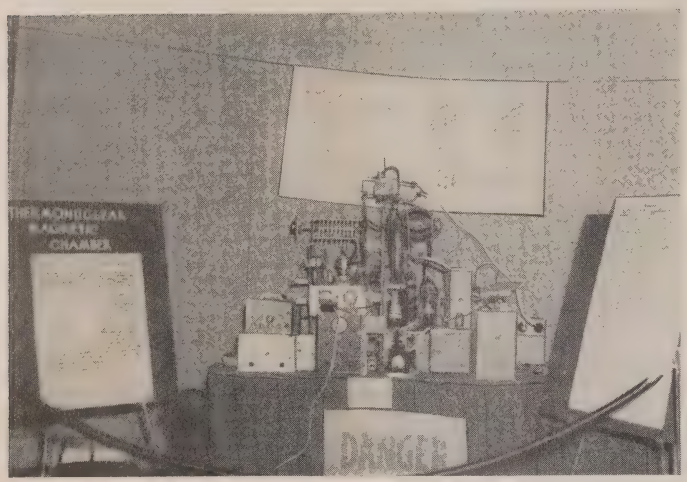

Teen-ager Allan Hill's demonstration of the pinch effect for containment of thermonuclear reactions.

THE annual WESCON show, held in the Pan Pacific building in Hollywood, Calif., in late August, displayed 900 exhibits of electronic equipment for the trade and engineers attending the conference and lectures organized by the IRE. In contrast with last year's show, when many displays were consumer-oriented, this year's presentations were aimed primarily at industry.

Another outstanding aspect of the show was the limited budget, evidenced by the holdover of last year's display decorations and a number of booths with only mockups, slides and charts or a tape-recorded sales pitch. Not marked by outstanding discoveries or new devices, the show nevertheless drew a capacity audience and had many points of interest for the technician, ham, and student as well as the professional engineer.

Most thought-provoking were the displays of the Future Engineers—equipment built by high-school students, some highly original, some very professional-looking. Besides the usual Tesla coils and ultrasonic cleaning and homogenizing apparatus, there was the setup of high-school student Allan Hill of Durango, Colo., demonstrating a new method of confining thermoneuclear reactions away from vessel walls. Allan built for pennies apparatus which would cost thousands if done in the nation's laboratories.

Of particular interest

For the technician: Multicore solder by *Multicore Corp.* containing a special alloy which tends to plate the soldering-iron tip and reduce tip wear.

A printed-circuit desoldering kit by *Ungar* with tips designed especially for the removal of parts from circuit boards without the usual point-by-point prying loose of one connection at a time. For those dealing with TV sets and radios using printed-circuit boards, this can be a tremendous time saver.

New scopes by *Waterman* and a British firm called *The Scopes*. *Waterman* has come out with a portable unit measuring only 4¾ inches high, 5½ inches wide and 10 inches deep. Dc to 250-kc response, 10-mv/cm sensitivity, using a full 1½ x 3-inch flat cathode-ray tube. Waterman also showed the prototype of a slightly larger scope with a specially developed short 5-inch CR tube only 12 inches long.

The Scopes instrument is a conventional-looking 3-inch model with an unconventional dc to 6-mc bandwidth, 60-mμsec rise time and 100 mv/cm sensitivity. Also in evidence was the *Heath* professional scope which has unusual sweep generator capabilities for a kit type oscilloscope.

For the ham: *Heath* showed two new receiver–transmitter combinations and a single-sideband adapter. Particulars appear in *Heath's* new catalog.

Texas Instruments demonstrated a palm-sized transistor transceiver with a ½-mile range. It operates in the 27-mc band, requiring a special permit from the FCC, but can be adapted for the ham bands.

Knight (Allied Radio Corp.) had on hand their new four-band shortwave receiver, the "Spanmaster," and their Deluxe amateur receiver using printed-circuit switches and printed-wiring boards throughout.

For the engineer: Since this show was oriented toward industry many items appealed to almost any classification of engineer. Of general interest were the enormous Klystron displayed by *Eimac*, ceramic tubes by *Sylvania*, the CK 1053 time-measuring tube by *Raytheon*, the *Amperex* indicator for transistor circuits and a host of new transistors introduced by all major firms. TI has new power transistors, G-E commercially available tetrodes (3N36 and 3N37) and Sylvania a new

Deak Atkinson (left) and W. E. Trantham of Texas Instruments demonstrate an all-transistor 27-mc transceiver. Special FCC license was required.

Helmet transceiver developed for carrier jet-landing instructions by Dr. Webster and Mr. Gibson of the Naval Electronics Laboratory in San Diego, Calif.

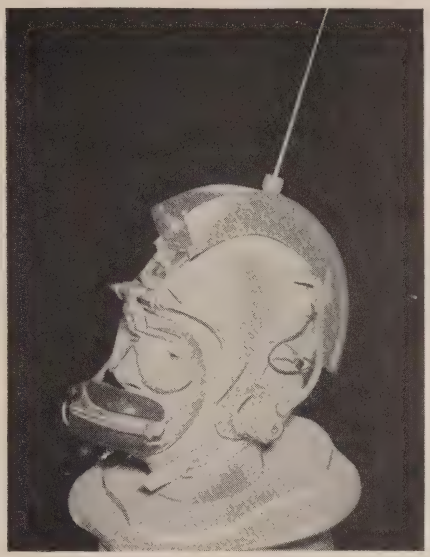

1-watt 70-mc unit. Worth owning is the new G-E *Transistor Handbook* listing all the latest data with circuit applications.

The *Naval Electronic Laboratory* in San Diego showed a "Man from Mars" Trojan helmet, containing a newly developed vhf communication system for carrier landings of jet aircraft. The unit is entirely self-contained, uses rechargeable nickel-cadmium batteries, is entirely transistorized and is designed to take advantage of the physiology of the head. Supports for the unit are designed to press on the areas of the head containing very few nerves and blood vessels, assuring wearer comfort. Special noise-attenuating mouthpiece and earphones are attached.

A new approach to tape recording of telemetered data was shown by *Precision Instrument Engineering* with their typewriter-sized case containing all-transistor data-recording equipment usually requiring one full-size relay rack. The seven-channel recorder requires only 1.54 cubic feet of space, weighs less than 50 pounds and uses all standard tape speeds from 3¾ to 30 inches per second.

For everyone

Westinghouse showed their models of electronic refrigeration, employing semiconductor thermocouples and the well known Peltier effect to produce an electronic baby-bottle cooler–heater which can be set for various combinations of cooling and heating cycles automatically.

Allied Radio demonstrated their new stereo and stereo adapter kits and an interesting new inexpensive tube checker.

Triplett showed their new line of "Unimeters," a series of basic meter movements and separate scales which can be combined in many combinations to provide for easy scale changes.

Missing: Conspicuous by their absence were devices like the flat picture tube, the flat, wall-hung electroluminescent CR screen; all-transistor hi-fi amplifiers; stereo discs and cartridges (none were present in the show); small and lightweight portable tape recorders; portable all-transistor TV sets (the *Texas Instruments* prototype was not demonstrated at the show proper) and many other advances we have been conditioned to expect from our electronic technology. END

a new service for our readers . . .

When you see this emblem on a constructional article in RADIO-ELECTRONICS, build with confidence. It is your assurance that the equipment has been actually bench-tested, either by the editors or by a reputable outside testing facility, and that the schematic has been carefully checked against the equipment. A short test report will be published with each article. The only construction articles not included in this plan will be (1) equipment whose performance can be accurately predicted by study of the schematic and (2) articles which were purchased before this policy went into effect.

BENCH R-E TESTED

COVER FEATURE

Part I—Opportunities are increasing in the small-boat radio installation and service field. What's it all about and what do you need to go into the marine radio business?

RADIO for WEEKEND SAILORS

By LEO G. SANDS

THE pleasure-boat industry found 1958 to be its best year yet, according to reports from many engaged in the manufacture and sale of boats and boating equipment. Estimated sales in 1958 are running 10% above 1957, when more than 35,000,000 people took part in recreational boating activities. Attendance at the boat shows in 1958 was reported to be better than 10% above 1957 figures and one marine radio equipment manufacturer reported a complete sellout of a new model it introduced this year.

The latest available figures published in a joint report of the National Association of Engine and Boat Manufacturers and the Outboard Boating Club of America show that more than 7,000,000 pleasure boats are in use in the United States, compared to only 1,500,000 two decades ago. And the number is growing rapidly.

The latest annual report of the Federal Communications Commission notes that only 65,000 vessels are licensed to use radio. These FCC figures include fishing boats, cargo vessels, passenger liners and other commercial vessels as well as a very small percentage of the more than 7,000,000 pleasure boats.

Sales of marine radio equipment have climbed sharply as will be evidenced when the next FCC annual report is published. The public is getting extremely safety conscious and because of the widespread use of mobile radio on land, the weekend sailor also is becoming extremely cognizant of the conveniences of modern communications. The big spurt in marine radio sales this year was caused by the introduction of lower-priced radiotelephones especially designed for use on outboard motorboats which heretofore had to do without radio.

Marine radio sales also spurted in 1958 when operators of party boats and passenger vessels carrying six or more persons for hire bought radio equipment to comply with an FCC requirement that such vessels have radiotelephones. Approximately 5,000 vessels were affected by this FCC mandate. Passenger-carrying vessels over 65 feet in length operated on the Great Lakes are also required to carry radio. There is a move in Congress at present to waive the requirement for radio on vessels operating within 1,000 yards from shore. However, for safety as well as convenience, a radiotelephone should be required on all passenger-carrying vessels.

Two-way radio can be used in pleasure craft as well as commercial vessels. Most common is the radiotelephone operating in the 2–3-mc band, which lies between the 80-meter and 160-meter ham bands. Many vessels also have vhf radiotelephones on marine frequencies in the 152- to 162-megacycle band.

Vhf–uhf radio

Boats used in a commercial enterprise may be equipped with LPI (low-power industrial) or Citizens radiotelephones for private ship-to-ship or ship-to-shore communications. When operating in these radio services, licensees can also communicate from boats to similarly equipped automobiles and other vehicles on shore. LPI or Citizens systems are most frequently used by yacht clubs and organizations which service other vessels. The LPI communicating range (25–50-mc or 152–162-mc band) is relatively short (1 to 5 miles) due to limitations on antenna height and transmitter power.

Any US citizen over 18 years of age may operate his own private ship-to-shore radio communications system in the 460–470-mc Citizens band. Standard 450-mc mobile radio equipment is available from a variety of manufacturers and is of the same type as used in automobiles and trucks. Range depends upon the height of the base-station antenna above surrounding terrain and varies from 10 to 20 miles and more.

Railroads and other industrial users who are eligible for licensing in the 152–162-mc band sometimes operate private vhf ship-to-shore communications systems to cover marine extensions of their land operations. Gener-

ally the equipment is conventional vehicular mobile radio equipment or heavy-duty railroad radio equipment, often housed in special enclosures to prevent damage by salt water. Range from a private shore station to tugboats and other commercial vessels at sea may be as long as 30 miles.

Medium-frequency radio

The vast majority of marine radios are licensed in the Marine radio service and operate in the 2–3-mc band. Ships and pleasure boats thus equipped can communicate with other boats, with the Coast Guard and with public shore stations operated by common carriers such as the telephone companies. Private shore stations are not permitted. However, there is no prohibition against a moored boat communicating with another boat off shore.

There are 48 public coast stations in the United States which pleasure boat owners may contact. The Pacific Telephone & Telegraph Co., for example, maintains coastal harbor radiotelephone stations in Seattle, Wash.; Portland and Astoria, Ore.; Eureka, San Francisco and San Pedro, Calif. All these stations operate on a 24-hour basis. They are interconnected with the telephone system. A boat owner can contact the nearest coastal harbor radiotelephone station by radio and then via wire line any telephone in the United States, or in almost every part of the world. Furthermore, calls between boats may be routed via one of the telephone company stations. A minimum toll of $1 is charged for this kind of service. The toll varies with the distance.

The range of a marine radiotelephone depends upon the antenna system and transmitter power. There is a rough rule-of-thumb which states that communicating range is 1 watt per mile. However, this is not considered accurate. Transmitter power is usually spoken of in terms of power input to the final rf stage. Using this barometer, the over-water daytime communicating range of a 20-watt (output) transmitter when fed to an efficient antenna system is 50 miles. Increasing power to 30 watts produces slight increase in range. A 150-watt transmitter generally is capable of providing a 100–125-mile range during the day. Nighttime range may be considerably greater because of skip transmission. However, dependence should be placed only on the rated daytime range.

Various frequencies in the 2–3-mc band are assigned to marine radio services. The international calling and distress frequency is 2182 kc. Ordinarily, boat radios are left tuned in on 2182 kc so calls may be intercepted, except when monitoring one of the coastal harbor or inland telephone stations in anticipation of a telephone call.

After calling another boat or intercepting a call from another boat, both stations shift to another frequency for carrying on a conversation. On the Great Lakes, 2003 kc is the ship-to-ship

Low-power industrial or Citizens band radiotelephones can be used for private ship-to-shore communications.

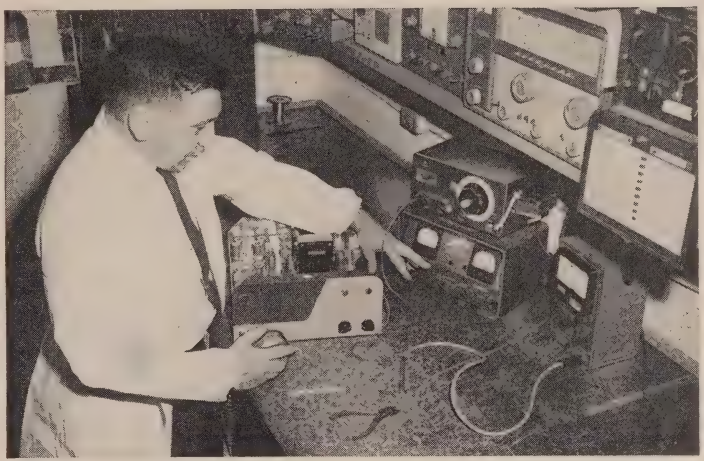

Measuring frequency and deviation of a 450-mc mobile unit.

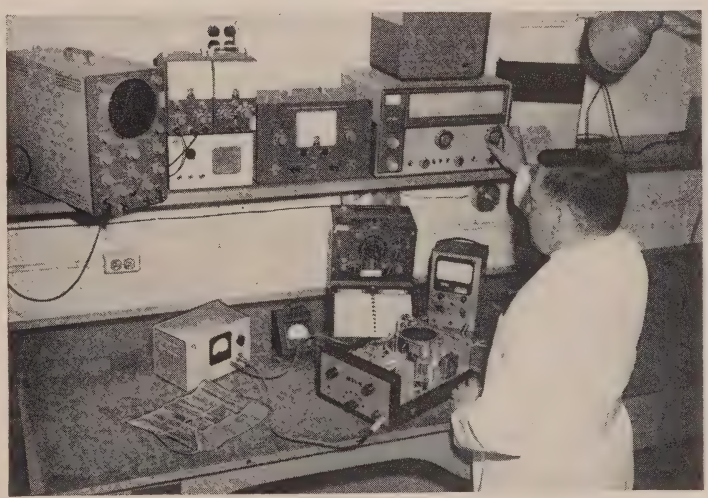

Marine radio channels can be monitored and spurious radiation from a transmitter being checked can be noted with a professional communications receiver.

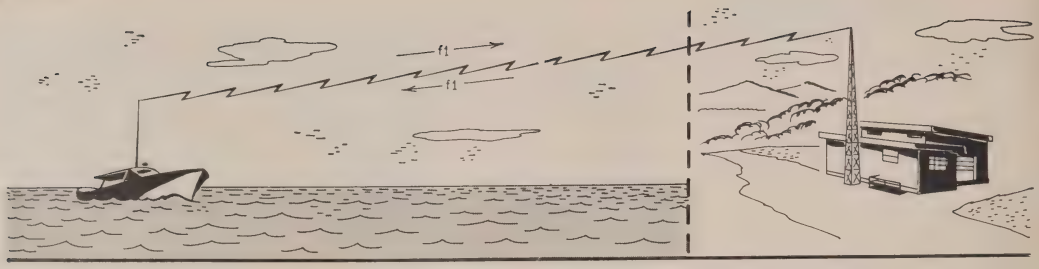

Fig. 1—Simplex transmission uses the same frequency for transmitting and receiving.

frequency. On the Gulf of Mexico the frequency is 2830 kc, and 2738 kc may be used anywhere, except in the Great Lakes and the Gulf of Mexico. The frequency 2638 kc is used for ship-to-ship communication at sea, in tidewaters, inland lakes, canals and rivers.

Marine radiotelephone transmitters are crystal-controlled to meet FCC frequency-stability requirements. Receivers also tend to be crystal-controlled so the user does not have to fiddle with tuning knobs.

A boat which normally operates along the Pacific Coast near the Golden Gate, in San Francisco and San Pablo bays and up the Carquinez straits and the Sacramento and San Joaquin rivers would have its transmitter and receiver set up as follows:

Frequency in Kc		
Transmitter	*Receiver*	*Function*
2182	2182	calling and distress
2003	2430	telephone
2406	2506	telephone
2638	2638	ship-to-ship
2738	2738	ship-to-ship

One channel is set to a 24-hour telephone channel and another channel is set to a daytime-only telephone channel, both for contacting the coastal harbor station at San Francisco.

In other areas, other telephone channels would be used. Sometimes the same telephone frequencies are used in more than one area. For example, the pair 2598–2206 kc is common to the coastal harbor stations at San Pedro, Calif., and Astoria and Portland, Ore.

Marine radiotelephones are intended for *safety*, *operational* and *business* purposes, with priorities in that order. The calling frequency, 2182 kc, may not be used for extensive conversations as improper use could interfere with distress calls.

The *operational* function is for the exchange of information pertaining to navigation, movement and management of vessels. The *business* function permits boat crews and passengers to transact business between vessels and—via a commercial shore station—with points on land. The purpose of the *safety* function is obvious.

Boats operating on inland rivers, particularly those which have locks, communicate with stations at these locks and with other ships on 2738 kc.

When calling another boat, the radio is set to transmit and receive on 2182 kc. The call is made by reciting the name of the desired boat followed by the name and radio-station call letters of the calling vessel. After contact is established, both boats shift to ship-to-ship frequency.

Telephone calls

To call a land-based telephone, the radio is set to one of the coastal harbor telephone channels. If the channel is busy, a conversation or conventional *busy* signal is heard. When the channel is clear, the calling vessel announces the station being called, followed by the name of the ship and its call letters. This call is repeated slowly at least three times.

When the marine operator replies, the calling vessel gives the city telephone number and, if required, the name of the desired person as well as the boat's position. The operator then gives instructions on how to proceed. At the end of the conversation, the boat's name and call letters are repeated followed by the words "signing off."

To place a call from a land-based telephone, the caller dials the long-distance operator and gives the name, call sign and location (if known) of the desired ship.

The call is intercepted by the desired boat if the radio receiver is turned on and set to the appropriate telephone channel and if someone is listening. Obviously, the boat must be within radio range of the shore station through which the call is routed.

Some ships, particularly passenger liners, are equipped with selective-calling devices, obviating the need for continuous aural monitoring. A receiver, whose output is muted, is tuned to a shore station and connected to the selective-calling device. When the tone-pulse code which matches the setting of that specific decoder is received, a bell or other alarm is sounded.

Simplex–duplex

A typical marine radiotelephone consists of a multichannel AM transmitter and a multichannel AM receiver, packaged as a single unit. Frequencies are selected with a switch that controls transmitter and receiver simultaneously.

For calling and ship-to-ship communication, single-frequency simplex operation is used. This means that transmission and reception take place on the same frequency (see Fig. 1) and that transmission takes place in one direction at a time only. To transmit, the push-to-talk button on the microphone or handset is operated. To listen, the push-to-talk button is released.

When communicating with a coastal or Great Lakes shore station to place or receive telephone calls, transmission takes place on one frequency, reception on another (see Fig. 2). The boat operator uses the press-to-talk technique but the shore station transmits and receives at the same time. By using this technique, communication with ordinary telephones, which are not equipped with push-to-talk buttons, can be maintained.

Since the transmitter and receiver can be tuned separately, each channel can be set for transmission and reception on the same or differing frequencies as required.

Marine radio servicing

Marine radio equipment is sold by dealers who are technically competent to install and service it. It is seldom feasible for a dealer to sell equipment and farm out the installation and service work to an independent technician.

The marine dealer sells "systems" which fit the requirements of specific boats. Sometimes a short-range radio will do. In other cases, a more powerful radio which needs a more efficient antenna system and a more adequate power source is required. The dealer must be able to specify the required equipment, the modifications that must be made on the boat and the estimated cost.

Most marine electronics shops are located on or near the water. One dealer in Portland, Ore., has a floating shop on the giant Columbia river. His customers can tie their boats alongside or sail into a sheltered berth where the radio can be serviced on the boat even in bad weather.

Shop test equipment, in addition to the usual vtvm's and hand tools, should include a frequency meter which meets FCC requirements for accuracy, an instrument for measuring percentage of modulation, an rf signal generator and a dummy antenna.

Transmitter frequency can be measured with a direct-reading electronic

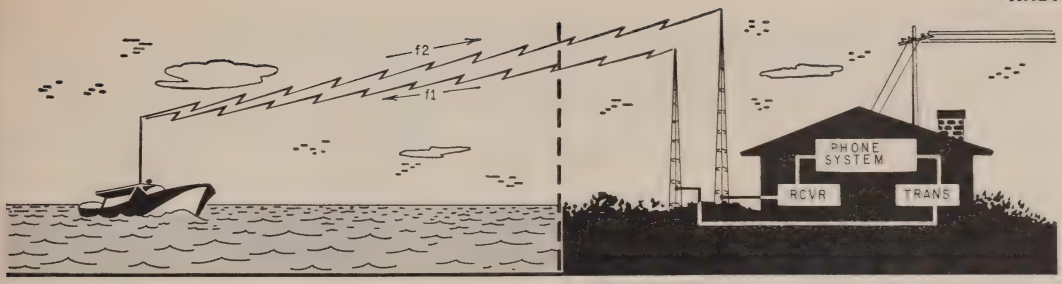

Fig. 2—Duplex transmission uses one frequency for transmitting and another for receiving.

counter or a surplus BC-221 (or equivalent) frequency meter. A direct-reading modulation meter or an oscilloscope is used to determine a transmitter's modulation capability.

While most rf signal generators used for servicing home radio receivers also cover the marine band, a professional-grade rf signal generator will help the technician do a better job. A BC-221-M frequency meter which produces a modulated signal may also be used as an rf signal source for receiver alignment.

Unfortunately, direct-reading, laboratory type rf wattmeters are designed for measurements at a 50-ohm impedance and serve as a 50-ohm dummy load. While impedance-matching networks can be used, an rf ammeter in series with a 10-ohm (typical marine antenna) dummy load is generally used for measuring transmitter output.

Tube failures and erratic operation are minimized by checking tubes on a really critical tube tester which measures dynamic mutual conductance. In addition, tubes should be checked for grid emission with grid-circuit testers or general-purpose tube testers equipped for grid-emission tests. A tube which checks out OK on an ordinary tube tester may have grid emission that can cause erratic receiver performance.

Another useful shop tool is a high-grade communications receiver for monitoring marine radio channels as well as for checking transmitters for spurious radiation.

Field servicing

A boat owner can remove his radiotelephone from his boat and bring it to a shop for servicing by a licensed technician. He can also reinstall it himself. But he may adjust only the front-panel controls, leaving all other adjustments to a licensed technician.

For optimum results the radiotelephone should be tuned up on the boat, at least initially. This must be done by a licensed technician.

Among his chores is determining the transmitter frequencies. This is done with a portable frequency meter such as a surplus BC-221 which was recently checked for accuracy. He measures the transmitting frequency of each channel, noting in the log the exact frequency measured, not just "OK."

He can also align the receiver, using the BC-221 as a signal generator. (The BC-221-M produces a modulated signal.) Or he can bring along a portable rf signal generator. It should be a battery-operated type unless he also wants to bring along a dc-to-ac converter.

When extensive transmitter adjustments have to be made, a dummy antenna is used to avoid interfering with others on the same channel.

With the radiotelephone connected to the boat's antenna and ground, the transmitter is tuned for maximum output. An antenna current indicator is a built-in feature on most sets, and generally consists of a shunted pilot lamp in series with the antenna. When the transmitter is adjusted properly, the antenna indicator lamp increases in brilliance when the transmitter is modulated.

Sometimes it is convenient to know if the transmitter is putting out its rated power. This is determined by using a dummy antenna load equipped with a series rf ammeter as shown in Fig. 3.

Transmitter power output is calculated by multiplying the square of the antenna current in amperes by the load resistance in ohms ($W = I^2R$). If the current is 0.5 ampere and the load is 10 ohms, the power output is 2.5 watts. If the current is 1 ampere, the output is 10 watts since $1 \times 1 \times 10 = 10$.

Some technicians like to use an rf ammeter for tuning a transmitter to its antenna. This may create problems. Inserting the meter into the antenna circuit, especially if it is mounted in a metal box, can add capacitance to the circuit which will not be there when the meter is removed. It is best to tune the transmitter to its own antenna, using the built-in antenna current indicator only.

Personnel requirements

Technicians who service transmitters must either have a suitable license or work under the direct supervision of another person who holds the proper license. For servicing radiotelephone equipment, a first- or second-class radiotelephone operator's license is required.

This license may be obtained by any citizen of the United States who can pass the written test. The test covers basic electronics theory, radio transmitters and FCC regulations. No code test is required. The test for the first-class license is the same as for a second-class license except that additional questions on advanced electronic theory are included.

The test may be taken at any of the FCC field offices which are located in most of the nation's key cities. Information about operator licenses and location of field offices may be obtained by writing to the Federal Communications Commission, Washington 25, D.C.

Hams have an advantage in the marine radio field since they are already familiar with tuning of transmitters. However, a ham ticket won't do for servicing commercial marine transmitters. You must also have a commercial ticket.

FCC licenses

A radio station license, available without cost from the FCC, is required for all marine radio equipment. The license covers a specific boat only and permits the use of a specific transmitter. Hence, a radiotelephone may not be used except on the specified boat without the express authority of the FCC.

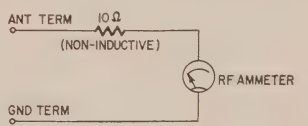

Fig. 3—Dummy antenna equipped with an rf ammeter measures transmitter output.

FCC form 501-A-1 is used for applying for a ship radiotelephone license. These forms are available from the Federal Communications Commission, Washington 25, D.C., or any of its field offices as well as from manufacturers of marine radio equipment and their dealers.

Only US citizens are eligible for FCC ship and operator's licenses. The ship radio can be operated only by a licensed operator or under his supervision. A restricted radiotelephone operator permit, obtained by filing FCC form 753-1, will suffice.

So far we have seen what a tremendous business marine radio is and we have gone over the procedures of radiotelephone operation and what it takes to run a marine radio repair shop. Next month we will take a look at a typical radiotelephone's construction and go over a few hints leading to more effective use of marine radio by the weekend sailor. TO BE CONTINUED

TWO MULTIBAND TRANSISTOR SETS

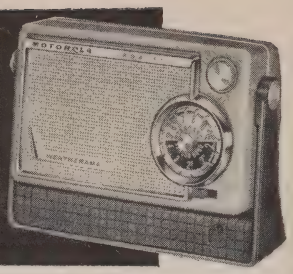

Philco Trans-World

Motorola Weatherama

By ROBERT F. SCOTT
TECHNICAL EDITOR

ONLY a few years ago transistor receivers were insensitive novelties that picked up a few local broadcast stations. Now, there are literally hundreds of transistor models whose sensitivity, selectivity and output equal or surpass many tube type portables. Also, the transistor has made possible multiband portables whose tube versions were often impractical because of bulk, weight, cost and frequent unavailability of special batteries. Transistor portables are less expensive to operate, are generally smaller and lighter, and use standard flashlight batteries that can be obtained almost anywhere in the world.

In the August, 1958, issue of RADIO ELECTRONICS we discussed the Magnavox and Zenith all-wave transistor portables. Now we will describe the Philco model T-9 Trans-World and Motorola 6X39 Weatherama receivers.

Philco model T-9

This is a nine-transistor model covering from the bottom of the broadcast band to 18.2 mc in seven ranges: 540–1620 kc and 2.0–4.0, 4.0–8.0, 9.4–9.9, 11.4–12.0, 14.8–15.6 and 17.2–18.2 mc. A logging scale is directly coupled to the wave-band switch and always comes to rest under the band in use.

The set uses six standard flashlight cells—two as a stabilized 3-volt supply for the oscillator and four as a 6-volt supply for the rf amplifier, mixer, detector and if and af amplifiers. The circuit of the T-9 is shown in Fig. 1. Partial schematics of rf, mixer and oscillator circuits are shown in Figs. 2 and 3.

The rf amplifier is a Philco T1010 transistor similar to the SB103/2N346 surface-barrier type designed for rf and video amplifier service and for oscillators working up into the 60–75-mc range. The rf amplifier is connected in a common-base circuit—equivalent to a grounded-grid vacuum-tube amplifier. Collector and emitter currents are common to the base circuit, providing 100% negative current feedback. This results in a current gain of less than unity and good isolation between the input and output circuits.

Although current gain is less than 1, the common-base circuit provides approximately the same voltage gain you would get with this transistor in a common-emitter arrangement.

On the broadcast band the receiver uses a built-in ferrite-rod (Magnecore) antenna or an optional external antenna coupled to the set through a 7.5-$\mu\mu$f capacitor. The incoming signal is developed across a parallel-tuned circuit consisting of the primary of the ferrite-rod antenna tuned by a 442-$\mu\mu$f capacitor.

The developed signal is transformer-coupled to the emitter of the rf amplifier through a secondary winding which matches the comparatively low impedance of the transistor's input circuit. Emitter bias is provided by a well-filtered and decoupled voltage divider consisting of R5, R8, R14 and R15 and dropping resistors R1 and R9. This bias is stabilized by the comparatively heavy bleeder current through R14 and R15. The base is grounded for rf by a .04-μf capacitor and is returned to the avc line.

The rf amplifier's output is developed across the primary of an rf transformer tuned by the second 442-$\mu\mu$f section of the six-section tuning capacitor. The small amount of neutralization that may be required to offset feedback through stray coupling is provided by feeding some collector signal voltage back to the emitter through C6, the secondary of the antenna coil and the 3.3-μh rf choke.

The oscillator uses a Hartley circuit with feedback between collector and emitter. The oscillator coil is tuned by the remaining 442-$\mu\mu$f section of the tuning gang in series with a 560-$\mu\mu$f padder. Oscillator operating conditions are critical for optimum performance, so separate flashlight cells are used to stabilize oscillator voltage and current.

The mixer is a common-base arrangement with the signal voltage fed into the base circuit through the secondary of the rf transformer. Oscillator voltage is injected into the emitter circuit from a tap on the oscillator coil. The mixer's emitter bias and the oscillation injection are adjusted for maximum conversion gain for the band in use. The 455-kc if signal is taken from the collector and fed to the if amplifiers.

Fig. 2 shows the T-9's front-end circuitry for the broadcast band. A similar arrangement is used on shortwave bands 1 and 2, covering 2–8 mc. On the 2–4-mc band, antenna transformer T1 and its trimmer replace ferrite-rod antenna and trimmer VC10; rf transformer T8 and its associated trimmer replace T7 and its trimmer, and oscillator transformer T15 with trimmers and padders replaces T14 and allied components. Similar substitutions are made when switching to the 4–8-mc range. Note well that the three 442-$\mu\mu$f sections of the tuning capacitor are used on the three lower frequency bands.

On the 31-, 25-, 19- and 16-meter bands the circuit is as shown in Fig. 3 with the oscillator operating *below* the

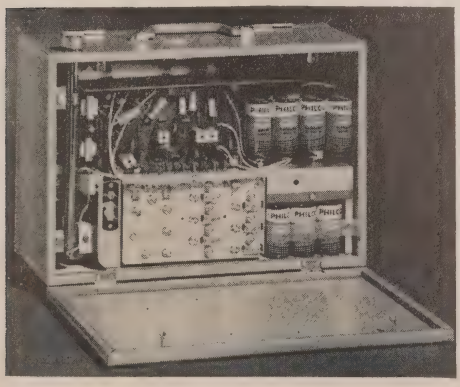

Inside the Trans-World's case. Storage space for four extra batteries is provided.

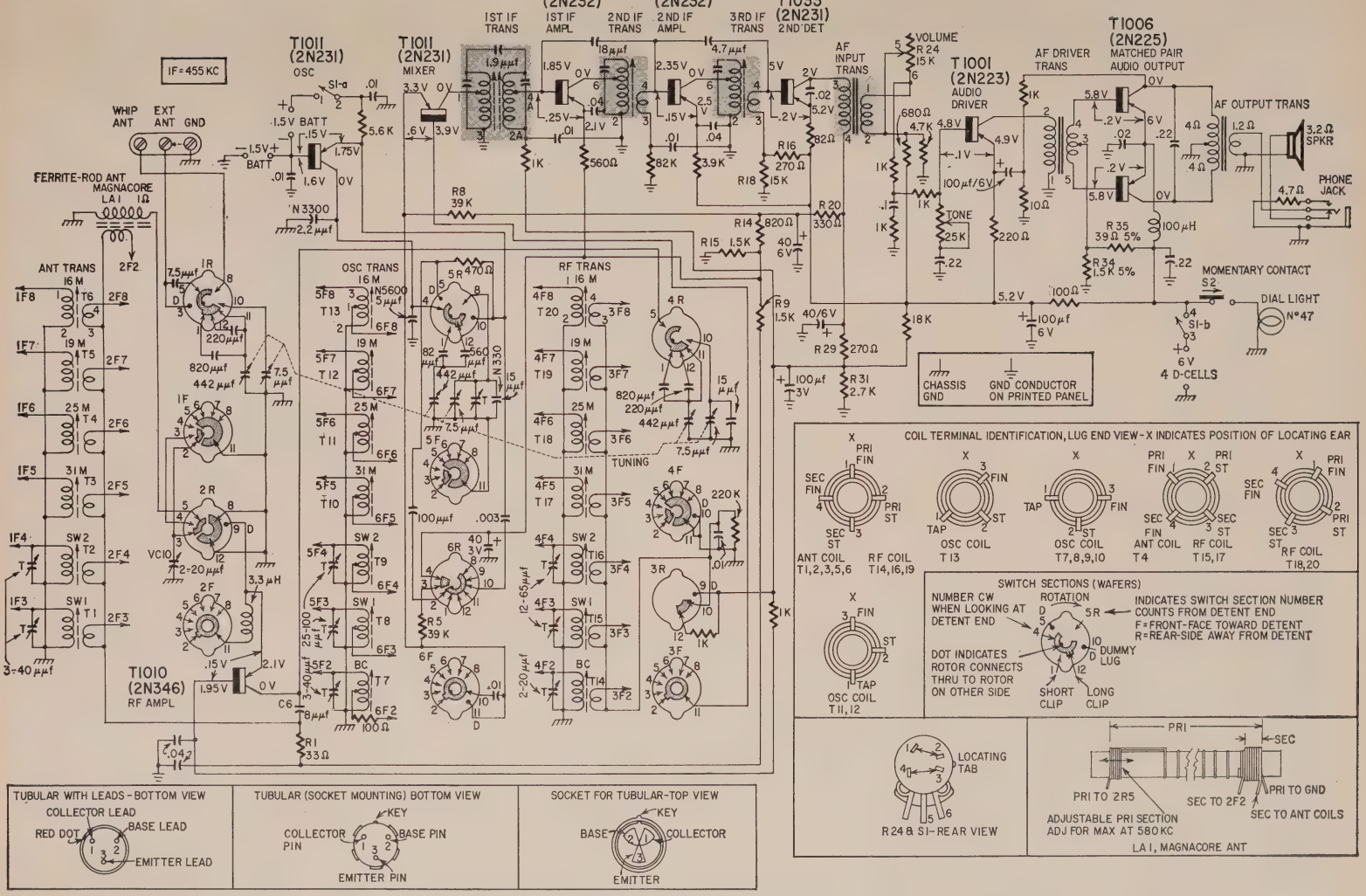

Fig. 1—Circuit of the T-9 portable. The bandswitch is in the broadcast position.

signal frequency. Here the circuits are tuned by the 7.5-$\mu\mu$f sections of the tuning capacitor. The emitter bias for the mixer is varied by altering the values of the biasing resistors to maintain optimum conversion gain.

The 455-kc if amplifier uses high-gain p-n-p surface-barrier transistors in common-emitter circuits. Some early sets use T1012's as if amplifiers, and later sets have T1360 and T1361 transistors in the first and second stages, respectively. In emergencies, either can be replaced by a 2N232. The base–collector capacitance is high enough to develop considerable positive feedback from collector to base. To counteract this feedback and reduce the tendency to oscillate, the stages are neutralized by a negative feedback voltage from the collector to the input circuit.

This voltage is taken from the secondary of the if transformer and applied to the base through an 18-$\mu\mu$f capacitor in the first if stage and a 4.7-$\mu\mu$f unit in the second. The voltage available for neutralization varies inversely as the stepdown ratio of the if transformer, so larger neutralizing capacitors are needed on stages with the greatest stepdown ratio on the output transformer.

The detector is biased class B by current flowing through a voltage divider consisting of R16 and R18 in series between the 5.2-volt line and ground. The voltage across R16 is very low and the bias current through the base is almost zero. Thus the detector transistor is almost cut off and very little current flows in its collector circuit.

Collector current flows through two parallel dropping networks. One consists of R15, R14 and R20, and the other is formed by R29 and R31. When no signal is being received, little or no collector current flows through the networks.

However, when a signal is tuned in, collector current increases and the collector becomes more positive in proportion to signal strength. The variable dc voltage developed across the load networks is tapped and used for avc. The voltage across R31 is applied to the rf and first if amplifiers on all bands and to the mixer on the broadcast band only.

The detector is transformer-coupled to the audio amplifier through the collector circuit. The first audio stage (driver) is a common-emitter type with the volume and tone controls in its base circuit. The driver is transformer-coupled to the 0.25-watt class-B push-pull output stage using 2N225's. The output stage uses a common-emitter circuit with base bias provided and stabilized by a voltage divider consisting of R34 and R35. The phone jack is arranged to cut out the speaker when

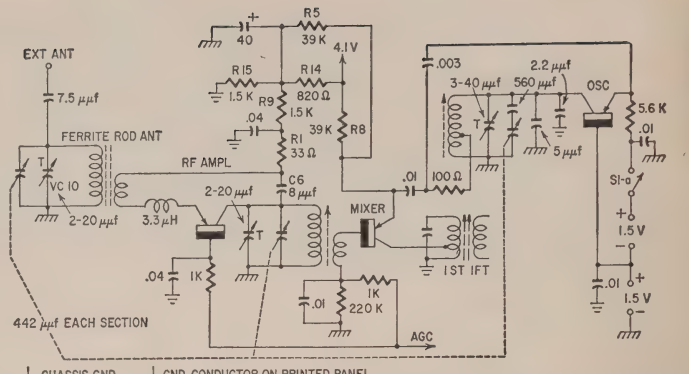

Fig. 2—Partial schematic shows the T-9's broadcast-band antenna, rf, oscillator and mixer circuits. Except for coils and trimmers, SW1 and SW2 bands are similar.

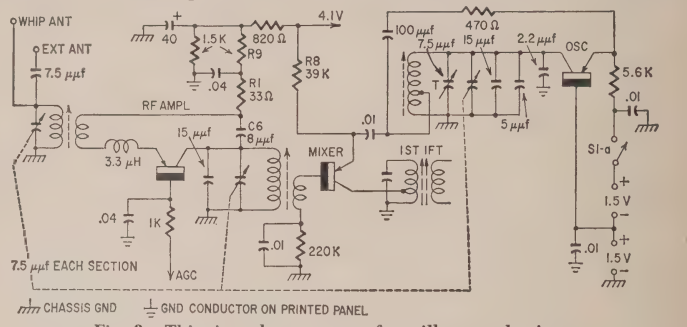

Fig. 3—This time the antenna, rf, oscillator and mixer circuits of the T-9 are shown for the 16-meter band.

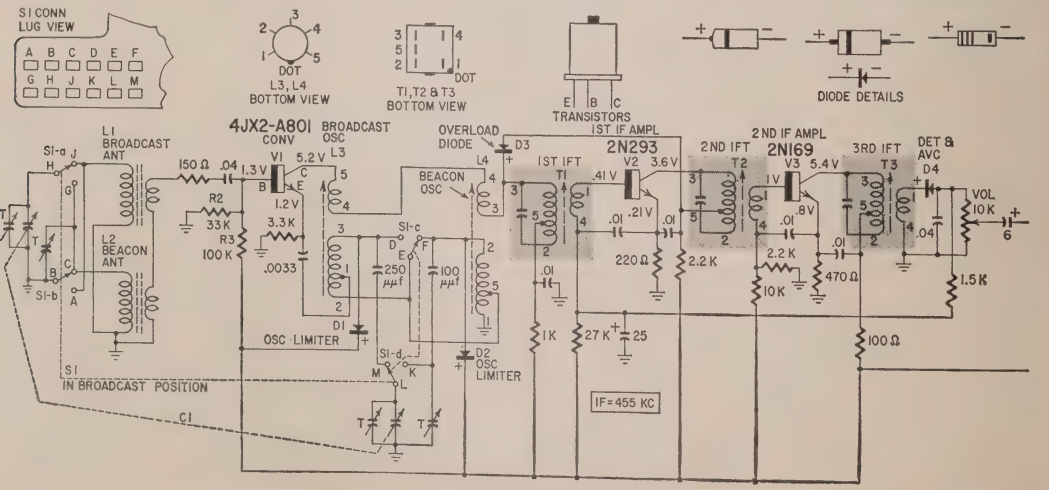

Fig. 4—The

phones are used.

Motorola Weatherama

The little Motorola model 6X39 is a compact, pocket-size transistor portable covering the standard broadcast and the 200–420-kc weather and aircraft beacon bands. It will probably be very popular with private pilots, boat owners, hunters and others whose hobbies or vocations depend on frequent accurate weather reports. The set is 6½ inches wide, 4⅞ inches high (with handle down) and 2½ inches deep. Weight is only 2¼ pounds.

The Weatherama uses six transistors and four germanium diodes. It runs for about 200 hours on four penlight cells and considerably longer on type ZM-9 or equivalent mercury cells. It has two ferrite-rod antennas built into the handle.

The circuit of the 6X39 is shown in Fig. 4. Bandswitch S1 is a four-pole double-throw slide type located just below the tuning dial. The antenna is selected by S1-a and the unused loop is shorted out by S1-b. The secondaries of the loop are in series and capacitance-coupled to the shunt-fed base of the converter. This is a special n-p-n transistor (Motorola 4JX2-A801) with its base biased slightly positive with respect to the emitter for detection. Base bias is provided by voltage divider R2–R3.

Oscillation is provided by regenerative coupling between the collector and emitter. This is a tickler–feedback oscillator similar to its vacuum-tube equivalent. The emitter connection is tapped down on the tuned winding to provide optimum matching and to reduce damping. The ticklers are close-coupled to the tuned windings and are in series with the collector circuit. S1-c short-circuits the unused oscillator coil and S1-d connects the tuning capacitor across the coil for the band being used.

The converter uses an interesting innovation to insure uniform operation on both bands without using factory-selected or hand-picked transistors. Characteristics of transistors vary considerably—even in identical types—so performance as a converter may vary over wide ranges. If the oscillator supplies too much signal, the set will have birdies, spurious oscillations and other troubles. D1 and D2 are amplitude limiters and prevent these troubles when an over-active transistor is used.

These diodes are connected between the hot ends of the oscillator-coil primaries and the positive side of the battery. They are back-biased so they do not conduct under normal conditions. A transistor that is too active on either or both bands develops an rf voltage that overrides the blocking bias and lets the diode conduct on positive half-cycles. This damps the tuned oscillator coil and reduces the oscillator output.

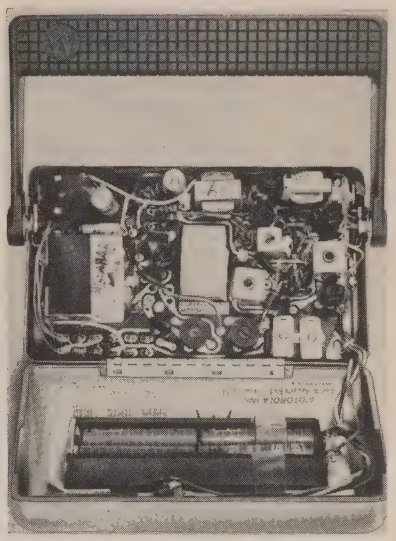

The Weatherama with back open for battery replacement.

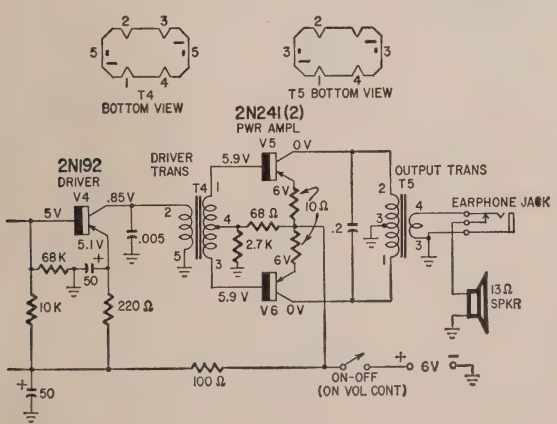

2-band Weatherama's circuit.

The first and second if amplifiers are common-emitter types using high-gain n-p-n type 2N293 and 2N169 transistors, respectively. The circuit design and wiring layout combine with comparatively low operating voltages to make neutralization unnecessary. Avc voltage is applied to V2's base.

In addition, diode D3 is used to help prevent overloading on signals too strong for the avc circuit to handle. The diode is biased by dc with its cathode approximately 0.9 volt positive with respect to its anode, so it cannot conduct on signals of average strength. Incoming signals exceeding a specific level develop enough rf voltage across the diode to cause it to conduct. During conduction, D3 reduces the gain of the first if stage by damping and reducing the effective Q of the tank circuit of the first if transformer.

The detector diode is connected to T3's low-impedance secondary. The cathode returns to ground through the transformer. The ac signal output from the anode has a dc component that is filtered and applied to the first if transistor for avc. The stronger the incoming signal, the more negative the dc voltage, so the if gain is reduced in proportion.

The detector's ac output is R-C-coupled to the 2N192 p-n-p driver. This stage is stabilized by tying its base to a voltage divider and by the 220-ohm resistor in its emitter return.

The 2N241 power amplifiers are operated class B and are biased to cutoff by the drop across the 2,700-ohm resistor in the common base return. Temperature stability is provided by the 10-ohm resistors in the emitter returns. The speaker has a 13-ohm voice-coil impedance. It is disconnected when phones are plugged into the jack on the rear of the case. A 15-ohm earphone is available as an accessory. END

THE QRM DODGER

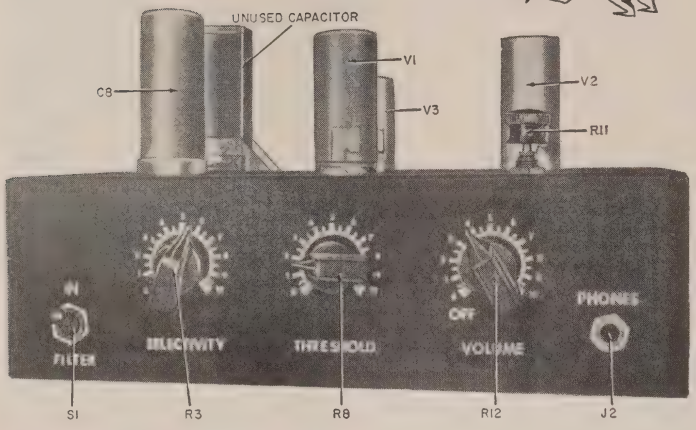

By DON M. WHERRY, W6EUM

Three-tube circuit ends background noise, fading and ringing. Passes a clear, clean CW signal to your phones

HOW would you like to sit down to your schedule tonight and copy that CW traffic with absolutely no QRM or background noise, complete silence between characters, an S8 signal 200 cycles away completely inaudible, no fading, ignition noise or racket from the XYL's vacuum cleaner, none of the ringing so common to highly selective circuits—just a pleasant tone of your own choosing? Impossible? Not at all.

It has long been my objective to develop an auxiliary unit to go with a standard amateur receiver which would increase the readability of code signals. The limiting factor has always been the ringing when sharply peaked circuits are used, especially at audio frequencies. There are low-frequency and magnetostrictive if circuits which give remarkable results but they are costly enough to be beyond most of us. Therefore the unit shown in Fig. 1 was developed. It consists of a 12AU7 cathode-follower input, an audio filter, amplifier, rectifier, keyer tube and neon-lamp sawtooth oscillator.

The input, which may come from the phone jack or any other convenient audio takeoff point, is fed into the grid of the cathode-follower input tube. This type of input circuit is used for two reasons: to isolate the unit from the signal source and to furnish a low-impedance input of approximately 125 ohms to the tone filter.

The filter is a series-resonant circuit consisting of a choke (L1) and a series capacitor (C2) which, with the SELECTIVITY control (R3) and cathode resistor (R2), form a resonant circuit. The resonant frequency of the circuit is approximately 550 cycles. This may seem low, but remember that selectivity is a percentage proposition, so the lower the frequency, the higher the selectivity.

A lower frequency than specified here may be used, provided it doesn't present tuning problems to the operator. I have used experimental circuits of about 180 to 200 cycles with astonishing results, getting tremendous selectivity before ringing became objectionable. However,

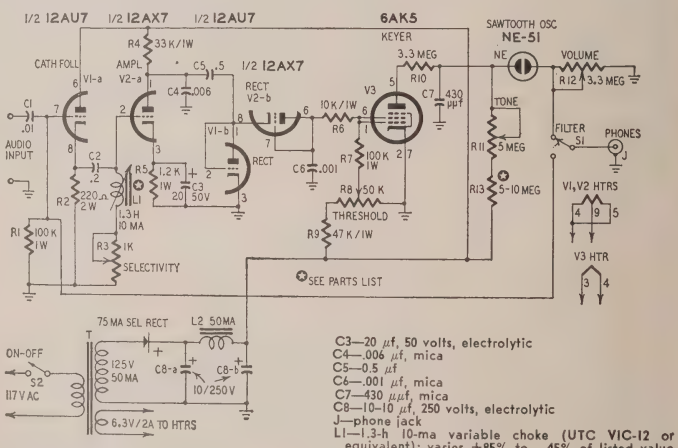

R1, 7—100,000 ohms
R2—220 ohms, 2 watts
R3—pot, 1,000 ohms, wirewound
R4—33,000 ohms
R5—1,200 ohms
R6—10,000 ohms
R8—pot, 50,000 ohms
R9—47,000 ohms
R10—3.3 megohms
R11—pot, 5 megohms
R12—pot, 3.3 megohms, with spst switch S2
R13—5–10 megohms, adjust for proper range of tone on R11
All resistors 1 watt unless noted
C1—.01 μf
C2—0.2 μf, mica if possible
C3—20 μf, 50 volts, electrolytic
C4—.006 μf, mica
C5—0.5 μf
C6—.001 μf, mica
C7—430 μμf, mica
C8—10-10 μf, 250 volts, electrolytic
J—phone jack
L1—1.3-h 10-ma variable choke (UTC VIC-12 or equivalent); varies +85% to —45% of listed value
L2—50 ma, ac-dc choke
RECT—selenium, 130 volts, 75 ma
S1—spdt toggle
S2—spst on R12
T—power transformer: primary, 117 volts; secondary, 125 volts, 50 ma; 6.3 volts, 2 amp
V1—12AU7
V2—12AX7
V3—6AK5
NE-51, neon bulb
Chassis, 10 x 5 x 3 inches
Tube sockets, 9-pin miniature (2)
Tube socket, 7-pin miniature
Tube shields, for 9-pin miniatures (2)
Tube shield, for 7-pin miniature
Miscellaneous hardware

Fig. 1—Circuit of the QRM dodger.

There's no crowding under this chassis.

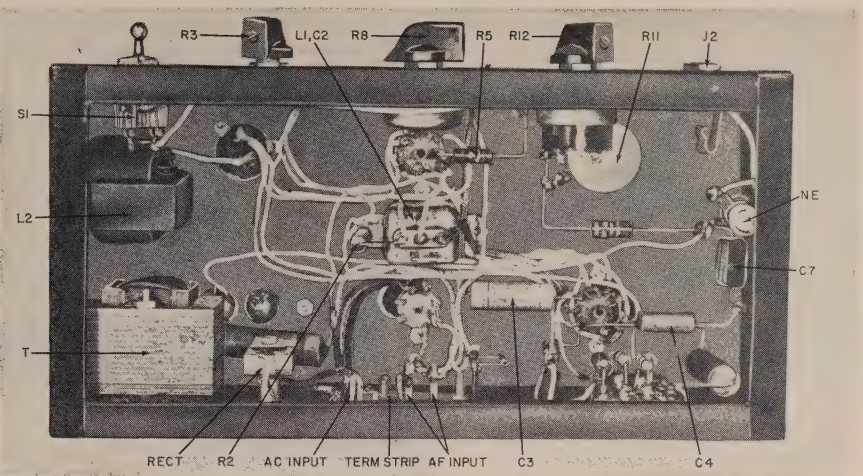

Fig. 2—Minimum and maximum filter characteristics afforded by the simple unit.

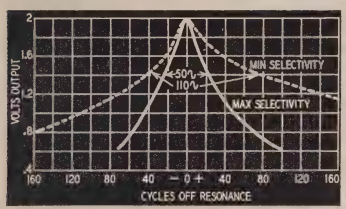

such low frequencies may present an impossible tuning situation unless the receiver has a wide bandpass.

Returning to the circuit, the SELECTIVITY control (R3) operates on the principle that, as the series resistance of a tuned circuit increases, the Q decreases and bandpass increases. Actually overall bandpass is not appreciably increased but rather the gain of the resonant circuit is decreased, which moves the nose down, giving an apparent increase. However, the results are the same.

L1 is an audio choke, which may seem to have a low inductance for the frequency used but was chosen deliberately. If the circuit is to resonate at the desired frequency, a rather large capacitor C2 is necessary. Resistor R2 in the cathode circuit of V1-a, which sets the current through that tube, also limits the selectivity.

The two selectivity curves (Fig. 2) show "cycles off resonance vs. volts output." The value of the output voltage is chosen arbitrarily for explanation purposes only. The half-power point is approximately 50 cycles wide at the maximum selectivity position, and approximately 110 cycles at the minimum.

A different value of resistance for the SELECTIVITY control, or a different resonant frequency, gives a different curve. It would seem possible that by simply adding more filter sections the amount of selectivity would be unlimited in a device of this sort. But with an excessive amount of filter the high Q of the circuit causes ringing. This appears as tails to the code characters and also excessive softness at the beginning. The ringing normally permissible in this unit far exceeds that which would be objectionable for ordinary use. This is partly due to the ear being a very poor audio-level indicator and also that this unit uses only a small portion of the code character envelope.

The use of a variable inductance for L1 is desirable but not necessary. Any good audio choke can be substituted if the proper value capacitor, for the frequency desired, is used in series. In fact a common filter choke can be used but with reduced selectivity due to the low Q of such reactance.

The output from the audio filter is fed to the grid of a 12AX7 triode amplifier. The plate of this tube is bypassed quite heavily to attenuate the higher frequencies which get by the tone filter.

The output of this tube is then fed, through capacitor C5, to a voltage-doubler rectifier circuit made up of the remaining halves of V1 and V2. These triodes operate satisfactorily as rectifiers when they are diode-connected.

The rectifier's output is then filtered and applied to the 6AK5 keyer or trigger tube, which is connected as a high-mu triode. This keyer tube has a neon sawtooth oscillator in its plate circuit. The keyer turns the neon oscillator on and off to correspond to the code characters received. It does this by drawing, with no signal present, such a large current through resistors R13 and R11, that the voltage at the neon lamp is insufficient to allow it to ionize, hence no oscillation and no output. In use, receiver noise, etc., puts a dc voltage at the keyer's input, sufficient to cut off plate current and allow the neon oscillator to run continuously. The THRESHOLD control (R8) removes this noise voltage by applying a small positive potential to the keyer tube's grid, which holds it at a value that permits the tube to conduct at all times, when no signal is present. It, in effect, cancels out the small negative noise voltage present. The negative voltage developed by a signal then overrides the bias or threshold voltage, allowing the neon to oscillate. Potentiometer R11 controls the oscillator frequency. The output voltage is taken from across the VOLUME control (R12) which is inserted in the ground lead of the neon lamp.

In setting up this unit for operation, the audio input is connected to the receiver. The receiver's gain is set at approximately the normal operating position. Then with the power on and the filter in, adjust the THRESHOLD control until, with no signal tuned in, background noise just fails to trigger the neon bulb. Now, as signals are tuned, the voltage rises, cutting off the trigger tube and keying the neon oscillator. A signal of 0.25 to 0.5 volt to the keyer grid will key the neon oscillator.

With the proper adjustment of the THRESHOLD, the keying voltage level can be set above any interfering signal. Suppose a signal is placing 1.5 volt at the keyer's grid. The THRESHOLD could be set at 1.5 volts bias and no trigger action will occur. Now, if the signal we wish to copy places 2 volts at the keyer's grid, we have a differential of 0.5 volt available for keying. We are now copying a signal only 0.5 volt stronger than another on the same frequency.

This unit opens a large field of applications for highly selective audio circuits as a simple, reliable way to obtain and use high audio selectivity without the effects of prohibitive ringing. It opens the possibility of multiple code channels on one rf frequency, each using a different audio tone. (This would not apply to amateurs of course.) One transmitter could carry a number of simultaneous code transmissions into the ultrasonic region; ultrasonic code on voice channels and a means of QRM–QRN-free communication for amateurs. END

2–30-cycle very-low-distortion sine waves, for testing amplifiers, oscilloscopes and speakers are delivered by this handy instrument

BENCH R-E TESTED

By TOM JASKI

DOWN LOW with an AUDIO OSCILLATOR

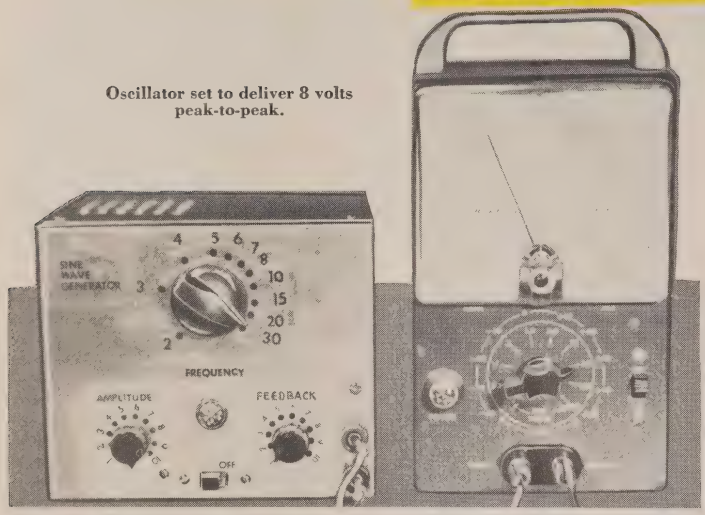

Oscillator set to deliver 8 volts peak-to-peak.

MOST kit type audio oscillators produce a good sine wave down to about 20 cycles. But if you should want to test anything below 18 or even 10 cycles, not much is available as a sine-wave source.

Why might you want to go down that low? Well, most oscilloscope amplifiers are rated down to 2 or 3 cycles per second, many speakers and some amplifiers down as low as 10 cycles. To test their performance at these low ranges, you'll need a signal source. If you are interested in developing or building an electronic organ, and need a source for 32-foot low C, you need an oscillator that can produce 16 cycles. And again, you might want to use a temporary tremolo or vibrato setup requiring frequencies as low as 4 cycles.

For all such uses, the little inexpensive oscillator described here is useful. It produces a very good sine wave from 2 to 40 cycles, supplementing the low range of your present equipment. Generating pure 2-cycle sine waves is difficult, unless you are willing to use a beat oscillator actually containing two oscillators and producing the low-frequency sine wave by beating one against the other. A beat oscillator has the disadvantage that it is difficult to stabilize—any instability in the basic oscillators may be added to produce annoying drift.

This little oscillator does not produce an absolutely pure sine wave, but it does not have more than a few percent distortion, and we will explain how you can get rid of even that with some extra parts. It has turned out to be remarkably stable. The one critical part for stability is the Wien-bridge dual potentiometer (R1), which should be rated at 2 watts for satisfactory stability.

Tested by a member of the staff of RADIO-ELECTRONICS, the oscillator's lowest frequency was 2.93 cycles and the maximum frequency above 30 cycles. No-load maximum output was 30 volts. Oscilloscope traces agreed with those of Fig. 2 of the article.

Output (volts peak-to-peak)	Load (ohms)
30	none
20	1,000
15	470
3	82
2	52

Overall operation is highly satisfactory but the compactness of the unit results in a large amount of heat given off by the unit (the case measured 100°F after 2 hours operation). A slightly larger case will eliminate this problem.

Fig. 1 shows the complete circuit diagram. As you can see, it is a conventional Wien-bridge oscillator, but with very large capacitive values and more than usual number of filament lamps. (Thermistors have been used in some low-frequency units in place of the lamps to get greater stability.) The extra lamps are in the cathode of the 6AQ5 feedback tube and help to clean up the waveform. V3 is a simple cathode follower which prevents oscillator circuit loading which would result in a frequency change.

With R5 at minimum resistance the oscillator just oscillates, but the waveform is purest at this point. Figs. 2-a and 2-b show actual oscillograms made with this oscillator at 4 and 20 cycles, respectively. Some distortion of the sine wave is visible at the lower peaks but, as you can see, it is not a very serious amount.

Construction and circuit details

Parts placement is not at all critical. If you like a different arrangement, there is no reason why you shouldn't use it. The underchassis photo makes things look very crowded, but underneath the large capacitors, C3 and C4, there is plenty of room.

If you need a very pure sine wave at these low frequencies, the simplest solution is to include a low-pass filter network at the oscillator's output. This works because, no matter how distortion is originally created on the sine wave, most of it represents the creation and inclusion of higher harmonics. Eliminating the higher harmonics will clean up the wave. Fig. 3 shows a typical low-pass filter which will do a creditable job at all the frequencies produced by this oscillator, but it will, of course, result in some attenuation at the upper end of the range. Attentuation is not a serious problem; the oscillator puts out (for most purposes) a large signal anyway. Incidentally, the oscillograms in Fig. 2 were taken without any filter.

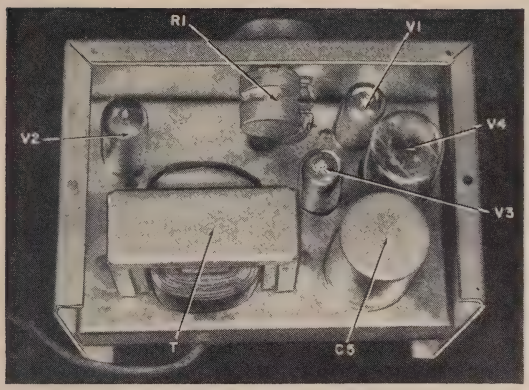

Top inside view of the oscillator.

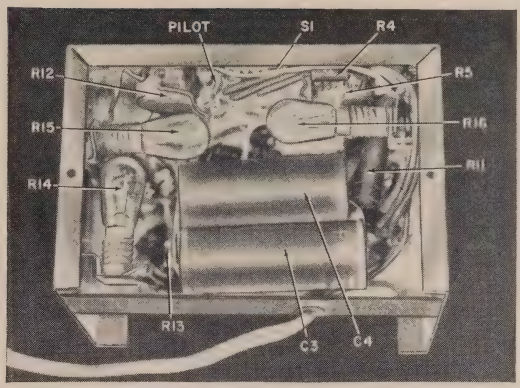

The three lamps are mounted under the chassis.

With the filter shown, no distortion could be detected visually.

Other than testing amplifiers, scopes and speakers, what are some uses for this little oscillator? Well, you could use it to determine rumble frequency of a turntable by making Lissajous figures on a scope, using the oscillator for horizontal deflection. You could amplify the signal with a very simple power amplifier and apply it to a solenoid to rock a photographic tray or tank slowly. You can apply the signal to a reactance tube to frequency-modulate another oscillator, giving a vibrato effect for electronic organs or other musical instruments. Vibrato and tremolo usually require 4 to 6 cycles per second. Originally designed to provide a subsonic signal for psychophysiological tests, there are many other uses for it. An important use is in checking modern feedback amplifiers whose response below 15 cycles is important in determining stability.

Calibration is a simple process. The 30-, 20-, 15-, 10- and 5-cycle points, and even 3 cycles, can easily be checked with Lissajous figures on an oscilloscope, using 60-cycle line voltage for comparison. Below 5 cycles, a stopwatch and counting will work.

[J1 is positive to ground, so use a blocking capacitor when feeding an amplifier that does not have one in its input circuit. Also, V3's bias may be upset when driving a low-resistance load. To avoid these difficulties, connect the positive side of a 250-volt, 100-μf (or higher) electrolytic to the arm of R12 and the negative side to J1. Connect a 1-megohm resistor between J1 and J2.—*Editor*] END

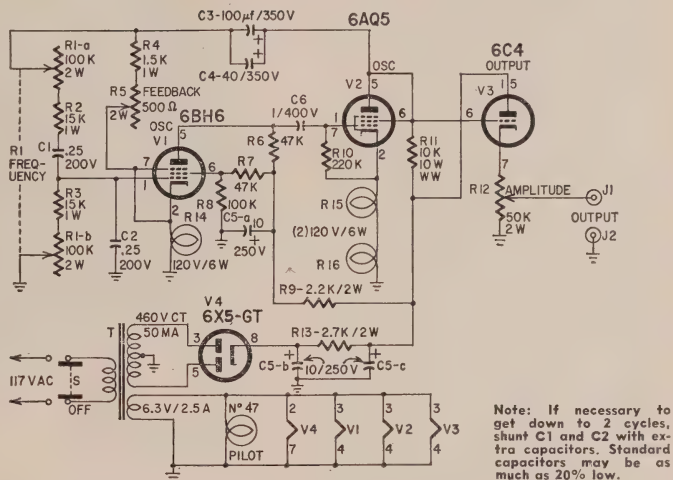

Note: If necessary to get down to 2 cycles, shunt C1 and C2 with extra capacitors. Standard capacitors may be as much as 20% low.

R1—dual pot, 100,000 ohms, 2 watts, linear taper (Ohmite CCU1041 or equivalent)
R2, 3—15,000 ohms, 1 watt
R4—1,500 ohms, 1 watt
R5—pot, 500 ohms, 2 watts, linear taper
R6, 7—47,000 ohms, ½ watt
R8—100,000 ohms, ½ watt
R9—2,200 ohms, 2 watts
R10—220,000 ohms, ½ watt
R11—10,000 ohms, 10 watts, wirewound
R12—pot, 50,000 ohms, 2 watts, log taper
R13—2,700 ohms, 2 watts
R14, 15, 16—6 watts, 120 volts, candelabra lamps
C1, 2—0.25 μf, 200 volts
C3—100 μf, 350 volts
C4—40 μf, 350 volts
C5—10-10-10 μf, 250 volts, electrolytic
C6—1 μf, 400 volts
J1, 2—3-way binding posts
S—dpst slide
T—power transformer: primary, 117 volts; secondary, 460 volts, 50 ma; 6.3 volts, 2.5 amps (Stancor PC-8418 or equivalent)
V1—6BH6
V2—6AQ5
V3—6C4
V4—6X5-GT
Case, 4 x 5 x 6 inches
Chassis, 1½ x 4⅞ x 5¾
Lamp sockets, candelabra (3)
Pilot-light assembly with No. 47 bulb
Miscellaneous hardware

Fig. 1—Circuit of the 4-tube unit.

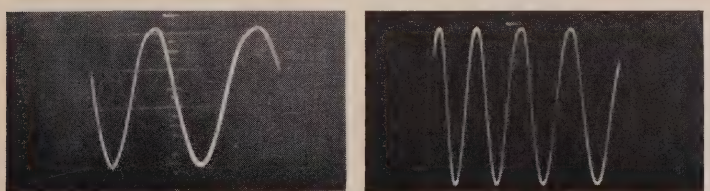

Fig. 2—Oscillograms of the sine wave turned out by the oscillator: a—4 cycles; b—20 cycles.

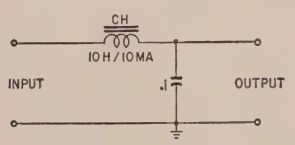

Fig. 3 — Low-pass filter to reduce further the slight amount of distortion present in the sine-wave output.

DC AC ATTENUATOR has many uses...

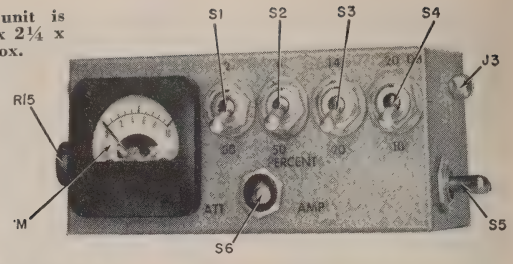

The compact unit is housed in a 5 x 2¼ x 2¼-inch box.

By I. QUEEN
EDITORIAL ASSOCIATE

A handful of valuable instrument that can be used for meter and oscilloscope calibration, as a db and output meter and for measuring voltage gain

THIS compact device makes little voltages out of big ones. It works on ac (line frequency and af) as well as dc, and is conveniently controlled by switches. Among its applications are: meter and oscilloscope calibration; db and output meter; measurement of voltage gain.

By flicking switches you can insert 2-, 6-, 14-, 20-db losses or any combination thereof. Loss maximum is 42 db, when all switches are up. When all are down (or out as shown in Fig. 1), the loss is zero—output equals input.

The complete circuit (Fig. 2) has four T-networks in series. Each requires three resistors to attain the desired loss and maintain correct impedance match. Attenuation values selected for this particular instrument are listed in the table. This also shows the *exact* resistance needed for the network plus the nearest *preferred* value.

From available resistors select those closest to the required values, using either an ohmmeter or bridge. If you plan to incorporate other attenuation values in addition to or instead of those given here, see page 98 of *Basic Audio Course** for resistors required.

The following table lists attenuation in db, corresponding percentage and switches to flip to obtain the desired values:

Loss db	*Loss %*	*Output— % of Input*	*Switches Thrown*
2	20	80	S1
6	50	50	S2
8	60	40	S1–S2
14	80	20	S3
16	84	16	S1–S3
20	90	10	S4
22	92	8	S1–S4
26	95	5	S2–S4
28	96	4	S1–S2–S4
34	98	2	S3–S4
36	98.4	1.6	S1–S3–S4
40	99	1.0	S2–S3–S4
42	99.2	0.8	S1–S2–S3–S4

Thus, if we want to attenuate a signal by 26 db, the table shows that we must flip S2 and S4. The loss will be 95% and the output will fall to 5% of the input. The third column is convenient because if it is multiplied by 10 it gives the *output in mv* when the input is exactly 1 volt. For example, if we need 40 mv for a certain test, we have it by switching to 28 db.

*No. 66, Gernsback Library.

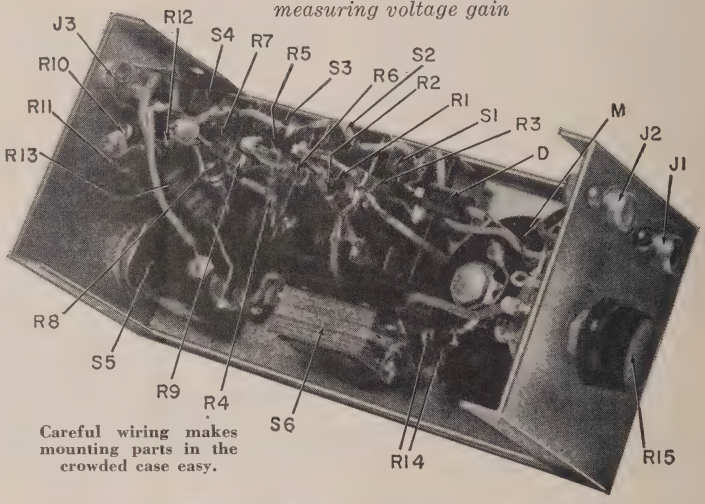

Careful wiring makes mounting parts in the crowded case easy.

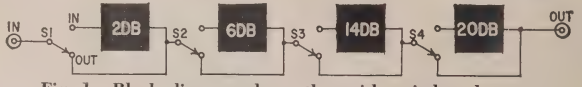

Fig. 1—Block diagram shows that with switches down—in out position—loss introduced by attenuator is zero.

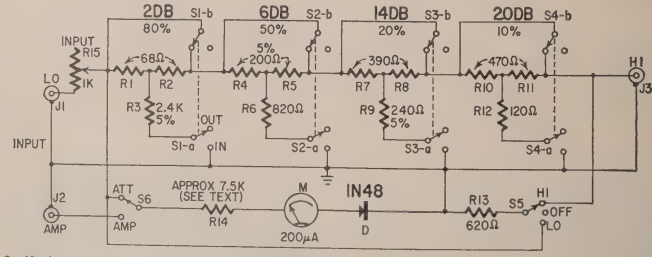

R1, 2—68 ohms
R3—2,400 ohms, 5%
R4, 5—200 ohms, 5%
R6—820 ohms
R7, 8—390 ohms
R9—240 ohms, 5%
R10, 11—470 ohms
R12—120 ohms
R13—620 ohms
R14—7,500 ohms
R15—pot, 1,000 ohms, miniature
All resistors ½ watt 10% unless noted
D—1N48
J1, 2, 3—phono jacks
M—200 μa, dc meter
S1, 2, 3, 4—dpdt toggle
S5—spdt, center off, toggle
S6—spst toggle
Chassis, aluminum box, 5 x 2½ x 2¼ inches
Knob
Miscellaneous hardware

Fig. 2—Circuit of the simple unit. Four T-networks in series provide variable attenuation. See text and chart for nearest attenuator resistor values. The circuit shows nearest preferred values to select from.

Radio-Electronics

17
ISSUES FOR
$3.74

SPECIAL
INTRODUCTORY
OFFER

Price is equivalent to 22c a copy. Saves you $2.21 over the newsstand price...or *6 ISSUES FREE!*

Please enter my subscription to **Radio-Electronics** for **17** months at **$3.74**

☐ I enclose payment ☐ Bill me ☐ New ☐ Renewal

NAME_____
please print

STREET_____

CITY_____ ZONE_____

STATE_____

These rates apply to U.S.A. (and possessions) and Canada only. **11-58**

FIRST CLASS
Permit 3062
Sec. 34.9, P. L. & R.
New York, N. Y.

BUSINESS REPLY CARD

NO POSTAGE STAMP NECESSARY IF MAILED IN THE UNITED STATES

Postage will be paid by

Radio-Electronics

154 West 14th Street

New York 11, N. Y.

Required Resistance Ohms		Nearest Preferred Value		Db Loss
Series	Shunt	Series	Shunt	
68.8	2,582	68	2,400*	2
199.3	803.4	200*	820	6
400.4	249.4	390	240*	14
490.4	121.2	470	120	20

* 5%

There are a few gaps in the db column, the maximum being 6 db (such as between 8 and 14). To interpolate within these spaces, note that each 0.1 volt change (from 1 volt) is equal to a change of approximately 1 db. Now suppose we wish to generate a signal that is 10 db below 1 volt dc. The number 10 does not appear in the chart, so we can proceed as follows: Adjust the input for a meter reading of 0.8 volt and switch to 8 db, or adjust the input for a meter reading of 1.4 volts and switch to 14 db. It is better to use *minimum* deviation from the midscale reading of 1 volt, so the first plan is better. Except when interpolating as above, the most convenient procedure is to set the meter to midscale.

If you are using ac instead of dc, note that a 0.2 volt change from the 2-volt midscale corresponds to 1 db. In any case each db is equal to a *10%* change from midscale or standard setting.

Circuit details

A sensitive meter mounted on the front panel indicates voltage. Resistor R14 is selected to provide mid-scale deflection with 1 volt dc. I found that 33,000 ohms across 10,000 ohms did the trick, so this pair became R14. This value will vary and must be determined by experimenting.

The meter circuit also accepts *ac*. Diode D simply chops off half of each ac cycle, leaving the other half to be read on the dc meter. On dc, the current flows through D into the meter.

Perhaps I was lucky, but tests show that my meter reads mid-scale with exactly 2 volts ac, so no calibration chart is needed. If the 2-volt ac point happens to be in some other spot, make a note of it so you can set the input to 2 volts ac at any time.

Each T-network is designed for 600 ohms. This means that when a 600-ohm load resistor is across its *output* terminals, the *input* will also measure 600 ohms. For example, consider the 6-db network shown in Fig. 3. Resistor values are approximate, and the dotted line shows the required load. Note that R_b is shunted by 800 ohms ($R_c + R_L$) to give an equivalent (between A and B) of 400 ohms, in series with R_a. Thus the input to this T-network is 600 ohms *when (and only when) the terminating load is 600 ohms.*

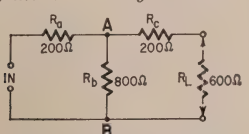

Fig. 3—This 6-db network delivers 50% of the input to the load.

It is also easy to show that the circuit of Fig. 3 delivers 50% of its input voltage to R_L. R_a is in series with an equivalent of 400 ohms. Thus one-third of the input is lost in R_a and *two-thirds* is transmitted. Of this fraction, one-fourth is lost in R_c and *three-fourths* is transmitted to R_L. The fraction appearing across the load is ¾ of ⅔, which is ½.

Whether one or more networks are used, only one load resistor is needed. It should always be across the last network. As shown for Fig. 3, when the output is 600 ohms (R_L) so is its input. Therefore any previous T-network (if used) is automatically terminated in 600 ohms, and so on.

In Fig. 2, R13 is the load resistor. It is selected from among low-reading 620-ohm resistors (5%). S5 is a spdt toggle switch with a center-off position. It switches R13 either across the HI (J3) or the LO (J1) terminals, whichever happens to be used as output. R13 is not needed when an external load across the attenuator is already terminated in 600 ohms. In that case, S5 is left in the off position.

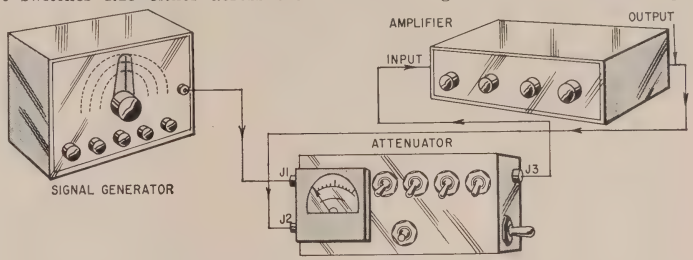

Fig. 4—This setup shows how to use attenuator to measure voltage gain of an amplifier.

The input potentiometer (R15) is normally left at zero resistance so that the device acts as a 600-ohm attenuator. The pot adjusts an input signal to a desired voltage and its use is described later.

All resistors in this device are ½-watt units, selected (as mentioned previously) from available preferred values.

After completing this instrument (and it shouldn't take long), be sure to test it. Switch in maximum attenuation and apply 20 volts dc at J3 (all switches up). The meter should hardly deflect. Switch off all but S4 (20 db), at which the deflection should read full scale (2 volts). In other words, the attenuator is set for 10% output or a 90% loss. Now add 2 db more (S1) and the needle should fall to 80% of full scale.

Switch off S1 and substitute S2 instead, leaving the needle at mid-scale. Switch S2 off and S3 on, at which the reading should drop to 20% of full scale. You may also test input resistance. Switch S5 to HI and measure the resistance across J1. It should be 600 ohms, no matter what combination of switches is left up.

If these readings are approximately correct (5% or better), your job is well done. For very high precision you will need careful selection of the resistors that go into these networks.

What will it do?

1. Meter calibration (dc)

Apply a known dc at J1. Adjust the INPUT potentiometer for a meter reading of exactly 1 volt. The output must be 600 ohms. Therefore, if the external circuit impedance is very high, switch in R13 across J3 the HI terminal.

You now have small fractions of a volt available. For example, if you need .08 volt, switch in 22 db. Note that accuracy is controlled by *resistors* and does not depend upon errors inherent in a meter or battery.

2. Ac calibration

The method is similar to dc calibration, except that the source may be a low-voltage transformer or audio generator. Either a meter or oscilloscope may be calibrated. To measure the amplitude of an unknown waveform on an oscilloscope, compare it with the known outputs from the attenuator. The resistive networks used here can be relied upon at all audio frequencies.

Calibration of ac meters is especially important. From time to time articles have described excellent meters for measuring weak ac voltages. The real problem is in how to *calibrate* the meters. Many ac meters have nonlinear scales, and the linearity becomes worse at lower ranges. This attenuator offers a very convenient means for accurate calibration.

3. Larger voltages

The setup used for ac calibration is limited by the meter's capability. Suppose you wish to measure in the range of 20 volts or more. Apply the unknown voltage at the HI terminals. This places the attenuator between signal and meter, and you can insert adequate loss to protect the meter. Suppose your meter reads 1 volt when S3 is the only switch in the circuit. This corresponds to 20% output, so your input is 5 volts. The 600-ohm termination must now be across J1. A maximum of about 25 volts is permissible across J3.

4. Db or output meter

Obviously this instrument can be used to measure or monitor the output of an amplifier, recorder or other device which has an output of about 1

volt or more. Just set the switches for a reading near mid-scale, so there will be room for increase or decrease. Changes in signal amplitude show up on the meter. If the rise is too great, insert additional attenuation as needed. Either dc or ac signals may be monitored.

5. Voltage-gain measurement

Although this is a variable-*loss* device, it can be used conveniently to measure *gain*. See Fig. 4. An amplifier is shown in series with the attenuator. By switching S6 between AMP and ATT, the meter compares outputs from the oscillator and the amplifier. When the readings are equal, attenuator loss must be the same as amplifier gain (in volts). Either value is read off the switch combination. To maintain accuracy, the attenuator output must be 600 ohms. Fortunately this is approximately the input to most common-emitter stages so additional termination (R13) is not needed. The amplifier should be terminated in its specified impedance load.

When equal readings are obtained (at both AMP and ATT positions of S5), note the setting of S1–S4 in db and convert to percentage. If, for example, the answer is 1%, the amplifier's voltage gain is 100.

Because of the gap in the db scale (such as between 8 and 14) it may not be possible to find the exact db gain of an amplifier. In other words, switching between ATT and AMP may not permit identical readings. When this happens, the meter itself is used to interpolate. Suppose, for example, that the switches are set to 8 db for closest comparison between AMP and ATT readings. When switched to AMP the meter deflects higher than midscale (which is convenient for the ATT setting).

As mentioned earlier in the article each 10% of change from a midscale reading means 1 db. If the meter shows 2.4 volts ac (as against 2 volts at midscale) the actual gain is 8 db plus 2 db or a total of 10 db. END

Notes on Soldering

By DARWIN H. HARRIS

WHEN I became absorbed in electronics some 10 years ago, one of the first things I learned was that connections have to be secured by winding, wrapping or twisting the wire about the terminal before soldering. Being experimentally inclined, which implies making changes, I soon learned that these junctions are not easy to disassemble. This led to the obvious course of eliminating mechanical joints and depending entirely on the solder for strength. During the long period I have followed this practice, I have had *no joint failures* due to mechanical causes. The very few bad ones were plainly caused by the usual thing—sloppy soldering, resulting in cold joints. (Some of the soldering observed was subjected, without any trouble, to vibration in car radios.)

Therefore, my philosophy is simply that a properly soldered connection requires no provision to secure it other than the solder itself. This applies to all ordinary connections made in electronic hookups, where wires are soldered into lug holes. There are some obvious exceptions—places where unusual strength is required. For example, an antenna lead, where you naturally make a strong twisted splice before soldering. The admonitory adjective "properly soldered" should be kept in mind. More on this presently.

I have a notion that the wrapped-joint dictum might have come from three things: Certain manufacturing practices require that one person make the connection, another solder it. It must then be self-supporting between operations. The old electrical code required this type construction. Low-tin solder might make it advisable. Personally I believe no solder should be used that contains less than 50% tin. Best of all is eutectic solder (60% tin, 40% lead), which I now use almost exclusively.

When two metals are melted together in different proportions, some particular composition has the lowest melting point. This is the eutectic alloy. It has the important property of melting sharply—of passing from solid to liquid (or vice versa) at a constant temperature, as pure metals do. Mixtures on either side of the eutectic do not have a true melting point, but have instead a semisolid zone persisting through a certain range of temperature before becoming liquid. Within limits, the more the composition differs from the eutectic, the wider this semisolid range is, temperature wise.

The tin–lead eutectic contains 62% tin. The commercial 60% grade is so near the eutectic as to be practically equal to it. This solder not only melts most easily, but sets quickly and strongly on slight cooling. Low-analysis alloy (40% tin) requires a considerably higher temperature to become fluid and sets on slight cooling to a soft state which is brittle and weak until it cools far enough to be truly solid. (The semisolid characteristic of this grade is useful in the wiping-solder method of joining lead pipes.) Obviously, medium-analysis solder (50% tin) is intermediate in properties between the extremes discussed. It has enough good qualities to be satisfactory, although markedly inferior to the eutectic grade of solder.

Based on these facts, it is my opinion that a well-soldered wire connection requires solder containing at least 50% tin and preferably 60%. It is hardly necessary to mention the other ingredients of good soldering, cleanliness and sufficient heat, since these are matters that anyone trying to do good work soon learns. END

NEXT MONTH

ECONOMY TUBE CHECKER

An easily built tester that will obtain for you many of the results expected from much higher priced units.

RING RADIATOR

A complete description of the new Jim Lansing tweeter which uses a special principle to produce and radiate high audio frequencies.

SIMPLE SUPER TIME BASE

This generator supplies your scope's horizontal oscillator with a sweep that can be triggered to give a single trace at rates ranging from 0.2 second to 0.2 μsec per inch. Also operates free-running.

A checker that detects shorts, opens, leakage and low power gain in auto radio power transistors

This Tester Checks Power Transistors

By W. F. JORDAN and H. C. LIN *

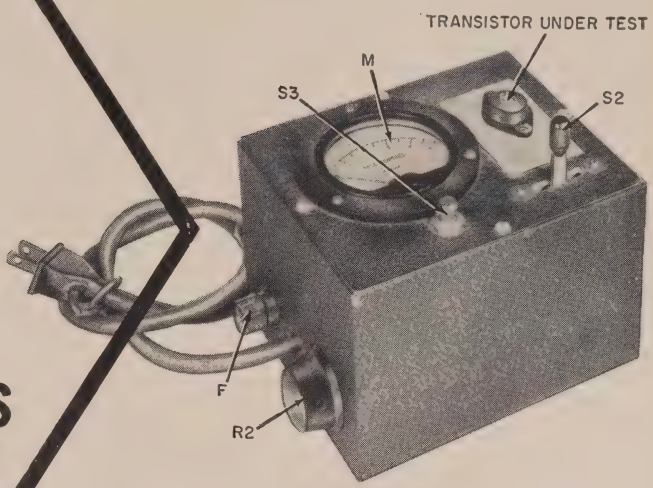

The finished unit. This is the ac version.

SERVICE technicians and dealers need a simple and inexpensive device for checking the power transistors used in hybrid and all-transistor auto radios. The instrument described in this article accurately tests for power gain and any one of or combination of opens, shorts, leakage and voltage breakdown in the transistor.

To measure power gain you usually need bulky and expensive instruments, such as an audio signal generator and ac voltmeter. The tester makes ac power-gain measurements by using a dc test. This simplifies operation and reduces the tester's cost.

Power gain

Power gain in a transistor amplifier, as defined by most auto radio manufacturers, is the ratio (in decibels) of output power to the maximum power available from a generator of a specified impedance (R_{gen}). The equivalent input circuit of an amplifier can be represented by a *current* generator and shunt impedance R_{gen} as in Fig. 1.

Essentially, power gain depends on two quantities—collector-to-base current amplification (h_{fe}) and the input resistance. Measuring either alone does not measure power gain, since both vary over a wide range.

On the other hand, when output power and generator impedance are fixed, generator current I_g is proportional to the square root of the available power input:

Available input power $= I_g^2 R_{gen}/4$

(The equation is divided by 4 as auto radio manufacturers feel this represents actual available input power—it takes into account all receiver losses.)

Therefore, I_g is inversely proportional to the power gain in decibels because power gain in decibels equals

$$10 \log \frac{\text{Output power}}{\text{Available input power}}$$

In the tester, this generator current indicates power gain and is simulated with a dc source (the battery in Fig. 2). Using dc is justified because the ac signal amplification (h_{fe}) is very nearly proportional to the direct-current amplification (h_{FE}) for these transistors.

Dc output power is maintained constant by holding collector current constant. Since collector current is nearly equal to emitter current, consistency of collector current is handled by emitter degeneration (R2 and R3 in Fig. 2). The input circuit is represented by current source I_s (3-volt battery section) shunted by the specified source resistance. I_s is then a "straightline" function of power gain (in db). A graph comparing them is shown in Fig. 3 and using it you can calibrate the milliammeter dial in decibels.

Emitter current in the test circuit (Fig. 4) is essentially equal to the 3-volt supply divided by R2 plus R3. Any

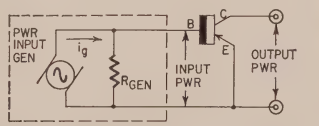

Fig. 1—Equivalent input circuit of a power transistor amplifier stage.

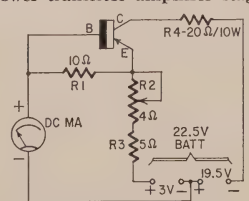

Fig. 2—This circuit tests for gain. R1 is the constant generator impedance and R4 is the constant load impedance.

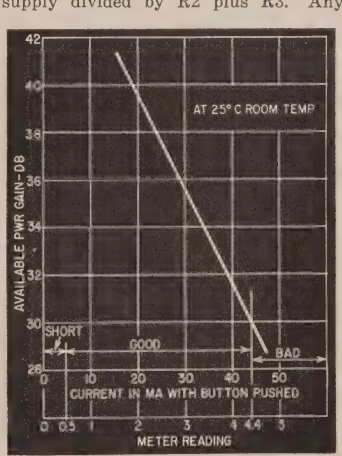

Fig. 3—Power gain vs meter reading for use on gain tests. Above 2.2 ma can be marked *bad* on the meter face and below 2.2 ma can be marked *good*.

*Semiconductor Operations, CBS-Hytron, Lowell, Mass.

TABLE I—OPERATING INSTRUCTIONS

Calibrate

(Do not push button)

Dc tester: Set to 2 (400 ma). If you can't, replace battery.
Ac tester: Set to 1.5 (300 ma).

Leakage

Greater than 0.1 meter reading (20 ma) is C–B, C–E or C–B–E short.

Less than 0.1 meter reading. Push button.
(1) Greater than 2 (2 ma) is excessive leakage.
(2) Upscale creeping is leakage.

Gain

(Good–bad based on 30-db gain point)

Greater than 0.5 (100 ma) is B–E short or any open.

Less than 0.5 meter reading. Push button.
(1) Less than 1.0 (10 ma) is C–B, C–E or C–B–E short.
(2) Greater than 4.4 (44 ma) is poor gain.

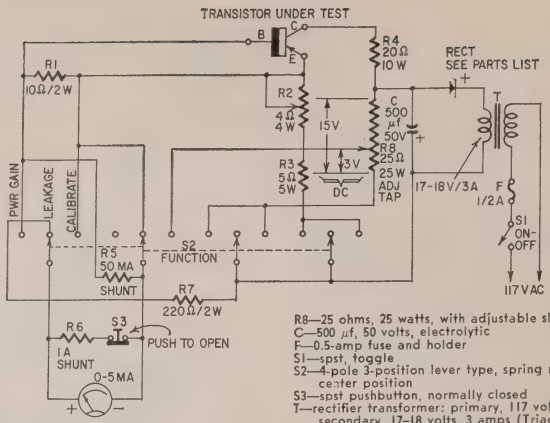

R1—10 ohms, 2 watts
R2—pot, 4 ohms, 4 watts
R3—5 ohms, 5 watts
R4—20 ohms, 10 watts
R5—50-ma shunt to suit meter
R6—amp shunt to suit meter
R7—220 ohms, 2 watts
R8—25 ohms, 25 watts, with adjustable slider
C—500 μf, 50 volts, electrolytic
F—0.5-amp fuse and holder
S1—spst, toggle
S2—4-pole 3-position lever type, spring return to center position
S3—spst pushbutton, normally closed
T—rectifier transformer: primary, 117 volts; secondary, 17–18 volts, 3 amps (Triad F-47U or equivalent)
Rectifier, 1 amp, 50 piv; collector-base junction of discarded power transistor is satisfactory
Socket, 9-pin miniature (to plug transistor into)
Meter, 5-ma full scale
Case, to suit
Miscellaneous hardware

Fig. 7—Ac version of the auto power-transistor checker.

change in the 3-volt supply is compensated for by adjusting R2 to maintain emitter current constant at the predetermined level.

Leakage and shorts

In the leakage test, the circuit is connected as in Fig. 5. The meter reads the collector reverse current with the base connected to the emitter through a 10-ohm resistor. If the collector is shorted or has excessive leakage to either the base or emitter, the meter will give a high reading. A base-to-emitter short is detected by the power-gain test.

A pushbutton shunt and a series resistance protect the meter. Always test first without the pushbutton depressed. If the reading is high—over 0.1 on leakage or 0.5 on gain—the meter may be damaged if the pushbutton is depressed.

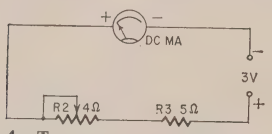

Fig. 4—To set a constant output current, adjust R2 in this calibrate circuit.

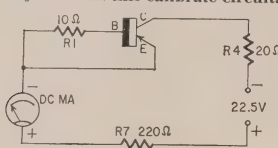

Fig. 5—Leakage test circuit checks the reverse biased diode current of the collector.

Checking for opens

During power-gain tests, open electrodes are detected. If the collector is open, emitter current is diverted to the base, resulting in a heavy current through the meter.

When the emitter is open, no emitter current flows through R2 and R3 and the voltage drop across these resistors is greatly reduced, voltage at the emitter rises and again current through the meter is high.

If the base lead is open, collector current is equal to h_{FE} times I_{CBO}, where h_{FE} is the collector-to-base current amplification and I_{CBO} is the open-emitter collector current. If h_{FE} times I_{CBO} is high, the meter reads high in the leakage test. If h_{FE} times I_{CBO} is low, the voltage drop across R2 and R3 in the power gain test is small and a high voltage appears across the meter, making the reading high. A base-to-emitter short is also detected during this test. Heavy base current flows through the meter due to zero power gain.

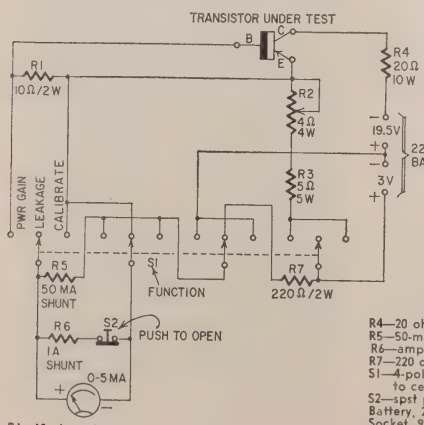

Fig. 6—Complete battery-powered transistor checker.

R1—10 ohms, 2 watts
R2—pot, 4 ohms, 4 watts
R3—5 ohms, 5 watts
R4—20 ohms, 10 watts
R5—50-ma shunt to suit meter
R6—amp shunt to suit meter
R7—220 ohms, 2 watts
S1—4-pole 3-position lever type, spring return to center position
S2—spst pushbutton, normally closed
Battery, 22.5 volts, tapped at 3 volts
Socket, 9-pin miniature (to plug transistor into)
Meter, 5-ma full scale
Case, to suit
Miscellaneous hardware

The complete tester

Two versions of the tester were constructed[1], one for dc operation (Fig. 6) and another for ac (Fig. 7). The dc tester uses a 22.5-volt battery as its power supply. The ac tester uses a stepdown transformer and a half-wave rectifier.

There are three test positions—LEAKAGE, POWER GAIN and CALIBRATE.

The normal operating position is LEAKAGE and a spring-return switch is used to insure that the switch returns to this position when released. In the leakage position, power consumption is low, while in the other positions it is high. If the tester were left in either of the high-consumption positions for an extended period, a larger transformer or battery would be needed. The spring-return switch makes this unnecessary.

Operation

Use the tester following the steps

[1]The designs shown are accurate for transistors rated up to 5 watts. Higher-power transistors may be tested, but operation at full power will not be indicated. The current level must be raised by redesigning the circuit to simulate higher-power operation.

Transistor Low-cost Frequency Standard

By PAUL S. LEDERER

A 100-kc frequency standard is an extremely useful item around the ham shack or experimenter's lab. Such a standard, using two inexpensive surplus crystals (type FT-241), is described here.

These surplus crystals were originally used for equipment operating on adjacent channels from 20.9 to 27.9 mc. The channels were 0.1 mc apart and the crystals' 54th harmonic was the desired channel frequency. The actual fundamental frequencies of the crystals range from 370,370 to 516,667 kc. Such odd frequency values are not very useful, but it is possible to obtain a useful frequency from *the difference in frequency of two selected crystals*. The choice of crystals is based on the following consideration: Since each channel is the 54th harmonic of the crystal's fundamental frequency, if the difference between two channel frequencies is *exactly* divisible by 54, then the difference between corresponding crystal fundamental frequencies is an even number without fractions.

The transistor frequency standard uses one crystal marked channel 0, 20.0 mc, and one crystal marked channel 54, 25.4 mc. The difference between channel frequencies, 5.4 mc when divided by 54, is 0.1 mc or 100 kc.

The crystals are used in Pierce oscillators (see diagram). The oscillators' outputs are mixed in a germanium diode circuit. This is followed by a parallel-resonant filter circuit tuned to 100 kc, which feeds a grounded collector transistor amplifier acting as buffer and impedance matcher.

The circuit uses inexpensive, readily obtained components. The Pierce oscillators use CK722's, while the buffer uses a CK721. It is interesting to note that these transistors were not selected. The circuit was built with the first units received. Although these transistors are considered for use at only comparatively low frequencies, other experimenters have reported their successful use in oscillators at radio frequencies.

The Pierce type of crystal oscillator is simple and reliable, and requires a minimum of adjustment. In this circuit, the crystals are connected directly between collector and base. Since the crystal has a low impedance near its series-resonant frequency, there is enough feedback at this frequency to maintain oscillation. With the low input impedance of the grounded-emitter circuit, a low value of voltage gain in the stage sustains oscillation. This may explain why these circuits oscillate near the transistor's alpha-cutoff frequency.

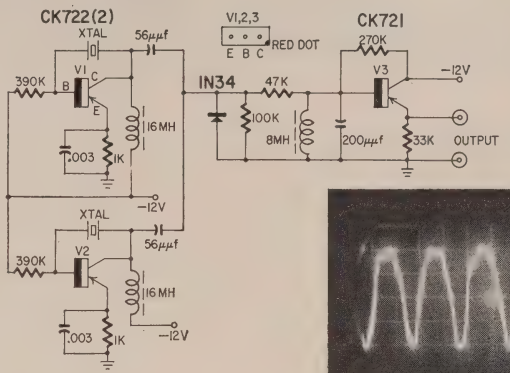

Schematic of transistor frequency standard and waveform of its 100-kc output.

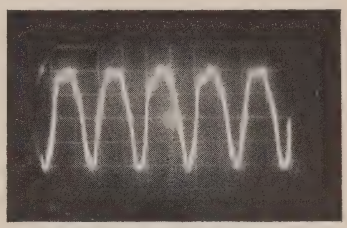

Since the input impedance of the stage is capacitive, the crystal must appear inductive to give the proper phase shift between collector and base. At most, this phase shift is less than 180° and the required additional phase shift must be achieved by loading the plate circuit with a detuned resonant circuit whose resonant frequency is less than the crystal frequency. In this particular circuit a 16-mh ferrite-core choke is used with the collector-to-ground output capacitance. The output of these oscillators is combined in a mixer circuit consisting of a 1N34 germanium diode shunted by a 100,000-ohm resistor. A parallel-resonant circuit, tuned to 100 kc and consisting of a 8-mh ferrite-core choke and a 200-μμf mica capacitor, is coupled to the mixing circuit through a 47,000-ohm resistor and acts as a filter passing the 100-kc component on to the common-collector buffer circuit.

The common-collector circuit uses a CK721. Its fairly high input impedance does not load down the parallel-resonant circuit, preserving its filtering action. At the same time, the low output impedance (about 3,000 ohms) of the grounded-collector circuit is desirable for matching low-impedance rf circuits.

The frequency standard is powered by a 12-volt battery. Its total current drain is 2.6 ma. The output waveshape is shown in the photo. The output voltage depends on the amount of capacitance across the output. It varies from a maximum of about 1.5 volts peak to peak to about 0.6 volt peak to peak with 330 μμf across the output. The most important property of a frequency standard, of course, is its ability to deliver an accurately known frequency. This was checked by feeding the output of the standard into a Berkeley electronic frequency counter (with an accuracy of ±1 part in 10⁸). Results showed the standard frequency to vary from 100,013 ±1 cycle to 100,008 ±1 cycle over a period of about 1 hour. Thus the absolute accuracy of the 100 kc standard is at least 14 parts in 100,000 or .014%. END

THIS TESTER CHECKS POWER TRANSISTORS (Continued)

shown in Table I. This chart also shows what the meter readings represent.

Any inaccuracy in power-gain measurements is caused by variations in the initial bias of the dc input characteristics for different transistors or under different temperatures and the variations in collector cutoff currents.

Initial bias may vary from transistor to transistor. However, for the same type of transistor the variation is usually quite small.[2] The initial bias value also goes down about 2.5 mv for every °C increase in temperature.[3] To correct for temperature, add 1 db to the power-gain reading for every 20° temperature increase.

The cutoff current (I_{CBO}) creates a forward bias when it flows through the base circuit resistances. This bias tends to offset the collector current's consistency. Making base circuit resistances small removes this objection.

If the temperature is within 10° of 27°C (80°F), power-gain measurements are accurate within 1 db.

Leakage current is a function of voltage and temperature. Therefore, the accuracy of this reading is good only if the supply voltage and temperature are held relatively constant. END

[2]L. J. Giacoletto, "Study of PNP Alloy-Junction Transistor from Dc through Medium Frequencies," *RCA Review, 15*, December, 1954.

[3]H. C. Lin and A. A. Barco, "Temperature Effects in Circuits Using Junction Transistors," *Transistor I*, RCA Labs, 1956.

"HEATHKITS®

gave me my start and I'm still sold!"

"... they are my lowest cost way to real quality and dependability in electronic equipment of any kind ...

... The clean, modern styling of HEATHKITS make me proud to own them. They make a handsome and useful addition to my workshop.

... Rigid quality standards of components used in HEATHKITS assure me of performance equal to or surpassing instruments costing many times more.

... after assembling a HEATHKIT myself, I know what "makes it tick"... I know that the thoughtful circuitry design and name-brand components used throughout guarantee me years of trouble-free service.

... HEATHKITS cost me half as much as ordinary equipment ... and I get so much more. In assembling my own instruments I am sure of the quality that goes into them. Plus the complete assembly and operating instructions as well as detailed schematics that are at my fingertips for future reference."

NEW: Stereophonic Sound for your home with the new HEATHKIT STEREO CENTER. This, and other exciting new high fidelity developments are now available from the world's largest maker of "do-it-yourself" electronic kits.

NEW: For the Ham Radio fans—an all new Ham Transmitter and companion Receiver—featuring all the latest developments in Ham communication—including single-sideband operation.

NEW: A competely up-to-date Oscilloscope answering the long felt needs of electronic engineers and servicemen everywhere.

NEW: A host of newly developed marine instruments for the safety and convenience of the boat owner.

HEATH COMPANY Benton Harbor 20, Michigan

a subsidiary of Daystrom, Inc.

The HEATH TIME PAYMENT PLAN allows you to outfit your whole workshop at one time with needed test instruments while you pay in easy monthly installments.

HEATHKIT

PROFESSIONAL OSCILLOSCOPE KIT

An exciting development in the Heathkit test instrument line is the introduction of the Heathkit model OP-1 Professional Oscilloscope. Emphasizing complete flexibility in any application, the OP-1 features DC coupled amplifiers and also DC coupled CRT tube un-blanking. The triggered sweep circuit will operate on either internal or external signals and may be either AC or DC coupled. The polarity of the triggering signal may also be selected, and any point on the wave form may be selected for the start of the sweep by using the "triggering level" control. An automatic position is also provided, in which the sweep recurs at a 50 cycle rate, but can be driven over a wide range of frequencies with no additional adjustments. The sweep frequencies are provided by switch-selected base rates of 2 and .2 milliseconds/CM, and 20, 2, and 1 microseconds/CM, in conjunction with a continuously variable 10 to 1 multiplier. Sweep frequencies are calibrated to within 10% at all control settings, and the sweep frequency may be reduced by adding capacity to the "ext. cap" binding post on the front panel. A 5ADP2 flat face CR tube is used for accurate readings on an edge lighted grid screen. A high quality conetic-fernetic CR tube shield prevents stray AC fields from distorting trace. A 12-position vertical attenuator is calibrated in volts-per-CM and the horizontal sweep is calibrated in time-per-CM. Prewired terminal boards are used for rapid, easy assembly of all critical circuits. Simply install and connect the color coded leads. Power supply is transformer operated utilizing silicon diode rectifiers and is fused for protection. Under development for over a year the OP-1 promises outstanding results in any application requiring the use of an oscilloscope.

HEATHKIT OP-1 **$179.95**

Here's the scope you've been waiting for!

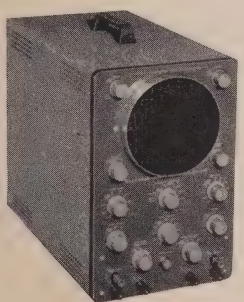

Laboratory Performance At Less Than Utility Scope Price

HEATHKIT O-12 **$65.95**

A Scope You Will Be Proud To Own

HEATHKIT OM-3 **$39.95**

"EXTRA DUTY" 5" OSCILLOSCOPE KIT

Top quality features at half the cost of ordinary equipment sum up the advantages of this popular kit. Critical observations in your laboratory or shop are handled easily, with clear, sharp pattern displays in every application. Vertical frequency response extends from 3 CPS to 5 mc +1.5 db —5 db without extra switching. Response is down only 2.2 db at 3.58 mc. The Heath patented sweep circuit functions effectively from 10 CPS to better than 500 kc in five steps, giving you 5 times the usual sweep obtained in other scopes. An automatic sync circuit with self-limiting cathode follower provides excellent linearity and lock-in characteristics. Extremely short retrace time and efficient blanking action. Both vertical and horizontal output amplifiers are push-pull and the scope incorporates a 1 V peak-to-peak calibrating source, step attenuated and frequency compensated vertical input, plastic molded capacitors and top quality parts throughout. The 11-tube circuit features a 5UP1 cathode ray tube, and provision is made for Z-axis input for intensity modulation of the beam. Frequency response of the horizontal amplifier is within ±1 db from 1 CPS to 200 kc. Horizontal sensitivity is 0.3 volts RMS per inch. Construction is simplified through the use of two metal circuit boards and precut, cable wiring harness. Shpg. Wt. 22 lbs.

GENERAL PURPOSE 5" OSCILLOSCOPE KIT

For servicing and routine laboratory work this fine kit is a favorite with technicians throughout the country. It incorporates many extras not expected at this low price. Features wide vertical amplifier frequency response, extended sweep generator operation, and improved stability. Frequency response of the vertical amplifier is within ± 3 db from 4 CPS to 1.2 mc. Vertical sensitivity is .09 volts RMS per inch at 1 kc. Sweep generator functions reliably from 20 CPS to over 150 kc. A modern etched circuit board is featured for high stability and reduces assembly time considerably. Standard components are mounted on this board with each position clearly marked preventing wiring errors. Both vertical and horizontal amplifiers are push-pull types. Uses a 3BP1 CRT. Provision for external or internal sweep or sync, built in 1 V peak-to-peak reference voltage and calibrated grid screen. An adjustable "spot shape" control is provided to insure a sharp trace. Input to the vertical amplifiers is through a step attenuated, frequency compensated circuit. The OM-3 is an extremely versatile instrument and has a multitude of practical uses in electronic testing fields. Particularly useful in alignment of television receivers, for testing audio amplifiers and circuits, and checking the quality of modulated RF signals in Ham Radio transmitters. Shpg. Wt. 22 lbs.

Equip Your Service Bench...

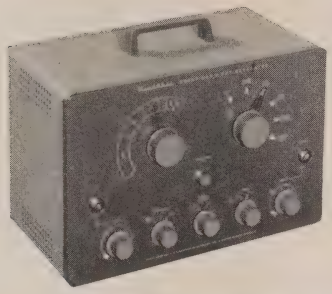

HEATHKIT CD-1 **$59.95**

Cash In Now On Color TV

★ 10 VERTICAL COLOR BARS
★ CRYSTAL CONTROLLED ACCURACY
★ CHOICE OF 6 DIFFERENT PATTERNS

COLOR BAR AND DOT GENERATOR KIT

Colored television is now a reality and as the number of these sets increase the need for a reliable service instrument is apparent. Nothing on the market . . . in this type of generator has as many features as the CD-1 at such a tremendous price saving. This unit combines two basic color service instruments, a color bar generator, and white dot generator in one versatile portable unit which has crystal controlled accuracy and stability for steady locked-in patterns (requires no external sync leads). Color receivers converged with the CD-1 will still be converged properly on a television program from the station. The 13-tube circuit has been carefully laid out for ease of assembly and provides choice of six different patterns. Produces white-dots, cross hatch, horizontal and vertical bars, ten vertical color bars, and a new shading bar pattern for screen and background adjustments. Variable RF output on any channel from 2 to 6. Positive or negative video output, variable from 0 to 10 volts peak-to-peak. Crystal controlled sound carrier with off-on switch. Voltage regulated power supply uses long-life silicon rectifiers. Kit includes three crystals and test lead, plus an information packed instruction manual covering convergence, and screen and background adjustments of a color TV set. Compare with other generators on the market and you will see that this instrument is loaded with extras and top quality all the way through. Shpg. Wt. 13 lbs.

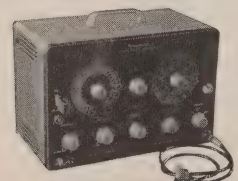

HEATHKIT TS-4A **$49.50**

For fast, easy alignment of TV sets

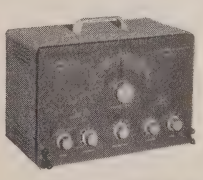

HEATHKIT AG-10 **$49.95**

Sine and square waves for countless uses

HEATHKIT MM-1 **$29.95**

High accuracy in a portable meter

HEATHKIT M-1 **$17.95**

An all-round meter of many uses

TV ALIGNMENT GENERATOR KIT

This generator has many special design features for flexible, easy operation and reliability. The all-electronic sweep circuit insures stability and covers 3.6 mc to 220 mc in four bands. Sweep deviation is controllable from 0 to 42 mc. Crystal and variable marker oscillators are built in. Crystal (included with kit) provides output at 4.5 mc and multiples thereof. Variable marker provides output from 19 to 60 mc on fundamentals and from 57 to 180 mc on harmonics. Effective two-way blanking and phasing control also provided. A truly outstanding number of features at a tremendous price saving. Shpg. Wt. 16 lbs.

SINE-SQUARE GENERATOR KIT

High quality sine and square waves are produced by this generator over a wide range. Frequency response is ±1.5 db from 20 CPS to 1 mc on both sine and square waves, with less than .25% sine wave distortion, 20 to 20,000 CPS. Output impedance is 600 ohms on sine wave and 50 ohms on square wave (except on 10 volt range). Square wave rise time less than .15 microseconds. Five-position bandswitch—continuously variable tuning—shielded oscillator circuit—separate step and variable output attenuators in ranges of 10, 1 and .1 volts with extra range of .01 volt on sine wave. Shpg. Wt. 12 lbs.

20,000 OHMS/VOLT VOM KIT

This meter is ideal for use in field applications where accuracy is important. Employs a 50 ua 4½" meter, and features 1% precision multiplier resistors for high accuracy. Requires no external power for operation (batteries supplied). Sensitivity is 20,000 ohms-per-volt DC and 5,000 ohms-per-volt AC. Measuring ranges are 0-1.5, 5, 50, 150, 500, 1500 and 5,000 volts AC and DC. Measures direct current in ranges of 0-150 ua, 15 ma, 150 ma, 500 ma and 15 a. Resistance multipliers are x 1, x 100 and x 10,000 Covers -10 db to +65 db. Batteries and test leads are also included with this kit. Shpg. Wt. 6 lbs.

HANDITESTER KIT

Small enough to carry with you wherever you go, this fine handitester is ideal for use in portable applications when making tests away from the work bench or as an "extra" meter in the service shop, when the main instruments are occupied. The combination function-range switch simplifies operation. Measures AC or DC voltage from 0-10, 30, 300, 1000 and 5000 volts. Direct current ranges are 0-10 ma and 0-100 ma. Ohmmeter ranges are 0-3000 and 0-300,000. Top quality precision components employed throughout. Very popular with home experimenters and electricians. Shpg. Wt. 3 lbs.

with Low-Cost Dependable Heathkits

HEATHKIT

ETCHED CIRCUIT VTVM KIT

The fact that this instrument is outselling all other VTVM's says a great deal about its accuracy, reliability, and overall quality. The precision and quality of the components used in this VTVM cannot be duplicated at this price through any other source. Its attractive appearance as well as its performance will make you proud to own it. A large 4½" panel meter is used for indication, with clear, sharp calibrations for all ranges. Front panel controls consist of a rotary function switch and a rotary range selector switch, zero-adjust and ohms-adjust controls. Precision 1% resistors are used in the voltage divider circuit. An etched circuit board is employed for most of the circuitry, cutting assembly time and eliminating the possibility of wiring errors. It also assures duplication of laboratory instrument performance. This multi-function VTVM will measure AC voltage (RMS), AC voltage (peak-to-peak), DC voltage and resistance. There are 7 AC (RMS) and DC voltage ranges of 1.5, 5, 15, 50, 150, 500 and 1500. In addition there are 7 peak-to-peak AC ranges of 0-4, 14, 40, 140, 400, 1400 and 4,000. Seven ohmmeter ranges providing multiplying factors of x 1, x 10, x 100, x 1000, x 10 k, x 100 k and x 1 megohm. Center scale resistance readings are 10, 100, 1000, 10 k, 100 k ohms, 1 megohm and 10 megohms. A zero-center scale db range is also provided. Battery and test leads included with kit. Shpg. Wt. 7 lbs.

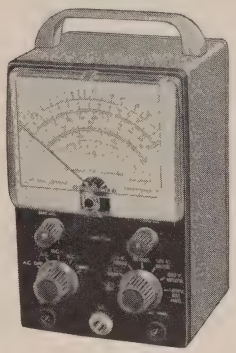

HEATHKIT V-7A **$25.95**

World's largest selling VTVM kit

★ LARGE EASY-TO-READ 4½" 200 UA METER
★ 1% PRECISION RESISTORS EMPLOYED FOR HIGH ACCURACY

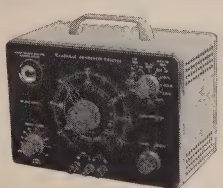

HEATHKIT C-3 **$19.50**

Checks all types of condensers accurately

HEATHKIT T-4 **$19.95**

Locate faults quickly by tracing signals

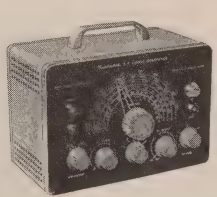

HEATHKIT SG-8 **$19.50**

Easy-to-build—prewound and calibrated coils

CONDENSER CHECKER KIT

Check unknown condenser and resistor values quickly and accurately. Capacity measurements are made in four ranges of .00001 mfd-.005 mfd; .001 mfd-.5 mfd; .1 mfd-50 mfd; 20 mfd-1,000 mfd. Checks paper, mica, ceramic, and electrolytic condensers. Leakage test provides switch selection of five polarizing voltages, 25 volts to 450 volts DC to indicate condenser operating quality under actual load conditions. Electron beam "eye" tube indicates balance and leakage. A spring return test switch automatically discharges condenser under test and eliminates shock hazard to the operator. Measures resistance from 100 ohms to 5 megohms in two ranges. Shpg. Wt. 7 lbs.

VISUAL-AURAL SIGNAL TRACER KIT

Here is a brand new signal tracer completely redesigned with compact dimensions and new circuit layout. Features built-in speaker and electron beam "eye" tube for signal indication and a unique noise locator circuit. Ideal for use in AM, FM and TV circuit investigation. RF and audio inputs are provided in one convenient probe with switch on probe to select either input. Useful for checking microphones, phono cartridges, record changers, tuners, etc. Makes a handy substitution speaker for servicing TV sets at the shop. Transformer operated for safety and high efficiency. Complete with test leads and informative construction manual. Shpg. Wt. 6 lbs.

RF SIGNAL GENERATOR KIT

Save valuable time in aligning RF tuned circuits of all kinds with this easy-to-use kit. Also a quick way to trace signals in faulty RF, IF and audio circuits. Designed for general service applications-the SG-8 covers 160 kc to 110 mc on fundamentals in five bands, and from 110 mc to 220 mc on calibrated harmonics. The entire oscillator circuit is built on a special sub-chassis, using prewound and calibrated coils. No further calibration is required so it is ready to use as soon as construction is completed. RF output is in excess of 100,000 microvolts, controlled by both step and continuously variable controls. Complete with output cable and instructions. Shpg. Wt. 8 lbs.

HEATH COMPANY • a subsidiary of Daystrom, Inc. • **Benton Harbor 20, Mich.**

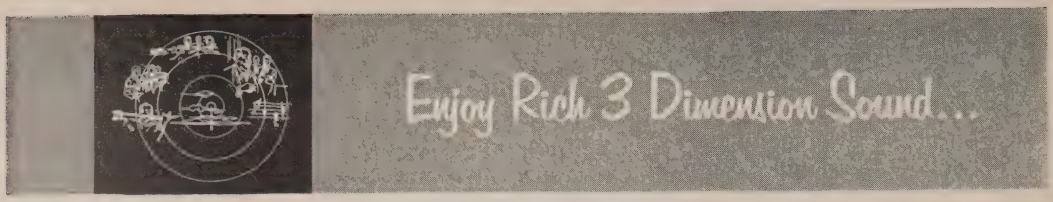

Beautifully Styled with Plenty of Room for the Most Complete Stereo System

AVAILABLE IN THE FOLLOWING MODELS:
Model SE-1B—Stereo Equipment Cabinet (birch)
Model SE-1M—Stereo Equipment Cabinet (mahogany)
$149.95 ea.

Model SC-1BR—Stereo Wing Speaker Enclosure (birch—right end)
Model SC-1BL—Stereo Wing Speaker Enclosure (birch—left end)
Model SC-1MR—Stereo Wing Speaker Enclosure (mahogany—right end)
Model SC-1ML—Stereo Wing Speaker Enclosure (mahogany—left end)
$39.95 ea.

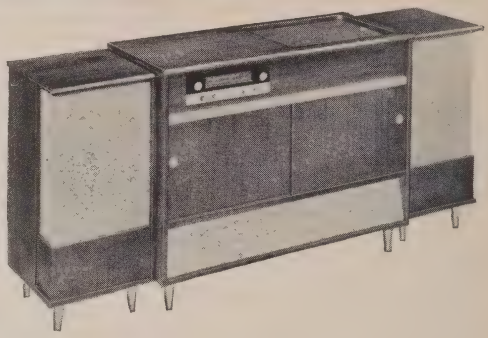

STEREO EQUIPMENT CABINET KIT

Imagine!... Stereophonic sound in your own home. This superbly designed cabinet holds all of your hi-fi stereo equipment and lends striking elegance to your living room. The attractive gold and black panels, trim and hardware brilliantly highlight the overall effect. Rich toned grille cloth, flecked in gold and black, complement the cabinet. The unit has ample room provided for an AM-FM tuner, tape deck, stereo preamplifier, amplifiers, record changer, record storage and speakers. Beautifully grained ¾" solid core Philippine mahogany or select birch plywood is used for construction. The top features a shaped edge and sliding top panel for easy access to the stereo tape deck and stereo preamplifier. Sliding doors are employed for convenient front access to the changer and record storage compartment. All parts of the cabinet are precut and predrilled for simple assembly. The speaker wings and center cabinet may be purchased separately if desired. Note: the kit is delivered equipped with panels precut to accommodate Heathkit components and also blank panels to cut out for your own equipment. Measurements of the individual component areas follow: tape deck and preamplifier area 20¾" L. x 17¾" W. x 10" D., record changer area 21" W. x 16" D. x 9⅝" H., record storage area 22⅝" W. x 14½" H. x 12½" D., speaker wing area (inside) 14" W. x 29½" H. x 15¾" D., AM-FM Tuner area 20½" W. x 5¼" H. x 14" D., amplifier (2 areas) 15¼" W. x 10¾" H. x 13¼" D.

Model HH-1B Birch
Model HH-1M Mahogany
Now only **$299.95** each

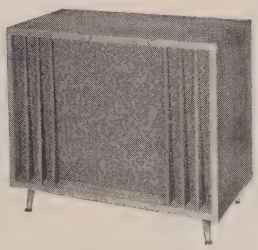

The Same Superior Performance At a New Low Price

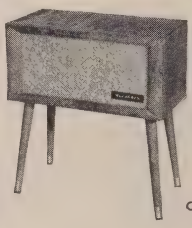

HEATHKIT SS-2 **$39.95**

OPTIONAL LEGS EXTRA

Economical Hi-Fi For Your Home

"LEGATO" HI-FI SPEAKER SYSTEM KIT

The increasing sales of the Legato has made more economical quantity production possible so we are passing the savings on to you by offering you this magnificent speaker system at a reduced price. Truly a "queen" among hi-fi speaker systems, the Legato was specially designed to meet and surpass the most stringent requirements of high fidelity sound reproduction. Two 15" Altec Lansing low frequency drivers cover frequencies of 25 to 500 CPS while a specially designed exponential horn with high frequency driver covers 500 to 20,000 CPS. A unique crossover network is built in making electronic crossovers unnecessary. Internal reflections are absorbed by splayed back panel and a 3" fiber glass lining. The Legato emphasizes simplicity of line and form to blend with modern or traditional furnishings. Cabinet construction is ¾" veneer surface plywood in either African mahogany or white birch and measures 41" L. x 22¼" D. x 34" H. All parts are precut and predrilled for easy assembly. Shpg. Wt. 195 lbs.

"BASIC RANGE" HI-FI SPEAKER SYSTEM KIT

True high fidelity performance at modest cost make this basic speaker system a spectacular buy for any hi-fi enthusiast. The amazing performance of this popular kit is made possible by the use of high quality speakers in an enclosure specially designed to receive them. The cabinet is a ducted port bass reflex type enclosure 11½" H. x 23" W. x 11¾" D. It features an 8" mid range woofer to cover 50 to 1600 CPS and a compression-type tweeter with flared horn covering 1600 to 12,000 CPS. Both speakers are by Jensen. The adjustable flared tweeter horn allows speaker to be used in either upright or horizontal position. The cabinet is constructed of ½" veneer surfaced plywood suitable for light or dark finish of your choice. All wood parts are precut and predrilled for easy assembly. Shpg. Wt. 25 lbs.

Attractive brass tip accessory legs convert SS-2 into attractive consolette. Legs screw into brackets provided. All hardware included. Shpg. Wt. 3 lbs. No. 91-26 $4.95

with a Heathkit Stereo System

HEATHKIT

HIGH FIDELITY TAPE RECORDER KIT

Popular request for high quality, low cost tape recording and playback facilities have prompted the addition of this fine unit to our line. The TR-1A provides monaural record/playback with fast forward and rewind functions. Incorporates separate erase and combination record/playback heads. Two speeds, 7½ and 3¾ IPS, are selected by changing belt drive. Flutter and wow are held to less than 0.35%. Frequency response at 7½ IPS ±2.0 db 50-10,000 CPS, at 3¾ IPS ±2.0 db 50-65,000 CPS. The extremely simple mechanical assembly is ideally suited to kit construction. One control lever selects all functions on deck, greatly simplifying operation. Mount in vertical or horizontal position. The model TE-1 record/playback tape preamplifier, supplied with the mechanical assembly, provides NARTB playback equalization. A record interlock prevents accidental tape erasure. Recording level is indicated by a 6E5 "magic eye" tube. A two-position input selector switch provides for mike or line input. Separate record and playback gain controls. Filament balance control allows adjustment for minimum hum level. Cathode follower output from playback channel is approximately 600 ohms impedance. Two circuit boards are used for easy assembly. Templates and instructions are provided to cut out panels for mounting. Overall dimensions of tape deck and preamp are 15½" W. x 13½" H. x 8" D. Signal-to-noise ratio is better than 45 db below normal recording level with less than 1% total harmonic distortion. (Tape mechanism not sold separately.) Shpg. Wt. 22 lbs.

TAPE RECORDER ELECTRONICS KIT

The model TE-1 Electronics Kit can be purchased separately to replace the electronics in your present tape recorder, or used in addition to it for stereo playback of pre-recorded tapes where a second playback channel is required. Circuit may be modified for use with different head types. Shpg. Wt. 9 lbs.

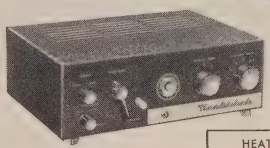

HEATHKIT **TR-1A** **$99.95**

(Includes tape deck, tape recorder electronics, mike and roll of tape.)

Make Your Own Home Recordings

HEATHKIT **TE-1** **$39.95**

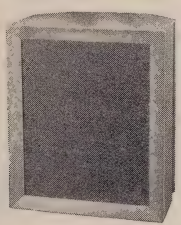

HEATHKIT **SS-1B** **$99.95**

Fill out the Hi-Fi Range of Your SS-2 Speaker

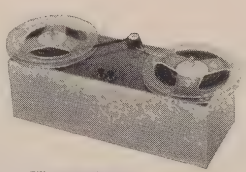

HEATHKIT **SW-1** **$24.95**

Save Time Rewinding Tape

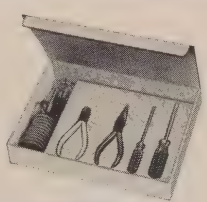

HEATHKIT **TK-1** **$9.95**

All The Tools You Need For Building Heathkits

"RANGE EXTENDING" HI-FI SPEAKER SYSTEM KIT

This is not a complete speaker system in itself, but is designed to extend the range of the SS-2. The SS-1B uses a 15" woofer and a small super tweeter to supply the very high and very low frequencies to fill out the response of the basic SS-2. The SS-2 and SS-1B when used together, form an integrated four speaker system. The SS-2 and SS-1B combination provide an overall response of ±5 db from 35 to 16,000 CPS. The kit includes circuit for crossover at 600, 1600 and 4,000 CPS. Impedance is 16 ohms and power rating is 35 watts. A control is also provided to limit output of super tweeter. The handsome cabinet measures 29" H. x 23" W. x 17½" D. Constructed of beautiful ¾" veneer surface plywood. Complete step-by-step instructions make this kit easy to build. No woodworking experience required. Shpg. Wt. 80 lbs.

"SPEEDWINDER" KIT

This handy device leaves your tape recorder free for operation while it rewinds tape at the rate of 1200' in 40 seconds. Prevents unnecessary wear to the tape and recorder by eliminating wear against guides and heads. It will handle up to 10½" tape reels as well as 800' reels of 8 and 16 millimeter film. A very useful aid to operators of movie projection equipment. The Heathkit Speedwinder features an automatic shutoff which prevents whipping of tape when it has rewound. A manual shutoff is also provided. An automatic braking device is built in for protection against power failure. Driven by a heavy duty four pole motor. Handsome cabinet is constructed of furniture grade plywood. Step-by-step instructions are provided to make this kit easy to assemble even by one with no experience. Shpg. Wt. 12 lbs.

COMPLETE TOOL SET

A clear illustration of just how easy Heathkit building is. The pliers, diagonal sidecutters, two screw drivers and soldering iron are all the basic tools you need for building practically any Heathkit. Pliers and sidecutters are equipped with insulated rubber handles. The American Beauty soldering iron has a replaceable tip to facilitate cleaning. All the tools are of top quality case hardened steel for rugged duty and long life. With these simple, inexpensive tools in your hand you need not be afraid to tackle the most elaborate kit. The manual included with this handy kit provides you with many useful tips on the use and care of your tools. It shows the all important step of making proper solder connections. A truly worthwhile investment for the beginner in electronic kit building. Shpg. Wt. 3 lbs.

HEATH COMPANY • a subsidiary of Daystrom, Inc. • **Benton Harbor 20, Mich.**

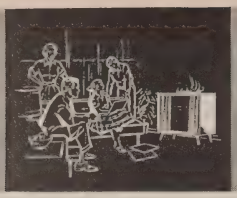

Plan Your Hi-Fi System...

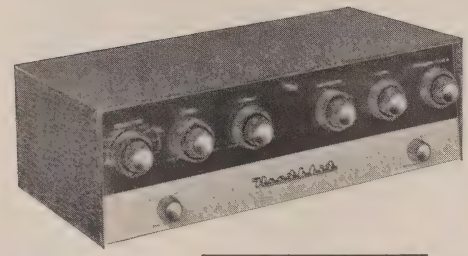

HEATHKIT SP-2 **$56.95**

Model SP-1 (monaural) $37.95

Model C-SP-1 (converts SP-1 to SP-2) $21.95

Control both stereo channels simply and conveniently

MONAURAL-STEREO PREAMPLIFIER KIT

This expertly designed preamplifier provides all the controls required for either standard monaural (single channel) or stereo (dual channel) sound reproduction. Features building block design . . . you can start with a basic preamplifier and add a second channel for stereo later on, without rewiring. Second channel plugs in for fast conversion. The complete model SP-2 (stereo) features twelve separate inputs, six on each channel with input level controls. Six dual-concentric controls consist of: two 8-position selector switches, two bass, two treble, two volume level and two loudness controls, a scratch filter switch and a 4-position function switch (separate on-off switch). The function switch provides settings for stereo, two-channel mix, channel A or B for monaural use. Inputs consist of tape, mike, mag phono and three high-level inputs. Tape input has NARTB equalization and input selector provides for RIAA, LP, 78 record compensation. EF86 tubes are used in the input stages along with hum balance controls to assure low hum and noise. Two cathode follower outputs with level controls provided in addition to two separate tape outputs for stereo recording. A remote balance control with twenty feet of cable allows balancing the stereo system from listening position. Construction is greatly simplified through the use of two printed circuit boards (one in each channel) and encapsulated printed circuits. The beautiful vinyl clad steel cover has leather texture in black with inlaid gold design. Built-in power supply.

HEATHKIT WA-P2 **$19.75**

Finger-tip controls for your operating convenience

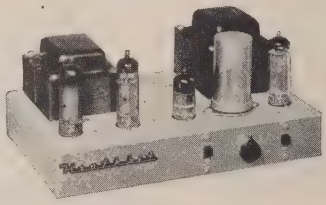

HEATHKIT UA-1 **$21.95**

A low cost versatile performer

"MASTER CONTROL" PREAMPLIFIER KIT

Designed as a control center for basic amplifiers the WA-P2 provides you with true high fidelity performance for the finest audio systems. Five switch-selected inputs accommodate a record changer, tape recorder, AM-FM tuner, TV receiver, microphone, etc., each with level control. Provision is also made for a tape recorder output. Ideal for "remote" installations, the WA-P2 features a low impedance cathode-follower output circuit allowing greater length of output lead. Full frequency response is obtained within ±1½ db from 15 to 35,000 CPS and will do full justice to the finest available program sources. Equalization is provided for records through separate turnover and rolloff switches for LP, RIAA, AES, and early 78's. A special hum balance control allows setting for minimum hum level. Power for operation is required from basic amplifier or external source. Shpg. Wt. 7 lbs.

"UNIVERSAL" 12-WATT AMPLIFIER KIT

A true high fidelity performer in every sense of the word, the UA-1 makes an ideal basic amplifier for any hi-fi system and is a perfect addition to gear your present hi-fi system for stereo sound. Uses 6BQ5/EL84 push-pull output tubes for less than 2% harmonic distortion throughout the entire audio range (20 to 20,000 CPS) at full 12 watt output. The on-off switch is located right on the chassis and an octal socket is provided for connecting a preamplifier for remote control operation. The specially designed output transformer provides excellent stability and frequency response. Taps for 4, 8 and 16 ohm speakers, with switched damping for "unity" or "maximum" on the 16-ohm tap. An input level control is provided for use in wired music systems where a preamplifier is not required. This versatile unit is the latest addition to the fine line of Heathkit basic amplifiers. Shpg. Wt. 13 lbs.

With Flexible Heathkit Components

HEATHKIT

DELUXE AM-FM TUNER KIT

Outstanding features in both styling and circuitry are combined in this 16-tube deluxe AM-FM combination tuner to bring you the very finest in program sources, for your listening enjoyment. Features include three circuit boards for easy construction and high stability—prewired, prealigned FM front end—built-in AM rod antenna—tuning meter—AFC (automatic frequency control) with on-off switch and flywheel tuning. AM and FM circuits are separate and individually tuned making it ideal for stereo applications. Cathode follower outputs with individual controls are provided for both AM and FM. Other features include variable AM bandwidth, 10 kc whistle filter, tuned-cascode FM front end, FM AGC and amplified AVC for AM. The unique IF limiter design automatically provides the number of limiting and IF stages required for smooth non-flutter reception. The silicon diode power supply is extremely conservatively rated and is fuse protected assuring long service life. A tuning meter shows when the station is tuned-in for clearest reception on AM or FM. Use of three circuit boards greatly simplifies construction of circuit, you do only a minimum of wiring. All IF transformers and coils are prealigned so it will be ready to operate as soon as construction is completed. Appearance of this top-quality unit is further enhanced by the vinyl-clad steel cover in black with inlaid gold design. A multiplex jack is provided for addition of converter unit to receive multiplex stereo broadcasts on FM. A top dollar value.

HEATHKIT PT-1 **$89.95**

A deluxe AM-FM tuner combination loaded with extras!

HEATHKIT BC-1A **$26.95**

Wide range broadcast reception

HEATHKIT FM-3A **$26.95**

Enjoy static-free FM entertainment

HIGH FIDELITY AM TUNER KIT

This AM tuner was designed especially for high fidelity applications. It incorporates a special detector using crystal diodes, and the IF circuit features broad bandwidth to assure low signal distortion. Audio response is ±1 db from 20 CPS to 9 kc, with 5 db of pre-emphasis at 10 kc to compensate for station rolloff. Sensitivity and selectivity are excellent and the tuner covers the entire broadcast band from 550 to 1600 kc. Quiet performance is assured by a 6 db signal-to-noise ratio at 2.5 uv. Prealigned RF and IF coils eliminate the need for special alignment equipment. Incorporates AVC, two outputs, two antenna inputs, and built-in power supply. Edge-lighted glass slide rule dial for easy tuning. Your "best buy" in an AM tuner. Shpg. Wt. 9 lbs.

HIGH FIDELITY FM TUNER KIT

FM programming, your least expensive source of high fidelity will provide you with years of real enjoyment. This beautifully styled FM tuner features broad-banded circuits for full fidelity and better than 10 uv sensitivity for 20 db of quieting to pull in stations with clarity and full volume. Covers the complete FM band from 88 to 108 mc. Stabilized, temperature-compensated oscillator assures negligible drift after initial warmup. A ratio detector provides high-efficiency demodulation without sacrificing hi-fi performance. IF and ratio transformers are prealigned, as is the front end tuning unit, making special alignment equipment unnecessary. Edge-lighted glass slide rule dial for easy tuning. You need not wait to have FM in your home at this low price. Shpg. Wt. 8 lbs.

HEATH COMPANY • a subsidiary of Daystrom, Inc. • **Benton Harbor 20, Mich.**

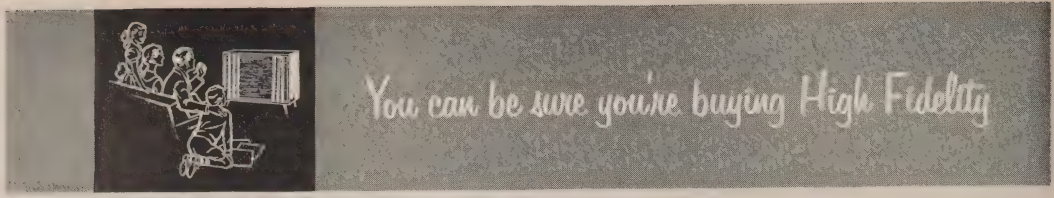

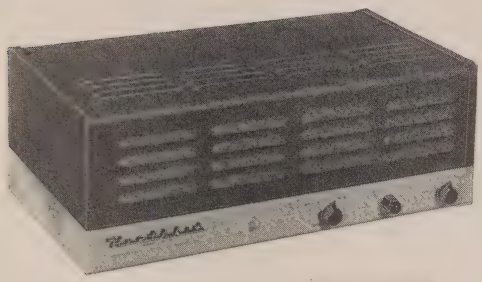

HEATHKIT W-7M **$54.95**

55 watts of hi-fi power at only $1 per watt

★ BEAUTIFULLY STYLED IN BLACK AND GOLD

★ UNITY OR MAXIMUM DAMPING

"EXTRA PERFORMANCE" 55 WATT HI-FI AMPLIFIER KIT

Another Heathkit first! An honestly rated high power amplifier with many top quality features at less than a dollar per watt. Full audio output is conservatively rated at 55 watts from 20 CPS to 20 kc with less than 2% total harmonic distortion throughout the entire range. Unique paired output connections permit instant switch selection of "unity" or "maximum" damping factors for all 4, 8 or 16 ohm speakers. Each output has an optimized current feedback circuit for unity damping so that there will be no compromise in performance when any of the impedances is used. This current feedback circuitry is entirely shorted out when not in use to obtain the highest possible damping factor. Features include level control and "on-off" switch right on the chassis plus provision for remote control from preamp, etc. Famous "bas-bal" circuit conveniently balances EL-34 output tubes. These heavy duty push-pull tubes operate into a high quality tapped-screen transformer designed especially for this unit. A 70-volt output on the transformer provides for P.A. or large music systems. The silicon diode power supply features a protection device that controls current until tubes have warmed up, greatly increasing service life of all components. The stylish black and gold case measures 6" H. x 8½" D. x 15" W. Convenient pilot light on the chassis. Thoughtful circuit layout makes this kit easy to build. Dollar for watt you can't beat this buy. Shipped express only. Shpg. Wt. 28 lbs.

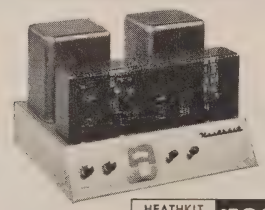

HEATHKIT W-6M **$109.95**

Plenty of Reserve Power Without Distortion

"HEAVY DUTY" 70-WATT HI-FI AMPLIFIER KIT

Here is an amplifier that will provide the extra "push" needed to drive any of the fine speaker systems available today, for truly fine performance at any power level. Silicon-diode rectifiers are used to assure long life and a heavy duty transformer gives you extremely good power supply regulation. Variable damping control provides optimum performance with any speaker system. Quick change plug selects 4, 8 and 16 ohms or 70 volt output and the correct feedback resistance. Frequency response at 1 watt is from 5 CPS to 80 kc with controlled HF rolloff above 100 kc. At 70 watts output harmonic distortion is below 2%, 20 to 20,000 CPS and IM distortion is below 1%, 60 and 6,000 CPS. Hum and noise 88 db below full output. Metered balance circuit. Designed especially for easy assembly and years of dependable service. Shipped express only. Shpg. Wt. 52 lbs.

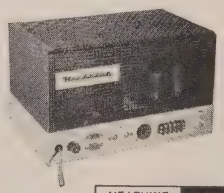

HEATHKIT W-5M **$59.75**

Top-Flight Performance for the Critical Listener

25-WATT HI-FI AMPLIFIER KIT

Considered top value in its power class by leading independent research organizations, the W-5M incorporates all the design features required by the super critical listener. Features include a specially designed Peerless output transformer and KT66 tubes. The circuit is rated at 25 watts and will follow instantaneous power peaks of a full orchestra up to 42 watts. A "tweeter saver" suppresses high frequency oscillation and a new type balancing circuit facilitates adjustment of the "dynamic" balance between output tubes. Frequency response is ±1 db from 5 CPS to 160,000 CPS at 1 watt and within 2 db from 20 to 20,000 CPS at full 25 watts output. Harmonic distortion is less than 1% at 25 watts and IM distortion is 1% at 20 watts (60 and 3,000 CPS, 4:1). Hum and noise are 99 db below 25 watts for truly quiet performance. Rich black and gold colored styling. Shipped express only. Shpg. Wt. 31 lbs.

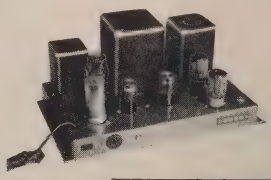

HEATHKIT W4-AM **$39.75**

Faithful Sound Reproduction with Minimum Investment

20-WATT HI-FI AMPLIFIER KIT

This fine amplifier will amaze you with its outstanding performance. It features a true Williamson circuit with extended frequency response, low distortion, and low hum levels. Enjoy true hi-fi with only a minimum investment compared to other units on the market. 5881 tubes and a special Chicago-Standard output transformer are employed to give you full fidelity at minimum cost. Frequency response extends from 10 CPS to 100 kc within ±1 db at 1 watt assuring you of full coverage of the audio range. Clean, clear sound amplification takes place in circuits that hold harmonic distortion at 1.5% and IM distortion below 2.7% at full 20 watt output. Hum and noise are 95 db below full output. Taps on the output transformer are at 4, 8 or 16 ohms to match the speaker system of your choice. An outstanding performer, this investment will bring you years of listening enjoyment. Shipped express only. Shpg. Wt. 28 lbs.

All basic amplifiers recommended for use with model WA-P2, SP-1 or SP-2 preamplifiers

...When You Buy Heathkits

HEATHKIT

"BOOKSHELF" 12-WATT AMPLIFIER KIT

The model EA-2 combines eye-pleasing style and color with many extra features for high quality sound reproduction. This fine amplifier provides full range frequency response from 20 to 20,000 CPS within ±1 db. Harmonic distortion is less than 1% at full 12 watt output over the entire range (20-20,000 CPS). IM distortion is less than 1.5% at 12 watts with low hum and noise. Miniature tubes are used throughout the advanced circuitry, including EL84 output tubes in a push-pull tapped-screen output circuit using a special designed output transformer. Transformer has taps at 4, 8 and 16 ohms. The model EA-2 has its own built-in preamplifier with provision for three separate inputs, mag phono, crystal phono and tuner. The mag phono input features RIAA equalization. Separate bass and treble controls are provided with boost and cut action. A special hum-balance control assures quiet operation. The luxury styled cabinet has a smooth simulated leather texture in black with inlaid gold design and is constructed of vinyl plastic bonded to steel. It resists scuffing, wear, abrasion, and chemicals. The front panel features brushed-gold trim and buff knobs with gold inserts for a very pleasing appearance. An amber neon pilot lamp indicates when the amplifier is on. Cabinet measures 12½" W. x 3 3/16" D. x 4⅜" H. making it suitable for use on a bookshelf, end table, etc. High quality is emphasized throughout for performance matching amplifiers costing many times more. Shpg. Wt. 15 lbs.

HEATHKIT EA-2 **$28.95**

Combines beauty, style and quality

★ LESS THAN 1% DISTORTION AT FULL OUTPUT OVER ENTIRE AUDIO RANGE.

★ BUILT-IN PREAMPLIFIER

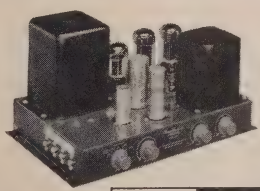

HEATHKIT A9-C **$35.50**

A Bargain Package of Power and Performance

HEATHKIT AV-3 **$29.95**

Invaluable for Hi-Fi Testing

HEATHKIT AW-1 **$29.50**

Measure Exact Power Output

GENERAL-PURPOSE 20-WATT AMPLIFIER KIT

The A9-C combines a preamplifier, main amplifier and power supply all on one chassis providing a compact unit to fill the need for a good high fidelity amplifier with a moderate cash investment. Designed primarily for home installations, it is also capable of fulfilling P.A. requirements. The preamplifier section features four separate switch selected inputs. Separate bass and treble tone controls offer 15 db boost and cut. A true high fidelity performer, the A9-C covers 20 to 20,000 CPS within ±1 db. Front panel is detachable, and can be installed on the outside of a cabinet where the chassis comes through, for custom installations. A fine unit with which to start your hi-fi system. Shpg. Wt. 23 lbs.

AUDIO VTVM KIT

Critical AC voltage measurements are made easy with this high quality vacuum tube voltmeter which emphasizes stability, broad frequency response and sensitivity. Features large 4½" 200 microampere meter, with increased damping in the meter circuit for stability in low frequency tests. Extremely high voltage range handles measurements from a low value of 1 millivolt to a maximum of 300 volts. AC (RMS) voltage ranges are: 0-.01, .03, .1, .3, 1, 3, 10, 30, 100 and 300 volts. Db ranges cover −52 to +52 db. Employs 1% precision multiplier resistors for maximum accuracy. High input impedance (1 megohm at 1,000 CPS). Frequency response is essentially flat from 10 CPS to 200 kc. Shpg. Wt. 6 lbs.

AUDIO WATTMETER KIT

Here is a fine meter to accurately measure output wattage. Five power ranges cover 0-5 mw, 50 mw, 500 mw, 5 w and 50 w full scale. Five switch selected db ranges cover −10 db to +30 db. All indications are read directly on the large 4½" 200 ua meter. Frequency response is ±1 db from 10 CPS to 250 kc. External or internal load resistors are selected with convenient front panel switch. Non-inductive load resistors are built in for 4, 8, 16 or 600 ohms impedance. Precision multiplier resistors are used for high accuracy and incorporates a crystal diode bridge for wide-range frequency response. Modern styling and convenient front panel design. Cabinet is ventilated to allow efficient cooling of load resistors. Shpg. Wt. 7 lbs.

HEATH COMPANY • a subsidiary of Daystrom, Inc. • **Benton Harbor 20, Mich.**

Easy to Buy - Easy to Build - Easy to Use...

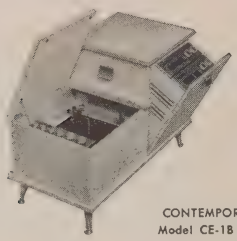

HEATHKIT
CE-1
$43.95 each

CONTEMPORARY
Model CE-1B Birch
Model CE-1M Mahogany

TRADITIONAL
Model CE-1T Mahogany

Combine all your Hi-Fi equipment in this attractive cabinet

CHAIRSIDE ENCLOSURE KIT

This Chairside Enclosure lets you combine all of your hi-fi equipment into one compact control center and, at the same time add a beautiful piece of furniture to your home. The CE-1 is designed to house the AM and FM tuners (BC-1A and FM-3A) and the WA-P2 preamplifier along with the majority of record changers which will fit into the space provided. Adequate room is available in the rear of the unit to house any of the Heathkit amplifiers designed to operate with the WA-P2. The enclosure is flexible enough to give you a large choice in component installation. If only one tuner and the preamplifier are used, the two units can be installed in the tilt-out drawer, or if more convenient, either unit can be placed in the space provided in front of the changer compartment. The tilt-out shelf can be installed on either right or left side and the lift-top lid is similarly designed to lift from either side depending on your choice during construction. Good ventilation is achieved through appropriately placed slots in the bottom and back of the enclosure. Overall dimensions are 18"W. x 24" H. x 35½" D. The changer compartment measures 17¾" L. x 16" W. x 9⅝" D. All parts are precut and predrilled for easy assembly and attractive hardware is supplied to match each style. The contemporary cabinet is available in either mahogany or birch and the traditional cabinet is available in mahogany only. Furniture grade plywood can be finished to your taste. Shpg. Wt. 46 lbs.

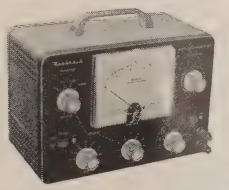

HEATHKIT AG-9A $34.50

Your own source of Hi-Fi audio signals

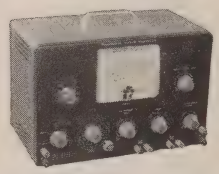

HEATHKIT AA-1 $49.95

3 Audio test instruments in one compact unit

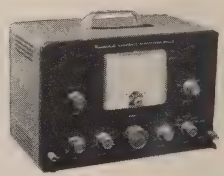

HEATHKIT HD-1 $49.50

Check amplifier distortion quickly

AUDIO SIGNAL GENERATOR KIT

The model AG-9A is "made to order" for high fidelity applications, and provides quick and accurate selection of low-distortion signals from 10 CPS to 100 kc. Three rotary switches select two significant figures and a multiplier to determine audio frequency. Incorporates step-type and a continuously variable output attenuator. Output indicated on large 4½" panel meter, calibrated in volts and db. Attenuator system operates in 10 db steps, corresponding to meter calibration, in ranges of 0-.003, .01, .03, .1, .3, 1, 3 and 10 volts RMS. "Load" switch permits use of built-in 600-ohm load, or external load of different impedance. Output and frequency indicators accurate to within ±5%. Distortion less than .1 of 1% between 20 and 20,000 CPS. Shpg. Wt. 8 lbs.

AUDIO ANALYZER KIT

Complete high fidelity testing facilities are yours in the AA-1. It combines the functions of three separate instruments; an AC VTVM, audio wattmeter and a complete IM analyzer with filters and high and low frequency oscillators built in. VTVM ranges are: 0-.01, .03, .1, .3, 1, 3, 10, 30, 100 and 300 volts (RMS). Db scale reads from −65 to +52 dbm. Wattmeter ranges are: .15 mw, 1.5 mw, 15 mw, 150 mw, 1.5 w, 15 w and 150 w. IM scales are 1%, 3%, 10%, 30% and 100% full scale. Provides internal load resistors of 4, 8, 16 or 600 ohms. Combining and consolidating functions reduces the number of test leads and controls required for the same test. Complete instructions are provided for easy assembly, also valuable information on use of instrument. Shpg. Wt. 13 lbs.

HARMONIC DISTORTION METER KIT

Valuable in both designing and servicing of audio circuits, the HD-1 used with an audio signal generator, will accurately measure harmonic distortion at any or all frequencies between 20 and 20,000 CPS. Distortion is read on panel meter in ranges of 0-1, 3, 10, 30 and 100% full scale. Full scale voltage ranges of 0-1, 3, 10 and 30 volts are provided for the initial reference settings. Signal-to-noise ratio is measured on a separate meter scale calibrated in db. Features high input impedance (300,000 ohms) and 1% precision resistors in the VTVM voltage divider circuit for excellent sensitivity and accuracy. High quality components insure years of dependable service. Complete instructions provided for easy assembly and operation. Shpg. Wt. 13 lbs.

Heathkits are Your Best Dollar Value

HEATHKIT

TRANSISTOR PORTABLE RADIO KIT

The overwhelming sales of this outstanding transistor portable have made a substantial price reduction possible . . . in addition, an all new plastic molded case adds the finishing touch to the exceptional circuitry. Six name-brand (Texas Instrument) transistors are used for extra good sensitivity and selectivity. The 4" x 6" PM speaker with heavy magnet provides excellent tone quality. Use of this large speaker and roomy chassis make it unnecessary to crowd components adding greatly to the ease of construction. Transformers are prealigned so it is ready for service as soon as construction is completed. A touchup in alignment is easily accomplished on a station by following simple instructions in manual. Alignment tool furnished. Has built-in rod-type antenna for reception in all locations. Six standard size "D" flashlight cells are used for extremely long battery life (between 500 and 1000 hours) and they can be purchased almost anywhere. Cabinet is two-tone blue molded plastic with pull-out carrying handle. Dimensions are 9½" L. x 7¼" H. x 4" D. Shpg. Wt. 6 lbs.

Model XR-1-L: Identical to XR-1-P except in genuine leather case. Rich, warm sun-tan tone. Leather carrying strap included. Shpg. Wt. 7 lbs.

Leather Case: can be purchased separately if desired. Fits all XR-1P's and XR-1's. No. 93-1. Shpg. Wt. 3 lbs. $6.95.

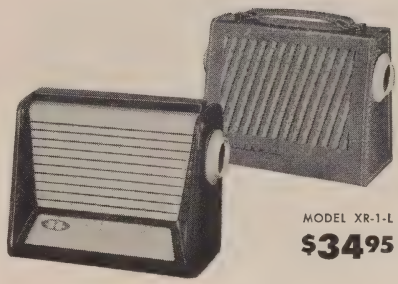

MODEL XR-1-L
$34.95

HEATHKIT XR-1-P **$29.95**

Newly designed plastic case . . . new low price!

★ 4" X 6" SPEAKER FOR "BIG SET" TONE
★ LONG BATTERY LIFE (500 to 1000 Hours)

HEATHKIT CT-1 **$7.95**

Test condensers right in the circuit

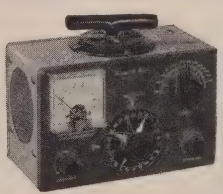

HEATHKIT DF-1 **$54.95**

Pin-point your exact location

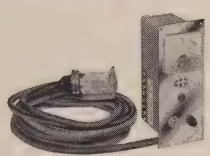

HEATHKIT FD-1 **$35.95 each**
(6 volt model FD-1-6)
(12 volt model FD-1-12)

Detects gas fumes

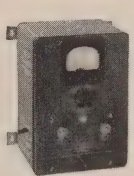

HEATHKIT MC-1 **$42.95**

Save your boat batteries

IN-CIRCUIT CAPACI-TESTER KIT

Check most capacitors for "open" or "short" right in the circuit with this handy kit. Detects open capacitors from about 50 mmf up, not shunted by an excessively low resistance value. Checks shorted capacitors up to 20 mfd (not shunted by less than 10 ohms). (Does not detect leakage nor check electrolytic condensers.) Employs a 60-cycle frequency for the short test and a 19 megacycle frequency for the open test. Uses electron beam "eye" tube for quick indication. Test leads included. Shpg. Wt. 5 lbs.

TRANSISTOR RADIO DIRECTION FINDER KIT

This transistor radio compass will double as a portable radio. Covers the standard broadcast band from 540 to 1600 kc. Ideal for use aboard boats and also on land by hunters, hikers, etc. A directional high-Q ferrite antenna rotates from the front panel to obtain a fix on a station. A 1 ma meter serves as null and tuning indicator. Prealigned IF transformers—six transistor circuit. Powered by tiny 9-volt battery with spare included. Dimensions 7½" W. x 5⅜" H. x 5⅜" D. Shpg. Wt. 5 lbs.

FUEL VAPOR DETECTOR KIT

Protect your boat and passengers against fire and explosion with one of these fuel vapor detector kits. Indicates the presence of fumes on a three-color "safe-dangerous" meter scale and immediately shows if it is safe to start the engine. A pilot lamp shows when the detector is operating. Easy to build and install, even by one not having previous experience. Operates from your boat battery. The kit is complete with heavy-duty neoprene insulated cable and includes spare detector unit. Shpg. Wt. 4 lbs.

MARINE CONVERTER KIT

Charge 6 or 12 volt batteries with this marine converter and battery charger. A panel mounted 25 ampere meter continuously monitors the charging current. Moisture and fungus proofed for rugged marine use. Convection cooling prevents unsafe temperature rise. The MC-1 has no moving parts, tubes nor blowers to wear out or break. Mounting brackets are supplied for easy installation on any boat. Ideal for keeping batteries fully charged or to supply extra current for appliances, Shpg. Wt. 16 lbs.

HEATH COMPANY • a subsidiary of Daystrom, Inc. • Benton Harbor 20, Mich.

HEATHKIT TX-1 **$229.50**

Complete Versatility for Top-Notch Amateur Communications

★ NEWLY DESIGNED VFO—ROTATING SLIDE RULE DIAL
★ MODERN STYLING—PROVISION FOR SSB ADAPTER

"APACHE" HAM TRANSMITTER KIT

Fresh out of the Heath Company laboratories, the brand-new "Apache" model TX-1 ham transmitter features modern styling and the latest in circuitry for extra fine performance. The "Apache" is a high quality transmitter operating with a 150 watt phone input and 180 watt CW input. In addition to CW and phone operation, built-in switch selected circuitry provides for single-sideband transmission through the use of a plug-in external adapter. These SSB adapters will be available in the near future. A compact, stable and completely redesigned VFO provides low drift frequency control necessary for SSB transmission. A slide rule type illuminated rotating VFO dial with vernier tuning provides ample bandspread and precise frequency settings. The bandswitch allows quick selection of the amateur bands on 80, 40, 20, 15 and 10 meters. (11M with crystal control). This unit also has adjustable low level speech clipping and a low distortion modulator stage employing two of the new 6CA7/EL-34 tubes in push-pull class AB operation. Time sequence keying is provided for "chirpless" break-in CW operation. The final amplifier is completely shielded for greater TVI protection and transmitter stability. Die-cast aluminum knobs and front panel escutcheons add to the attractive styling of the transmitter. Pi network output coupling matches antenna impedances between 50 and 72 ohms. Shpg. Wt. 107 lbs.

$50.00 deposit required on C.O.D. orders. Shipped motor freight unless otherwise specified.

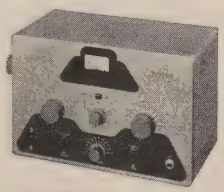

HEATHKIT DX-20 **$35.95**

An Ideal Code Transmitter

HEATHKIT DX-100 **$189.50**

You'll be Proud to Own This Outstanding Performer

HEATHKIT DX-40 **$64.95**

Phone & CW Facilities at Low Cost

DX-20 CW TRANSMITTER KIT

Designed especially for CW work, the DX-20 features high efficiency at low cost. An ideal rig for the novice or advanced-class CW operator. Plate power input is 50 watts, and covers 80, 40, 20, 15, 11 and 10 meters with single knob bandswitching. Features a single 6DQ6A tube in the final amplifier stage and a 6CL6 as a crystal oscillator. Pi network output circuit matches various antenna impedances between 50 and 1000 ohms and reduces harmonic output. Top-quality parts are featured throughout, including "potted" transformers, etc., for long service life. Complete shielding to minimize TVI. Removable metal pull-out plug on left end of cabinet provides access for crystal changing. Very easy to build with complete instructions supplied. Shpg. Wt. 19 lbs.

DX-100 PHONE AND CW TRANSMITTER KIT

Well known for its high quality and fine performance the DX-100 features a built-in VFO, modulator, and power supply, complete shielding to minimize TVI, and a pi network coupling to match impedances from 50 to 600 ohms. RF output is in excess of 100 watts on phone and 120 watts on CW, for clean strong signals on all ham bands from 10 to 160 meters. Single knob bandswitching and illuminated VFO dial and meter face add real operating convenience. RF output stage uses a pair of 6146 tubes in parallel, modulated by a pair of 1625's. High quality components are used throughout, such as potted transformers, silver-plated or solid coin silver switch terminals, aluminum-heat dissipating caps on the final tubes, copper plated chassis, etc. Shpg. Wt. 107 lbs.

$50.00 deposit required on C.O.D. orders. Shipped motor freight unless otherwise specified.

DX-40 PHONE AND CW TRANSMITTER KIT

An outstanding buy in its power class the DX-40 provides both phone and CW operation on 80, 40, 20, 15, 11 and 10 meters. A single 6146 tube is used in the final amplifier stage to provide full 75 watt plate power input on CW, or controlled carrier modulation peaks up to 60 watts for phone operation. Modulator and power supplies are built in and single-knob bandswitching is combined with the pi network output circuit for complete operating convenience. Complete shielding to minimize TVI. Provision is made for three crystals. A four-position switch selects any of the three crystals or a jack for external VFO. Crystal sockets are reached through access door in rear of cabinet. High quality D'Arsonval movement panel meter. Shpg. Wt. 25 lbs.

For Real Ham Enjoyment

HEATHKIT

"MOHAWK" HAM RECEIVER KIT

Here is a ham receiver that any radio operator would be proud to own. The "Mohawk" has all the functions required for high quality communications with clear, rock-steady reception on all bands. This 15-tube receiver features double conversion with IF's at 1682 kc and 50 kc and covers all of the amateur frequencies from 160 through 10 meters on seven bands with an extra band calibrated to cover 6 and 2 meters using a converter. Receiver accommodations are provided for these converters which will be available in Heathkits soon. The "Mohawk" is specially designed for single-sideband reception with crystal controlled oscillators for upper and lower sideband selection. A completely preassembled, wired and aligned front end coil assembly assures ease of construction and top performance of the finished unit. Other features include five selectivity positions from 5 kc to 500 CPS, bridged T-notch filter for maximum heterodyne rejection, and a built-in 100 kc crystal calibrator. The set provides a 10 db signal-to-noise ratio at less than 1 microvolt input. Front panel features S meter, separate RF, IF and AF gain controls, T-notch tuning, T-notch depth, ANL, AVC, BFO, bandswitch, tuning, antenna trimmer, calibrate set, calibrate on, CW-SSB-AM, receive-standby, upper-lower sideband, selectivity, phone jack and a wide band rotating slide rule type vernier tuning dial with easy to read calibrations. Shpg. Wt. 67 lbs.

$50.00 required on C.O.D. orders. Shipped motor freight unless otherwise specified.

HEATHKIT RX-1 **$274.95**

Now in Kit Form a Top Quality Ham Band Receiver

★ PREWIRED AND ALIGNED FRONT END COIL ASSEMBLY.
★ CRYSTAL CONTROLLED OSCILLATORS FOR DRIFT-FREE RECEPTION.

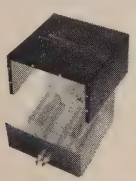

HEATHKIT B-1 **$8.95**

Get Proper Match Between Transmitter and Antenna

BALUN COIL KIT

Unbalanced coax lines used on the most modern transmitters can be matched to balance lines of either 75 or 300 ohms impedance by using the model B-1 Balun Coil Kit. Can be used with transmitters and receivers without adjustment over the frequency range of 80 through 10 meters, and will handle power inputs up to 200 watts. Cabinet size is 10" square by 5" D. and may be located any distance from the transmitter or antenna. A protective cover is supplied to prevent damage in outdoor installations. Shpg. Wt. 4 lbs.

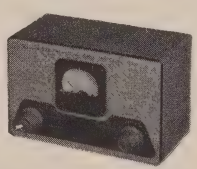

HEATHKIT AM-2 **$15.95**

Measure Standing Wave Ratio

REFLECTED POWER METER KIT

The match of your antenna transmission system can be checked by measuring the forward and reflected power or standing wave ratio from 1:1 to 6:1 with this fine unit. Designed to handle a peak power of well over 1 kilowatt of energy the AM-2 may be left in the antenna system feed line at all times. Band coverage is 160 meters through 2 meters. Input and output impedances for 50 or 75 ohm lines. No external power required for operation. Cabinet size is 7⅛" x 4⅛" x 4⅛". Shpg. Wt. 3 lbs.

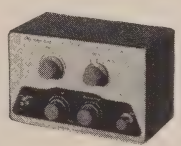

HEATHKIT VX-1 **$23.95**

Eliminates Hand Switching

ELECTRONIC VOICE CONTROL KIT

This unique device allows you to switch from receiver to transmitter merely by talking into your microphone . . . you get the advantage of "telephone-type conversation" as in single sideband but with regular AM transmission. The unit is adjustable to all conditions by sensitivity controls provided. A variable time delay control changes the "hold" time. Provision is made for receiver and speaker connections and also for a 117 volt antenna relay. Built-in power supply. Complete instructions provided. Shpg. Wt. 5 lbs.

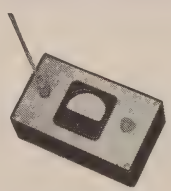

HEATHKIT PM-1 **$14.95**

Quick Check of Transmitter Operation

RF POWER METER KIT

This self contained unit requires no power for operation. You simply place it close to the transmitter antenna to sample the RF field which is then indicated on the panel meter. Operates with any transmitter having an output frequency between 100 kc and 250 mc, regardless of power. Sensitivity is 0.3 volts RMS full scale, and a special control on the panel allows for further adjustment of the sensitivity. Measures 3¼" W. x 6¼" L. x 2" D. An easy way to put your mind at ease concerning transmitter operation. Shpg. Wt. 2 lbs.

HEATH COMPANY • a subsidiary of Daystrom, Inc. • **Benton Harbor 20, Mich.**

Choose from a wide variety of Heathkits

DUAL-CHASSIS 20 WATT HI-FI AMPLIFIER KIT

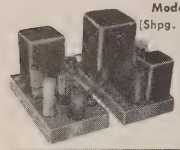

Model W3-AM
(Shpg. Wt. 29 lbs.)
$49.75

12" UTILITY SPEAKER

Model 401-6
(Shpg. Wt. 7 lbs.)
$7.50

ALL-BAND RADIO KIT

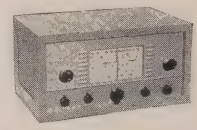

Model AR-3
(Shpg. Wt. 12 lbs.)
$29.95
(less cabinet)

CRYSTAL RADIO KIT

Model CR-1
(Shpg. Wt. 3 lbs.)
$7.95

BROADCAST BAND RADIO KIT

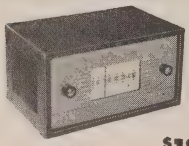

Model BR-2
(Shpg. Wt. 10 lbs.)
$18.95
(less cabinet)

ELECTRONIC CROSSOVER KIT

Model XO-1
(Shpg. Wt. 6 lbs.)
$18.95

"Q" MULTIPLIER KIT

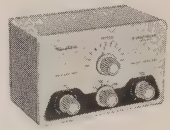

Model QF-1
(Shpg. Wt. 3 lbs.)
$9.95

"AUTOMATIC" CONELRAD ALARM KIT

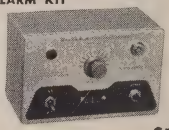

Model CA-1
(Shpg. Wt. 4 lbs.)
$13.95

GRID DIP METER KIT

Model GD-1B
(Shpg. Wt. 4 lbs.)
$21.95

VIBRATOR POWER SUPPLY KIT

6 volt Model VP-1-6
12 volt Model VP-1-12
(Shpg. Wt. 4 lbs.)
$7.95 ea.

VARIABLE FREQUENCY OSCILLATOR KIT

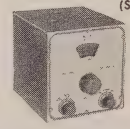

Model VF-1
(Shpg. Wt. 7 lbs.)
$19.50

PROFESSIONAL RADIATION COUNTER KIT

Model RC-1
(Shpg. Wt. 8 lbs.)
$79.95

ISOLATION TRANSFORMER KIT

Model IT-1
(Shpg. Wt. 9 lbs.)
$16.50

ELECTRONIC SWITCH KIT

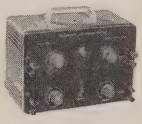

Model S-3
(Shpg. Wt. 8 lbs.)
$21.95

REGULATED POWER SUPPLY KIT

Model PS-3
(Shpg. Wt. 17 lbs.)
$35.50

VOLTAGE CALIBRATOR KIT

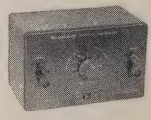

Model VC-3
(Shpg. Wt. 4 lbs.)
$12.50

DIRECT-READING CAPACITY METER KIT

Model CM-1
(Shpg. Wt. 7 lbs.)
$29.50

TUBE CHECKER KIT

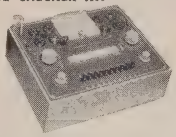

Model TC-2
(Shpg. Wt. 12 lbs.)
$34.95

EASY TIME PAYMENTS

AVAILABLE FOR YOUR CONVENIENCE . . .

Any order totaling $90 or more can be paid for in small monthly payments (send for complete details).

RESISTANCE SUBSTITUTION BOX KIT

Model RS-1
(Shpg. Wt. 2 lbs.)
$5.50

CONDENSER SUBSTITUTION BOX KIT

Model CS-1
(Shpg. Wt. 2 lbs.)
$5.50

CATHODE RAY TUBE CHECKER KIT

Model CC-1
(Shpg. Wt. 10 lbs.)
$24.95

LABORATORY RF GENERATOR KIT

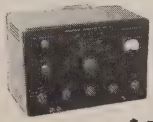

Model LG-1
(Shpg. Wt. 16 lbs.)
$48.95

"Q" METER KIT

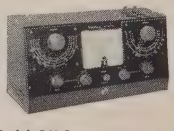

Model QM-1
(Shpg. Wt. 14 lbs.)
$44.50

DECADE CONDENSER KIT

Model DC-1
(Shpg. Wt. 3 lbs.)
$16.50

DECADE RESISTANCE KIT

Model DR-1
(Shpg. Wt. 4 lbs.)
$19.50

...to Fill Your Exact Needs

HEATHKIT

PORTABLE TUBE CHECKER KIT

Model TC-2P
(Shpg. Wt. 15 lbs.)

$38.95

TV PICTURE TUBE TEST ADAPTER FOR TC-2 AND TC-2P

Model 355
(Shpg. Wt. 1 lb.)

$4.50

BINDING POST KIT

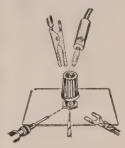

Model 362
(Shpg. Wt. 1 lb.)

$4.00

BATTERY TESTER KIT

Model BT-1
(Shpg. Wt. 2 lbs.)

$8.50

ELECTRONIC IGNITION ANALYZER KIT

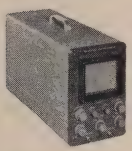

MODEL IA-1
(Shpg. Wt. 20 lbs.)

$59.95

SCOPE PROBES

Scope Demodulator Probe Kit
Model 337-C
(Shpg. Wt. 1 lb.)

$3.50

Low Capacity Probe Kit
Model 342
(Shpg. Wt. 1 lb.)

$3.50

VTVM PROBES

30,000 Volt DC HV
Probe Kit No. 336
Shpg. Wt. 2 lbs. **$4.50**

Etched Circuit RF
Probe Kit No. 309-C
Shpg. Wt. 1 lb. **$3.50**

Peak-to-peak Voltage
Probe Kit No. 338-C
Shpg. Wt. 2 lbs. **$5.50**

ENLARGER TIMER KIT

Model ET-1
(Shpg. Wt. 3 lbs.)

$11.50

IMPEDANCE BRIDGE KIT

Model IB-2A
(Shpg. Wt. 12 lbs.)

$59.50

"LOW RIPPLE" BATTERY ELIMINATOR KIT

Model BE-5
(Shpg. Wt. 21 lbs.)

$39.95

ELECTRONIC ANALOG COMPUTER KIT
Full Computer Group C

$945.00

Write for free folder.

Free Catalog

Send for this informative booklet describing these and many other do-it-yourself kits.

ORDER DIRECT BY MAIL . . . from the WORLD'S LARGEST MANUFACTURER

OF ELECTRONIC INSTRUMENTS IN KIT FORM

Save ½ or more over equivalent ready-made products by buying direct and assembling them yourself. You gain priceless knowledge through complete and informative construction manuals.

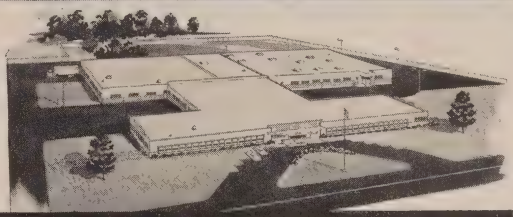

HEATH COMPANY A Subsidiary of Daystrom, Inc. **BENTON HARBOR 20, MICH.**

ORDER BLANK

NOTE: All prices and specifications subject to change without notice.

Enclosed find ( ) check ( ) money order for_____
Please ship C.O.D. ( ) postage enclosed for_____pounds.

On Express orders do not include transportation charges—they will be collected by the express agency at time of delivery.

On Parcel Post Orders include postage for weight shown. All prices are NET F.O.B. Benton Harbor, Michigan, and apply to Continental U.S. and Possessions only.

Name_____

Address_____

City & Zone_____State_____
(PLEASE PRINT)

SHIP VIA
☐ Parcel Post
☐ Express
☐ Freight
☐ Best Way

QUANTITY	ITEM	MODEL NO.	PRICE
	☐ SEND FREE Heathkit Catalog	POSTAGE	
		TOTAL	

LOWDOWN ON TAPE PLAYBACK EQUALIZATION

For proper reproduction of prerecorded tapes, your tape playback amplifier should have NARTB equalization. Unfortunately, many tape recorders don't have it. Here's how it works, and some simple circuits to add the NARTB curve to your hi fi or tape recorder

By HERMAN BURSTEIN and HENRY C. POLLAK*

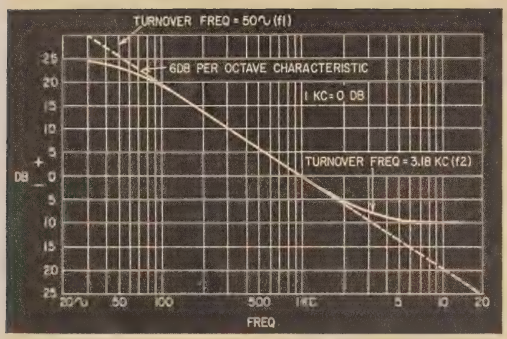

Fig. 1—The NARTB playback equalization curve.

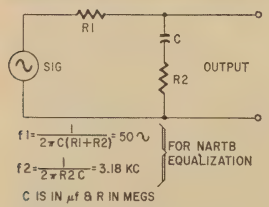

Fig. 2—Fundamental losser-type bass-boost circuit.

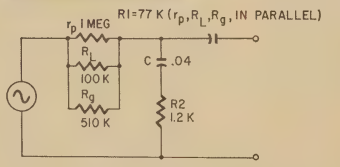

Fig. 4—Equivalent circuit of Fig. 3.

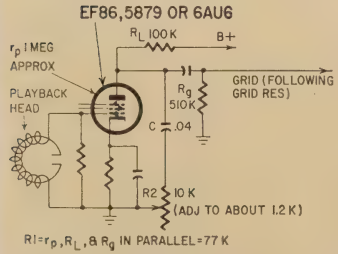

Fig. 3 — Practical bass-boost circuit using a pentode.

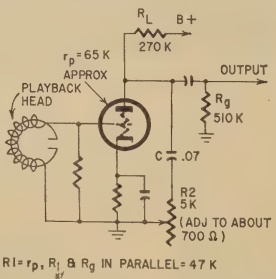

Fig. 5—Practical bass-boost circuit using a high-mu triode.

Fig. 6—A medium-mu triode in a practical bass-boost circuit for a tape playback amplifier.

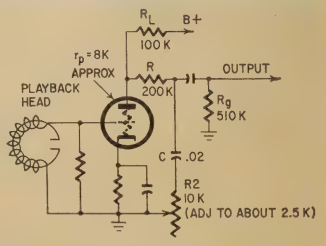

COMMERCIAL prerecorded tapes generally use NARTB equalization at the 7.5-ips speed. For flat response when playing these tapes, the playback amplifier must provide NARTB playback compensation, mainly a lot of bass boost (see Fig. 1). However, many home tape recorders, particularly the older and less expensive ones, do not have NARTB playback equalization, but some other kind of bass-boost characteristic instead. Also, a number of control amplifiers that have a special input for a tape head fail to supply NARTB compensation. Such tape machines and control amplifiers generally provide a smaller amount of boost, starting at a lower frequency. Therefore, a prerecorded tape played on such a machine tends to sound thin in the bass region.

To get flat response when playing prerecorded tapes, you may have to change the playback equalization circuit of the tape machine or control amplifier to produce the curve of Fig. 1. If playback equalization of a tape recorder is changed, the machine's record equalization must be changed correspondingly to yield flat response when playing tapes recorded on this machine. Therefore, you may prefer to introduce NARTB playback equali-

*Authors of *Elements of Tape Recorder Circuits*, Gernsback Library, No. 67.

zation using a switch. This lets you use the original equalization when playing tapes recorded on the modified machine and NARTB equalization when playing commercial tapes. As you will soon see, the components in the equalization circuit are so few that the problem of switching between the two circuits is not complicated. Generally, a simple double-throw switch will do the job.

So the technician or handy audiophile can incorporate the correct circuit values for NARTB equalization, we will analyze the most commonly used playback boost circuits. First, however, it would be helpful to explain *why* bass boost is required when playing a tape, and to state some general principles of playback equalization.

Bass boost in playback

The playback head is an inductive device — essentially a ferromagnetic material with a winding. Its output voltage is proportional to the rate at which the magnetic field on the tape changes—proportional to frequency. Thus the head's output decreases 6 db per octave as frequency declines, making a very substantial quantity of compensating bass boost necessary—up to 36 db of it for NARTB equalization. Where the NARTB curve is employed, bass boost starts (3-db rise) at 3,180 cycles and continues to rise with declining frequency, but eventually levels off so that at 50 cycles it is 3 db below the maximum bass boost eventually attained.

Since the declining output of the playback head follows a 6-db-per-octave slope, the bass-boost curve must do the same. Therefore, R-C circuits which have such a characteristic are used in playback bass-boost circuits, whether of the losser or feedback type. In feedback circuits, only voltage-feedback types are used. Use of current feedback—produced by a large cathode resistor—would necessitate bypassing the resistor with an inductor to boost the bass, a practice that is objectionable because of the disadvantages of inductors for such use—hum pickup, cost, lack of precise NARTB equalization.

Although the output of the playback head continually drops 6 db per octave with decreasing frequency, note that the curve of Fig. 1 does not continue upward throughout the bass range, but levels off instead. This moderates the problem of hum amplification, a severe one in all cases. The loss of bass response due to leveling off of the playback curve is made up in recording by supplying a slight amount of corresponding bass boost.

Playback losser circuits

Fig. 2 shows the fundamental losser type bass-boost circuit. The practical circuits discussed all refer to the elements of Fig. 2, whose roles may be explained as follows:

At very high frequencies, where capacitor C is a virtual short circuit, Fig. 2 is in effect a voltage divider made up of R1 and R2. This sets a limit to the maximum drop in response. The maximum drop is referred to as the insertion loss. The limit to which gain declines is called the *lower shelf*. The original signal level is referred to as the *upper shelf*.

As frequency decreases, the reactance X_c of capacitor C rises and approaches the resistance of R2. At the upper turnover frequency, f2 (3,180 cycles), R2 and X_c are equal and the output is 3 db above the lower shelf. As frequency declines further, X_c continues to increase and the output goes up until the value of X_c approaches that of R1 + R2. When X_c becomes equal to R1 + R2 (at f1, 50 cycles), the output voltage is within 3 db of the input voltage and a further rise is therefore very limited. In most cases R1 is much bigger than R2 (62 times as large for NARTB equalization), so the lower turnover frequency f1 is essentially determined by R1 and C. The upper turnover frequency, as already indicated, is determined by R2 and C.

Fig. 3 is a practical version of Fig. 2, employing an EF86, 5879 or 6AU6 pentode. R1 (thinking in terms of Fig. 2) consists of the 100,000-ohm load resistor R_L in parallel with the much larger plate resistance (r_p) of the tube, assumed to be about 1 megohm, and the following 510,000-ohm grid resistor R_g. For easier visualization see Fig. 4, the equivalent circuit. The 77,000-ohm parallel resistance R1 (r_p, R_L and R_g in parallel) and the .04-μf capacitor esesentially determine the lower turnover frequency of 50 cycles. R2, adjusted to about 1,200 ohms, and C determine the upper turnover frequency of 3,180 cycles.

Using triodes

Fig. 5 is essentially the same as Fig. 3, except that a triode is used instead of a pentode. The triode is assumed to have a plate resistance of 65,000 ohms, although this value differs according to tube type. R1, again made up of r_p, R_L and R_g in parallel, is 47,000 ohms. R1 is essentially determined by r_p, which is considerably smaller than R_L and R_g. R1 and C essentially produce the lower turnover of 50 cycles. R2 adjusts to about 700 ohms and C produces the 3,180-cycle turnover.

Sometimes triodes are considered preferable to pentodes as input tubes because, as a rule, they produce less hum and noise (although this rule has very definite exceptions). Therefore, on the grounds of hum and noise, the circuit of Fig. 5 might be preferred to that of Fig. 3. On the other hand, a pentode has an important advantage over a triode in possessing much lower input capacitance, preventing high-frequency loss. Thus it might seem that the equalization circuit using the triode is at a disadvantage.

This is not true of Fig. 5. Input capacitance consists mostly of that between plate and grid and in effect varies directly with gain, due to Miller effect. (For example, when the grid goes positive, the plate goes negative—the more tube gain, the greater the negative voltage on the plate. The signal source sends a charging current into the grid–plate capacitance, whose ability to absorb current from the input signal varies with the potential across this capacitance. Hence the greater the gain, the more signal current is absorbed by plate–grid capacitance and the greater are the signal losses. This effect is equivalent to that produced by a larger capacitance between plate and grid than the actual physical capacitance.) In Fig. 5, equalizer capacitor C approaches a short circuit at high frequencies and the load consists mainly of R2, a relatively small value. Since the load, principally R2, is in series with the plate resistance, by voltage-divider action there is very little output voltage across R2. In brief, the tube's gain is greatly reduced at high frequencies. Along with this reduction in gain, there is a decrease in Miller effect. In other words, the input capacitance becomes

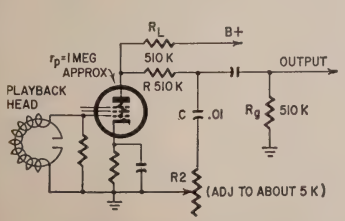

RI=R IN SERIES WITH r_p & R_L IN PARALLEL, & THESE PARALLEL WITH R_g=313 K

Fig. 7—Pentode bass-boost circuit designed to keep changes in plate resistance from affecting equalization.

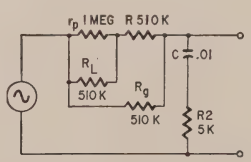

Fig. 8—Equivalent circuit of Fig. 7.

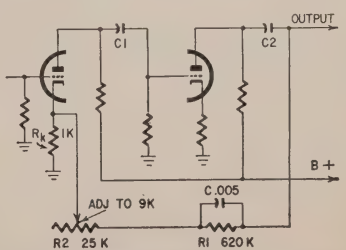

Fig. 9—Voltage feedback over two amplifier stages gives bass boost.

"Silver runs in veins,
GOLD is where you find it."

THE GOLD RUSH

to PYRAMID'S new "Gold Standard" Mylar® Capacitor, ±10% Tolerance, is on!

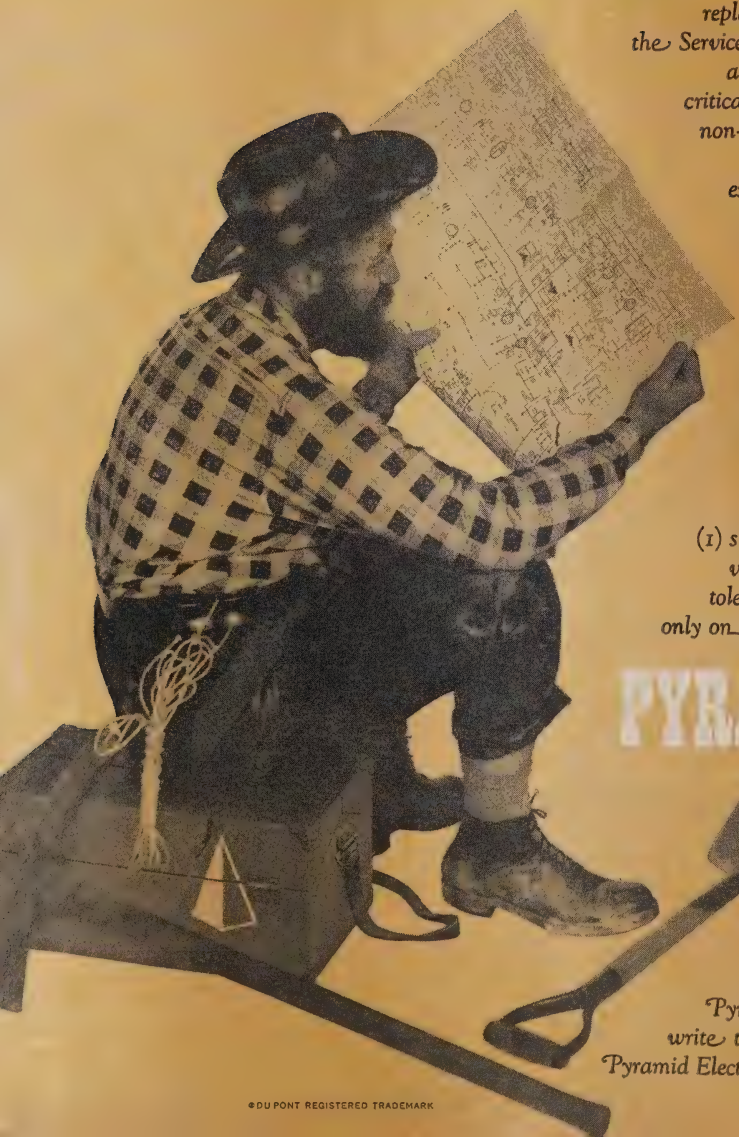

For the first time in the radio and TV replacement market, Pyramid offers the Service Technician for his everyday use, a new high reliability capacitor with a critical tolerance factor of ±10, featuring non-hygroscopic Mylar® dielectric. This construction additionally, provides extreme high resistance to moisture plus high insulation resistance.

The Pyramid "Gold Standard" Mylar capacitor absolutely guarantees the reliability that makes other types of by-pass and coupling capacitors obsolete.

Now at a price competitive with paper capacitors currently in use, Pyramid's new "Gold Standard" Mylar capacitor is available in (1) standard capacity values (2) standard voltage ratings (3) standard capacity tolerance of ±10%, formerly available only on special orders at premium prices.

PYRAMID

The Gold Rush is on at your Pyramid distributor or for information, write to "Gold Standard" Assayers Office, Pyramid Electric Company, North Bergen, N. J.

®DU PONT REGISTERED TRADEMARK

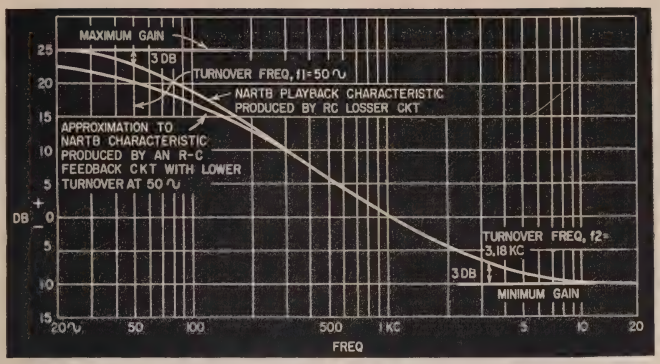

$$f1 = \frac{1}{2\pi R1C} = 50 \text{ cps}; f2 = \frac{1}{2\pi C\,(R2 + R_K)} = 3{,}180 \text{ cps}$$

Fig. 10—Comparison of bass-boost curves produced by R-C losser and feedback circuits.

very small and high-frequency response is not endangered.

Still, there is a slight disadvantage to the circuit of Fig. 5. To the extent that plate resistance departs from its nominal value due to voltage changes, age, or the individual tube used, the low turnover frequency of 50 cycles is affected. Therefore bass equalization will not be absolutely precise. However, this variation is usually small enough to be acceptable for practical operation.

Fig. 6 represents the use of a medium-mu triode, such as half of a 12AU7. Here the plate resistance, assumed to be 8,000 ohms, is too low to serve as the principal component of R1. That is, C would have to be quite substantial, about 0.4 μf, which is relatively expensive, space-consuming and subject to hum pickup because of size. Therefore, a 200,000-ohm resistor is used as the principal component of R1, which figures out to 147,000 ohms. This value, in conjunction with a .02-μf capacitor, produces a low turnover frequency of about 50 cycles. Potentiometer R2 is adjusted to about 2,500 ohms to produce a 3,180-cycle turnover frequency in conjunction with C.

Fig. 7 is similar to Fig. 6, except that a pentode is used. Although the load resistance in parallel with the tube's plate resistance and with the following grid resistor is high enough to serve as R1, the designer has sought to reduce the effect of changes in plate resistance upon equalization by inserting R, a 510,000-ohm resistor. Consequently R1 is determined to a substantial extent by R. The plate and load resistances are in parallel with each other (combined value about 330,000 ohms) and in series with R. All these are in parallel with the 510,000-ohm grid resistor, making a toal resistance for R1 of 313,000 ohms. R1 and the .01-μf capacitor produce a turnover frequency close to 50 cycles. R2 is adjusted to about 5,000 ohms to produce the 3,180-cycle turnover frequency.

To help unravel the complications of Fig. 7, the equivalent circuit is shown in Fig. 8. Except for the values of the components, Fig. 8 is also the equivalent of Fig. 6.

Feedback circuits

Bass equalization circuits using voltage feedback have two worth-while advantages over losser circuits. Distortion is reduced particularly at the high frequencies where signal output of the tape head is greatest. The effective plate resistance of the tube is reduced and therefore its output impedance is also reduced. This makes it easier to maintain high-frequency response, since shunt capacitance (stray capacitance and capacitance of the following stage) produces less treble loss across a small resistance than a large one.

A typical feedback bass-boost circuit with good characteristics is shown in Fig. 9. R2 is relatively small, so at high frequencies—where C is a virtual short circuit—a large amount of negative feedback is applied to the cathode of the first stage. R2, R_k and C essentially determine the upper turnover frequency (3,180 cycles). As frequency decreases, the reactance of C becomes equal to R2 + R_k, feedback starts decreasing, and gain starts increasing. R1 and C essentially determine the lower turnover frequency (50 cycles). As frequency continues to decrease, the reactance of C becomes equal to R1, C no longer bypasses R1, feedback stops increasing and gain approaches a maximum. (At very low frequencies the value of coupling capacitors C1 and C2 must be properly selected to avoid subsonic peaking due to feedback.)

The roles of R1, R2 and C in Fig. 9 correspond to those of the same components in losser bass-boost circuits. However, the response curve may not be as precisely shaped by feedback as by losser networks. That is, the shift from flat response to a 6-db-per-octave characteristic tends to be considerably more gradual at the low end with a feedback equalizer. Fig. 10 compares the bass boost achieved by an R-C losser and an R-C feedback circuit. The turnover frequencies are nominally 50 and 3,180 cycles for both circuits. It can be readily seen that the feedback

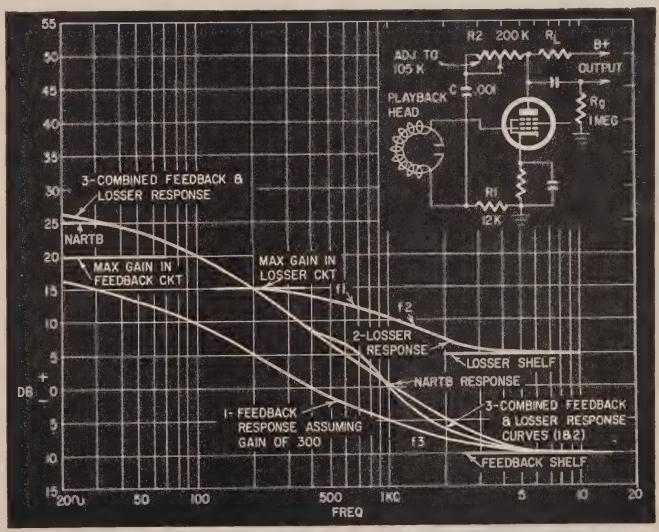

Feedback boost: $f3 = \frac{1}{2\pi R2C} = 1{,}500$ cps; feedback factor, maximum $= 1 + A\beta = 1 + \left(\text{gain} \times \frac{R1}{R1 + R2}\right) = 1 + (300 \times 0.1) = 31 = 30$ db; losser boost: $f1 = \frac{1}{2\pi R_L C} =$ $= 660$ cps; $f2 = \frac{1}{2\pi (R1 + R2)C} = 1{,}350$ cps; insertion loss $= \frac{R1 + R2}{R1 + R2 + R_L} = 10$ db

Fig. 11—Approximation of NARTB bass boost produced by plate-to-grid feedback combined with a losser circuit.

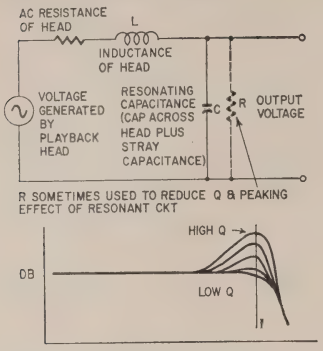

Fig. 12 — Playback treble boost produced by resonating the playback head.

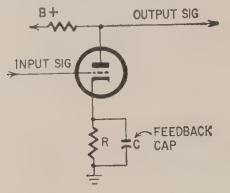

Lower turnover frequency (3 db rise in response $= \frac{1}{2\pi RC}$; treble boost tapers off when voltage across C becomes much smaller than input signal voltage.

Fig. 13—Treble boost through R-C current feedback.

circuit produces a more gradual transition from flat to 6-db-per-octave response at the low end, so bass response suffers a bit. From a practical aspect, however, this deficiency in bass response can be made up by designing for a lower turnover frequency than 50 cycles, say about 30 cycles. If approximately 30 cycles is taken as the design frequency, R2 in Fig. 9 would become about 1 megohm.

You can also get feedback equalization with a single tube, preferably a pentode for sufficient gain. Actually, a losser circuit is combined with the feedback network so that the corresponding curves add up to a characteristic closely approaching NARTB equalization. Fig. 11 is such a circuit. R1, R2 and C constitute the feedback network, with R1 and R2 forming a voltage divider. As frequency declines, the reactance of C becomes equal to R2 and the feedback voltage across R1 begins to decrease, with a resulting increase in gain at the low-frequency end. The feedback curve shown in Fig. 11 has a turnover frequency (f3) of 1,500 cycles. The losser circuit is made up of R1 and R2 in series, R_L and C. It operates in the same manner as Fig. 3, with R_L playing the same role and R1 + R2 in Fig. 11 playing the role of R2 in Fig. 3. The resulting curve has turnover points at 660 (f1) and 1,350 cycles (f2). Adding the feedback and losser curves produces a bass-boost characteristic close enough

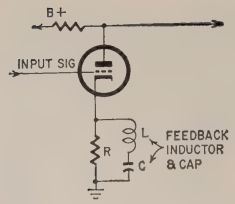

Treble boost reaches maximum when reactance of L = reactance of C; $f = \frac{1}{2\pi\sqrt{LC}}$

Fig. 14 — Treble boost through R-L-C current feedback.

to the NARTB for practical purposes.

The response curve can be adjusted in a number of the playback bass-boost circuits shown. This flexibility permits fairly precise equalization, at the same time allowing for the effects of other factors upon high frequencies. For example, if in playback there are treble losses due to cable capacitance, the upper turnover frequency, 3,180 cycles, can be reduced somewhat. This means that the equalization curve does not drop as much at the high end. Thus, in a specific situation a turnover of 2,000 instead of 3,180 cycles might approximately balance out high frequency losses elsewhere—in the playback amplifier, the head or connecting cable.

Playback treble boost

To correct for treble losses in playback, which are most likely to be caused by the gap of the playback head (the wider the gap, the greater the losses), tape amplifiers frequently provide high-frequency boost, particularly above 8,000 cycles or so.

The shape of the required treble-boost curve depends upon the factors primarily responsible for playback losses. If gap width is the principal factor, losses take place at a rapidly accelerating rate. Therefore a circuit with a sharply rising characteristic is needed. This may be obtained by an R-L-C circuit. Such a circuit can add a very important half-octave to the high-end response.

One way of achieving this effect is to shunt a suitable capacitor across the playback head, as shown in Fig. 12. The playback heads commonly employed in home tape machines typically have an inductance in the range of 0.5 henry. Therefore, capacitors of about 200–400 $\mu\mu$f could be used to resonate the head in the region of 12,000 to 15,000 cycles. The capacitor and the inductance of the head form a tuned circuit. Voltage across the capacitor reaches a maximum approximately at resonance, and output voltage can therefore be appreciably increased, depending upon the Q of the tuned circuit.

Here it may be seen that although capacitance across the playback head (in the form of cable, interwinding or input tube) is usually viewed as a threat to high-frequency response because of its shunting effect, yet *properly controlled capacitance* can produce just the opposite result. If the head and the various capacitances resonate within the audio range, there are losses above resonance. But if resonance occurs slightly beyond the audio range, it can improve response at the upper end of the audio spectrum.

If the peaking effect due to the tuned circuit is too great, try a resistor across the head to reduce the Q of the circuit and thereby reduce the rise in response as shown in Fig. 12. If the recorder has a head with a very narrow gap or operates at high speed, say 15 ips, so that gap losses do not significantly enter the picture, and if there are no treble losses due to other factors, you may have a situation where rising output due to head resonance is undesirable. Then it is necessary to make sure that head resonance occurs well above 20,000 cycles or to use a resistor to reduce the Q of the resonant circuit. While the value of the resistor has to be experimentally determined, it should be in the region of 50,000 ohms.

You can also get treble boost by using current feedback. A moderate amount of boost is obtained, as in Fig. 13, by shunting the cathode resistor with a suitable capacitor. A more sharply rising curve can be obtained by shunting the cathode resistor with an inductor and capacitor in series as in Fig. 14. A sharp rise can also be achieved by repeating the circuit of Fig. 13 in several stages.

If a bass-boost circuit such as that of Fig. 6 or 7 is employed, it can also be used to provide treble boost if resistor R is shunted by a suitable capacitor. Thus in Fig. 6, where R is 200,000 ohms, you could get a rise of 3 db at 15,000 cycles by placing a 50-$\mu\mu$f capacitor across R. END

STEREO PHONO CARTRIDGES

Part III—High-quality higher-priced magnetic cartridges are this month's targets—Audiogersh Stereotwin 200; Fairchild model 232; Grado stereo cartridge; London-Scott type 1000; and the Shure model M3D

By JULIAN D. HIRSCH

SEVERAL new cartridges and pickups have been announced since the previous article in this series was prepared. The units described this month are all relatively high-priced magnetic types.

Shure model M3D

The Shure Professional Dynetic stereo cartridge, model M3D, employs the same moving-magnet principle as the monophonic Dynetic cartridges.

The external appearance of the model M3D is similar to the standard M5D monophonic cartridge. It comes in a black bakelite case with standard ½-inch mounting centers. As with several magnetic stereo cartridges, each channel has separate output terminals so grounds for the two channels can be kept separate.

Frequency response is within 3 db from 20–15,000 cycles. The output voltage per channel is approximately 5 mv at 1,000 cycles. The recommended load impedance is 50,000 ohms and higher load resistances may be used to get a slight increase in high-frequency response.

The stylus is a 0.7-mil diamond, with lateral and vertical compliances of 3×10^{-6} cm/dyne. Recommended tracking force is 3–6 grams. The channel separation is said to be greater than 20 db at 1,000 cycles.

The price of the Shure Stereo Dynetic cartridge is $45.00. Shure has announced a novel plan that protects the consumer against financial loss due to obsolescense of his monophonic pickup. Anyone who now has a monophonic Dynetic cartridge or pickup will be given a trade-in allowance of 75% of its cost toward the purchase of a stereo pickup. The offer is good through Dec. 31, 1959, and covers all Shure Dynetic cartridges and pickups, no matter when they were purchased.

London-Scott type 1000

The London-Scott type 1000 is an integrated pickup design, sold only as a unit. It was developed in England by London Recording Laboratories and is marketed in the US by Hermon Hosmer Scott, Inc.

The London-Scott cartridge is a moving-iron or variable-reluctance type.

(*Continued on page* 88)

Stereo Dynetic model M3D, by Shure.

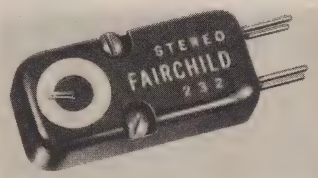

Fairchild model 232.

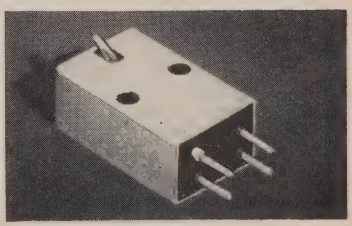

The Grado stereo cartridge is of the moving-coil type.

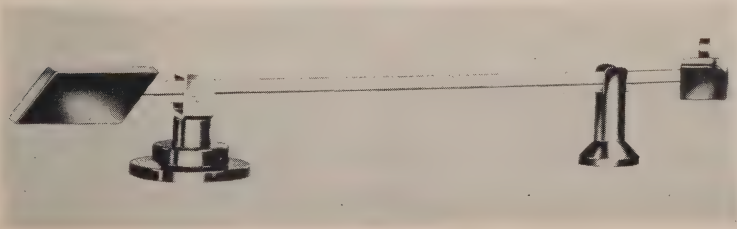

London-Scott type 1000 is a complete arm and cartridge assembly.

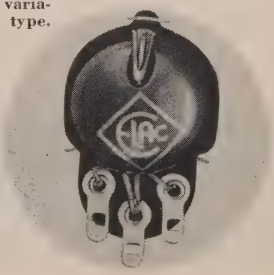

Audiogersh Stereotwin 200 is a variable-reluctance type.

SUPERIOR'S NEW MODEL TW-11

STANDARD PROFESSIONAL TUBE TESTER

★ Tests all tubes, including 4, 5, 6, 7, Octal, Lock-in, Hearing Aid, Thyratron, Miniatures, Sub-miniatures, Novals, Sub-minars, Proximity fuse types, etc.

★ Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TW-11 as any of the pins may be placed in the neutral position when necessary.

★ The Model TW-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.

★ Free-moving built-in roll chart provides complete data for all tubes. All tube listings printed in large easy-to-read type.

★ NOISE TEST: Phono-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.

Model TW-11 — TUBE TESTER . . . Total Price $47.50 — Terms: $11.50 after 10 day trial, then $6.00 per month for 6 months.

EXTRAORDINARY FEATURE

SEPARATE SCALE FOR LOW-CURRENT TUBES. Previously, on emission-type tube testers, it has been standard practice to use one scale for all tubes. As a result, the calibration for low-current types has been restricted to a small portion of the scale. The extra scale used here greatly simplifies testing of low-current types.

The Model TW-11 operates on 105-130 Volt 60 Cycles A.C. Comes housed in a beautiful hand-rubbed oak cabinet complete with portable cover.

$47.50 NET

SUPERIOR'S NEW MODEL TD-55

EMISSION TYPE TUBE TESTER

★ FOR THE EXPERIMENTER or PART-TIME SERVICEMAN, who has delayed purchasing a higher priced Tube Tester.

★ FOR THE PROFESSIONAL SERVICEMAN, who needs an extra Tube Tester for outside calls.

★ FOR THE BUSY TV SERVICE ORGANIZATION, which needs extra Tube Testers for its field men.

Speedy, yet efficient operation is accomplished by: 1. Simplification of all switching and controls.

2. Elimination of old style sockets used for testing obsolete tubes (26, 27, 57, 59, etc.) and providing sockets and circuits for efficiently testing the new Noval and Sub-Minar types.

YOU CAN'T INSERT A TUBE IN WRONG SOCKET
It is impossible to insert the tube in wrong socket when using the new Model TD-55. Separate sockets are used, one for each type of tube base. If the tube fits in the socket it can be tested.

CHECKS FOR SHORTS AND LEAKAGES BETWEEN ALL ELEMENTS
The Model TD-55 provides a super sensitive method of checking for shorts and leakages up to 5 Megohms between any and all of the terminals. Continuity between various sections is individually indicated. This is important, especially in the case of an element terminating at more than one pin. In such cases the element or internal connection often completes a circuit.

"FREE-POINT" ELEMENT SWITCHING SYSTEM
The Model TD-55 incorporates a newly designed element selector switch system which reduces the possibility of obsolescence to an absolute minimum. Any pin may be used as a filament pin and the voltage applied between that pin and any other pin, or even the "top-cap."

ELEMENTAL SWITCHES ARE NUMBERED IN STRICT ACCORDANCE WITH R.M.A. SPECIFICATION
One of the most important improvements, we believe, is the fact that the 4 position fast-action snap switches are all numbered in exact accordance with the standard R.M.A. numbering system. Thus, if the element terminating in pin No. 7 of a tube is under test, button No. 7 is used for that test.

Model TD-55 — TUBE TESTER . . . Total Price $26.95 — Terms: $6.95 after 10 day trial, then $5.00 per month for 4 months.

The Model TD-55 comes complete with operating instructions and charts. Housed in rugged steel cabinet. Use it on the bench—use it for field calls. A streamlined carrying case, included at no extra charge, accommodates the tester and book of instructions.

$26.95 NET

SHIPPED ON APPROVAL
NO MONEY WITH ORDER — NO C.O.D.

Try for 10 days before you buy! If completely satisfied, send down payment after trial and pay balance at indicated monthly rate — NO INTEREST OR FINANCE CHARGES ADDED. If not completely satisfied, return to us, no explanation necessary.

SEE PAGE 87 FOR COMPLETE DETAILS

MOSS ELECTRONIC, INC. 3849 TENTH AVE., NEW YORK 34, N. Y.

SUPERIOR'S NEW MODEL 82

Multi-Socket Type TUBE TESTER

TEST ANY TUBE IN 10 SECONDS FLAT!

(1) Turn the filament selector switch to position specified.

(2) Insert tube into a numbered socket as designated on our chart (over 600 types included).

(3) Press down the quality button —

THAT'S ALL! *Read emission quality direct on bad-good meter scale.*

Model 82 — TUBE TESTER . . . Total Price $36.50 — Terms: $6.50 after 10 day trial, then $6.00 monthly for 5 months.

Primarily, the difference between the conventional tube tester and the multi-socket type is that in the latter, the use of an added number of specific sockets (for example, in Model 82 the noval is duplicated eight times) permits elimination of element switches thus reducing testing time and possibility of incorrect switch readings.

To test any tube, you simply insert it into a numbered socket as designated, turn the filament switch and press down the quality switch—THAT'S ALL! Read quality on meter. Inter-element leakage, if any indicates automatically.

Production of this Model was delayed a full year pending careful study by Superior's engineering staff of this new method of testing tubes. Don't let the low price mislead you! We claim Model 82 will outperform similar looking units which sell for much more — and as proof, we offer to ship it on our examine before you buy policy.

- Tests over 600 tube types.
- Tests OZ4 and other gas-filled tubes.
- Employs new 4" meter with sealed air-damping chamber resulting in accurate vibrationless readings.
- Use of 22 sockets permits testing all popular tube types and prevents possible obsolescence.
- Dual Scale meter permits testing of low current tubes.
- 7 and 9 pin straighteners mounted on panel.
- All sections of multi-element tubes tested simultaneously.
- Ultra-sensitive leakage test circuit will indicate leakage up to 5 megohms.

Model 82 comes complete, housed in portable, hand-rubbed oak cabinet with removable cover. Only **$36.50 NET**

SUPERIOR'S NEW MODEL TV-12

TRANS-CONDUCTANCE TUBE TESTER

Model TV-12—TUBE TESTER . . . Total Price $72.50 — Terms: $22.50 after 10 day trial, then $10.00 monthly for 5 months.

ALSO TESTS TRANSISTORS!

TESTING TUBES

★ Employs improved **TRANS-CONDUCTANCE** circuit. An in-phase signal is impressed on the input section of a tube and the resultant plate current change is measured. This provides the most suitable method of simulating the manner in which tubes actually operate in Radio & TV receivers, amplifiers and other circuits. Amplification factor, plate resistance and cathode emission are all correlated in one meter reading.

★ **NEW LINE VOLTAGE ADJUSTING SYSTEM.** A tapped transformer makes it possible to compensate for line voltage variations to a tolerance of better than 2%.

★ **SAFETY BUTTON** — protects both the tube under test and the instrument meter against damage due to overload or other form of improper switching.

★ **NEWLY DESIGNED FIVE POSITION LEVER SWITCH ASSEMBLY.** Permits application of separate voltages as required for both plate and grid of tube under test, resulting in improved Trans-Conductance circuit.

TESTING TRANSISTORS

A transistor can be safely and adequately tested only under dynamic conditions. The Model TV-12 will test all transistors in that approved manner, and quality is read directly on a special "transistor only" meter scale.

The Model TV-12 will accommodate all transistors including NPN's, PNP's, Photo and Tetrodes, whether made of Germanium or Silicon, either point contact or junction contact types.

Model TV-12 housed in handsome rugged portable cabinet sells for only **$72.50 NET**

SHIPPED ON APPROVAL

NO MONEY WITH ORDER—NO C.O.D.

Try for 10 days before you buy! If completely satisfied, send down payment after trial and pay balance at indicated monthly rate — NO INTEREST OR FINANCE CHARGES ADDED. If not completely satisfied, return to us, no explanation necessary.

SEE PAGE 87 FOR COMPLETE DETAILS

MOSS ELECTRONIC, INC. 3849 TENTH AVE., NEW YORK 34, N. Y.

SUPERIOR'S NEW MODEL 77

VACUUM TUBE VOLTMETER

WITH NEW 6" FULL-VIEW METER

Model 77 — VACUUM TUBE VOLTMETER... Total Price $42.50 — Terms: $12.50 after 10 day trial, then $6.00 monthly for 5 months.

Compare it to any peak-to-peak V. T. V. M. made by any other manufacturer at any price!

- Model 77 completely wired and calibrated with accessories (including probe, test leads and portable carrying case) sells for only $42.50.
- Model 77 employs a sensitive six inch meter. Extra large meter scale enables us to print all calibrations in large easy-to-read type.
- Model 77 uses new improved SICO printed circuitry.
- Model 77 employs a 12AU7 as D.C. amplifier and two 9006's as peak-to-peak voltage rectifiers to assure maximum stability.
- Model 77 uses a selenium-rectified power supply resulting in less heat and thus reducing possibility of damage or value changes of delicate components.
- Model 77 meter is virtually burn-out proof. The sensitive 400 microampere meter is isolated from the measuring circuit by a balanced push-pull amplifier.
- Model 77 uses selected 1% zero temperature coefficient resistors as multipliers. This assures unchanging accurate readings on all ranges.

AS A DC VOLTMETER: The Model 77 is indispensable in Hi-Fi Amplifier servicing and a must for Black and White and color TV Receiver servicing where circuit loading cannot be tolerated.

AS AN AC VOLTMETER: Measures RMS values if sine wave, and peak-to-peak value if complex wave. Pedestal voltages that determine the "black" level in TV receivers are easily read.

AS AN ELECTRONIC OHMMETER: Because of its wide range of measurement leaky capacitors show up glaringly. Because of its sensitivity and low loading, intermittents are easily found, isolated and repaired.

SPECIFICATIONS

• **DC VOLTS** — 0 to 3/15/75/150/300/750/1,500 volts at 11 megohms input resistance. • **AC VOLTS (RMS)** — 0 to 3/15/75/150/300/750/1,500 volts. • **AC VOLTS (Peak to Peak)** — 0 to 8/40/200/400/800/2,000 volts. • **ELECTRONIC OHMMETER** — 0 to 1,000 ohms/10,000 ohms/100,000 ohms/1 megohm/10 megohms/100 megohms/1,000 megohms. • **DECIBELS** —10 db to + 18 db, + 10 db to + 38 db, + 30 db to + 58 db. All based on 0 db = .006 watts (6 mw) into a 500 ohm line (1.73v). • **ZERO CENTER METER** — For discriminator alignment with full scale range of 0 to 1.5/7.5/37.5/75/150/375/750 volts at 11 megohms input resistance.

Model 77 comes complete with operating instructions, probe and test leads. Use it on the bench—use it on calls. A streamlined carrying case, included at no extra charge, accommodates the tester, instruction book, probe and leads. Operates on 110-120 volt 60 cycle. Only .....

$42.50 NET

SUPERIOR'S NEW MODEL 79

The Most Versatile All-Purpose Multi-Range Tester Ever Designed!

SUPER-METER

WITH NEW 6" FULL-VIEW METER

Model 79 — SUPER-METER . . . Total Price $38.50 — Terms: $8.50 after 10 day trial, then $6.00 per month for 5 months.

A Combination **VOLT-OHM MILLIAMMETER.**
Plus **CAPACITY, REACTANCE, INDUCTANCE AND DECIBEL MEASUREMENTS.**
Also Tests **SELENIUM AND SILICON RECTIFIERS, SILICON AND GERMANIUM DIODES**

The Model 79 represents 20 years of continuous experience in the design and production of SUPER-METERS, an exclusive SICO development.

In 1938 Superior Instruments Co. designed its first SUPER-METER, Model 1150. In 1940 it followed with Model 1250 and in succeeding years with others including Models 670 and 670-A. All were basically V.O.M.'s with extra services provided to meet changing requirements.

Now, Model 79, the latest SUPER-METER includes not only every circuit improvement perfected in 20 years of specialization, but in addition includes those services which are "musts" for properly servicing the ever increasing number of new components used in all phases of today's electronic production. For example with the Model 79 SUPER-METER you can measure the quality of selenium and silicon rectifiers and all types of diodes—components which have come into common use only within the past five years, and because this latest SUPER-METER necessarily required extra meter scale, SICO used its new full-view 6-inch meter.

Specifications

D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500.
A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000.
D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes.
RESISTANCE: 0 to 1,000/100,000 Ohms. 0 to 10 Megohms.
CAPACITY: 001 to 1 Mfd. 1 to 50 Mfd.
REACTANCE: 50 to 2,500 Ohms, 2,500 Ohms to 2.5 Megohms.
INDUCTANCE: .15 to 7 Henries, 7 to 7,000 Henries.
DECIBELS: —6 to +18, +14 to +38, +34 to +58.

The following components are all tested for QUALITY at appropriate test potentials. Two separate BAD-GOOD scales on the meter are used for direct readings.

All Electrolytic Condensers from 1 MFD to 1000 MFD.
All Selenium Rectifiers. **All Germanium Diodes.**
All Silicon Rectifiers. **All Silicon Diodes.**

Model 79 comes complete with operating instructions and test leads. Use it on the bench—use it on calls. A streamlined carrying case included at no extra charge accommodates the tester, instruction book and test leads.....Only

$38.50 NET

SHIPPED ON APPROVAL
NO MONEY WITH ORDER—NO C.O.D.

Try for 10 days before you buy! If completely satisfied, send down payment after trial and pay balance at indicated monthly rate — NO INTEREST OR FINANCE CHARGES ADDED. If not completely satisfied, return to us, no explanation necessary.

See following page for complete details

MOSS ELECTRONIC, INC. **3849 TENTH AVE., NEW YORK 34, N. Y.**

SUPERIOR'S NEW MODEL TV-50A

GENOMETER

7 Signal Generators in One!

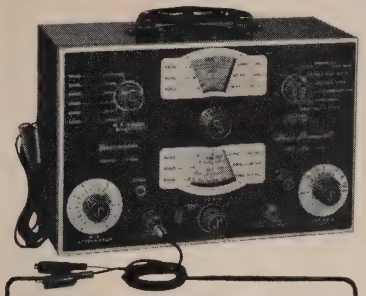

- √ R.F. Signal Generator for A.M.
- √ R.F. Signal Generator for F.M.
- √ Audio Frequency Generator
- √ Bar Generator
- √ Cross Hatch Generator
- √ Color Dot Pattern Generator
- √ Marker Generator

A versatile all-inclusive GENERATOR which provides ALL the outputs for servicing:

A.M. Radio • F.M. Radio • Amplifiers • Black and White TV • Color TV

Model TV-50A GENOMETER . . . Total Price $47.50 — Terms: $11.50 after 10 day trial, then $6.00 monthly for 6 months.

Specifications

R. F. SIGNAL GENERATOR: The Model TV-50A Genometer provides complete coverage for A.M. and F.M. alignment. Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics.

VARIABLE AUDIO FREQUENCY GENERATOR: In addition to a fixed 400 cycle sine-wave audio, the Model TV-50A Genometer provides a variable 300 cycle to 20,000 cycle peaked wave audio signal.

The Model TV-50A comes complete with shielded leads and operating instructions. Only

BAR GENERATOR: The Model TV-50A projects an actual Bar Pattern on any TV Receiver Screen. Pattern will consist of 4 to 16 horizontal bars or 7 to 20 vertical bars.

CROSS HATCH GENERATOR: The Model TV-50A Genometer will project a cross-hatch pattern on any TV picture tube. The pattern will consist of non-shifting, horizontal and vertical lines interlaced to provide a stable cross-hatch effect.

DOT PATTERN GENERATOR (FOR COLOR TV) Although you will be able to use most of your regular standard equipment for servicing Color TV, the one addition which is a "must" is a Dot Pattern Generator. The Dot Pattern projected on any color TV Receiver tube by the Model TV-50A will enable you to adjust for proper color convergence.

MARKER GENERATOR: The Model TV-50A includes all the most frequently needed marker points. The following markers are provided: 189 Kc., 262.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc., (3579 Kc. is the color burst frequency).

$47.50 NET

For the first time ever: ONE TESTER PROVIDES ALL THE SERVICES LISTED BELOW!

SUPERIOR'S NEW MODEL 76

ALL PURPOSE BRIDGE

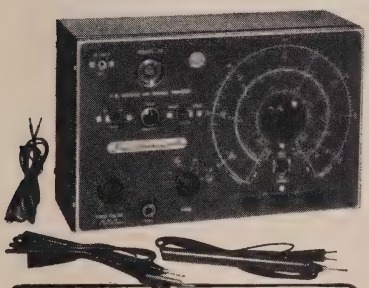

Model 76 . . . Total Price $26.95 — Terms: $6.95 after 10 day trial, then $5.00 monthly for 4 months.

IT'S A

CONDENSER BRIDGE

with a range of .00001 Microfarad to 1000 Microfarads (Measures power factor and leakage too.)

IT'S A

RESISTANCE BRIDGE

with a range of 100 ohms to 5 megohms

IT'S A

SIGNAL TRACER

which will enable you to trace the signal from antenna to speaker of all receivers and to finally pinpoint the exact cause of trouble whether it be a part or circuit defect.

CAPACITY BRIDGE SECTION

4 Ranges: .00001 Microfarad to 1000 Microfarads. Will also locate shorts and leakages up to 20 megohms. Measures the power factor of all condensers from .1 to 1000 Microfarads. (Power factor is the ability of a condenser to retain a charge and thereby filter efficiently.)

SIGNAL TRACER SECTION

With the use of the R.F. and A.F. Probes included with the Model 76, you can make stage gain measurements, locate signal loss in R.F. and Audio stages, localize faulty stages, locate distortion and hum, etc. Provision has been made for use of phones and meter if desired.

IT'S A

TV ANTENNA TESTER

The TV Antenna Tester section is used first to determine if a "break" exists in the TV antenna and if a break does exist the specific point (in feet from set) where it is.

RESISTANCE BRIDGE SECTION

2 Ranges: 100 ohms to 5 megohms. Resistance can be measured without disconnecting capacitor connected across it. (Except, of course, when the R C combination is part of an R C bank.)

TV ANTENNA TESTER SECTION

Loss of sync., snow and instability are only a few of the faults which may be due to a break in the antenna, so why not check the TV antenna first? 2 Ranges: 2' to 200' for 72 ohm coax and 2' to 250' for 300 ohm ribbon.

Model 76 comes complete with all accessories including R.F. and A.F. Probes; Test Leads and operating instructions. Nothing else to buy. Only

$26.95 NET

SHIPPED ON APPROVAL

NO MONEY WITH ORDER — NO C. O. D.

MOSS ELECTRONIC, INC.
Dept. D537 3849 Tenth Ave., New York 34, N.Y.

Please send me the units checked on approval. If completely satisfied I will pay on the terms specified with no interest or finance charges added. Otherwise, I will return after a 10 day trial positively cancelling all further obligation.

Name .....

Address .....

City ..... Zone..... State.....

All prices net, F.O.B., N. Y. C.

- ☐ Model TW-11 ..... Total Price $47.50
  $11.50 within 10 days. Balance $6.00 monthly for 6 months.
- ☐ Model TD-55 ..... Total Price $26.95
  $6.95 within 10 days. Balance $5.00 monthly for 4 months.
- ☐ Model 82 ..... Total Price $36.50
  $6.50 within 10 days. Balance $6.00 monthly for 5 months.
- ☐ Model TV-12 ..... Total Price $72.50
  $22.50 within 10 days. Balance $10.00 monthly for 5 months.
- ☐ Model 77 ..... Total Price $42.50
  $12.50 within 10 days. Balance $6.00 monthly for 5 months.
- ☐ Model 79 ..... Total Price $38.50
  $8.50 within 10 days. Balance $6.00 monthly for 5 months.
- ☐ Model TV-50A ..... Total Price $47.50
  $11.50 within 10 days. Balance $6.00 monthly for 6 months.
- ☐ Model 76 ..... Total Price $26.95
  $6.95 within 10 days. Balance $5.00 monthly for 4 months.

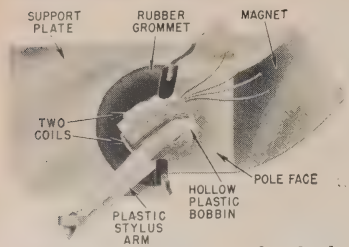

Fig. 1—Coil assembly in the Grado stereo cartridge.

(*Continued from page* 83)

The moving mass is exceptionally low, less than 1 milligram, which is conducive to wide frequency response and low record wear. The compliance is 3.5×10^{-6} cm/dyne. Frequency response is rated at 20–20,000 cycles, within 2 db.

The cartridge is fully shielded for low hum pickup. Its output per channel is 4 mv at a stylus velocity of 5 cm/sec. When both channels are paralleled for lateral response, the output is 3 mv.

The cartridge comes with a 0.5-mil diamond stylus. The recommended tracking force is 3.5 grams. Coil impedance is 4,000 ohms per channel at 400 cycles, and the recommended load resistance is 47,000 ohms. Channel separation is stated as better than 20 db.

The arm which forms an integral part of the London-Scott pickup has an overall length of 12.5 inches. Its height is adjustable from 1⅜ to 2½ inches. The arm pivots on frictionless roller bearings.

The price of the London-Scott type 1000 pickup is $89.95.

Audiogersh Stereotwin 200

The Audiogersh Stereotwin 200 is a variable-reluctance cartridge, housed in a rather unusual-looking cylindrical case which mounts on standard centers.

Frequency response of the Stereotwin 200 is within 2 db from 30 to 18,500 cycles. Its output voltage at 1,000 cycles is 25 mv for a stylus velocity of 10 cm/sec—relatively high for a magnetic cartridge.

The stylus is a 0.7-mil diamond, with a compliance of 4×10^{-6} cm/dyne. Recommended tracking force is 4–6 grams. Channel separation is better than 20 db.

Like other variable-reluctance cartridges, the Stereotwin 200 is rugged and immune to damage from ordinary handling. The stylus assembly is easily replaced by sliding out the stylus and the protective sheath which surrounds it and inserting the replacement.

The recommended load resistance is 37,000 ohms. The Stereotwin 200 has a negligible external magnetic field and will not exert any measurable pull on a steel turntable. The audiophile net price is $59.50.

Fairchild model 232

The Fairchild model 232 is a production version of the XP-4 stereo cartridge. It uses the same type of dual rotating-coil construction as the XP-4, (see RADIO ELECTRONICS, July, 1958, page 28) and has somewhat greater output.

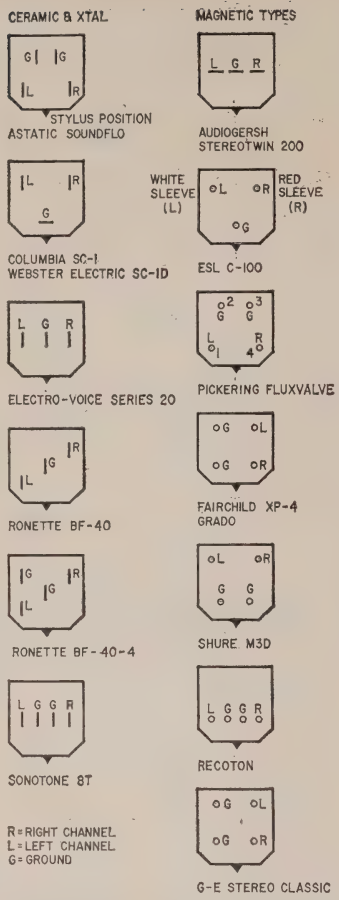

Fig. 2—These are some of the terminal arrangements you will run into on the stereo cartridges described in this series. Some of the markings shown actually appear on the cartridge, others don't.

The model 232 has standard ½- to 7/16-inch mounting centers and fits any standard arm. Its terminals are arranged so it can be plugged into the Fairchild 282 arm.

Rated frequency response of the model 232 is 10–20,000 cycles. Its output is 5 mv per channel for a 7-cm/sec stylus velocity. Like the XP-4, the model 232 has a 0.6-mil diamond stylus. The cartridge weighs 12 grams.

Both vertical and lateral compliance are 6×10^{-6} cm/dyne. Channel separation is rated as better than 25 db. The two channels are brought out to four terminals with complete electrical separation. Coil impedance is 600 ohms per channel. The price is $49.50.

Grado stereo cartridge

The Grado stereo cartridge is a moving-coil type, featuring very low moving mass and high compliance.

The coils are wound at right angles to each other on a hollow plastic cube about 1/16 inch on a side. Attached to this bobbin is a plastic stylus arm with the diamond stylus at its other end. The coil structure is mounted in the hole of a tiny rubber grommet, with the coils at a 45° angle to the record surface. The grommet in turn is mounted in a support plate which positions the coils in the gap of a powerful magnet (see Fig. 1).

The coil-and-magnet arrangement acts in the same way as the system Fairchild uses. Movement of the stylus in one channel produces an output only from the coil corresponding to that channel. It rotates like a d'Arsonval coil between the pole pieces, producing an output. At the same time, the coil for the other channel is rotating on its axis, does not cut any lines of force and therefore delivers no output.

Frequency response of the Grado cartridge is stated as 10–35,000 cycles. Its output is 5 mv per channel at a stylus velocity of 10 cm/sec. It weighs 16 grams.

Like the monophonic Grado cartridge, the stereo model has a very low moving mass and high compliance. The mass of the moving system referred to the stylus is 1 milligram, and the compliance is 8×10^{-6} cm/dyne. Because of the symmetrical mounting system, compliance is the same in any plane. Recommended tracking force is 2 grams.

Coil impedance is 600 ohms per channel, essentially resistive. The terminating resistance is not critical and may be any value over 5,000 ohms.

Grado Laboratories states that channel separation is greater than 25 db, and points out that the limitation is in the cutter heads used in making the stereo records. In other words, channel separation in the test records used to measure cartridge performance is not as good as the cartridge's inherent performance.

The coils in the Grado cartridge are electrically separate and are brought out to four terminals at its rear. The cartridge has standard mounting centers and may be installed in any standard arm.

For use with low-gain preamps, a stereo transformer to step up cartridge output voltage is available. The frequency response of the transformer is 10–30,000 cycles ±1 db. Channel output balance is ±0.2 db. Channel separation is 50 db and the hum level is −90 db. Distortion is said to be unmeasurable with a 40-mv input.

The Grado stereo cartridge is priced at $49.50 and the transformer costs $23.50.

Terminal configurations

Since monophonic cartridges have only two terminals, which are usually not polarized, there has been a certain degree of standardization among manufacturers as to contact spacing and dis-

Simply by checking all the tubes in the TV set with **B&K DYNA-QUIK**

YOU CAN INCREASE YOUR INCOME

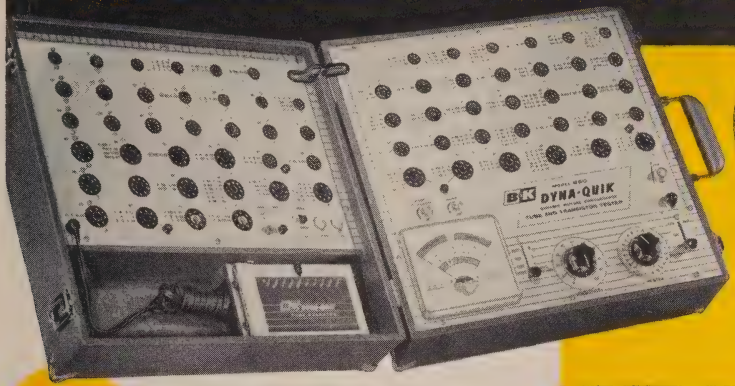

$50* PER WEEK

*ACTUAL EXPERIENCE SHOWS TV SERVICEMEN AVERAGE

2 extra tube sales per call
5 calls per day in
5 days equal $50.00

NEW MODEL 650

Fastest, Most Complete, Portable
DYNAMIC MUTUAL CONDUCTANCE TUBE & TRANSISTOR TESTER

Checks over 99% of the tubes most widely used in television receivers, plus popular home and portable radio tubes. Tests over 500 tube types. Lists over 125 tube types, with settings, on socket panels for maximum operating speed. Complete listing in fast telephone-index type selector. Includes 16 spare sockets and sufficient filament voltages for future new tube types. **Tests each section of multiple tubes separately** for Gm—Shorts—Grid Emission—Gas Content—and Life. Provides instantaneous Heater Continuity check. Shows tube condition on "Good-Bad" scale and in micromhos. Special bridge assures automatic line compensation. No multiple switching—No roll chart. Includes pin straighteners. **Transistor Tester** checks junction, point contact and barrier transistors, germanium and silicon diodes, selenium and silicon rectifiers. Net, **$169.95**

- *Each Dyna-Quik Tube Tester completely tests each tube in seconds*
- *Eliminates substitution testing*
- *Shows customer true condition and life expectancy of tubes*
- *Sells more tubes right on-the-spot*
- *Cuts servicing time, wins customer confidence*
- *Saves costly call-backs, brings more profit*

FAST AND ACCURATE
Quickly Pays for Itself

NEW MODEL 500B *Money-Making Portable*
DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER

Thousands of the famous B&K Dyna-Quik are in profitable use today by service technicians everywhere. **Servicemen say:** *"Best tube tester I've ever owned for speed and dependability." "Makes money. Really indispensable." "Have two...one for the shop and one for house calls."*

Now, with more tube sockets, the new Model 500B makes it easy to test more tubes faster and make more money. Accurately quick-checks most of the TV and radio tubes usually encountered in everyday service work. **Tests tubes** for shorts, grid emission, gas content, and leakage. Measures true dynamic mutual conductance with laboratory accuracy in the home or shop. Makes complete tube test in seconds, tests average TV set in a few minutes. Quickly detects weak or inoperative tubes. Shows tube condition on "Good-Bad" scale and in micromhos. Life Test shows customer the tube life expectancy. Makes it easy to **sell more tubes** right-on-the-spot.

One switch tests everything. No multiple switching. No roll chart. Automatic line voltage compensation. 7-pin and 9-pin straighteners. New tube reference charts are made available by the factory at regular intervals. Net, **$129.95**

See your B & K Distributor, or write for Bulletin **AP12-E**

B&K

B&K MANUFACTURING CO.
3726 N. Southport Ave., Chicago 13, Illinois
Canada: Atlas Radio Corp., 50 Wingold, Toronto 10, Ont.
Export: Empire Exporters, 458 Broadway, New York 13, U.S.A.

tance of terminals from the mounting centers. Practically all cartridges have their terminals side by side in a horizontal plane. This has made it possible for at least one arm design (the Fairchild 280/281) to accommodate practically any magnetic cartridge and many ceramic types without any soldered connections. Nevertheless, there are wide differences between makes in such matters as terminal lead diameter, cross-section and length.

The situation is much more complicated with stereo cartridges. Here we have the possibility of either three- or four-terminal outputs, with a requirement for definite polarity (to identify the left and right channels).

These three or four terminals may be arranged in a variety of ways across the rear of the cartridge body. An examination of the various cartridges described in this series reveals several terminal configurations (see Fig. 2). In a few cases there appear to be similar terminal arrangements for two groups of cartridges, but as a general rule the ceramic types have thin, flat-lug terminals with very close spacing (less than ⅛ inch). On the other hand, magnetic cartridges usually have cylindrical wire terminals with relatively wide spacing in the order of 5/16 inch.

Of course, the same differences have always existed to some extent between monophonic cartridges, and it probably does not impose too great a hardship on the user to solder wires to clips which are pushed onto the cartridge terminals, wherever they may be located.

In stereo cartridges the possibility of error in connecting four clips in a small space is obviously much greater, and the desirability of a standardized terminal layout increases. Practically all stereo arms are designed so contact clips can be soldered to the ends of the lead wires and fitted to the cartridge terminals. So far, the only evidence of an attempt at standardization is the Fairchild model 282 stereo/monaural arm. This is designed along the same lines as the Fairchild 280 series of arms, with contact springs which make a solderless connection to the pins of any Fairchild stereo or monophonic cartridge. The Grado stereo cartridge appears to have the same terminal configuration and should also be usable in this arm.

Considering the many years required for the development of monophonic cartridges it is not too surprising to find that there is diversity of terminal shapes and dimensions. However, virtually all stereo cartridge development has taken place within the last year, and much more work will be done in years to come. In view of this, the standardization of stereo terminal configurations should be seriously considered in the near future, before too many types become widely used. In the meantime, the least that should be done is to mark each cartridge with the left and right channel designations near the corresponding terminals. END

new DISCS and TAPES

STEREO and MONO

Reviewed by
Chester Santon
Station WQXR
New York City

AT THE time of writing (September 1958), I am looking forward to the New York High Fidelity Music Show to clarify one phase of stereo's progress on discs. That is the performance of stereo cartridges released on that occasion. We'll know considerably more about the stereo medium when stereo versions of today's most highly refined monophonic pickups are unveiled and demonstrated at the show. In recent days, I have been sampling a prototype of a forthcoming stereo cartridge of ambitious design. With lower stylus pressure, reduced stylus mass and greater overall compliance, records played with earlier cartridges revealed less surface noise and better definition of sound. Once incorporated into production models, specifications formerly considered luxuries in monaural cartridges may well become everyday necessities in stereo. In the meantime, tape producers are not neglecting the luxury stereo market.

Stereo Mosaic
Stereo Age Recordings
(7-inch; playing time 12 min.)

This 600-foot sampler tape is available free of charge with the purchase, of any $12.50 Stereo Age tape. A. Stewart Hegeman, whose loudspeaker was described in the September issue of RADIO-ELECTRONICS, was the recording engineer for six of the first seven releases represented on this sample reel. Only the very finest sound systems will reveal how far above average is the sound on these tapes. Fabulous presence and completely natural, wide-open response in the categories of solo voice, solo harp and solo piano. The jazz sample is also outstanding. If these releases do not surpass virtually all other tapes on your present rig, audition a better system with this sampler tape.

TCHAIKOVSKY: *Piano Concerto No. 1*
Van Cliburn, Pianist, and Orchestra conducted by Kiril Kondrashin
RCA Victor Stereo Tape ECS-187
(7-inch; playing time, 35 min. $14.95)

When a release assumes international importance, it deserves the best in sound. Stereo tape rises wonderfully to the occasion. In this eagerly awaited tape, emphasis quite naturally has been placed on the Cliburn piano in plotting out the pickup. Superior in sound to previous RCA piano concerto tapes, the range, depth and presence of the instrument as heard here surpass the LP version. In comparison, the piano's great moments sound tame on records.

Songs From Great Films
Herman Clebanoff and His Strings
Mercury Stereo Tape MDS 2-35
(7-inch; playing time, 36 min. $12.95)

This is the first Mercury tape I've heard with their new "sonic signal" between selections to aid cuing at fast wind or rewind speed. This beep was meant to be low enough in pitch to be inaudible at the 7.5-ips playing speed. To my pleased amazement, the tone overlaps the low-end response of my system at a shade above normal playback level. Many tape fans who discover this tone may favor its retention by Mercury. I can think of no easier check on a system's bass response. Excellent violin ensemble work topped with high, soft-tinkling percussion.

Dancing and Dreaming
Jay Norman Quintet
Concertapes (Stereo) 24-2
(7-inch; playing time, 32 min. $11.95)

Piano, vibes, guitar, drums and bass heard in vivid, completely straightforward sound. No tricks but simply the best that can be done with today's equipment to keep alive old favorites such as *Time on My Hands, Easy to Love*, etc. Worthy of the very best sound systems.

Music for Non-Thinkers
Guckenheimer Sour Kraut Band
RCA Victor Stereo Tape CPS-133
(7-inch; playing time, 27 min. $10.95)

While fracturing music for small German bands, the Guckenheimers toss our way some of the most technically alert sound in the Victor tape library. Response is as broad as the humor.

Top Percussion
Tito Puente
RCA Victor Stereo Tape APS-120
(7-inch; playing time, 16 min. $6.95)

Pandemonium by Tito Puente, the outstanding exponent of Latin percussion. With five wildly earnest colleagues at the assisting drums, Puente presides at the timbales (Cuban drums played with sticks). On a good system, he delivers wavefronts considerably steeper than those found on most drum recordings. Widely separated stereo expedites the delivery.

DVORAK: *Violin Concerto*
Nathan Milstein, violinist
William Steinberg conducting Pittsburgh Symphony Orchestra
Capitol Stereo Tape ZF-26
(7-inch; playing time, 29 min. $14.95)

From any standpoint, this is the best-sounding stereo tape recording of a violin concerto available at moment of review. No other tape in the catalog has the combination found here, the warm, rich tone contributed by Milstein and the flawless engineering and processing provided by Capitol. The solo violin goes out to the top of its range without a trace of peak anywhere. Unlike the Pittsburgh tape of the Beethoven Seventh Symphony, the orchestra is heard in relatively close pickup. Its colorful comments in the course of the concerto surround the soloist in completely natural stereo. If you have room for only one violin concerto in your tape collection, get this one.

STRAVINSKY: *Song of the Nightingale*
Fritz Reiner conducting Chicago Symphony Orchestra
RCA Victor Stereo Tape CCS-97
(7-inch; playing time, 22 min. $10.95)

In this fairy tale set to music, the Chicago Orchestra is heard in one of its better demonstration tapes to date. So minimal is the tape hiss, a new extension of dynamic range is possible here without marring the low-level passages. The flecks of ultra wide-range tonal color, in stereo, are easily spotted throughout the orchestra is Fritz Reiner depicts an Oriental setting with his customary attention to detail.

RAVEL: *Bolero and Ma Mère L'oye*
CHABRIER: *Bourrée Fantasque*
Paul Paray Conducting Detroit Symphony Orchestra
Mercury Stereo Record SR-90005

Mercury has tackled the *Bolero* in its first stereo disc release. The gain in technical yardage is a significant one. Although stereo records do not match the dynamics and aural impact now on tapes, distortion here is held to an impressive low. The added value of stereo puts this item ahead of the monaural disc version recorded some time ago. Effective stereo in the *Mother Goose* and *Bourrée*.

BARTOK: *Concerto for Orchestra*
Fritz Reiner Conducting Chicago Symphony Orchestra
RCA Victor Stereo Record LSC-1934

I have noticed that RCA's stereo pressings tend to vary according to cartridge output, coming over very well on a 25-mv magnetic job feeding RCA's favorite speaker in two enclosures. Under those circumstances, the comparatively flat response on the record rejuvenates this long-popular version of Bartok's challenging score.

BEETHOVEN: *Symphony No. 7 in A Minor*
Guido Cantelli Conducting Philharmonia Orchestra
Angel Stereo Record S-35620

Its second batch of stereo releases finds Angel still cautious in the dynamic range used on their records. Distortion is lower than that on a companion release (*Tchaikovsky Symphony No. 4*, S-35565). Apparently Beethoven's clearer tonal texture is easier to record at this juncture than Tchaikovsky's uninhibited sonorities. To sample Angel's best current sound, try the new monaural Rossini overtures led by Markevitch (35548) and the Berlioz album (35431).

Overtures in Hi-Fi
Albert Wolff Conducting Paris Conservatoire Orchestra
London Stereo Record CS-6015

London continues to set the pace in classical stereo discs. This record is the cleanest-sounding of their latest releases. Close-range stereo recording as practiced here offers fresh insight into dramatic effects used in these familiar overtures to three French and three German comic operas. A must for audiophiles familiar with Wolff's monaural *Overture* record of a few years ago (London FFRR LL-1157).

Gerry Mulligan Songbook, Vol. 1
Gerry Mulligan and Sax Section
World Pacific Stereo Record 1001

Is proximity to Westrex a factor explaining the exceptional cleanness of West Coast stereo discs? I've noticed that feature in other California products. This World Pacific jazz release ranks with the very best. Mulligan's imagination is converted to sound by carefully chosen personnel. Transparent texture of the stereo sound is particularly noticeable in the sweet "tsing" of drummer Dave Bailey's wire brushes. Don't miss this one.

Sea of Dreams
Nelson Riddle and His Orchestra
Capitol Stereo Record ST-915

The sweetest massed violin sound I've heard so far on stereo discs, stemming in part from the nature of the tunes used. With lower strings used to deepen the already excellent perspective, these warm arrangments by Nelson Riddle should sell stereo to persons unmoved by classical music in two-channel sound.

United States Air Force
Narrated by Arthur Godfrey
Vox Stereo Record ST-PL 10.520

Recorded at the Air Proving Ground Command, Eglin Air Force Base, the main attraction in the stereo disc version of this documentary is still the sonic boom. That is the sound created by an F-100 jet passing the sound barrier about 50 feet above the Astatic 988 dynamic mikes used in the recording. Strictly for the air-minded.

Breaking the Sound Barrier, Vol. 1
Paul Price Conducting American Percussion Society
Urania Stereo Record USD-1007

Already widely known in monaural disc and stereo tape versions, this percussion extravaganza arrives with quiet surfaces on this stereo record. This permits good volume levels when testing stereo cartridges. The Edgar Varese *Ionisation*, a famous test item in the early '50's enters upon a new career, separating this time the compliant from the reluctant in stereo pickups.

Sounds . . . Out of This World
Stereo Balance/Test/Demonstration disc
Omega OSD-1

This stereo test record arrived too late for full evaluation in this column. I'll report next month on its behavior under several cartridges. In the frequency response test, the two channels start at opposite ends of the spectrum and are said to contain, with no cross-modulation, 30 to 15,000 cycles. Cross-talk is stated to be 45 db.

COPLAND: *Billy the Kid*
Rodeo
Morton Gould and His Orchestra
RCA Victor Stereo Record LSC-2195

Room acoustics as heard on this disc deserve fresh examination in the light of stereo. New York's Manhattan Center, scene of this recording, is RCA Victor's most reverberant hall. In monaural days, a distant mike placement there lent a valuable illusion of depth. Now, on a space-revealing stereo record, the reverberation is excessive. There is greater range of dynamics on the monaural disc (LM-2195).

The King and I
Motion Picture Sound Track
Capitol Stereo Record SW-740

The latest appearance of this familiar Rodgers and Hammerstein score as heard in the movie. A single-track best seller now offered in the finest sound-stage acoustics I've heard so far on stereo disc.

VIVALDI: *The Four Seasons*
Antonio Janigro conducting I Soloist di Zagreb
Vanguard Stereolab Record BGS-5001

Vanguard, in company with many other firms, is getting better results on stereo discs with material that makes small demand on the medium. Slightly inferior technically to the monaural version, this splendid performance of Vivaldi's music offers adequate stereo realism.

MENDELSSOHN: *Quartet in E Flat*
GLINKA: *Quartet in F*
Westwood String Quartet
Stereo Records S-7006

First recordings of quartets uncovered by the Society for Forgotten Music. The monaural version (SFM-1001) has a dry, too-close sound. On stereo disc, that effect is gone yet the four strands of music are easier to follow. Excellent signal-to-noise ratio.

Note: Records below are 12-inch LP and play back with RIAA curve unless otherwise indicated.

BERLIOZ: *Symphonie Fantastique*
Ataulfo Argenta conducting Paris Conservatoire Orchestra
London FFRR LL-3016

Seldom before has the wild imagination of Hector Berlioz been translated into such recorded sound. The fourth movement, *March to the Scaffold*, punctuated by blood-curdling percussion, gives way to a seething caldron of sound in the last movement. Greater miking distance than that in *The Rite of Spring* above sharpens the bite in the sound. Very clean at the top level of the best systems.

MENDELSSOHN: *A Midsummer Night's Dream*
SCHUBERT: *Rosamunde*
George Szell conducting Concertgebouw Orchestra
Epic LC-3433

Is there today an active conductor more fortunate than George Szell? An audiophile of some years standing, his recording assignments for Epic take him to two of the more exhilarating halls in use today, Severance Hall in Cleveland and the Concertgebouw Hall in Amsterdam. Conductor, orchestra and hall are in rare form in this exceptional disc.

Beauty and the Brute Force
Dot Evans and Brute Force Steelband of Antigua
Cook 1049

The oil-drum steelbands of the West Indies were brought into prominence by Cook Labs some years ago. Here they are given a new lease on popularity with the addition of the lazy, torchy voice of Dot Evans. An unlikely combination proves to be a likable one.

Josef Hofmann plays Chopin
Rondo 1002

In the year 1888, pianist Josef Hofmann, at the age of 12, was the first name artist to engrave a wax record for Thomas Edison. Although his career was legendary, he made very few records. These three Chopin works, transferred from player-piano rolls, have far better sound than the only other Hofmann record in general circulation, Columbia KL-4929. Dynamics indicated in later years by the performer have been recently added electronically, restoring the dynamic range unobtainable on piano rolls. Each phrase was processed on tape run at half-speed. On a broadcast VU meter, the performance now behaves like a modern record, peaking zero from —20 db with total freedom.

MAHLER: *Symphony No. 2 in C Minor*
Bruno Walter Conducting New York Philharmonic and Westminster Choir
Columbia M2L-256

The recording sessions devoted to this gigantic work were interrupted for a year by the illness of Bruno Walter. Recording director David Oppenheim, drawing upon his years of work in Carnegie Hall, has matched the various takes with unfailing skill. Here's the first recording with string lows rich enough to give meaning to this dark-hued symphony. Anticipating the very low noise level on the finished disc, gain was properly left low in the quiet choral passages. Breathtaking effect on a pair of truly flat speaker systems.

BARTOK: *Concerto for Violin*
Issac Stern, Violinist
Leonard Bernstein conducting New York Philharmonic
Columbia ML-5283

The finest recording of this music currently available. The transparent, ultra-clean recording reveals the true bite in Bartok's orchestration. Stern's great performance forces one to forget that this concerto is supposed to be difficult to follow.

The ABC's of Hi-Fi
Cook 5022

Some audio old wives' tales are disposed of and a few new ones are started in this salty two-record discourse by Emory Cook on the acquisition and practice of high fidelity. A few opinions expressed are already going out of date at the end of August. The practical tips on handling records and tapes have durable value and the aural illustrations are very helpful. Sure to stimulate many happy hours of argument in the months ahead.

Sylvia Zaremba Plays Brahms
Unicorn UNLP-1058

A major Brahms solo piano work, *The Variations and Fugue on a Theme of Handel*, and three Brahms rhapsodies are played with seasoned style in Miss Zaremba's first recording. Recording engineer Peter Bartok and the fine acoustics of New York's Town Hall give us an outstanding concert-hall piano sound.

Sound Ideas
Les and Larry Elgart Orchestra
Columbia CL-1123

The Elgarts' keen interest in top-notch sound pays off handsomely at the loudspeaker with popular music of durable appeal. Try their latest arrangements when experimenting for maximum monaural depth from two speakers.

GRIEG: *Piano Concerto in A Minor*
RACHMANINOFF: *Rhapsody on a Theme of Paganini*
Phillipe Entremont, Pianist
Eugene Ormandy conducting Philadelphia Orchestra
Columbia ML-5282

Your ear will inform you to keep an eye on this rising young French pianist (Columbia's answer to Van Cliburn?) Stunningly captured is the uniquely confident tonal production of an already seasoned artist. Very highly recommended. END

Name and address of any manufacturer of records mentioned in this column may be obtained by writing Records, RADIO-ELECTRONICS, *154 West 14 St., New York 11, N.Y.*

READY FOR STEREO?

Part II—Add a second channel to your monophonic system in easy steps

By DONALD C. HOEFLER

GETTING ready for stereo should be a logical building-block process, at a rate determined by the availability of components and funds. For, while the effect of stereo on the hearer is revolutionary, the equipment which produces it is not.

This means that you have to throw away very little, if any, of your present system. Some pieces must be modified and you must add some equipment for the second channel. But converting to stereo is a process of building up, not tearing down.

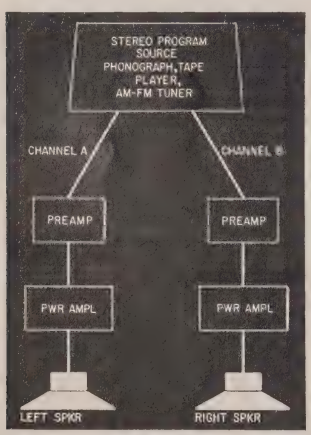

Fig. 1 — Fundamental stereo arrangement. Converting existing equipment involves modifying the source components and adding a second audio channel.

The basic elements of any two-channel stereo system are shown in Fig. 1.

This arrangement differs from conventional monophonic systems on two fundamental points. First, the *program source* is *stereo*. Second, an additional channel has been introduced.

Each component in the stereo system will be taken up in turn in this series, beginning with stereo phonos next month. But for those thinking about buying equipment now, here are a few general suggestions.

Sources and equipment

Even if you don't want to go into stereo right now, any new phono pickup you buy should be a stereo unit. Remember, that stereo discs cannot be played with monophonic cartridges without damaging the record severely. On the other hand, both sides of a stereo cartridge can be paralleled to reproduce both types of discs, through a monophonic system. As soon as you have a stereo cartridge you can begin building your library of stereo records, playing them monophonically until your stereo system is complete.

Stereo tapes aren't damaged when played on a monophonic machine, but only one track is heard and the sound is rather anemic. However, you can temporarily parallel the outputs of a stereo machine into a single channel for monophonic reproduction. An existing tape recorder can easily be modified for stereo. This will be described in a future article. But if you don't already have tape equipment and are intending to buy some, by all means go stereo.

If you plan to purchase new tape apparatus, you must decide on the ultimate form of your own setup, to adapt to your own equipment and available stereo tape facilities. These range from the stereo tape deck—simply a bare transport mechanism equipped with stereo heads, but without tape preamps or amplifiers—to the complete stereo tape system, including dual power amplifiers and speakers.

In between are systems which include equalized tape preamps. These must be coupled to external power amplifiers. This is the best arrangement for those who already have a hi-fi system.

When it comes to stereo tuners, there are only two things to remember. If separate AM and FM tuners are not used, the AM–FM tuner must be able to receive and detect AM and FM *simultaneously*, so both channels of the AM–FM stereocast can be reproduced. Further, the FM tuner should provide for the future addition of a multiplex adapter, as this single-carrier type of stereocast is destined to be important.

A step on the path

While rearranging your source devices takes you a few steps closer to

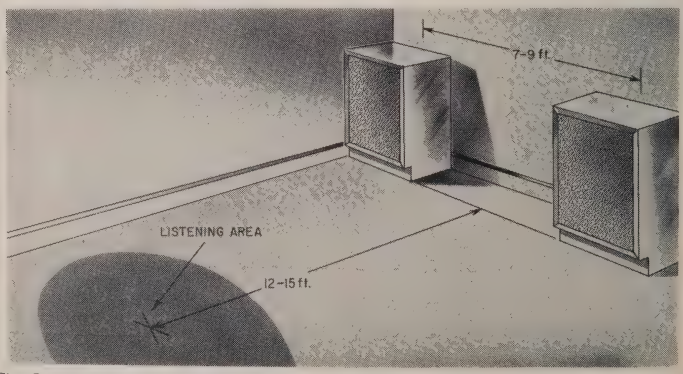

Fig. 2—Recommended relation between speakers and listener for 2-channel stereo. This may also be used for spread sound.

The data that launched thousands of careers is yours FREE

TELLS how you can be successful in ELECTRONICS . . . including:

Television . . . Broadcasting . . . Guided Missiles . . . Radar . . . Instrumentation . . . Computers . . . Automation . . . Astronautics . . . Servomechanisms . . . Aeronautical Electronics . . . Telemetering . . . Communications . . . Manufacturing

Send for your Free Copy today!

This is a brand new edition of the book which has launched thousands of men on good-paying careers in radio-TV-electronics.

It brings you completely up to date—answers important questions on newest career developments in Electronic Engineering Technology including Servomechanisms; Computers; Radar; Automation; Aeronautical Electronics; Broadcasting; Communications and Manufacturing, and the Electronic Principles Associated with Guided Missiles, Telemetering, Astronautics, and Instrumentation.

This book, "Your Future in the New World of Electronics," also shows you how CREI Home Study leads the way to greater earnings in the booming electronics world.

However, CREI does not promise you a "snap." With accredited technical school curricula such as CREI offers, you must study to convert your ambition into technical knowledge which you can sell in the fabulous field of Electronics.

Since its founding in 1927, CREI has provided thousands of professional electronics men with technical educations. During World War II, CREI trained thousands for the Armed Services. Leading firms recommend CREI training for their own personnel. Among them: United Air Lines, Canadian Broadcasting Corporation, Trans-Canada Airlines, Douglas Aircraft Co., The Martin Co., Columbia Broadcasting System, All-American Cables and Radio, Inc., Gates Radio Co., Canadair, Ltd., Federal Electric Corp., and U. S. Information Agency (Voice of America).

CREI courses are prepared by recognized experts, in a practical, easily understood manner, and constantly revised to meet the new electronic challenges of our time. You get the benefit of time-tested study assignments under the personal supervision of a CREI staff instructor. Your studies are accomplished on your own time, during hours selected by you, and controlled by your own will power. This complete training is the reason that graduates find their CREI diplomas keys to success in even the most advanced of electronic applications. CREI alumni hold top positions in America's leading firms.

At your service is the CREI Placement Bureau, which helps to find positions for advanced students, and graduates, although CREI does not guarantee jobs. Now is the time of decision for you. Luck will not propel you forward unless it finds you trained. Contacts won't budge you an inch unless you have the skill to back them up. The answer is: Technical Training . . . and willingness to learn. Together they will bring you increased earnings in the new Age of Electronics. Fill out the post card below *completely* and mail it now to Capitol Radio Engineering Institute, 3224 16th St. N.W., Washington 10, D.C. We'll promptly send you your free copy of "Your Future in the New World of Electronics." The rest—your future—is up to you!

CREI ALSO OFFERS RESIDENCE TRAINING in Washington, D. C. at the same high technical level. Day and evening classes start at regular intervals. Qualified residence school graduates earn degree, "Associate in Applied Science." Check coupon if you prefer residence study.

VETERANS: If eligible for training under the new G.I. Bill of Rights, check the coupon for full information.

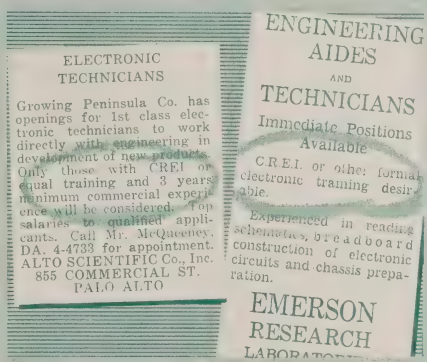

ELECTRONIC TECHNICIANS

Growing Peninsula Co. has openings for 1st class electronic technicians to work directly with engineering in development of new products. Only those with CREI or equal training and 3 years minimum commercial experience will be considered. Top salaries to qualified applicants. Call Mr. McQueeney, DA. 4-4733 for appointment.
ALTO SCIENTIFIC Co., Inc.
855 COMMERCIAL ST.
PALO ALTO

ENGINEERING AIDES AND TECHNICIANS

Immediate Positions Available

C.R.E.I. or other formal electronic training desirable.

Experienced in reading schematics, breadboard construction of electronic circuits and chassis preparation.

EMERSON RESEARCH
LABORATO...

INDUSTRY CALLS FOR CREI TRAINING BY NAME . . . . . SO SHOULD YOU!

Here you see actual help wanted ads—one from a San Francisco newspaper, another seen in Washington. They are just two of many which specify "CREI or equal" education. This shows that industry approves CREI training, even insists on it. Experience has taught many, many companies that CREI students are taught what industry needs and wants them to know. Let this be your cue when you choose your educational program.

FREE BOOKLET! MAIL THIS POSTAGE-FREE POST CARD TODAY

CAPITOL RADIO ENGINEERING INSTITUTE
ECPD Accredited Technical Institute Curricula • Founded 1927

3224 16th St., N.W., Washington 10, D. C.

(R.E. Nov. 58) B_2E_2

Please send me your course outline and FREE illustrated Booklet "Your Future in the New World of Electronics" . . . describing opportunities and CREI home study courses in Practical Electronic Engineering Technology.

CHECK FIELD OF GREATEST INTEREST
- ☐ Radar, Servo and Computer Engineering Technology
- ☐ Electronic Engineering Technology
- ☐ Broadcast (AM, FM, TV) Engineering Technology
- ☐ Television Engineering Technology
- ☐ Aeronautical Electronic Engineering Technology

Name.....Age.....

Street.....

City.....Zone.....State.....

Check: ☐ Home Study ☐ Residence School ☐ Korean Veteran

If you have had electronic education, or experience in electronics—and realize the need of a high-level technical knowledge to make good in the better electronic jobs—you can qualify for CREI home study training. (Electronics experience is not required for admission to CREI Residence School.) Please fill in the following information.

Employed By.....

Type of Present Work.....

.....

Education:
Yrs. High School.....
Yrs. College.....
Electronics Experience.....

.....

Train for a secure career —not just another job!

Success ahead for trained men only in

Electronics

including Guided Missiles . . . Radar . . . Instrumentation . . . Computers . . . Automation . . . Astronautics . . . Servomechanisms . . . Aeronautical Electronics . . . Telemetering . . . Television . . . Manufacturing . . . Communications . . . Broadcasting

Stop Dreaming! Start Planning!

START YOUR CREI CAREER TRAINING AT HOME TO INSURE MORE INCOME!

What would a $10 or $20 a week raise mean to you? Only one $10-a-week raise will repay your investment in CREI training, and leave you a substantial profit the very first year! Your increases in pay thereafter are all pure profit, and you'll be prepared for many more promotions and pay raises in the future years of your life!

WHAT YOU DO NOW—today, tomorrow, next week—will decide your success in the electronics field. Every day counts because the *well-trained* technicians are the ones who get the "plums" when promotions are handed out. How can you be sure to step ahead of competition, to earn more money, to get the position that carries more responsibility—and the pay that goes with it? The answer is contained in a CREI booklet called "Your Future in the New World of Electronics."

ERA OF ELECTRONICS

This is the era of guided missiles, automation, astronautics, instrumentation. This is the era of defense orders and a manufacturing industry which last year alone sold billions of dollars worth of electronic equipment, which will top ten billion dollars (without military) this year. This is the era of electronic development, research, design, production, testing, inspection, manufacture, broadcasting, telecasting and servicing. This is the era of electronic careers—well-paid, interesting, and secure.

PRACTICAL COURSES

Your work is under the supervision of a regular staff instructor who knows and teaches what industry needs. Training is accomplished on your own time, during hours chosen by you.

KEY TO SUCCESS—As a graduate you'll find your CREI diploma the key to success in the entire field of electronics. At your service is the CREI Placement Bureau which helps to find positions for advanced students and graduates. No short cuts are promised; no jobs are guaranteed—but requests for CREI-trained personnel come in regularly.

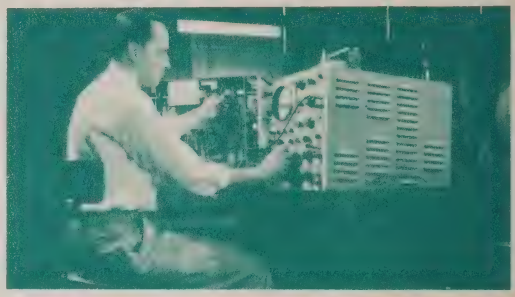

COLLEGE DEGREE NOT ESSENTIAL—This is *professional* training, not for beginners, but you don't have to be a college graduate to benefit from CREI's famed courses. You *do* have to be willing to study at home. You can do it while holding down a full-time job. Thousands have. If you have had *some* electronics experience, CREI has a course for you.

CREI's professional guidance is recognized all over the world. Since 1927 CREI has trained practical electronic engineers and engineering technicians; you find them in radio and television stations; you find them in electronics planning and manufacture; you find them everywhere and, generally, near the top. Leading firms recommend CREI training for their own personnel (among them are United Air Lines, Canadian Broadcasting Corp., Douglas Aircraft Co., The Martin Co., and All-American Cables & Radio, Inc.).

1st Class
Permit No. 288-R
Washington, D. C.

BUSINESS REPLY CARD
No Postage Stamp Necessary If Mailed in the United States

Postage Will Be Paid By
CAPITOL RADIO ENGINEERING INSTITUTE
3224 16th Street, N.W.
Washington 10, D. C.

THIS CAN BE YOUR BIG YEAR!

Write today for this FREE BOOKLET. Tuition is reasonable, terms are easy, information is free. Fill out the postage-paid reply card completely, and mail today to Capitol Radio Engineering Institute, 3224 16th St., N.W., Washington 10, D. C.

Available to Veterans Under GI Bill!

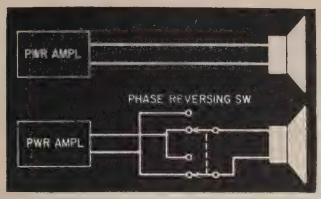

Fig. 3—A dpdt phase-reversing switch in one channel makes it easy to phase speakers properly.

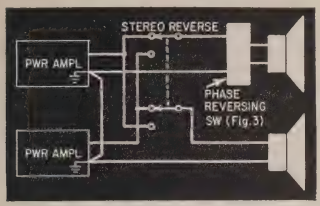

Fig. 4—A stereo reverse switch lets you reverse channels when necessary, without changing speaker leads around.

total stereo, the effect on your ears at this point has not changed. Lest you lose patience and get discouraged in midstream, there is one step on the way to stereo which has immediate and tangible results. Add the second speaker!

Two speakers, connected to a single amplifier and properly placed in the same room, provide a spread-sound effect which for most types of music is definitely superior to the point-source single speaker. Of course, it's not stereo. Preferably, the two speakers should be identical, as should all components in the two stereo channels. Otherwise the proper acoustic balance is more difficult to get and the effect on the ear can be fatiguing.

The speaker arrangement depends on room acoustics, listening level and personal taste. The general arrangement of Fig. 2 provides a good starting point, assuming an average listening distance of 12 to 15 feet. This puts the ideal listener position at the apex of a triangle whose sides form an angle of 30° to 40°. In a monophonic setup these factors are not highly critical, but you might as well start with them, experimenting with spread sound while building the balance of the stereo system.

Connecting the additional speaker to the single amplifier is simple. Connect the two speakers in parallel across the secondary of the output transformer, but remember you have cut the impedance in half.

Each speaker's output will be less than before for a given volume setting, but the combination's total output will remain about the same.

Two speakers working in a confined area must be in phase. That is, both cones must move forward at the same instant, and must also move back together. This is one place where "push-pull" is no good. In a monophonic spread-sound setup, the speakers are phased once when installed, and that's that. But when you get into stereo, the phase relationships between channels may vary with the sources, particularly on FM–AM stereo broadcasts, and a phasing switch will become a necessity.

This is simply a double-pole double-throw switch, connected as in Fig. 3. One switch is used as you have to swing only one of the channels into phase with the other. The switch may be connected anywhere in the chain, but if you are installing your own the best place is probably at the amplifier's output.

Phase cancellation is most noticeable in the bass region, so the correct setting of the phasing switch can be easily determined by ear, once your stereo system is operating. Simply adjust the system for equal loudness from each speaker, then stand at a spot about midway between them and flip the switch back and forth a few times. The correct position gives full bass, while the out-of-phase condition presents a very thin sound.

Having a second speaker and stereo program sources, all that remains is to add a second amplifying channel to complete the arrangement of Fig. 1. Existing equipment should be duplicated if possible, but any second amplifier will work in a pinch.

There is also the possibility of the channel-A part of the program appearing out of the right speaker, instead of the left where it belongs. This can be controlled with a stereo reverse switch, a two-pole double-throw arrangement shown in Fig. 4. The reverse switch actually swaps channels between left and right.

Even with these switches in place, the basic arrangement of Fig. 1 leaves something to be desired. One important factor is the volume setting. It takes some experimenting to get the correct balance between the two channels, and this is almost impossible to maintain if separate volume controls in each amplifier must be adjusted each time the level is set. A much better arrangement is a ganged control (like that found on many stereo preamps), which works equally on both channels.

Such a control is included in the stereo adapter described in RADIO-ELECTRONICS, July, 1958, page 36. This completely passive unit is connected between the preamps and the power amplifiers.

A dual 500,000-ohm potentiometer acts as the volume or loudness control for both channels—the loudness function is switched in. The selector switch includes a stereo reverse position and combines outputs from the stereo pickup when playing monophonic records. It also permits playing any other monophonic source from either channel through both amplifiers simultaneously. All these modes of operation can be handled through haywire connections or by slinging a lot of patch cords around, but a stereo adapter can save a lot of time and trouble.

Next month we'll see how you can modify monophonic phono equipment to play stereo discs. TO BE CONTINUED

LEARN BASIC ELECTRICITY *FIRST!*

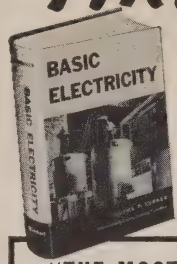

NEW! ***Complete electrical "know how" (including Basic Electronics) in one big, easily understood home-study book***

"THE MOST IMPORTANT TRAINING OF ALL"

A well-known leader in electronics says: "No radio-TV men ever knew too much Basic Electricity—and a lot of them only think they know it. A solid background in these so-called fundamentals IS THE MOST IMPORTANT TRAINING THEY'LL EVER GET!"

Learn basic electricity NOW! Learn it thoroughly! Then everything else in electronics, radio, TV, communications, hi-fi, etc. comes 10 times as easy—*because all of these developments are based on the same fundamental electrical principles.*

That's why this new, 396-page BASIC ELECTRICITY book brings you the most important training of all. For the beginner, it is as necessary as oars to rowing a boat. For more experienced amateurs, experimenters and servicemen, it paves the way to a clearer understanding of almost any problem, circuit, component, or piece of equipment.

GOODBYE TO GUESSWORK

In short, BASIC ELECTRICITY'S down to earth treatment of fundamental subjects can quickly clear up misunderstandings and matters that may be puzzling you. From basic circuits and currents to electromagnetism . . . from capacitance to resistance . . . from polyphase systems to 'phone principles . . . from instruments to testing . . . from tubes to transistors, it explains things *from the beginning.* Motors, generators, batteries, rectifiers and subjects such as polyphase and power factor—often neglected by ordinary books—are fully and clearly taught.

More than 300 pictures make subjects doubly clear. Use FREE EXAMINATION coupon today. You be the judge!

10-DAY FREE EXAMINATION

Dept. RE-118, RINEHART & CO., INC.
232 Madison Ave., New York 16, N.Y.

Send 396-page BASIC ELECTRICITY home training manual for 10-day FREE EXAMINATION. If I like book, I will then send $6.50 (plus postage) promptly in full payment. If not, I will return book in 10 days and owe nothing. **(SAVE! Send $6.50 with order and we pay postage. Same 10-day return privilege with money refunded.)**

Name.....

Address.....

City, Zone, State.....

OUTSIDE U.S.A.—$7.00 cash. Money back if you return book in 10 days.

Low-Cost TRANSISTOR HEARING AID

A 4-stage amplifier with a gain of 1,000 forms the heart of this tiny aid for the hard of hearing

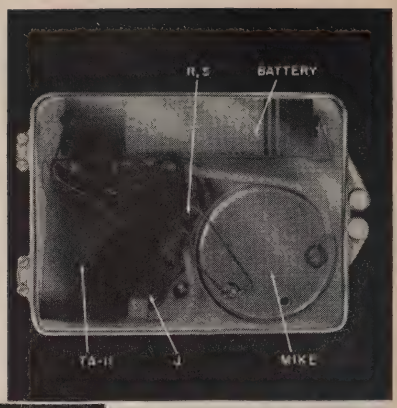

Despite its small size, there is no cramming in the case.

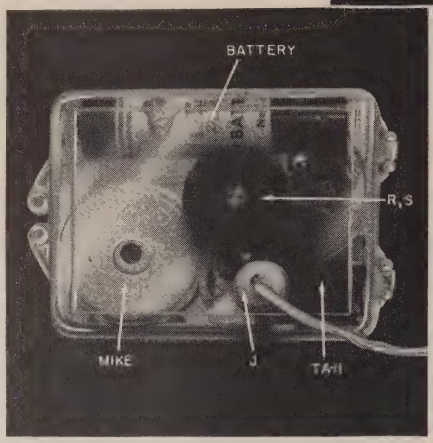

A look at the front side of the midget unit.

By FORREST H. FRANTZ, SR.

EVERY day large numbers of hard-of-hearing people in the United States purchase new transistor hearing aids to replace the older, bulkier, battery-hungry vacuum-tube variety. These people already own a headphone with a custom ear mold. Many others would purchase new hearing aids if the cost were not so high. And, of course, there are many potential hearing-aid buyers who have never purchased one.

Up to now, most hearing aids that have been described in the literature have been gadgets which illustrated an application for transistors. As practical hearing aids, they have been unattractive and bulky. From a business standpoint, the labor required to build one of these was prohibitive. The relatively new Centralab printed-circuit TA-11 four-stage transistor amplifier changes the picture. Now the service technician and electronic hobbyist are in a position to enter the profitable hearing-aid business with a unit that is attractive in size, appearance and cost. At the same time he can enjoy the satisfaction of performing a valuable service for his fellow-men.

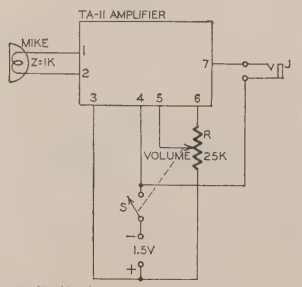

R—pot. 25,000 ohms, with spst switch S (Centralab B16-217)
S—spst on R
TA-11, transistor amplifier (Centralab)
Earpiece, 2,000 ohms (Lafayette MS-368 or equivalent)
Battery, 1.5 volts penlight or mercury
Microphone, 1,000 ohms (Shure MC-11 or equivalent)
Case, 1¾ x 2¼ x ½ inches
Miscellaneous hardware

Circuit of the finished transistor hearing aid.

Let's take a look at the hearing-aid business aspects. One general-merchandise mail-order house sells four-transistor hearing aids for prices ranging from about $100 to $135 without the earphone. The custom-brand hearing aids sold through dealers cost more. The hearing aid described in this article requires less than $40 worth of parts and can be built in 30 minutes to 2 hours, depending on the packaging arrangement you resort to and the quantity in which you produce them. You can easily meet competition and still enjoy a good profit.

The hearing aid shown here was built into a plastic case 1¾ x 2¼ x ½ inches—about the size of a book of matches. These cases are available in most hobby shops. I left the plastic clear for illustrative purposes. A unit you intend to sell can be made more attractive by spraying the inside of the case with enamel.

The amplifier connections are shown in the diagram. The numbers on the TA-11 in the diagram correspond to the numbers on the actual unit. I soldered the leads to the battery, but a unit to be marketed should have spring clips or a battery holder for easy battery replacement. Ray-O-Vac 400, RCA VSO 74 or Burgess No. 7 penlight cells may be used. You might wish to give some consideration to using a longer-life mercury cell. The penlight cells are attractive because they can be purchased almost anywhere.

Another suggested change for a commercial unit is locating the earphone jack on the side of the unit rather than on the front, to avoid pocket bulge. Since most anticipated sales will be to persons who already have earphones, you'll want to use an output jack to fit the plug on the user's earphone. For some, you'll need a small bracket to mount the jack.

I used a hot ice pick to cut the large hole for the volume control and a 3/32-inch drill for all other holes. The phone-jack and microphone openings were enlarged with a taper reamer. This reduces the risk of cracking the plastic. The microphone is cemented to the front of the plastic case. END

The Most Advanced TV ANTENNAS in the World!

TRIO®

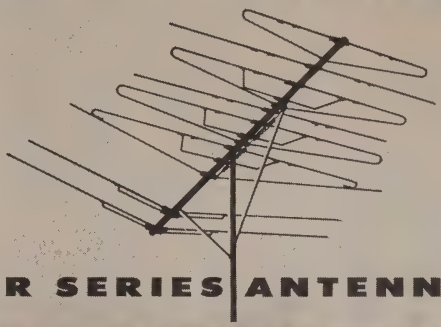

ZEPHYR AND COLOR SERIES ANTENNAS

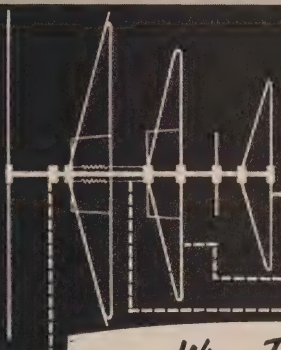

Look for these 4 Great Features in 1959

Wing Dipole

Today's most powerful dipole! Contains three active elements on the highs—forward Vee to the low band section—plus integrated director.

Wing Director

Today's most powerful director! A composite director designed to obtain results from the powerful Wing Dipole.

no-strip lead-in connector

Requires no stripping, no soldering, or wire holders—holds the complete insulated wire.

dyna-coil phasing

Increased performance from uniform transmission of signal strength of each active dipole in a multi-dipole system—AND MAKES POSSIBLE COMPLETE FACTORY ASSEMBLY.

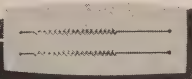

Choose from . . . TRIO'S COMPLETE LINE

COLOR ROYAL—The ultimate in color television reception—or black and white.
ZEPHYR ROYAL—Extraordinary power and sensitivity.
ZEPHYR PIONEER—For extreme distance.
COLORITE—For color and black and white in areas formerly using conicals.

Sharpshooters, Conicals and Yagis

Patents: U.S. 2772413—Canada 541670

Copyright 1958, Trio Mfg. Co.

TRIO® Manufacturing Company GRIGGSVILLE, ILL.

The TV Man Rides The GRAVY TRAIN

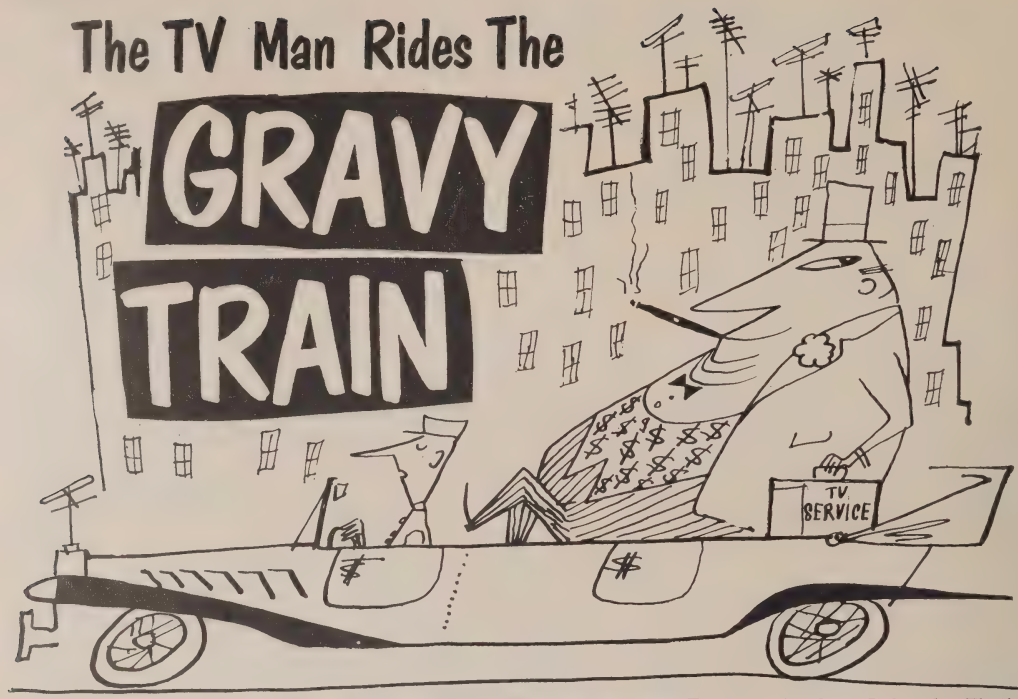

By E. H. LEFTWICH

We would have been more than a bit dubious about this article, had we not remembered Mr. Leftwich as that old-time service technician and author who wrote the famous article "Watch Out, Mr. Serviceman, or the Set-Owner Will Gyp You," in the April, 1942, issue of RADIO-CRAFT: The practices he describes can hardly be called typical, but may be widespread enough to indicate that the night-crawler and cut-rater are not the only ones who are giving the honest TV technician a black eye.

BECAUSE I'm an old-time ex-radio technician and knew very little about TV, in the past I was smart enough to lay off my 21-inch Magnavox combination (hi fi and TV) and call in some local TV man when I had trouble. I sometimes felt that I was getting rather high repair bills, but succeeded in keeping my big mouth shut—until this time. I felt that "live and let live" was a good rule to follow, and I was actually glad to see the TV man riding the gravy train, his ancestor (the radio man) having come up by the starvation route.

But when I read the headline, "Prices Too Low," in *Technicians' News* in RADIO-ELECTRONICS some months ago, my grids went positive and I shorted the bias on my output tubes! In this article, Mr. Russell Hansen of RCA Service Co. stated that the prices charged by TV repair firms were too low and that the gross income from a shop should total 2½ times payroll expenses.

On first thought, I felt that such a figure would jack up prices still more than they already are—and I was "all shook up." I now realize that this markup is quite reasonable. I only wish that the shops I dealt with had been satisfied with such a fair profit! The true experience which follows will show just what kind of a gravy train the TV men are riding in this area—at more than *twice* the figure Mr. Hansen recommended!

Regardless of what my TV trouble has been, the bill was always $24, plus or minus a dollar or so. The extent of such troubles was a couple of tubular capacitors in one case, two tubes in another; and finally an oscillator coil and a couple of tubes. Now, I'm sure there are many honest dependable TV men in this area and elsewhere. It's unfortunate that I've had only the other kind do my work.

For example, the last time my TV conked out, I noticed that the plate of the horizontal amplifier tube (6BQ6-GTB) was running red hot. By wiggling the adjustment screw on the horizontal oscillator coil, I was able to clear the short intermittently and the picture would come back in sync on the picture tube. All tubes had checked OK on my tube tester. Having read about an electrocution in RADIO-ELECTRONICS and horrified by the thought of "harmful X-rays" emanating from the 1B3 tube (reference *RCA Tube Handbook*, 1957), I was more "chicken" than ever. Because I knew right where the trouble was, I decided to let an experienced TV man take *his* chances with the high voltage and the X-rays. It should take only a few minutes to clear the short, I thought. That's what I *thought!*

Having had past experiences with fantastic charges, I never called the same TV man twice, everlastingly living in the hope that I would eventually find a reliable and reasonable technician. So, I looked in the Yellow Pages of the phone book.

"Trustworthy TV" sounded good, and had the biggest ad in the section! Trustworthy promised to send a man out right away and warned me that there would be a $5 charge for the service call. Nothing, I thought, could be more reasonable than that. Again, that's what I thought!

In a couple of hours, a neatly uniformed young fellow drove up in a sedan. He looked "trustworthy." I explained the trouble, which he verified. I also told him that the tubes were okay. He started to make out his bill.

"Just a minute," I said. "There's no need for you to take the set to your shop. I'll help you carry the chassis to my bench in the garage. I have a vtvm. You can clear up the short in a couple of minutes. I'll still have time to see the Alfred Hitchcock show."

He laughed as he continued to make out his bill. "Sorry," he said, "but we don't operate that way. I don't repair sets at all, except to replace tubes. I just diagnose the case and turn in a report. Tomorrow they'll send out and pick up your set."

"But look, bud," I protested, "it'll take only 15 minutes to do the job. Why not do it now and get it over with?"

But he shook his head and tore off

my copy of the bill (diagnosis, that is). "Look, mister," he said; "I wish all my customers were like you. It would make the job easy. We'll pick up your set and take it in to the shop, put in a new oscillator coil, and tune it up."

I examined the "preliminary" bill. On it, in addition to the $5 service charge, was the diagnosis, "Replace Hor. Osc. Coil and tune up." "How much will the whole job run?" I asked apprehensively.

"It will be $14 to take the set in and bring it back, plus the cost of the coil—about $1.75."

"Does the $14 include the $5 service call?"

"Yes, it does," he said.

Oh, well, I figured, having shot five bucks on the service call, I might as well shoot another $9. "Okay," I said, "I'll help you shack the chassis to your car."

This time, he laughed out loud. "Sorry, mister," he said, "I don't pick up sets, I just——"

"I know," I interrupted, "you just replace tubes and diagnose the case."

Before he left, I gave the TV man a cold Pepsi for the road, and we became quite congenial. He confided that he made about 25 service calls per day (six days per week) and told me that I should take a part-time job in his shop. "But I know nothing about TV," I argued, "I'm just an ex-radio-man."

"You found the trouble with this one," he said, "and TV's are easier to fix than radios—you've got a built-in scope."

I couldn't argue with that—the built-in scope, that is. Next morning at nine, I called Trustworthy and spoke to the service manager. After some 15 minutes, he located my ticket and said he'd get the pickup men out that night. Three nights later, a couple of husky country lads (the kind they had before the war) arrived in a station wagon. They looked like they were fresh from the hills. They came into the house. They took one look at the TV combination (as large as an upright piano and almost as heavy) and groaned. They started to lift the cabinet.

"Hold on," I protested. "Don't take the whole thing in, just the chassis—it's loose in the cabinet." Their jaws dropped and they stared at me.

"But, mister," one said, "We only pick up cabinets and all. We don't know nothin' about no chassis. We'd be afeared we'd break somethin'."

At this point, I could have been forced to admit that I had become a trifle impatient with the entire deal. Last time transfer men had moved "cabinet and all" they'd broken three legs (of the cabinet). "Either you take only the chassis," I said, "or you don't take anything."

They took the chassis, handling it as though it were a bushel basket of eggs.

One week later

After repeated hassles with the service manager (on the phone), I finally got Trustworthy to return the chassis. Meantime, I was a bit fretful, having missed a week of my favorite TV programs.

This time a different man appeared. He was alone, in a small sedan. I had to help him carry the chassis into the house and get it into the cabinet. The set worked, but the picture was out of focus just enough to be annoying to watch. "How about tuning it up a little?" I asked.

"Sorry," he said, "But I only deliver sets and turn 'em on. I'll turn in a report and there will be a man out to tune it up."

With these familiar words, he threw his bill in my face. Sure enough, there was the $14 pickup and delivery charge, plus $5 for the first service call, plus $2.75 for the coil, and plus $2.60 for two tubes—as usual, a total of $24.35! I, who had trusted Trustworthy, was disillusioned. I squawked. I explained that the $5 service call was to be included in the $14 pickup charge, and added that I didn't need any tubes.

"Don't blame me, mister," the man said, "I only deliver sets. They make out the bills at the office."

"I know," I said wearily, "But just for the sake of my own morbid curiosity, suppose you had to deliver a big chassis to a little old crippled lady who lived out in the country. And suppose, because of a forest, you couldn't drive in closer than half a mile from the house. What would you do then?"

His eyes bulged out and his jaw slackened, while he hung his head. "I just don't know, mister," he admitted.

Well anyhow, I thought, I'll get to see the weekly rerun of *The Honeymooners* tonight, even though the picture distortion makes me bug-eyed. That was something else I *thought!*

I paid the man and watched him, fascinated, while he jerked the line cord from the chassis. "Hey, wait!" I yelled. "What's the idea?"

"Why, that's *my* cord, mister. It's

Receipts		Day	Year
6 service diagnosticans, avg. 15 calls each per day	90 calls @ $5	$ 450	
2 crews, pickup & delivery, avg. 15 jobs each per day (includes labor charge)	30 jobs @ $14	420	
Avg. parts & tube sales per day	30 jobs @ $10	300	
Daily total		$1,170	
$1,170 per day, 6-day week, total $7,020 × 50 weeks			$351,000
Additional tubes & parts sold in shop $185 × 50 weeks			9,250
Total yearly receipts			**$360,250**

Expenses		Week	Year
Salaries			
6 service diagnosticians	@ $100 week	$ 600	
3 shop technicians	@ 100 week	300	
1 service manager	@ 130 week	130	
1 clerk-typist	@ 60 week	60	
4 pickup & delivery men	@ 40 week	160	
Weekly Payroll		$1,250	$62,500
Executive's (owner's) salary, pro-rated			6,000
Total yearly salaries			**$68,500**

Operating Expenses—Yearly	
Merchandise cost	$ 13,500
Mileage, depreciation, insurance, operating costs, 8 cars	39,600
Depreciation, shop & office equipment	2,000
Rent (pro-rated for 1/3 total store area)	3,600
Utilities	900
Insurance	600
Advertising (Yellow Pages, phone book, principally)	1,300
Office supplies	300
F.I.C.A. (social security)	1,185
Workman's compensation	1,107
Bookkeeping service	1,200
Attorney—retainer fees	500
Miscellaneous expenses	5,000
	$ 70,792
Plus yearly salaries	68,500
Total yearly expenses	**$139,292**
Gross receipts	**$360,250**
Less total expenses	139,292
	$220,958
Less California State Income Tax	11,758
Net Profit before Federal Income Tax	**$209,200**

NOTE: Gross receipts of $360,250 are more than 5.2 times payroll expense of $68,500.

the one I have to try out sets with—when I deliver them."

"Then, where's *my* cord?"

"I don't know. It should have been fastened to the back."

It appeared, then, that the pickup men had taken my cord when they took the chassis, and that the delivery man would not leave his cord. This was the last straw! I threw on my jacket, fired up the Chev and took off for the home office of Trustworthy TV.

The Sales Department was large and impressive—so was the shop. On the wall, prominently displayed, was a bronze plaque which read "Member—Better Business Bureau." This forestalled any ideas I may have had about reporting Trustworthy as a gyp outfit. After a wait of 30 minutes, I got in to see the general manager. I introduced myself, shook hands and explained that I was an electronics engineering writer and ex-radio service technician. I reviewed the entire deal, complaining bitterly about the $5 overcharge, the poor performance of the set and the loss of the cord without which I could not operate the set after waiting for a week to get it back.

The manager seemed concerned, but not enough to refund the $5 overcharge, which, he explained, resulted from an error on the part of the technician. He was generous enough, however, to give me a brand-new cheater cord. Then, using master sales techniques, he launched into a hard-luck story that was calculated to bring tears to my eyes—and almost did. He wailed and moaned about "overhead," emphasizing the point that it cost $4 to make a $5 service call and that if his service department would only just *break even*, he would be a happy man. He added that he was truly sorry that the TV was out of alignment and that he would send a man out right away to tune it up at "no charge." If it took several more trips to accomplish the tuneup, there would still be no further charge.

As I left, I patted his shoulder consolingly. Poor guy, I thought, what a burden he has to bear. That was two months ago, and Trustworthy has yet to send the man out to tune up my TV. Meantime, being free from the hypnotic influence of the manager's super salesmanship, I have done a bit of figuring. In the estimated figures for Trustworthy's business (see chart page 99) I feel I have been quite conservative. I have piled on the expenses as much as I could. I have discounted the diagnostician's statement that he averaged 25 calls per day, which in an 8-hour day would allow only 20 minutes per call. I have allowed 15 calls per day. Of course, the TV service business is seasonal, but since this was in the summer, I presume the year-round average would be better rather than worse than my figures would show.

"Okay," you may very well say, "so there is a net profit of $209,200 before Federal income tax—and *after* income tax, what does the owner have?" I'll tell you. This business is a "proprietorship" owned by one man. He would, therefore, pay income tax on his individual income, which is that of the shop. Figuring none except business deductions (total expenses), Uncle's cut would be $142,828 and so our store owner would *take home* a mere $66,372.

Although my estimated figures have been checked by two accountants and one business administrator, and have been judged "realistic," there may still be some who might question them. I want to please everyone, so for the benefit of doubters, let's cut the profits in half and come out with only $104,600 net profit before Federal income tax. On this amount, Uncle's cut would be $57,090, and the shop owner's "take-home pay" would be $47,510.

Definitely, this isn't hay! No, I never did call Trustworthy back on the tuneup job. Frankly, I don't trust Trustworthy and I wouldn't let them touch my TV with a 60-foot antenna mast. For self-preservation (and until I can find a fair TV man) I have done some studying, and am now repairing my own TV—no one else's, just my own.

TV repair charges too low? Maybe, in some areas—but *not* in mine! END

PENTRON STEREO

HIGH FIDELITY TAPE RECORDERS

professional performance at popular prices

NOW YOU CAN RECORD STEREO, TOO!

Pentron's totally new TM-4 Stereo Tape Deck is the ideal addition to your custom high fidelity system: records and plays stereo . . . 4-track as well as 2-track tape, records and plays monaural and has all the exclusive Pentron stereo features which assure you matchless performance of a professional quality never before possible at popular prices.

Pentron tape mechanisms are precision engineered with full-range frequency response, Azmur-X head azimuth adjustment, single Finger-Flite rotary control, easy dual-speed control lever, four outputs plus two AC convenience outlets, self-energized braking, stereo or monaural erase, designed to operate at any mounting angle.

The Pentron TM-4 is priced at $109.95 net and is available at professional high fidelity showrooms. For detailed information on Pentron high fidelity tape recorders, amplifiers, pre-amps, mike mixers, tape decks, and stereo conversion kits, write Dept. R-11 or see your yellow pages.

SEE THE NEW PENTRON EMPEROR II....

THE ONLY COMPLETE POPULAR-PRICED STEREO RECORDING SYSTEM

PENTRON CORPORATION 777 South Tripp Avenue, Chicago 24, Illinois

CANADA: Atlas Radio Ltd., Toronto EXPORT: Raytheon Manufacturing Company, Waltham, Massachusetts

SUBSTITUTE PARTS WITH-OUT SOLDERING

Quickly Easily with

NEW E-Z-Hook "SUB" Connectors

Has 1001 Uses!

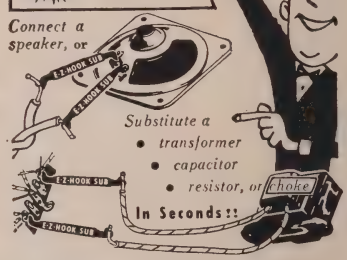

★ Makes connections instantly!
★ Won't pull off!
★ Insures positive contact!

Saves time, money and parts in servicing, experimenting, instructing and production.

E-Z-HOOK SUB

No. 71-1....SUB.....Only 69¢ ea.

Six Colors!-for Easy Lead-Identification

ORDER THROUGH YOUR PARTS DISTRIBUTOR

E-Z-HOOK TEST PRODUCTS SAFE • FAST • SURE

E-Z-HOOK TEST PRODUCTS
Dept. G-3, 1536 Woodburn Ave.
Covington, Ky.

Canadian Rep: Len Finkler & Co., Toronto, Ont.

Use Delco Radio Service Parts!

DS501—Highest power transistor used in auto radios.

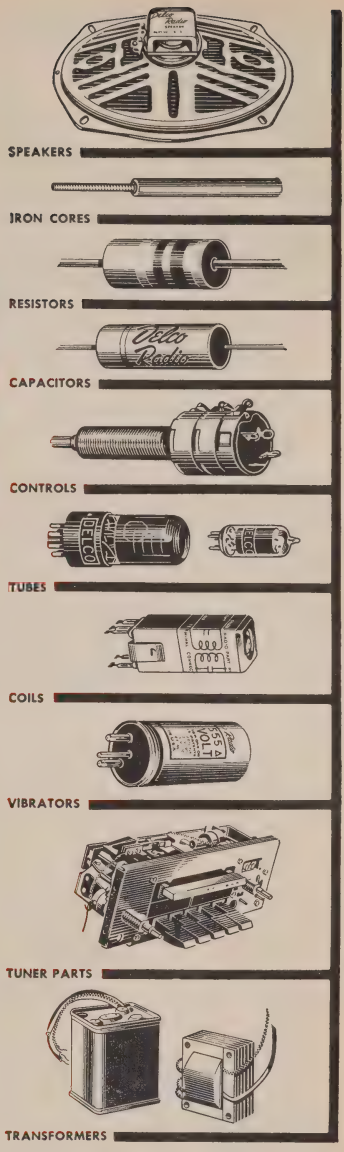

Your Delco Radio Electronic Parts Distributor carries the complete line, giving you fast, dependable service on the items you'll need for Delco Radio—and other radio—service work. Delco Radio also provides:

- Wide selection of special application parts
- Complete technical training program
- Effective warranty program
- Dealer identification signs

Get the facts today on this truly profitable dealer setup, and grow with General Motors!

Available everywhere through Electronic Distributors associated with . . .

GM U-M-S PARTS SALES
UNITED MOTORS SYSTEM

DELCO RADIO
DIVISION OF GENERAL MOTORS, KOKOMO, INDIANA

COYNE offers LOW COST TELEVISION Training in Spare Time AT HOME

The future is YOURS in TELEVISION—RADIO COLOR TV!

A fabulous field—good pay—fascinating work—a prosperous future! Good jobs, *or* independence in your own business!

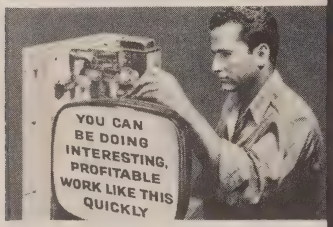

Coyne brings you MODERN—QUALITY Television Home Training; training designed to meet Coyne standards. Includes RADIO, UHF and COLOR TV. No previous experience needed. Practical Job Guides to show you how to do actual servicing jobs—make money early in course. You pay only for your training, no costly "put together kits."

SEND COUPON FOR FREE BOOK

and full details including easy Payment Plan. No obligation, no salesman will call.

B. W. Cooke, Jr., President

Coyne—the Institution behind this training . . . the largest, oldest, best equipped residential school of its kind. Founded 1899.

COYNE ELECTRICAL SCHOOL

500 S. Paulina, Chicago, Dept. 88-H5

A Technical Trade Institute Chartered Not For Profit

COYNE Television, Home Training Division
500 S. Paulina St., Chicago 12, Ill.
Dept. 88-H5

Send Free Book and details on how I can get Coyne Quality Television Home Training *at low cost and easy terms.*

Name.....

Address.....

City.....State.....

(It is understood no salesman will call)

TRY, TRY AGAIN

My most unusual service job was on an RCA model T-120. The complaint was an intermittent picture. Close observation showed poor sync stability in the horizontal oscillator and arcover in the horizontal output transformer and 1B3. The picture and raster would intermittently cut out with a loud click. When a picture was on the screen, the top part of the picture would bend and weave a little.

After probing around with a scope, I noticed that the peak-to-peak voltage at the grid of the 6BG6-G horizontal amplifier was greater than normal; the peak-to-peak voltage at the plate of the 6BG6-G would decrease as the brightness control was advanced, and the high voltage would drop to 8,650. The efficiency of the circuit was improved by replacing the horizontal output transformer, tubes, and some components. However the trouble was still there.

Reducing the horizontal drive cured the instability problem. But now the picture lacked brightness and focus. The high voltage was low, so I tried several 1B3's and checked all components in the high-voltage circuit—all to no avail.

By this time the set decided to act up intermittently. A blue glow appeared in the 1B3 and was traced to an intermittent arcover in the 12LP4A picture tube. Replacing the picture tube cured the intermittent condition. However, as before, the high voltage was still low. Advancing the horizontal drive control brought the high voltage up but also brought back the instability and overdrive.

After prolonged checking and self-consultation I asked: "Could the trouble be in the *new* horizontal output transformer as well as in the original?" I decided to substitute another exact replacement—it cured the trouble.—*G. P. Oberto*

"My boss doesn't understand me."

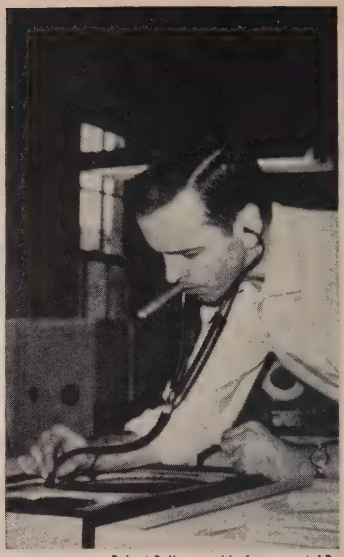

Robert Bell, assembly foreman at AR

FACTORY INSPECTION for AR SPEAKERS

A stethoscope is used in the production testing of every Acoustic Research speaker system, to detect possible air leaks in the cabinet. The speaker is driven by a twenty-cycle signal, and if there are any leaks a characteristic rushing sound can be picked up at the trouble spot.

This test procedure is necessary because the sealed-in air of an **acoustic suspension** enclosure is a basic working element of the speaker system. In conventional speakers the cone works against the springy stiffness of its mechanical suspensions; in AR speakers this stiffness is missing, and the cone works instead against the springiness of the enclosed air-cushion. Like the new air-suspension cars, the speaker literally rides on air.

The patented AR system requires a small cabinet, so that the enclosed air will be springy enough. And since the air-cushion does not bind or reach its elastic limit as do mechanical springs, the AR-1 has created new industry standards in the low-distortion reproduction of music. The "bookshelf" size of AR enclosures is associated with an absolute advance rather than a compromise in speaker bass performance.

AR speakers have been adopted as reference standards, as test instruments for acoustical laboratories, and as monitors in recording and broadcast studios. Their most important application, however, has been in the natural reproduction of music for the home.

The AR-1 and AR-2, two-way speaker systems complete with enclosures, are $185 and $98 respectively in either mahogany or birch. Walnut or cherry is slightly higher and unfinished fir is slightly lower in price.

Literature is available on request.

Dept. E

ACOUSTIC RESEARCH, INC.
24 Thorndike St., Cambridge 41, Mass.

DIPOLES and YAGIS

This is the first of a series of articles on the practical aspects of antenna installation. This installment presents the facts about stacking antennas and the effects of such stacking

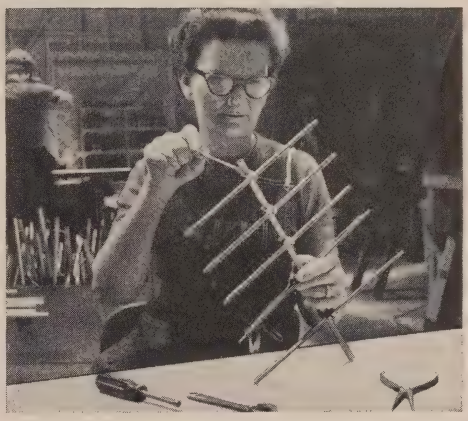

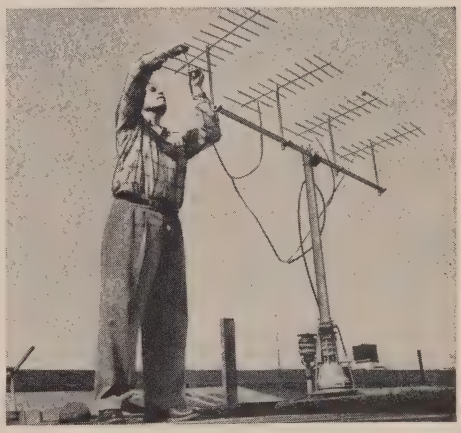

By Engineering Staff, Scala Radio Co.

Fig. 1 (above right)—Scale-model Yagi antenna is constructed with careful attention to detail.

Fig. 2 (right)—Yagi antennas are tested with installation which approaches ideal.

Fig. 3 (above left)—Radiation patterns are checked on accurate laboratory equipment. Electronic patterns are traced on scope screen.

Fig. 4 (below)—Polar patterns of single 10-element Yagi antenna: a — horizontal; b—vertical.

THERE are many good books on antenna theory. However, very few data are available on antenna installation techniques. Technical problems met in practical work have been almost completely avoided.

Generally, we stack antennas to increase gain. In practice a gain of approximately 3 db is possible each time the number of antennas is doubled. Two dipoles stacked vertically or horizontally have an approximate gain of 3 db over a simple half-wave dipole. A 4-bay antenna has a gain of approximately 6 db, an 8-bay job yields a gain of approximately 9 db and a 12-db approximate gain is possible from a 16-bay array. In stacking antennas we also automatically increase the directivity in the plane in which the antennas are stacked.

Basic dipole principles

A dipole is bi-directional. The two major lobes are at right angles to the elements. No energy is radiated from the ends of the dipole. Dipoles can be stacked vertically, and this confines the energy on the vertical plane. It gives a sharper radiating pattern on the vertical plane, without affecting the horizontal plane.

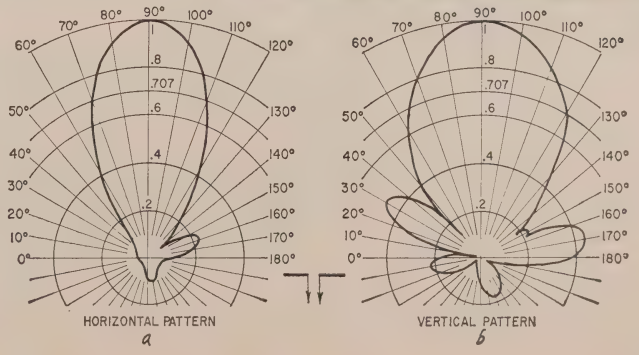

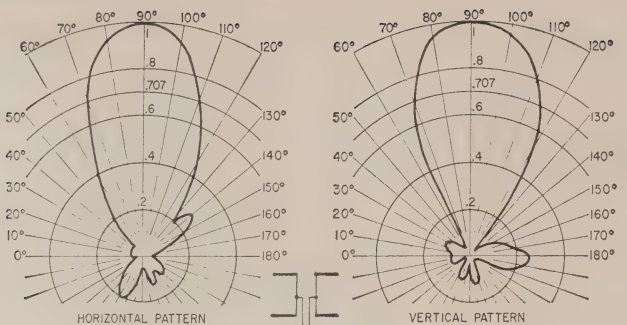

Fig. 5

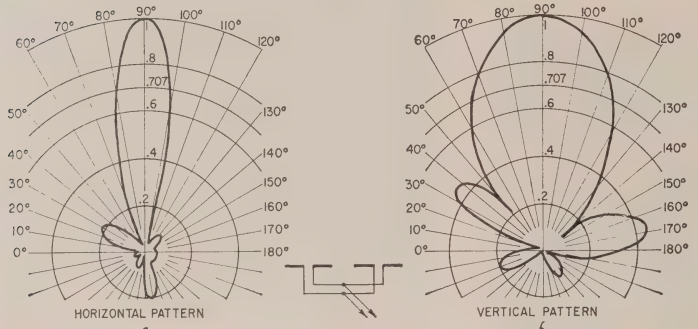

Fig. 6

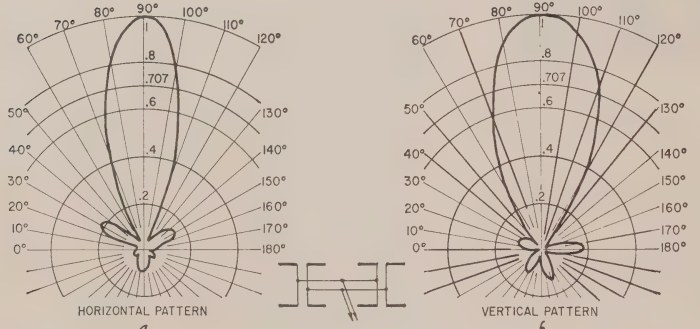

Fig. 7

Fig. 8

Stacking dipoles horizontally confines the horizontal radiating pattern, without affecting the vertical pattern. When dipoles are stacked both vertically and horizontally, energy is confined to both planes. A gain of about 5 db is obtained by merely adding a director to a dipole. A little more gain is obtained by using a reflector instead.

The forward radiating pattern of a dipole with reflector is reasonably similar to that of a dipole with a director. However, the effect on the rear lobe is more pronounced, and a higher front-to-back ratio is obtained with a reflector.

Properly terminated antennas do not cause radiation from the transmission line or noise pickup. This applies to a perfect termination, however, which may be difficult to obtain in practice. These considerations will be discussed in detail later.

Assuming a solid wavefront, when a given number of Yagi antennas are stacked, the same gain should be obtained whether stacking is vertical or horizontal. If the expected gain is not obtained the installation has been made incorrectly. Note that the *method* of stacking changes the directional characteristics greatly. Incorrect stacking can cause complete failure.

Hence, a study of both the horizontal and vertical radiating pattern was made on exact 10-to-1 scale models of 10-element Yagis. This means making *all* dimensions of the antenna 1/10 in size and energizing the structure at 10 times the frequency of the reference antenna. Fig. 1 shows such a test antenna.

The stacked antennas are then mounted on a test stand with rotator as shown in Fig. 2. Finally, the response is measured on a radiation pattern indicator, as illustrated in Fig. 3.

Radiation patterns of Yagis

The radiation patterns of a single Yagi are seen in Fig. 4. Note that the horizontal pattern in Fig. 4-a is symmetrical, except for a small lobe on the right. This disturbance is intentional and shows the effect of an unwanted signal. At a later point, it is shown how this disturbance can be reduced greatly by proper stacking.

Fig. 4-b depicts the vertical radiation pattern of the same antenna. The smaller lobes on either side of the major lobes are typical of a single Yagi. They result from side radiation of the driven element. We will show how these lobes are also eliminated by proper stacking.

If two Yagis are stacked vertically,

Fig. 5—Pattern of 2-bay vertically stacked Yagis: a—horizontal plane; b—vertical plane.

Fig. 6—Two-bay horizontal stack: a—horizontal pattern; b—vertical pattern.

Fig. 7—Four-bay array stacked horizontally and vertically: a—horizontal pattern; b—vertical pattern.

Fig. 8—Horizontally stacked, 4-bay array: a—horizontal pattern: b—vertical pattern.

Belden
WIRES · CABLES · CORDS
WIRE
THE WIRE YOU NEED
—for EVERY ELECTRONIC application
—Correctly Rated—Quality Controlled
—for positive performance
—for the most complete line for all electronic applications
—for most advanced construction designs, insulations, and shieldings correctly service-rated
—for dependable uniformity under strictest quality control
—for complete information in an easy-to-read catalog
—for fast service
You Can Depend on Belden . . . Ask Your Belden Jobber
Belden
WIRES · CABLES · CORDS
WIRE
One Wire Source for
Everything Electrical & Electronic
Belden
WIREMAKER FOR INDUSTRY
SINCE 1902
CHICAGO
Magnet Wire • Lead Wire • Power Supply Cords,
Cord Sets and Portable Cord • Aircraft Wires
Electrical Household Cords • Electronic Wires
Welding Cable • Automotive Wire and Cable
08A02I8

the pattern changes little horizontally. The half-power point (0.707 voltage point) is still at 40°. However, the vertical pattern is considerably changed. The half-power point is no longer at 60°; the pattern is now much sharper, and the two side lobes in Fig 4-b are greatly reduced (see Fig. 5).

Now, consider two Yagis stacked horizontally. You will note from Fig. 6-b that the vertical pattern is unaffected. It remains the same as for a single antenna. The horizontal radiating pattern (Fig. 6-a) is considerably changed. The half-power point is now 20°, not 40° as in Figs. 5-a and 4-a.

These tests show that the radiating patterns of antennas are changed only in the plane of stacking. Thus, if two antennas are stacked horizontally, the horizontal pattern is changed—the vertical pattern is not. Likewise, if two antennas are stacked vertically, the vertical pattern is changed—the horizontal pattern is not.

Controlling both planes

Installations often require polar control of both horizontal and vertical patterns. Hence, we give next the result of stacking four antennas. Two were stacked vertically and two horizontally. The two banks were phased together and the patterns observed in vertical and horizontal planes.

Fig. 7-b shows how the half-power point in the vertical plane becomes 38° in this configuration. The half-power point in the horizontal plane becomes 25°. It is interesting to note the similarity between the Fig. 7-b quad stack and the Fig. 5-b two-bay vertical stack. The same similarity is seen between the Fig. 7-a quad stack and the Fig. 6-a two bay horizontal stack.

The possibilities which can be realized by the field technician are further illustrated by stacking four antennas in the horizontal plane. Fig. 8-a shows the horizontal polar diagram of this configuration. Note the narrow beam width of 15°. Note also that the side lobe of Fig. 4-a has almost vanished.

The vertical pattern (Fig. 8-b) is practically unaffected and remains the same as in Fig. 4-b. As might be anticipated, similar tests results can be expanded to any number of antennas. However, the practical worker is seldom concerned with more than four.

If you observe the polar patterns which have been illustrated, you will be able to solve many practical problems easily. For example, if you have co-channel interference from the side, you can eliminate it by stacking antennas horizontally. Noise which arrives from below the installation can be reduced or eliminated by stacking the antennas in a vertical plane. If interference arrives from both sides and below or above the antenna site, stack antennas horizontally and vertically.

Following installments will explain how to control co-channel interference, reflections, space loss and similar practical field problems. END

SUITS NEED PRESSING—
MERIT DEFLECTION YOKES
DO NOT!

Merit deflection yokes are cosine wound TO FORM, not pressed. Pressing can lead to distortion and poor focusing. Pressing after winding frequently causes breakdown.

MERIT COILS AND TRANSFORMERS HAVE "BUILT-IN" ADVANTAGES.

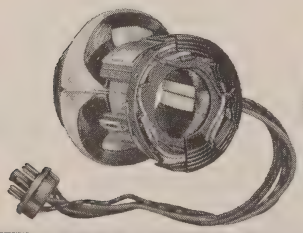

Each Merit yoke is
100% LIVE TESTED

COMPARE IT WITH
MERIT
MERIT COIL AND TRANSFORMER CORP.
MERIT PLAZA · HOLLYWOOD, FLORIDA

you can convert to stereo without a second woofer or expensive network

IF YOUR WOOFER HAS FOUR TERMINALS

These four terminals lead to an exclusive University feature... THE DUAL VOICE COIL... two electrically separate voice coils on a single woofer that provide perfect bass from both stereo channels, without the need for expensive or complicated stereo adapter networks or "control" filters.

This means the tonal magnificence of University stereo adapted speaker systems can be perfectly matched for stereo with the sole addition of an inexpensive, compact stereo "add-on" speaker, or other suitable limited range speaker. This is possible because stereo effect is created largely by frequencies above the nominal bass range.

How University dual voice coil woofers work: Voice Coil A of the woofer receives the full bass from one stereo channel. Voice Coil B receives the full bass from the other channel. Then...exactly as done in two-woofer stereo systems...*both* bass signals are blended *acoustically*. Result: authentic, balanced, full-bodied bass that will give you the enduring satisfaction of superb stereophonic sound.

Thus, you save the expense and space of an additional woofer and its enclosure. Whether you are investing in a complete stereo system...or starting with a monaural system for later conversion...a University speaker system* featuring a dual voice coil woofer proves once again... *with University it pays to own the very finest!*

**University woofers having dual voice coils are models: C-15W, C-12SW, C-15HC and C-12HC. These are employed in speaker systems: Debonaire-12 S-3, S-3S; Senior S-5, S-5S; Master S-6, S-6S; Dean S-7, S-7S; Classic S-8, S-8S, S-9, S-9S; Ultra Linear S-10, S-10S, S-11, S-11S; Troubadour S-12, S-12S. (System models in light type are fully stereo adapted. System models in bold type can be easily and inexpensively prepared for stereo with kit SK-1. User net: $5.95)*

LISTEN... University SOUNDS BETTER!

How to achieve your University stereo system

Select the stereo adapter speaker(s) that best suits your budget, decor and space requirements. Each of University's all-new stereo adapter speakers has been specially designed to provide a perfect stereo match by *direct* connection to your dual voice coil system. (For systems *not* having a dual voice coil woofer, a stereo adapter network is available.) Stereoflex I is well suited for bookshelf installations. Stereoflex II, with its narrow silhouette, makes a fine end table. Model SLC can be affixed to a wall or "lite-pole," its decorative fibreglass housing blending smartly with modern furnishings.

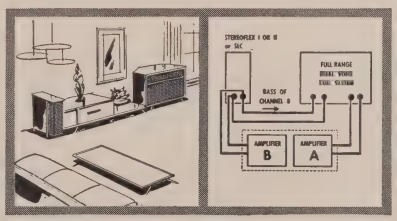

These illustrations are typical of how any of the University stereo adapter speakers may be used in 2-speaker and 3-speaker stereo system combinations. Above, is a Stereoflex II connected to a full-range speaker system. Below, are two Stereoflex I's used with just a dual voice coil woofer in a suitable enclosure.

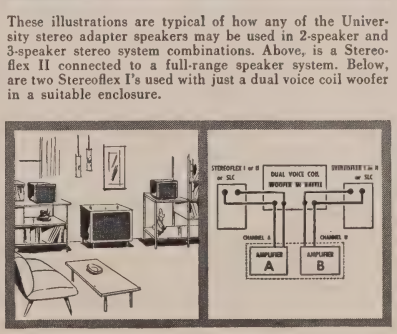

See your dealer for any desired additional information, or write to Desk J-6, Technical Service Department, University Loudspeakers, Inc., White Plains, N. Y.

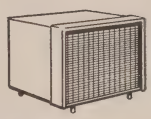

STEREOFLEX I: Double horn-loaded, with 6" mid-range driver and 2000 cps crossover wide-angle tweeter. Response: 150-15,000 cps. Hardwood furniture finishes. 11½"h.x12½"w. x10½"d. **User net:** Mahogany—$54.50, Blond or Walnut—$56.50.

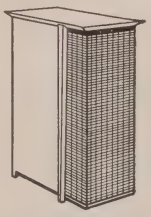

STEREOFLEX II: Double horn-loaded, using an extended air column mid-range with heavy duty compression driver and 3000 cps crossover wide-angle tweeter. Built-in BRILLIANCE control. Response: 150 cps to beyond audibility. Hardwood furniture finishes. 25½"h.x10"w.x19½"d. **User net:** Mahogany — $110.00, Blond or Walnut—$113.00.

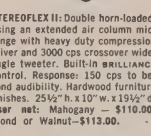

MODEL SLC: Same as Stereoflex I, but with decorator charcoal gray fibreglass housing and gold anodized front grille and adjustable tilting stand. 11½"h.x12¾"w.x10⅝"d. **User net:** $43.50.

STEREO ADAPTER NETWORK A-1: Available for use with any brand of speaker system not having a dual voice coil woofer. Not needed with University speaker systems: Debonaire-12, Senior, Master, Troubador, Dean, Classic, Ultra Linear-12 or -15. **User net:** $30.00.

fm tv dx

By ROBERT B. COOPER, JR.

IN last year's television DX columns (fall–winter, 1957) F2 television reception was covered piece-meal fashion. Unlike other forms of dx reception, F2 calls for making a few minor or major (depending on your experience in TV) modifications to the TV set, antenna system and your dxing habits. Unfortunately, too few dxers realized the possibilities of F2 reception and made no attempt to go out of their way to receive the numerous TV transmissions which bridged the Atlantic from England, France, Italy, Denmark, Russia and Germany.

To those who did bother with the circuit modifications, antenna installations and a study of what makes F2 tick, the results were by far the most noteworthy dx loggings reported in many seasons.

Foremost among the F2 dxers is Gordon Simkin of Loma Linda, Calif. Dxer Simkin has been most helpful to aspiring F2 dxers, offering information on receiver modifications, antennas and when and where to look for signals. On the opposite side of the continent, Ronald Boyd of Truro, Nova Scotia, Canada, has reported in detail his luck with English, French and Danish TV transmissions.

It remained for Stanley J. Penc, of Utica, N. Y., however, to provide us with a set of what we consider good to excellent photographs of F2 TV reception, as seen on *this* side of the Atlantic. Stan Penc has been dxing for several years in Utica, with a total of 124 stations in 30 states, Puerto Rico, Mexico, Cuba and Canada and now, thanks to F2, England, France and Germany.

Stan's setup is typical of the *Simkin modifications* found in use throughout the country. The heart of his system is a Heathkit FM-3A tuner feeding a Setchell-Carlson receiver. Many modifications (in fact a whole rebuilding job) were performed on the FM-3A, and will not be discussed at this time.

A conical antenna with a 45-mc center frequency (European TV operation begins at 41.25 mc), mounted with a conventional rotator some 30 feet above ground, is used. It is vertically polarized to match BBC TV transmissions in this frequency range. For the 48–54-mc range, a 6-meter amateur antenna is used. It covers BBC channel 2 and other dx stations in this range.

For detailed data on picking up European TV dx see "Looking in on London," RADIO-ELECTRONICS, September, 1958, page 52.

Unusual but true

The longest distance covered on a regular basis on the TV channels? 200 miles? Perhaps 300? In which case you guess it to be from a mountain-top receiving site? Try 700–1,000 miles for size. That's right . . . 700–1,000 miles!

Alberto A. Garcia of Merida, Yucatan State, Mexico, reports: "We have been doing some dxing of American stations for some time—usually we can get Texas or Louisiana stations. . . ." He continues, "We have been able to dx to the highest perfection with certain regularity KTBS-TV (3), Shreveport, La., and KTBC-TV (7), Austin; KRIS-TV (6) and KSIX-TV (10) Corpus Christi; KPRC-TV (2), Houston and WOAI-TV (4) San Antonio, Tex., and sometimes we get KTHV (11), Little Rock, Ark."

Not to be overlooked is the excellent over-water path which these signals follow along the western Gulf Coast, over most of the distance.

Also of dxer interest is a report from Joh. Richter of San Salvador, El Salvador, Central America. He reports that KPRC-TV (2), Houston, was received with good E-skip signals during the early evening of July 20, and many unidentified stations were seen on the evening of July 19. However, of particular note is San Salvador's channel 6 transmitter, a worthwhile shot for Southern dxers in the states.

Two unusual trops hauls

June 28–30 was generally a period of excellent ground-wave conditions throughout the Midwest and the mid-South Gulf states. Hundreds of loggings in the 300–500-mile range have been reported, and two noteworthy hauls of greater distances have turned up. Of particular interest, however, is the lack of reports for uhf loggings in excess of 250 miles during this time.

A new reporting station to this column is that of Mr. and Mrs. W. L. Bush of Mexico, Mo. They found the low and high bands (2–6, 7–13, respectively) loaded with stations in the 300–500-mile range when they flipped on the receiver at 0730 EST June 30. At 0735 WGR-TV (2), Buffalo, N. Y., overrode the channel 2 pileup long enough to be identified, a nice low-band ground-wave haul of 745 miles. Also seen were WWJ-TV (4), Detroit, and WOOD-TV (8), Grand Rapids, Mich.

Bill Eckberg of Walnut, Ill., also found June 28–30 profitable, although dx was not nearly as widespread at his location. At 2130 on the 28th, Bill intercepted 2 hours of reception from KGUL-TV (11), Galveston, Tex., 918 miles south of his location. Not a record, but a very nice logging.

FM dx

Our first FM dx report from Canada highlights the FM department this month. Lawrence G. Molish of Winnepeg, Manitoba, noted FM dx from KRLD-FM (92.5 mc) and KRR-FM (101.1 mc), both in Dallas, Tex., in the morning hours of July 6. Also heard were many unidentified FM stations between 88 and 102 mc. It is interesting to note that the only TV dx observed during this period came from KMID-TV (2), Midland, Tex., and KNAC-TV (5), Fort Smith, Ark. The receiving

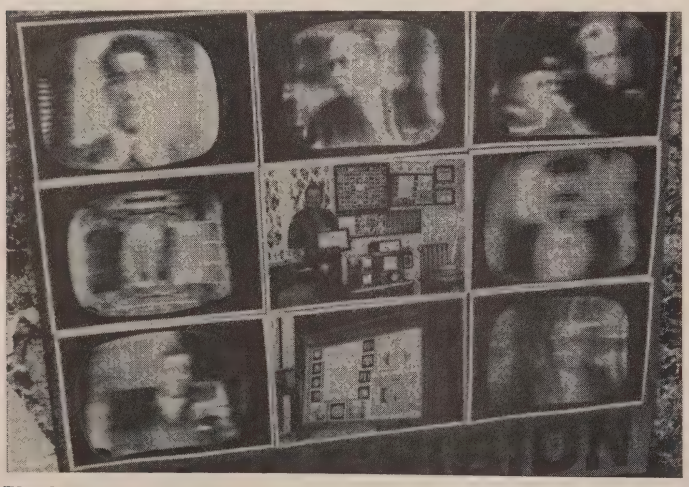

F2 television is very ghosty at best. Even against this problem, dxer Stanley J. Penc of Utica, N. Y., has surrounded himself and his equipment with several good photos of these elusive BBC transmissions. The center photo is of Penc himself.

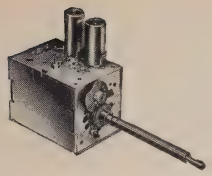

Now YOU can get TUNERS repaired, or replaced, in a hurry!

Send them to TARZIAN!

● Sarkes Tarzian, Inc., announces a new tuner repair service and factory replacement program for Tarzian-manufactured tuners. Distributors, dealers and servicemen will welcome this direct factory service program which is designed to take delay and confusion out of the tuner repair business.

We're set up to offer a 48 hour service from the date of receipt to shipment to you.

Cost is reasonable, too. Only $7.50 per unit ($15 for UV combinations) and that includes ALL replacement parts! Both repaired —or exchange units if available from stock—carry a 90 day warranty against defective workmanship and part failure.

Replacements will be offered at these current prices* on units not repairable:

VHF 12 position tuner...	**$17.50**
VHF 13 or 16 position tuner.....	**19.50**
VHF/UHF combination.	**25.00**
UHF only.....	**15.50**

*Subject to change

When inquiring about tuner service, always refer to tuner by part number. When inquiring about direct replacements for tuners other than Sarkes Tarzian-manufactured, please indicate tube complement, shaft length, filament voltage, series or shunt heater. Use this address for quickest service:

SARKES TARZIAN, Inc.

Att: **Service Mgr., Tuner Division**
East Hillside Drive
Bloomington, Indiana

TARZIAN Electronic Product and Services include TELEVISION TUNERS . . . SELENIUM AND SILICON RECTIFIERS . . . BROADCAST EQUIPMENT . . . AIR TRIMMERS . . . TV STATIONS WTTV and WPTA, and RADIO STATION WTTS.

TELEVISION

antenna is a simple pair of rabbit ears, with a Mallory FM tuner feeding a Crosley TV receiver.

Dx predictions

In the past months, impressions received indicate that the predictions portion of this column may not be of too great value. If this is true we would like to know, so we can make the best use of the available space.

The month of November is normally very poor for Es work. Any E skip which does occur appears in the early evening hours, generally in southern latitudes.

Watch the lowest channels (2–4) for signs of *venetian blinds* (see "Tips from a Tv-Dxer's Notebook," RADIO-ELECTRONICS, November, 1957, page 58) in a direction not normally occupied by local and fringe-area stations.

Auroral Es occurs for the most part along the border area of the United States and Canada, on east–west paths. Dxers throughout the northern United States and southern Canada should be aware of any garbled-fading signals on channels 2–6 during the early evening hours (1700–2000 local standard time) and late evening (2200–2400 LST). This is especially true when visible Auroral Borealis displays appear in the northern skies.

Beginning as early as 0700 LST some days and continuing as late as 1500 LST on peak afternoons, British, French, and German TV broadcasts should be received via F2 with good strength throughout November and the first two weeks of December in most every sector of North America. Possible reception of Russian, Italian, Swedish and Swiss TV stations should not be overlooked either.

Last call for totals

All dxers are urged to send their complete station totals to the TV Dx Column before Nov. 1, 1958. Be sure to include the total number of stations you have logged (including local stations), the greatest distance logged on each of the three bands (2–6, 7–13, uhf) and the number of uhf stations to your credit. All listings totaling 50 or more stations will find their way into the annual Tv dx review listing of the Over 50 TV Dx Club. Even if you report to the column on a regular basis, a last-minute postcard with the totals information will insure that your listing is accurate and up to date in the January, 1959, TV Dx column.

Report forms

As for the past 14 TV dx columns, RADIO–ELECTRONICS offers dxers a set of blank TV dx forms, to be used when reporting TV dx to this column. The forms are free and make convenient logging forms. Send a postcard with your name, address and the phrase "TV Dx Forms" to TV Dx Column, RADIO-ELECTRONICS Magazine, 154 West 14th St., New York 11, N. Y. (PS—they are excellent FM logging forms.) END

NEW
TRANSISTOR ELECTRONICS & SOLID STATE PHYSICS

Basic Reference Library

AVAILABLE NOW FOR FREE EXAMINATION

These 5 fully illustrated volumes by outstanding authorities give you the most straightforward guidance you can get anywhere on every aspect of transistors and solid state physical electronics.

1 TRANSISTOR PHYSICS AND CIRCUITS
By Robert L. Riddle and Marlin P. Ristenbatt, Senior Engineers, Haller, Raymond and Brown
Bridging the gap between theory and application this book provides a new simplified approach to the operation and design of transistor circuits by way of familiar physical and electrical law without sacrificing technical fidelity.

2 TRANSISTOR ELECTRONICS
By Lo, Endres, Zawels, Waldhauer, Cheng
Here's an exhaustive run-down of many specialized areas of transistor work, from transistor operation and circuit analysis to practical circuit design. Full coverage of high frequency operation, oscillators, modulation, demodulation, switching circuits. Convenient tabular forms help bring out fine points of operation.

3 TRANSISTORS HANDBOOK
By William D. Bevitt, Transistor Applications Engineer, CBS-Hytron
Practical, on-the-job guide to all major types of transistor circuits with full data on 56 different transistors. Gives scores of circuit diagrams each with typical values of circuit elements—material that helps you take out, try, and adapt these tested circuits to your own needs.

4 SOLID STATE PHYSICS
Prof. A. J. Dekker, Electrical Engineering Dept., University of Minnesota
Thorough study of the physical properties of crystalline solids. Contains full information on properties of metallic lattices, ionic crystals, semiconductors, magnetic properties of solids, electronic properties of ionic crystals.

5 SOLID STATE PHYSICAL ELECTRONICS
By Prof. Aldert Van Der Ziel, Electrical Engineering Dept., University of Minnesota
Provides complete source of information on solid state devices being used and developed in the electronics industry, PLUS essential theory. Covers: structure of the solid state, theory of semiconductors, electron emission devices, semiconductor devices, dielectric and magnetic devices.

EXAMINE FREE—SEND NO MONEY

Mail the coupon below to get complete 5-volume set on 10 DAYS' FREE TRIAL. If not completely satisfied, return in 10 days and owe nothing. Or keep the set and pay only $7.50 down and $8 a month for five months until full price of $47.50 is paid. Decide for yourself —without risk or obligation—just mail coupon to examine this valuable Library at our expense.

Prentice-Hall, Inc., Dept. 5744-P2
Englewood Cliffs, N.J.

Send me TRANSISTOR, ELECTRONICS & SOLID STATE PHYSICS LIBRARY (5 volumes) for 10 days' free examination. If fully satisfied in 10 days I will send you $7.50 plus few cents postage and then $8 a month for five months until full price of $47.50 is paid. Or I will return the Library within ten days and owe nothing.

Name .....

Address .....

City and State .....

TV Service CLINIC

conducted by

ROBERT G. MIDDLETON
TELEVISION CONSULTANT

INTEREST in dc restorer circuits continues, judging by our incoming mail. Hence, we are pointing out some further principles of this unique circuit.

Although a dc restorer boosts the low video frequencies, it must not be confused with a bass-boost type of circuit. It is entirely different, being a nonlinear device, with *clamping* action on the sync tips. A bass-boost circuit, on the other hand, is a linear configuration without clamping action. *It will not work as a dc restorer.*

The function of the dc restorer in reproducing true backgrounds has been previously noted and is illustrated in Fig. 1. It keeps the correct background level by clamping the sync tips at CRT cutoff, as shown in Fig. 2.

A complete circuit diagram for an efficient dc restorer is in Fig. 3. It can easily be added to an ac-coupled video amplifier lacking dc restoration.

This circuit is for a grid-driven picture tube. If cathode-driven, reverse the diode.

It is sometimes supposed that a cathode-driven picture tube does not require dc restoration. This is not true. Whether grid- or cathode-driven, the picture will not reproduce large gray areas correctly if ac-coupled without dc restoration.

If you do not wish to add a tube for dc restoration, use a 1N34-A crystal diode. The published ratings for the 1N34-A may make you look askance at this application, but these are dc ratings. They can be exceeded by a large percentage in pulse operation, with no damage to the diode. This is particularly true for the maximum peak inverse voltage rating.

It is advisable to select diodes for high back resistance in dc restorer circuits. A suitable diode will have at least 750,000 ohms back resistance at −10 volts, and at least 250,000 ohms back resistance at −50 volts.

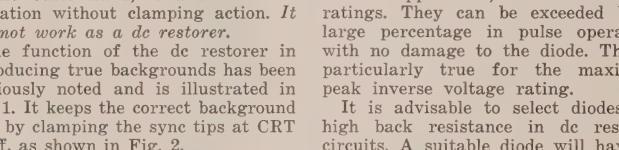

Fig. 1—Lack of dc restoration causes the video signal to operate at a false black level.

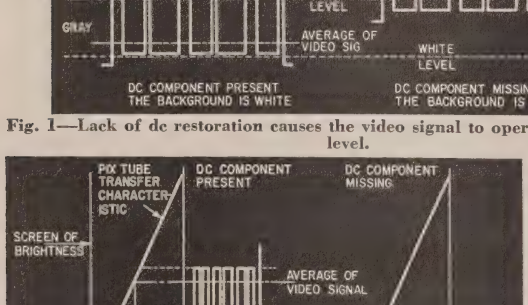

Fig. 2 — When sync tips are clamped to the CRT cutoff level, black, white and grays are correctly reproduced.

Trouble with the agc

I am having trouble with a Raytheon 21T25. When the agc lead is disconnected from the tuner, the lug on the tuner has −1 volt present. Shouldn't it measure zero? The voltage on the agc line is −4 with a strong signal. A tunable buzz is present, particularly on a light picture. The peak-to-peak output from the picture detector is 4 volts, instead of 2 volts. Please advise how to locate the trouble.—G. G. M., Troy, W. Va.

The −1 volt that you measure (see Fig. 4) is called contact potential. A floating grid will normally measure

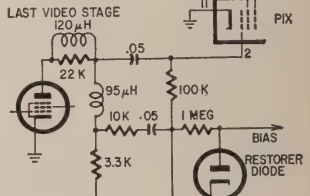

Fig. 3—An efficient dc restorer circuit, working from a grid-driven CRT.

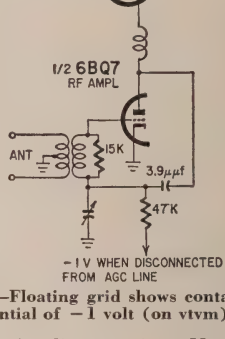

Fig. 4—Floating grid shows contact potential of −1 volt (on vtvm).

about −1 volt on a vtvm. Measuring 4 volts peak-to-peak at the picture-detector output indicates if overload and low agc bias. It is difficult to say exactly how much bias should be found, without knowing the actual signal strength. Try using override bias to see if normal reception results. This will verify suspicion of agc trouble. This receiver passes the intercarrier sound signal through the video amplifier. Hence, overload in the video amplifier could also cause buzz. A leaky coupling capacitor or low supply voltage to the video amplifier tube could be responsible. Also check the setting of the buzz control in the FM detector circuit.

Vertical foldover

A Brunswick receiver has a bad foldover at the bottom of the picture. Width and height are good, and vertical hold is very tight. Tubes have been replaced, and all capacitors and resistors in the output section, along with yoke and oscillator transformer. All voltages are within limits except the plate of the 6S4, which is low. Any informa-

RADIO SHACK SMASHES PRE-RECORDED STEREO TAPE MARKET WIDE OPEN!

ENTIRE FAMOUS Mercury LIBRARY PRICED BELOW DEALER COST!

Radio stations! Dealers! Schools! Audiophiles! For quick cash, Radio Shack bought this famous company's fabulous in-line Stereo tapes in carload quantities fantastically off price! Now, enjoy the ultimate in stereo (acclaimed by "High Fidelity," "Hi-Fi Music Review," "Audio," etc.) for little more than the cost of top quality *raw* tape! Standard stacked stereo 7½ ips tapes. Can also be played monaurally or on full-track heads. Even if you're just now planning to convert, rush your mail order while they last! Ship. wt. app. 1¾ lb. per reel.

A NEVER-BEFORE, NEVER-AGAIN OPPORTUNITY! CLASSICAL! SEMI-CLASSICAL! POPULAR!

REG. $7.95 & $8.95 **$4.99**

MVS2-16 DREAMLAND U. S. A. Hal Mooney & Orch. California Here I Come, Beautiful Ohio, Back Bay, When It's Sleepy Time Down South, Manhattan, Dreamland U. S. A. Reg. $7.95.

MVS2-14 FLORIAN ZaBACH. Till the End of Time, The Very Thought of You, I Married an Angel, Ain't Misbehavin', Tenderly, Lovely to Look At, Anniversary Waltz. Reg. $7.95.

MVS2-18 PATTI PAGE. Falling in Love With Love, The Boy Next Door, What'll I Do, Memories, Till We Meet Again, Remember. Reg. $7.95.

MVS2-19 THE FEATHERY FEELING. David Carroll Orch. Fascination, Swingin' Sweethearts, A Beautiful Lady in Blue, Dinner at Eight, Ski Song, I Love You Truly, Treadmill. Reg $7.95.

MS2-21 JIMMY PALMER ORCH. Three sparkling stereo hi-fi medleys of all-time favorite show and pop tunes arranged especially for dancing. Reg. $8.95.

MVS2-22 BILLY ECKSTINE. Boulevard of Broken Dreams, You Don't Know What Love Is, Babalu, Stella by Starlight; Where Have You Been, Zing! Went the Strings of My Heart. Reg. $7.95.

MVS2-24 GRIFF WILLIAMS SOCIETY ORCH. Let's Fly Away, Dance Medley, The Petite Waltz, I Know That You Know, When Day Is Done, The Girl Friend. Reg. $7.95.

MVS2-27 RALPH MARTERIE ORCH. Happy Ballerina, I'll See You in My Dreams, Mambocerto, Concerto, Eternally, Rhumba Concerto, Lonely Winter, Dancing Trumpet. Reg. $7.95.

MVS5-41 JOHANN STRAUSS. Voices of Spring, Champagne Polka, Roses From the South. Minneapolis Sym. Orch., Antal Dorati cond. Reg. $7.95.

MS5-48 SUPPE OVERTURES. Light Cavalry, Jolly Robbers, The Beautiful Galatea. The Halle Orch., John Barbirolli cond. Reg. $8.95.

MVS5-25 VARIATIONS ON A THEME BY HAYDN (BRAHMS). London Sym. Orch., Dorati cond. Reg. $7.95.

MS2-13 STEREO DANCE PARTY. Ralph Marterie Orch. All-time song hits specially arranged for dancing and brilliantly alive in stereo. Reg. $8.95.

MS2-17 SARAH VAUGHAN SINGS GEORGE GERSHWIN. Gershwin's most beloved song hits recorded in sparkling stereo by a great interpreter. Reg. $8.95.

REG. $12.95 **$6.99**

MDS2-1 SARAH VAUGHAN. Great Songs From Hit Shows. A Tree in the Park, Little Girl Blue, Comes Love, But Not For Me, Lucky in Love, Autumn in New York, It Never Entered My Mind, If This Isn't Love, September Song, My Ship. Reg. $12.95.

MDS2-2 HAVANA IN HI-FI Richard Hayman & Orch. Rhapsodero, My Hopeful Heart, Cordoba, Tropical Merengue, Maria-La-O, Caminito, La Compansa, I Won't Stand in Your Way, Love and the World Loves With You. Reg. $12.95.

MDS2-4 MUSIC FROM THE BIG TOP. Carl Stevens & Circus Band. William Tell Gallop, Mosquito Parade, The Thunderer, Asleep in the Deep, El Capitan, Dance of the Snake Charmer, Colonel Bogey, Muskrat Ramble, Fairest of the Fair, Bombasto, Invincible Eagle, Anchors Aweigh, Marines' Hymn, U.S. Air Force March, Semper Paratus, West Point March. Reg. $12.95.

MDS2-7 AMERICA'S MOST DANCEABLE MUSIC. Griff Williams Orch. The Lady Is a Tramp, I Could Write a Book, Tales From the Vienna Woods, Medley, When Spring Is in the Air, La Golondrina, Why?, What Is There to Say, Thou Swell, Artist's Life, Medley. Reg. $12.95.

MDS2-9 BILLY ECKSTINE, SARAH VAUGHAN. Alexander's Ragtime Band, Isn't This a Lovely Day, I've Got My Love to Keep Me Warm, All of My Life, Cheek to Cheek, You're Just in Love, Remember, Always, Easter Parade. Reg. $12.95.

MDS2-35 SONGS FROM GREAT FILMS. Herman Clebanoff Strings. Song From Moulin Rouge, Gigi, Wild Is the Wind, Sayonara, Song of Raintree County, Farewell to Arms Theme, Very Precious Love, Terry's Theme, Three Coins in the Fountain, Tammy, Moonglow & Theme From Picnic, Friendly Persuasion. Reg. $12.95.

MDS5-1 HARRY JANOS SUITE (KODALY). Antal Dorati & Minneapolis Sym. Orch., in astounding hi-fi. Reg. $12.95.

MDS2-11 BRASS IN HI-FI. Pete Rugolo Orch. My Mother's Eyes, All the Things You Are, God Child, Brass at Work, Temptation, A Rose For David, Everything Happens to Me, Salute, Song For Tuba. Reg. $12.95.

REG. $9.95 & $11.95 **$5.99**

MBS5-7 POLEVETZIAN DANCES (BORODIN) & CAPPRICCIO ITALIEN (TCHAIKOVSKY). London & Minneapolis Sym. Orch., Antal Dorati cond. Reg. $10.95.

MCS5-27 GRIEG'S PIANO CONCERTO. Richard Farrell & Halle Orch., George Weldon cond. Reg. $11.95.

MCS5-50 BOLERO (RAVEL), L'ARLESIENNE SUITE NO. 2 (BIZET) Detroit Sym., Paul Paray cond. Reg. $11.95.

MCS5-15 GAITE PARISIENNE (OFFENBACH). Minneapolis Sym., Dorati cond. Reg. $11.95.

MBS5-19 IBERIA (ALBENIZ). Minneapolis Sym. Orch., Dorati cond. Reg. $10.95.

REG. $6.95 **$3.99**

MWS5-29 MARCH TIME. Fred. Fennel Eastman Sym. Wind Ensemble. Bugles & Drums, Illinois March, Children's March, The Interlochen Bowl, Onward-Upward, Boy Scouts of America. Reg. $6.95.

REG. $14.95 **$7.99**

MFS5-10 VIOLIN CONCERTO (BARTOK). Yehudi Menuhin & Minneapolis Sym. Orch., Antal Dorati cond. Reg. $14.95.

REG. $17.95 **$8.99**

MJS5-17 SYMPHONY NO. 2 IN E MINOR (RACHMANINOFF). Detroit Sym. Orch., Paray cond. Reg. $17.95.

FREE!

Fabulous new 1959 232-page catalog.

Latest in stereo hi-fi, ham radio, electronics, parts, records, etc.

Mail orders to Dept. 11E

RADIO SHACK
730 Commonwealth Ave.
Boston 17, Mass.

☐ Check or money order enclosed. Please send following stereo tapes (please print order numbers clearly):

_____

_____

☐ Send free 232-page 1959 catalog.

NAME_____

ADDRESS_____

CITY_____ZONE____STATE_____

RADIO SHACK CORP.

Stores: 730 Commonwealth Ave., Boston 17 and 167 Washington St., Boston 8, Mass. and 230-240 Crown St., New Haven 10, Conn.

. . . another
MALLORY
P.R. MALLORY & CO. INC.
service-engineered
product
made to withstand
moisture and humidity
MALLORY
.05 MFD 600 VDC
GEM-615
MALLORY
"Gem" Capacitors
Nature's frog . . . and Mallory's "Gem" capacitors . . . are both capable of withstanding extremes of moisture and humidity. That's why Mallory Gem Capacitors are always your best choice for service replacements.
Mallory "Gems" are available in a complete range of standard capacity and voltage ratings. You'll find exact replacements for every circuit requirement. The closely checked tolerances of Gems assure correct circuit performance.
Insist on Mallory "Gems". They're a gem of a capacitor! Get them from your Mallory Distributor, in the self-service "5-pack."
P.R. MALLORY & CO. Inc.
MALLORY
P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA
• Capacitors • Controls
• Vibrators • Switches
• Resistors • Filters
• Power Supplies • Rectifiers
• Mercury and Zinc-Carbon Batteries

TELEVISION

tion will be greatly appreciated.—A. W. B., Brooklyn, N. Y.

The immediate clue here is the low plate voltage, which is a frequent culprit in foldover symptoms. Run down the cause of the low plate voltage, and I am certain that the foldover will disappear.

Dc restoration?

Has it been your experience that improvement results from adding dc restoration to circuits supposed to operate without it? Usually, a cathode-driven picture tube works well without dc restoration.—J. A. S., Philadelphia, Pa.

When a receiver uses ac-coupled video amplification, dc restoration is needed for best picture quality, whether the picture tube is grid-driven or cathode-driven. Dc restorers were used on all early TV receivers. Cost-cutting resulted in elimination of the dc restorer, because the public is not too critical of incorrect background reproduction. Nowadays, the design factors for dc-coupled video amplifiers are well known and have been rather widely adopted. Dc-coupled video amplifiers do not require dc restoration.

Co-channel interference

I would appreciate advice on co-channel interference. Most summer nights reception is bad, without a clear channel on the dial. The antennas are beamed at New York City, 70 miles away. Co-channel interference comes from all points on the map. Would a highly directional antenna help, or would an attenuator be better?—J. A. McD., Bellaire, N. Y.

This is basically an antenna problem. You need more directivity to minimize co-channel interference. You will need to stack several Yagi antennas, cut to channel. The antennas will have to be stacked in the vertical or horizontal plane, or tilted, as required by your field characteristics. Attenuators will not help.

Slow warmup

A G-E 21T30 does not come up to full brightness and contrast for at least 15 minutes after it is turned on. Where is the trouble likely to be?—B. J. O., Chicago, Ill.

Your report does not state whether you have tried a new picture tube. This is the most likely cause of the slow warmup. It would also be advisable to measure the heater voltage at the picture-tube socket and see if it is low. Also, make a test with a high-voltage dc probe and voltmeter to see how the high voltage comes up.

Intermittent pix and sound

A Motorola TS-119-B was brought to the bench with a complaint of intermittent picture and sound. At the bench there was only a raster. The 6AH6 video amplifier, 12AU7 video detector/first sound if, and 6CB6 first picture if tubes were shorted. I replaced the tubes, but picture and sound were still absent. Then, when the 12AU7

NEW Silicon Rectifier

Built for Reliability—Priced for Economy

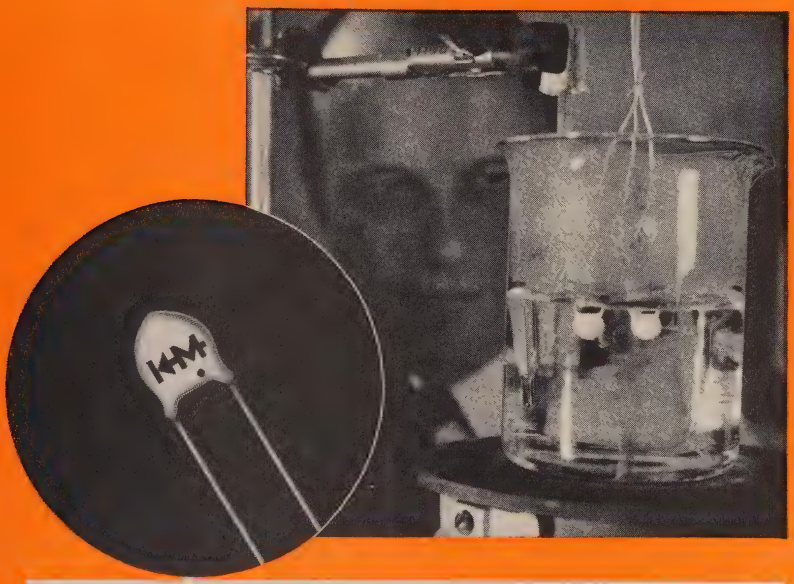

After 500 hours in boiling water, the new Mallory silicon rectifier is still going strong! That's just one of the ways we've proved that this new rectifier, product of Mallory semi-conductor research, gives you superior reliability and humidity resistance—at a price that is practical and profitable for TV and radio service jobs.

New Moisture-Proof Design, using unique Mallo-Seal* encapsulation, enables the rectifier to pass *four times* the tropical torture of military humidity tests . . . without a single failure.

New Performance. Compare these figures: reverse leakage less than 250 microamperes; forward drop less than 0.5 volt; no drop in characteristics after 2000-hour life test at 85° C ambient.

New Reliability. No premature failures, no call-backs—because 100% inspection assures quality in every rectifier.

New Economy. Highest quality and reliability at a new low price for commercial silicon rectifiers.

Several models are available: the encapsulated type for conversions, a plug-in model for sets already using silicon conversions—and a line of "top hat" and stud mounted models for military and industrial use. See your Mallory distributor soon for complete details.

*Trade Mark, P. R. Mallory & Co. Inc.

- Capacitors
- Controls
- Vibrators
- Switches
- Resistors
- Filters
- Power Supplies
- Rectifiers
- Mercury and Zinc-Carbon Batteries

P.R. MALLORY & CO. Inc.

MALLORY

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

Recoton-Goldring
VARIABLE RELUCTANCE
TURNOVER CARTRIDGE
now in STEREO

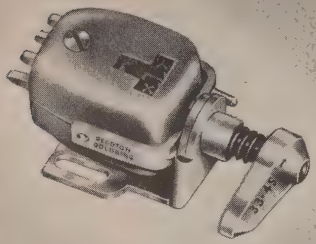

The famous Recoton-Goldring Magnetic Cartridge is now available for Stereo. One side has a diamond stylus for Stereo and is compatible for LP. The other side features a sapphire point for either LP or standard records. It can be used for all turntables or record changers with ½" standard mounting.

Giving faithful reproduction and full range symphonic channel separation, this new Stereo cartridge truly lives up to the high standard of quality set by Recoton-Goldring cartridges!

RG745-3SD With diamond stylus for stereo and monaural LP's and sapphire stylus for 78RPM.

RG745-1SD With diamond stylus for stereo and monaural LP's and sapphire stylus for LP's.

Audiophile Net $29.95

Ask your nearest dealer or write to

RECOTON CORPORATION 52-35 Barnett Ave., Long Island City 4, N. Y.

TEL-A-TURN
STOP
STRUGGLING

Here's How You Can Make MORE PROFIT on TV Repairs

PAYS FOR ITSELF IN A VERY SHORT TIME

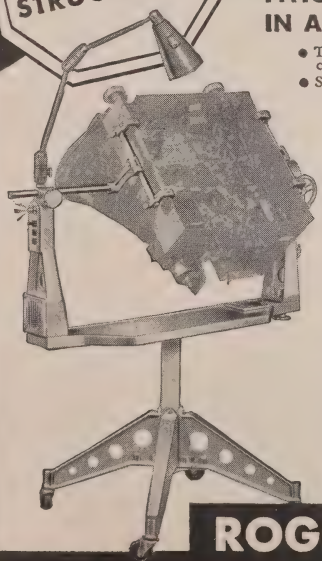

- The new Tel-A-Turn service cradle increases efficiency and output of any Electronic Technician.
- Simplifies part replacement, soldering, test probing.
- Prevents breakage and damage to above—chassis components.
- Ideal portable bench for "on-the-spot" work.
- A self-locking worm and gear provides 360° chassis rotation for the most convenient position for servicing above or below-chassis components.
- Quick-operating clamps hold chassis from 9" to 25" wide, and up to 200 pounds.
- Adjustable swivel lamp permits placing light for best visibility.
- A built-in PM speaker eliminates removing speaker from TV cabinet.
- Two hot outlets are provided for soldering iron and test equipment.
- Cheater cord, switch and pilot light provide safe, easy means of supplying and cutting off power to chassis under test.
- Tel-A-Turn is mounted on ball bearing rubber casters for smooth, easy mobility.
- Made of heavily ribbed cast aluminum. Weighs only 37 pounds.

"Here-at-Last", a practical service cradle for servicing Radio and TV chassis, Record Changers, Amplifiers and other Electronic Equipment. No service tool is more useful or profitable. Write Dept. SE-78 today for descriptive literature. Dealer inquires invited.

ROGERS MANUFACTURING CO.
LINDSEY, OHIO-U.S.A.

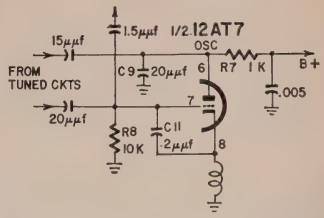

Fig. 5—12AU7 oscillates, but 12AT7 for which the circuit is intended doesn't.

was switched with the 12AT7 mixer, the chassis operated OK. What is the explanation?—W. L. H., Washington, D. C.

The 12AU7 and 12AT7 are similar, but the 12AU7 has about half the g_m of the 12AT7, and also operates with a different grid bias. The basic trouble, of course, is that the oscillator–mixer operates with the 12AU7, but not with the 12AT7. You might try some other 12AT7 tubes in the mixer to see if this helps. If not, there is trouble in the oscillator circuit. Check the plate voltage and R7 (see Fig. 5), and also R8, C9 and C11, if necessary.

Which flyback

What horizontal output transformer do you recommend for a 21EP4-B picture tube in an RCA 630-TS chassis?—H. E. A., Romulus, Mich.

The Merit HV07 transformer for 90° tubes will work well with the 21EP4-B. To get good linearity and full scan you will also require a 90° yoke. The present vertical output transformer will not be entirely satisfactory, and a heavier transformer should be used.

Correction

There is an error in the September TV clinic, page 59. The item, Big Screen to Bigger Screen, states that the 21AMP4-A is a 70° tube. Actually it is a 90° tube and therefore the mentioned conversion can be made without any need for circuit changes. Our thanks to Peter A. Keller of Alamogordo, N. M., for spotting the error.

Short tube life

I have a Westinghouse chassis that has a starting surge causing the 12B4 vertical output tube to light up much too brightly. The plate voltage at first is 290 volts, and in 5 seconds goes down to normal. Tube life is only about 3 weeks. What do you suggest?—H. C., Winter Haven, Fla.

This type of problem can be corrected easily by using a Surgistor in series with the power cord to the receiver. A Surgistor has 100 ohms of resistance for the first 10 seconds after the receiver is switched on, and prevents a heavy starting surge. At the end of 10 seconds, a bi-metal strip shorts out the resistor, and applies full line voltage to the receiver. END

TECHNICIANS' NEWS

NATESA CONVENTION

Warranty policies of some TV–radio–hi-fi manufacturers were unanimously condemned for "curtailing competition" in the service industry by more than 600 delegates representing 112 technicians' associations at the annual convention of the National Alliance of Television Electronic Service Associations (NATESA) in Chicago. A resolution attacked set makers "who have seen fit through their combination parts-and-service warranties to set a precedent in the establishment of fees for service."

At the recommendation of a special NATESA committee, the convention delegates decided to postpone any action on the issue of labeling new and rebuilt picture tubes.

Two new "Friends of Service Management" plaques were presented to the Merit Coil & Transformer Corp. and Tung-Sol Electric, Inc. Voted "Continuing Friends of Service Management" were CBS-Hytron, Raytheon, Sylvania and Howard W. Sams & Co. A special citation was awarded to station WWL-TV, New Orleans, for cooperating with Louisiana service associations in promoting a state-wide licensing law.

Vincent Lutz, of Lutz TV, St. Louis, was elected NATESA president, succeeding Russ Harmon, Weber TV, Cincinnati. Re-elected were secretary Mac Metoyer, A One TV, Kansas City, and treasurer Nelson Burns, Burns TV, Memphis.

The following were elected regional officers: Bert Bregenzer, Penn TV Service, Pittsburgh, Pa., eastern vice president; Irving Toner, Toner Radio & TV, Buffalo, N. Y., eastern secretary; Cordell Britt, May TV, Nashville, Tenn., east central vice president; Albert Mirus, Mirus TV, Cincinnati, Ohio, east central secretary; Wayne Lemons, A One TV, Buffalo, Mo., west central vice president; W. E. Johnson, Johnson Radio–TV, Beaumont, Tex., west central secretary; Winston Haines, E & H TV Co., Burlingame, Calif., western vice president; O. W. Andrews, Rocky Mountain Radio–TV, Denver, secretary.

Frank Moch was re-elected for a 2-year term as executive director, without opposition. The delegates selected Nashville as the site for the spring 1959 convention.

The Association Activities Forum was devoted principally to a series of questions posed by Frank Tesky of the Indianapolis Television Technicians Association (ITTA) and editor of the *Hoosier Test Probe* concerning the operations and finances of NATESA,

Mr. Service Dealer

PHILCO

OFFERS YOU A COMPLETE LINE OF

UNIVERSAL SERVICE PARTS

Your Philco Distributor has available for you a complete new line of universal parts that fit not only all Philco receivers but every competitive make and model. Eliminate your inventory problems and stock the one line of completeness . . . Philco.

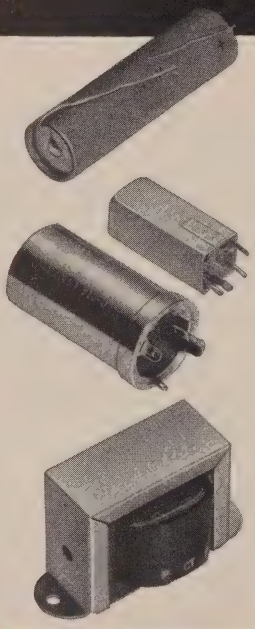

PHILCO UNIVERSAL SERVICE PARTS

- Sweep Components
- Coils
- Capacitors
- Vibrators
- Condensers
- Rectifiers

All Philco universal parts are precision engineered and quality tested to insure superior operation and longer life. Don't settle for inferior copies . . . insist on genuine Philco universal parts.

For a program of completeness . . . See Your Philco Distributor Today!

PHILCO® Accessory Division

World-Wide Distribution

Service Parts • Power-Packed Batteries • Universal Components • Long-Life Tubes • Heavy-Duty Rotors • Star-Bright 20/20 Picture Tubes • Long-Distance Antennas • Appliance Parts • Laundry Parts • Universal Parts and Accessories

Here's how to GET MORE WORK OUT OF YOUR Oscilloscope!

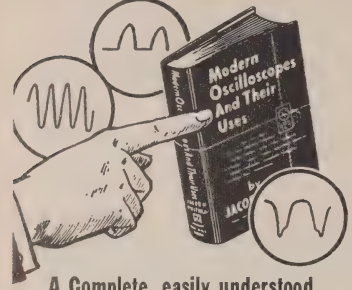

A Complete, easily understood guide to using the handiest service instrument of them all

MODERN OSCILLOSCOPES AND THEIR USES

By Jacob H. Ruiter, Jr.

Enlarged 2nd Edition

. . . contains the latest data . . . everything you need to know about 'scopes!

MORE THAN 30 NEW PICTURES

. . . plus 50 more pages on use of 'scopes in Color TV servicing . . . Industrial Electronics . . . Teaching . . . even in Atomic Energy work.

Oscilloscopes are gold mines for servicemen who learn to use them fast, fully and accurately on all types of work—and here is a new, enlarged 2nd edition of THE BOOK THAT REALLY SHOWS YOU HOW.

In clear, easily understood terms, it teaches you when, where and exactly how to use the oscilloscope . . . how to interpret patterns . . . how to use your 'scope to handle tough jobs easier, faster, and better.

It contains no involved mathematics — no complicated discussions. Instead, it gets right down to "brass tacks" in explaining how oscilloscopes operate. Then you learn exactly how to use them in lab work and on all types of AM, FM and television service—from locating troubles to handling tough realignment jobs.

'SCOPES ARE "GOLD MINES"

when you learn to use them right!

Each operation is explained step by step. You learn to determine just where and how to use the 'scope on specific jobs; how to make connections and adjust circuit components; how to set the controls; and HOW TO ANALYZE OSCILLOSCOPE PATTERNS fast and accurately.

370 illustrations including dozens of pattern photos make things doubly clear.

No other type of specific service training can mean so much to you in boosting your efficiency and earning power! Send coupon NOW for 10-day examination!

'SCOPE EXPERTS get better jobs . . . bigger pay!

PRACTICE 10 DAYS—FREE!

Dept. RE-118, RINEHART & Co., Inc.
232 Madison Ave., New York 16, N.Y.

Send MODERN OSCILLOSCOPES AND THEIR USES for 10-day FREE EXAMINATION. If book is satisfactory, I will then send you $6.50 (plus postage) promptly in full payment. If not, I will return book postpaid in good condition and owe you nothing. (SAVE! Send $6.50 cash with order and we pay postage. Same return privilege with money refunded.)

NAME .....

ADDRESS .....

CITY, ZONE, STATE .....

OUTSIDE U.S.A. $7.00 cash only. Money back if you return book within 10 days.

of which ITTA is not a member. Mr. Tesky indicated that all questions had been answered to his satisfaction.

KESCO MEET

Thirty-three papers on technical and business subjects were read and exhibits of 23 manufacturers, distributors, broadcast stations and electronic organizations were on view at the Keystone Electronic Service Conference and Exhibition held in Pittsburgh Sept. 10–13. Technical subjects accounted for 24 of the papers; 9 were on business management and practices.

Among the outstanding addresses was that of Dr. Ellsworth D. Cook, of General Electric, who discussed "The Economic and Technical Aspects of Industrial Electronics." Six others papers dealt with industrial electronics, the leading subject at two of the convention sessions.

The meetings were held in Carnegie Hall, and more than one visitor alternated between the electronic exhibits and those in the Carnegie Museum. The meeting terminated in a banquet in the Webster Hall Hotel, attended by 150 people. Total registrations at the meeting exceeded 450.

FIRST STATE LICENSE LAW

Louisiana became the first state to have a TV–radio technician licensing law when its State Legislature passed a watered-down version of a bill which was backed by most of the state's organized technicians. Amendments added to the bill on the House floor limited the licensing to cities of 20,000 population or more and gave three seats on the state licensing board to the International Brotherhood of Electrical Workers.

As finally passed, the law will apply to technicians in seven cities and provides that technicians must take an examination and be licensed by the State Radio & Television Technicians Board. Besides three union representatives, it will have eight members representing the servicing industry.

APPRENTICE PLAN STUDIED

To help assure a steady supply of competent trained service technicians and a standardized pay scale, the Radio–Television Association of Santa Clara Valley (RTASCV) has taken the first steps toward institution of an apprenticeship program.

President Richard J. Kelso named Al Limberatos to head an apprenticeship study committee to meet with state officials on the issue. Charles R. Mulkey, RTASCV educational advisor and electronics coordinator of the San Jose Unified School District, is adviser to the committee.

The apprenticeship program would be a form of on-the-job training involving up to 40 hours a week of practical paid shop work coupled with school training. Employers would pay a stand-

Let Electronics Serve The Family

Perma-Power Garage Door Opener

RADIO CONTROLLED

Just press the dashboard button . . . the garage door opens and the light goes on. Press again to close and lock securely. It protects at night and during bad weather. Any member of your family can open or close the door, as easy as ringing a bell . . . and from the comfort of your car.

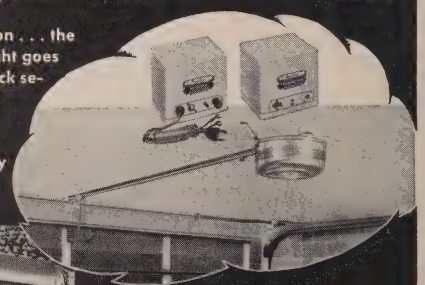

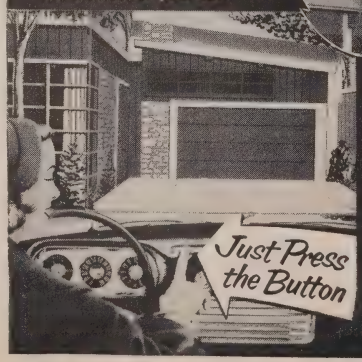

Perma-Power FEATURES:

- ★ ASSURED RELIABILITY
- ★ One year guarantee
- ★ Meets F.C.C. Requirements
- ★ Easy installation with illustrated instructions
- ★ Completely automatic safety devices
- ★ Operates from over 100 ft.
- ★ Low cost; complete package
- ★ BUY NOW!

Perma-Power COMPANY

3100 N. ELSTON AVE. CHICAGO 18, ILLINOIS

Manufacturers of Electronic Equipment Since 1928

ard wage to apprentices for their work in the shop, but not for school time. According to Mulkey, the program would funnel more trained men into the TV–radio service industry, and, because minimum wages would be standardized for apprentices and journeymen, it would tend to "stabilize the industry locally by setting up a pay scale that reflects local conditions."

WAR DECLARED ON GYPS

Acting swiftly following front-page stories on "TV repair cheats" in the *Los Angeles Mirror News* (RADIO-ELECTRONICS, September, 1958, page 126), the Los Angeles County Television Servicemen's Association launched a drive "to police out of existence those who reflect on the integrity of the entire industry by fleecing the public."

The first step in the campaign was a mass meeting attended by more than 250 independent technicians to draft a code of ethics which binds association members to "perform only work that needs to be done, to sell only quality parts and to collect only a fair charge for their labor."

The meeting was addressed by William Snelling of the Better Business Bureau.

The *Mirror-News* series stirred up plenty of controversy among technicians. A letter to the editor by Howard Bogue, secretary of the Board of Delegates of the California State Electronics Association (CSEA), praised the newspaper for stressing that the vast majority of technicians are ethical, while at least one other letter accused the paper of maligning technicians for the sake of sensationalism.

GLADU HEADS R.I. GROUP

The newly elected officers of the Electronic Dealers of Rhode Island are: Norman F. Gladu, East Providence, president; Donald DiBiaso, Providence, vice president; Len Erickson, East Providence, secretary; Ray Cohen, Providence, corresponding secretary and Ben Lauretti, Lonsdale, treasurer.

TSA'S HOSPITAL PROJECT

A community service that paid off in goodwill and personal satisfaction will be repeated as a continuing project by the Television Service Association (TSA) of Detroit. Technicians from 10 member organizations repaired all inoperative TV sets at the Veterans Memorial Hospital without charge. The entire job was accomplished in about 2 hours.

TSA received a special commendation from the hospital administration, and, as noted in *TSA News*, "after going through the corridors and various wards, the men agreed that the satisfaction derived was far greater than the small amount of time expended and that they would be happy to volunteer again."

Hearing of the project, Tung-Sol Electric Co. offered to furnish all circuit and picture tubes needed at the hospital. END

NO OTHER TUBE TESTER MADE-
AT ANY PRICE-can MATCH the VALUE of
the CENTURY
FAST-CHECK

SIZE:
H: 11¼"
W: 14⅝"
D: 4⅜"

Model FC-2—housed in rugged oak carrying case complete with CRT adapter . . . only

Guaranteed for One Full Year
$69.50 Net

20,000 SERVICEMEN CAN'T BE WRONG!

See for yourself—AT NO RISK—why over 20,000 servicemen selected the FAST-CHECK above all other tube testers—regardless of price. With the FAST-CHECK you will make every call pay extra dividends by merely showing your customer the actual condition and life expectancy of the tube. The extra tubes you will sell each day will pay for the FAST-CHECK in a very short time.

Special compartment accommodates line cord and Picture Tube Test Adapter

PICTURE TUBE TEST ADAPTER INCLUDED WITH FAST-CHECK

Enables you to check all picture tubes (including the new short-neck 110 degree type) for cathode emission, shorts and life expectancy . . . also to rejuvenate weak picture tubes. This feature eliminates the need of carrying extra instruments and makes the FC-2 truly an all-around tube tester.

FAST-CHECK'S low price is made possible because you are buying direct from the manufacturer.

Just 2 settings on the
FAST-CHECK TUBE TESTER
tests over 650 tube types completely, accurately — AND IN SECONDS!

- POSITIVELY CANNOT BECOME OBSOLETE
  Circuitry is engineered to accommodate all future tube types as they come out. New tube listings are furnished periodically at no cost.
- NO TIME CONSUMING MULTIPLE SWITCHING
  Only two settings are required instead of banks of switches on conventional testers.
- NO ANNOYING ROLL CHART CHECKING
  Tube chart listing over 650 tube types is conveniently located inside FAST-CHECK cover. New tube listings are easily added without costly roll chart replacement.

COMPARE FAST-CHECK WITH OTHER TESTERS RANGING FROM $40 TO $200

RANGE OF OPERATION

√ Checks quality of over 650 tube types, which cover more than 99% of all tubes in use today, including the newest series-string TV tubes, auto 12 plate-volt tubes, OZ4s, magic eye tubes, gas regulators, special purpose hi-fi tubes and even foreign tubes.
√ Checks for inter-element shorts and leakage.
√ Checks for gas content.
√ Checks for life-expectancy.

IMPORTANT FEATURES

● Checks each section of multi-section tubes and if only one section is defective the tube will read "Bad" on the meter scale ● Less than 10 seconds required to test any tube ● 41 long lasting phosphor-bronze tube sockets accommodate all present and future tube types . . . cannot become obsolete ● 7-pin and 9-pin straighteners mounted on panel ● Large D'Arsonval type meter is extremely sensitive yet rugged — fully protected against accidental burn-out ● Special scale on meter for low current tubes ● New tube listings furnished periodically at no cost ● Compensation for line voltage variation.

Other testers may have some of the above features . . . but only the FAST-CHECK has them all!

SHIPPED ON APPROVAL FOR 10 DAY FREE TRIAL

Try the FC-2 before you buy it! No obligation to buy.

PAY IN SMALL MONTHLY PAYMENTS

Easy to buy if you're satisfied. Pay at net cash price . . . no financing charges.

NO MONEY REQUIRED WITH ORDER . . .

CENTURY ELECTRONICS CO., INC.
Dept. 111, 111 Roosevelt Ave., Mineola, N. Y.

Rush the FAST-CHECK for a 10 day trial period. If not completely satisfied I will return the instrument within 10 days without further obligation. If fully satisfied I agree to pay the down payment within 10 days and the monthly installments as shown. No financing charges are to be added.

Model FC-2 . . . $69.50 — Pay $14.50 within 10 days. Balance $11.00 monthly for 5 months.

Name.....
Address.....
City..... State.....
F.O.B., Mineola, N.Y.

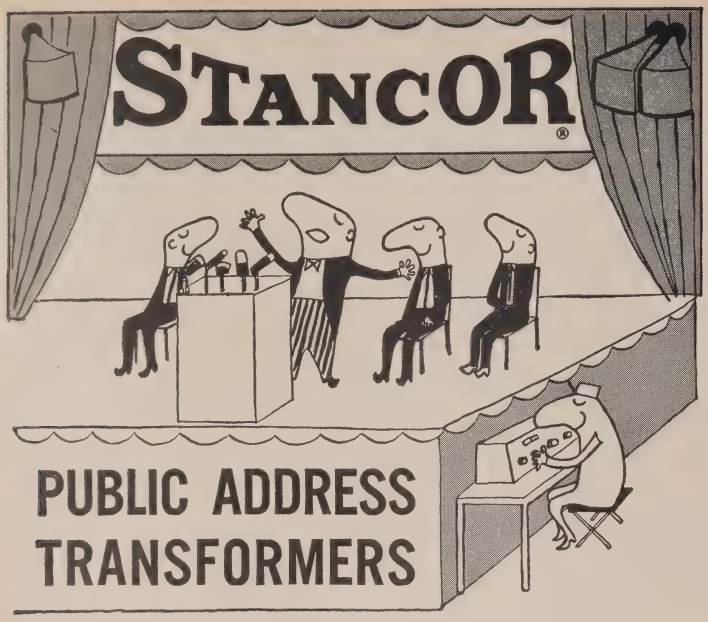

The **MOST COMPLETE LINE** *in the industry*

For all your public address needs, STANCOR offers your widest choice of transformer types and ratings:

- ✻ 25 Volt Line to Voice Coil
- ✻ 70.7 Volt Line to Voice Coil
- ✻ 140 Volt Line to Voice Coil
- ✻ Intercom and Transceiver
- ✻ Microphone to Grid or Line
- ✻ High Fidelity Output

FREE: STANCOR's General transformer catalog listing 700 transformers including over 200 units for public address use. See your STANCOR distributor or write Chicago Standard for your copy.

CHICAGO STANDARD TRANSFORMER CORPORATION
3509 ADDISON STREET • CHICAGO 18, ILLINOIS

SERVICE MEN KNOW THERE IS JUST ONE

HUSH
Reg. U. S. Pat. Off.
Chemically engineered for tuners and switching mechanism

Hush comes in a 6 oz. pressure can with sufficient pressure to reach all contacts to wash-away that dirt, leaving clean and positive contacts, protected with a lasting lubricant film.
Hush also available in 2 oz. 8 oz. and 32 oz. containers. **$2.25 net**

EVER-QUIET
Reg. U. S. Pat. Off.®
Since 1949 the Original Volume Control and Contact Restorer

EVER-QUIET is a free-flowing liquid that leaves no powder residue. Scientifically designed to seep around the shaft and penetrate the control or potentiometer, cleaning and contact, and leaving a safe protecting film. Harmless to metals, wire or carbon. Will not affect inductance, capacitance or resistance.

2 oz. bottle with handy dispenser (32 oz. size available) **79c net**

See your distributor or write to

CHEMICAL ELECTRONIC ENGINEERING, INC. Matawan, New Jersey

NEW TUBES and SEMI-CONDUCTORS

FEATURED this month is a tiny photojunction cell, about the size of a pencil eraser. A line of 50-amp Zener diodes, two medium-power transistors and a high-frequency alloy-junction silicon transistor round out the month's releases.

7224

Less than a ½ inch high (excluding leads), this photojunction cell is of the side-on type. It uses a germanium p-n alloy junction and is intended for sound

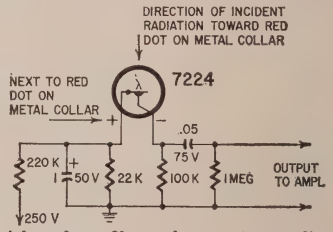

pickup from film and computer applications. Signal output is approximately proportional to the intensity of the incident radiation. The diagram shows a typical circuit using this unit.

Other design features include an illumination sensitivity of 0.7 μa per foot-candle and a power-dissipation capability of .030 watt. Spectral response of the 7224 covers the range from about 3,500 to nearly 19,000 angstroms. Maximum response is at about 15,000 angstroms. Therefore, it has high sensitivity to red and infrared radiation as well as good response over the visible portion of the spectrum. The 7224 photojunction cell is made by RCA.

50M10Z–50M200Z

These 50-watt Zener diodes have a voltage drop that is essentially independent of current and are designed for optimum performance over a wide range of conditions. The large power-handling capability and low Zener impedance of these units permit reducing circuit complexity of regulated power supplies, especially those using transistors.

Zener voltages range from 10–200 in 40 steps. The number after 50M tells you the Zener voltage of the particular Motorola unit. You have a choice of anode or cathode connected to the diode

RCA INSTITUTES OFFERS YOU THE FINEST OF HOME STUDY TRAINING

The equipment illustrated and text material you get with each course is yours to keep. Practical work with very first lesson. Courses for the beginner and the advanced student. Pay-as-you-learn. You need pay for only one study group at a time.

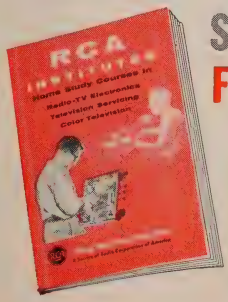

SEND FOR THIS FREE BOOK NOW

Resident School courses in New York City offer comprehensive training in Television and Electronics. Day and evening classes start four times each year. Detailed information on request.

RCA Institutes, Inc. Home Study Dept. **RE-118**
A Service of Radio Corporation of America
350 West Fourth Street, New York 14, N. Y.

Without obligation, send me FREE 52 page CATALOG on Home Study Courses in Radio, Television and Color TV. No Salesman will call.

Name.....
Please print

Address.....

City.....Zone....State.....

Korean Vets! Enter discharge date_____

CANADIANS—Take advantage of these same RCA courses at no additional cost. No postage, no customs, no delay. Send coupon to:

RCA VICTOR COMPANY, LTD.
5001 Cote de Liesse Rd., Montreal 9, Que.

To save time, paste coupon on postcard

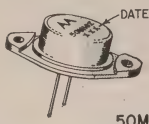

50M10Z TO
50M200Z

RED DOT, CATHODE
BLACK DOT, ANODE
CONNECTED TO CASE

base. Both pins connect to the same end of the diode (cathode or anode). The suffix R indicates cathode to base. Maximum Zener current runs from 4.3 amps for the 50M10Z to 200 ma for the 50M200Z.

If these units are used with a socket, the unregulated line should feed into one pin through a suitable current-limiting resistor and the load should be connected to the other pin. This will break the circuit to the load when the unit is removed.

2N413

A p-n-p alloy junction transistor designed and tested for use in high-frequency amplifier applications up to 3 mc. The case has a welded hermetic seal and a standard basing design which facilitates automatic mounting with printed circuits.

Maximum ratings of this Tung-Sol transistor at 25°C are:

V_{CBO}	30
V_{EBO}	20
V_{CEO}	18
V_{CE} (V_{BE} =0.1)	25
I_C (dc) (ma)	200
I_C (peak) (ma)	400

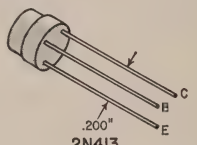

2N413

Design-center characteristics of the 2N413 are:

I_{CBO} (μa)	2 (V_{CB} =6, I_E =1 ma, f=1 kc)
h_{ib} (ohms)	25 (V_{CB} =6, I_E =1 ma, f=1 kc)
h_{fe}	30 (V_{CE} =6)
f_{ab} (mc)	2.5 (V_{CB} =6, I_E =1 ma, f=1 kc)
NF (db)	7 (V_{CE} =6, f=1.5 mc)
G_p (db)	10 (V_{CE} =6, f=1.5 mc)

2N551, 2N552

These two n-p-n silicon transistors are designed for medium-power switching and amplifying applications. These uses include output stages, servomotor

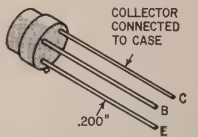

2N551, 2N552

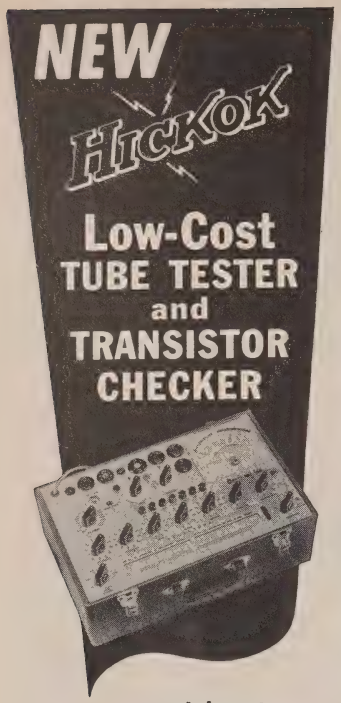

Model 800

NEW LEAKAGE AND SHORTS TEST—Checks leakage between tube elements up to 10 megohms.

INCLUDES TRANSISTOR AND DIODE CHECK

HIGH SPEED SERIES-STRING TEST—A new filament continuity test is provided to greatly speed the testing of series-string tubes.

METER REVERSE—A push-button control reverses the meter for testing special tubes such as the 117N7 types.

TUBE SOCKETS—4, 5, 6, 7-pin, octal, loctal, noval and 7-pin miniature. Top cap jacks are built into the panel and leads are included.

MICROMHO SCALES—Hickok Mutual Conductance circuits test tubes under simulated operating conditions and accurately evaluate all popular tubes encountered in electronic work. 0–3,000, 6,000, 15,000 micromhos are directly indicated on the meter dial.

COMPLETE, ACCURATE TEST—A new grid current (gas) test is very sensitive and will indicate even the slightest amount of gas.

BUILT-IN ROLL CHART—A time saving tube reference chart contains test data for all popular tubes in a new, faster-to-use group system.

The 800 will pay for itself in a short time . . . and give you many years of accurate, dependable service. **$159.50 NET**

Now is the time to...
TRADE UP TO A HICKOK

Ask for a demonstration of the new 800 from your Authorized Hickok Distributor.

THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Ave. • Cleveland 8, Ohio

ERIE

D-58 CATALOG
at your
Authorized
ERIE DISTRIBUTOR

The new ERIE D-58 Catalog, including the complete and enlarged line of ERIE Electronic Components is ready. Your authorized ERIE Distributor has a copy for you. If he can't supply you, write us, giving his name.

Make the ERIE Catalog
Your Catalog

ERIE *Electronics Distributor*
DIVISION
ERIE RESISTOR CORPORATION
ERIE, PA.

control, dc-to-dc converters, solenoid operation and medium-power oscillators.

Maximum ratings of these Transistron units are:

	2N551	2N552
V CE	60	30
V CB	60	30
V EB	10	10
P total (watts)		
at 100°C (case)	5	5
200°C (case)	0.5	0.5
100°C (amb)	0.6	0.6
200°C (amb)	.05	.05

Typical characteristics at 25°C are:

h FE 30 (IC =50 ma., VCE =6)
h fe 3 (VCB =20, I E =50 ma, f=1 mc)

IN1569, IN1570, IN1571, IN1572

A group of lead-mounted, axial, diffused-junction silicon rectifiers. All units handle 1 amp average half-wave rectified forward current at 25°C. This drops to 0.5 amp at 100°C. Peak half-cycle forward surge current (60 cycles, 25°C ambient) is 70 amps and peak recurrent forward current is 10 amps, again for all units. The cathode is connected to the case.

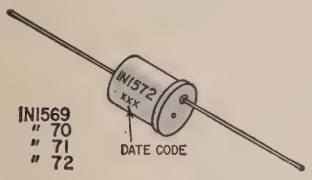

Voltage ratings of these Motorola rectifiers are:

	IN1569	-70	71	-72
Max continuous dc inverse	100	200	300	400
Max peak inverse	100	200	300	400
Max sine-wave rms input	71	141	212	283

Others

Power transistors capable of handling 65 watts and 13 amps were announced by Clevite Corp. Identified as CTP 1511, 1512, 1513 and 1514, all are germanium p-n-p types and are available with solder lugs for easy wiring.

Bell Telephone Labs has introduced a high-speed diffused silicon switching diode, the 1N696. It has a switching time of about 1 millimicrosecond. Diffusion techniques play a large part in making this possible.

SF (*Semi-Flat*) extra-short picture tubes have been released by Philco. They are the 17DAP4/SF17, a 17-inch rectangular tube which is 11 inches long, and the 21EAP4/SF21A, a 21-inch rectangular tube less than 13 inches long.

A Sensistor temperature probe was announced by Texas Instruments. This solid-state unit is made from a silicon crystal and has a positive temperature coefficient that results in a constant rate of change on the order of 0.7% per °C. END

STAMP OF APPROVAL! QUIETROLE

Only Known Merit marks a product as the "BEST"

. . . for quieting Noisy Controls and Switches QUIETROLE produces results superior to any other product. That's why it's known as the "Best" and that's why more users prefer it to any other . . . It's the dependable Original product of its kind . . . a first in the Industry.

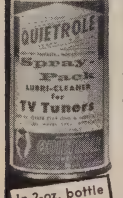

QUIETROLE Spray-Pack

or the QUIETROLE Bottle with the Eye Dropper Cap

QUIETROLE offers you both types of containers. Either way assures you of the same unfailing results that QUIETROLE is known for.

In 2-oz. bottle with dropper and 6-oz. QUIETROLE SPRAY-PACK

The *Lubricant Cleaner of the Electronic World.* Tailored for the industry by over 15 years of authentic research, plus 4 years of rigid and exacting tests before marketing.

Ask for QUIETROLE and be sure you get it!

manufactured by
QUIETROLE COMPANY
Spartanburg, South Carolina

NEW—Examine FREE

TRANSISTOR PHYSICS & CIRCUITS

by Riddle and Ristenball, Sr. Engineers, Haller, Raymond and Brown

Fills long-standing professional needs of electronics engineers and technicians by providing thorough grounding in transistor circuit theory and practice in the most straight-forward, direct way. Far more than just a "handbook" or "primer" it manages the tough job of combining simplicity of explanation with full technical fidelity.

Over 200 Topics—628 Information-Packed Pages

Divided into two main sections; physical operation of transistors and basic circuit theory of transistors . . . all material explained in terms of familiar principles with wide use of diagrams to aid visualization. Text includes special "brush-up" section on physics and electrical principles. Only one set of equations is needed for any type of transistor amplifier, grounded base, grounded emitter, and grounded collector with or without feedback. Math requirements: high school algebra and trigonometry. **Contents include** extensive coverage of: Semiconductors, Transistor types, Small Signal Amplifiers, Power Amplifiers, The Transistor as a circuit element, Cascade Amplifiers, Feedback, Bias Stability and Direct Current Amplifiers, Transistor Oscillators and Multivibrators.

SEND NO MONEY

Simply mail the coupon for your copy of this valuable book. Read it over for 10 days at our expense. See how quickly and enjoyably the subject can be mastered. Then, and only then, mail us your check. Otherwise, return the book and owe nothing.

Prentice-Hall, Inc., Dept. 5744-P1
Englewood Cliffs, N.J.

Send me TRANSISTOR PHYSICS AND CIRCUITS for 10 days' FREE examination. At the end of that time I'll either remit $10.00, plus small postage, or return the book and owe nothing.

Name.....

Address.....

City.....Zone.....State.....

SAVE! Send $10.00 now and we'll pay postage. Refund and return privilege guaranteed.

NEW HICKOK Low-Price PORTABLE CARDMATIC TUBE TESTER

121

Fully Automatic

Tests any tube in 8 to 12 seconds . . . including handling of tube test data card.

Here is the new, low cost version of the famous Hickok Cardmatic so popular with leading lab engineers. Especially designed for high speed service work, this new 121 is high quality in a lightweight portable . . . and the price is low, too.

The Hickok Cardmatic switch sets up all tests automatically and eliminates fussing around with adjustments. You can accurately check a tube for dynamic mutual conductance, controlled emission, cutoff point "Knee" point, shorts, leakage, gas and voltage drop . . . and rectifier tubes at their rated loads. Any way you look at it, this new automatic tube testing machine will be helpful to you in your work. It will pay for itself in a very short time ...and give you many years of accurate dependable service.

$249.50 NET (includes 800 cards)

Now is the time to . . .
TRADE UP TO A HICKOK

Ask for a demonstration of the new 121 or write for descriptive literature.

THE HICKOK ELECTRICAL INSTRUMENT CO.
Dupont Ave. • Cleveland 8, Ohio

FAST! ACCURATE!

SECO Test Equipment

Saves time . . . makes more money for you!

WRITE TODAY FOR COMPLETE SPECIFICATIONS AND FEATURES!

- Outstanding Reliability and Performance!
- Unique, Time-Saving Features!
- Low First Cost Makes You Money From the Start!

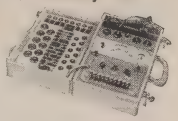

107 TUBE TESTER—Outstanding performance and accuracy—provides 3 important tests: amplifier types tested for gain by Dynamic Mutual Conductance method—power types tested for cathode current by Cathode Emission method—all types tested for shorts and grid error by Grid Circuit Test developed and patented by Seco. Dynamic Mutual Conductance Test pre-wired to eliminate elaborate set-up. Cathode Emission Test done by free point pin-selector method—will not be obsoleted. Completely self-contained in portable carrying case. Furnished with handy flip chart for fast tube set-up data.
MODEL 107 ..... **$139.50 NET**

GCT-8 GRID CIRCUIT TUBE TESTER—Perfect companion to any tester—checks critical "control grid" condition of vacuum tubes fast, accurately. Electron eye tube indicates faults at a glance. As many as eleven simultaneous checks—automatically.
MODEL GCT-8—Kit ..... **$19.95 NET**
MODEL GCT-B—Wired & tested.. **29.95 NET**

208VTVM—"Foolproof"—many new features! Easy-to-read 4½" 200 microamp meter mounted on sloping panel—7 DC, 7 AC, 7 ordinary Ohm ranges, plus RETMA (EIA) Ohm scale to check standard color-coded resistance values and tolerance limits. Specially designed "shift-lever" type function switch identifies and automatically connects proper probe. With stand, 40" leads, and common lead with clip.
MODEL 208 ..... **$74.50 NET**
Leather, felt-lined carrying case. **$9.95 NET**

PS-2 BATTERY ELIMINATOR—Compact unit takes place of battery normally used to operate and service low-powered transistorized equipment. Supplies clean, filtered DC—can't be damaged by a short. Quickly spots faulty batteries by substitution. Output continuously variable from 0 to 15 V.—ideal for experimenters. Complete with jacks, leads, and clips.
MODEL PS-2 ..... **$13.95 NET**

FB-4 FLYBACK CIRCUIT AND INDUCTANCE ANALYZER—Quick "yes" or "no" answer on condition of flyback transformer and yoke—100% accuracy!
MODEL FB-4 ..... **$38.95 NET**

NEW! HC-6 CURRENT CHECKER
Provides positive, on-the-spot method of checking TV horizontal output circuits—fast, accurate way to adjust horizontal drive and linearity. Easy to use—can be placed in circuit in seconds—compact size. Complete, ready to use.
MODEL HC-6 ..... **$12.95 NET**

Get the complete story on Seco's exciting line of test equipment. See your distributor—or write for complete information today!

SECO MANUFACTURING CO.
5015 Penn Avenue So.
Minneapolis, Minn.

Technotes

MOTOROLA TS-118A

Symptom: erratic sync.

Cause: the .005-μf coupling capacitor which feeds the composite sync signal

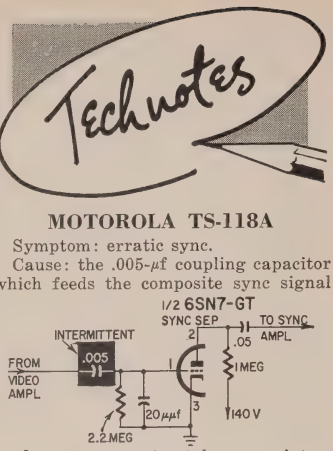

to the sync separator tube opens intermittently. Obviously, the result is no sync whenever the capacitor opens. Replace with a molded 600-volt unit.—*J. R. Vought*

PIX TUBE OPENS

It's easy enough to check for a short or leakage on the grid or cathode of a picture tube, but opens are another story. Here's one way to check for them.

While the picture tube heater is hot, pull its socket off and put an ohmmeter across the cathode and grid (pins 2 and 11), with the positive probe to the grid. A fairly low resistance reading should result. If the prods are now reversed, the meter should read infinity. The cathode and grid are being used as a diode, through which a small conduction current will flow when the ohmmeter applies a small positive voltage to the "plate."—*R. C. Eldridge*

G-E 21T20

Complaint: intermittent horizontal jitter, occurring on strong stations and more pronounced in the evening.

Fault: loss of capacitance in agc filter C320, a 1-μf electrolytic with positive ground to chassis. Value of the defective unit had gone down to .02 μf.

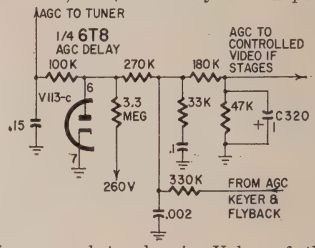

How it happened: spurious modulation of the if signal in the first and second if stages by sync pulses on the agc line. C320 normally smooths these pulses.—*E. A. Chung*

ZENITH 19Y22

The complaint was intermittent raster trouble with no high voltage. Visual inspection showed that the damper tube

NOW 2 ASSEMBLE-IT-YOURSELF Schober ELECTRONIC ORGANS

SAVE HALF
NO SPECIAL SKILLS
PAY KIT-BY-KIT

Now you can afford an electronic organ. Whether you choose the full Concert model or the smaller Consolette, you have an organ equal to any made by the foremost manufacturers. In addition, you save over ½ the cost because you assemble it yourself...and you enjoy the thrill of achievement. Too, you purchase each kit only when you are ready for it.

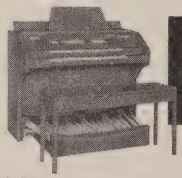

2 different MODELS
2 different SIZES
2 different PRICES

CONCERT MODEL
- ☆ TWO FULL SIZE PIPE-ORGAN MANUALS, 122 KEYS
- ☆ OCCUPIES 3'5" x 4'7" FLOOR SPACE
- ☆ 26 STOPS AND COUPLERS
- ☆ 32 BASS PEDALS
- ☆ ASSEMBLED CONSOLE
- ☆ CONFORMS TO AMERICAN GUILD OF ORGANISTS SPECIFICATIONS FOR PIPE ORGANS
- ☆ COMPLETE STEP-BY-STEP INSTRUCTIONS

CONSOLETTE MODEL
- ☆ OCCUPIES ONLY 2' x 3'2" FLOOR SPACE
- ☆ TWO FULL SIZE PIPE-ORGAN MANUALS, 122 KEYS
- ☆ 22 STOPS — ABOVE-KEYBOARD TABS
- ☆ 13 HEEL-AND-TOE BASS PEDALS
- ☆ 7 FULL OCTAVES OF TONE (DOWN TO 32 CPS)
- ☆ BUILT-IN SPEAKERS OPTIONAL
- ☆ ASSEMBLED CONSOLE
- ☆ COMPLETE STEP-BY-STEP INSTRUCTIONS

10" LP RECORD DEMONSTRATING BOTH MODELS AVAILABLE FOR $2, REFUNDABLE UPON PURCHASE

FREE NEW 1959 EDITION OF 16 PAGE ILLUSTRATED BOOKLET ON REQUEST

Write Now — See What Fine Instruments You Get At Such Great Savings

The SCHOBER ORGAN Corporation • 2248-B BROADWAY • NEW YORK 24, N.Y.

SCHOBER KITS ALL OVER THE WORLD

☆ Designed by Richard H. Dorf.

would sometimes turn red.

The trouble was traced to the horizontal section of the yoke, which was shorting intermittently to the width control, a brass sleeve mounted on the neck of the picture tube. Pulling the sleeve farther out from the yoke cured the trouble without affecting the width. —*G. P. Oberto*

MONTGOMERY-WARD MODEL GSE5010A

This set developed critical horizontal hold which could be alleviated slightly by tube substitution. The slug of the ringing coil is used as the horizontal-

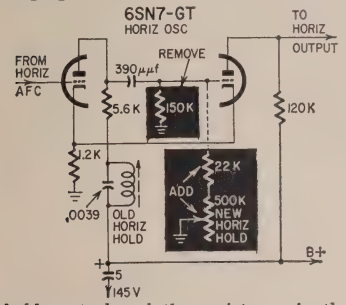

hold control and the resistance in the multivibrator grid circuit is fixed.

As the partial schematic shows, the 150,000-ohm grid resistor was removed and a 500,000-ohm pot in series with a 22,000-ohm resistor installed in its place. Adjusting this pot provided the necessary range for the horizontal-hold control.—*Lucian Palmer*

DUMONT RA-112

Weak sound in these sets sometimes has a strange cause. A length of ribbon line is used as a small fixed capacitor (2.5 μμf) to couple the sound if to the video if. One wire of the line is connected to the sound if while the other is connected to the video if, thus forming the necessary capacitance.

Severe audio attenuation may result if this line is dressed too close to the chassis or the if transformer cans which are grounded to the chassis. For weak sound in these receivers check the lead dress before spending time examining the audio circuits. It could save you a lot of work.—*Alfred Roberts*

USE A FUSED PLUG

Whenever we get a job that calls for replacing the set's power transformer, we always make it a point to include a fused plug along with the chassis on delivery. A customer finds it hard to tolerate an unrelated breakdown in a set, but will never forgive a "looks like the same thing" breakdown.

We find it much simpler to fuse the line than to try to explain another transformer job or other major overhauling because some filter capacitor decides to pop or a 5U4 shorts out.—*Frank A. Salerno*

END

Introducing the "new" BENCO UNIVERSAL AMPLIFYING SYSTEM

37 db gain. 75 or 300 ohm input, dual 75 ohm output. Built in level control, full 6 megacycle bandwidth.

Maximum output — 1 volt.

$31.50*

UNISTRIP

A reliable VHF to VHF converter. Voltage stablized circuit eliminates the need for a quartz crystal.

$85.00*

UNIVERTER V.H.F.

UNIBAND

$51.50*

High gain wide-band Channel 2-13 amplifier. 75 or 300 ohm single input, 75 ohm single output. Minimum gain 37 db, 6 tubes.

UNIPAK

Universal power pack takes up to 3 Unistrips or any combination of Unistrips or Univerters, as well as the Uniband all band amplifier.

Several Unipacks can be combined to take any number of amplifier and converter combinations.

$31.50*

*U.S. Dealer Net

UNIVERTER U.H.F.

A variable UHF to VHF converter. Any UHF to VHF combination can be taken care of. Specify channels.

WANTED U.S. DISTRIBUTORS

MORE U.S. DISTRIBUTORS AND REPRESENTATIVES ARE NOW BEING APPOINTED by Canada's Largest Manufacturer of Master Antenna Equipment. Write to-day for full information.

BENCO TELEVISION ASSOCIATES LTD - 27 Taber Rd., Rexdale, Ontario, Canada

COMPLETE TRAINING
FOR BETTER RADIO-TV SERVICE JOBS

Radio-TV RECEIVER CIRCUITRY and OPERATION
Radio-TV TROUBLESHOOTING and REPAIR
ONLY $13 for the complete 2-volume course
3 MONTHS TO PAY

Let these two world-famous Ghirardi training books teach you to handle all types of AM, FM and TV service jobs by approved **professional methods—and watch your efficiency and earnings soar!**

Completely modern, profusely illustrated and written so you can easily understand every word, these books pave the way to fast, accurate service on any type of home radio-TV-electronic equipment ever made. Each book contains the latest data on the latest methods and equipment —NOT a rehash of old, out-of-date material. Each is co-authored by A. A. Ghirardi whose famous RADIO PHYSICS COURSE and MODERN RADIO SERVICE were, for 20 years, more widely used for military, school and home study training than any other books of their type!

THE NEW Ghirardi
RADIO-TV SERVICE LIBRARY

Almost 1500 pages and over 800 clear illustrations show step-by-step how to handle every phase of modern trouble-shooting and servicing.

1—Radio and Television Receiver
TROUBLESHOOTING & REPAIR

A complete guide to profitable professional methods. For the novice, it is a comprehensive training course. For the experienced serviceman, it is a quick way to "brush up" on specific jobs, to develop improved techniques or to find fast answers to puzzling service problems. Includes invaluable "step-by-step" service charts. 820 pages, 417 illus., price $7.50 separately. See combination offer!

2—Radio and Television Receiver
CIRCUITRY AND OPERATION

This 669-page volume is the ideal guide for servicemen who realize it pays to know what really makes modern radio-TV receivers "tick" and why. Gives a complete understanding of basic circuits and circuit variations; how to recognize them at a glance; how to eliminate guesswork and useless testing in servicing them. 417 illus. Price separately $6.75.

New low price . . . You Save $1.25!

If broken into lesson form and sent to you as a "course," you'd regard these two great books as a bargain at $50 or more! Together, they form a complete modern servicing library to help you work faster, more efficiently and more profitably.

Under this offer you buy them both for only $13.00. You save $1.25 on the price of the two books—and have the privilege of paying in easy installments **while you use them.**

10-DAY FREE TRIAL

Dept. RE-118, RINEHART & CO., Inc.
232 Madison Ave., New York 16, N.Y.

Send book(s) below for 10-day FREE EXAMINATION. In 10 days, I will either remit price indicated (plus postage) or return books postpaid and owe you nothing.

☐ Radio & TV Receiver **TROUBLESHOOTING & REPAIR.** (Price $7.50 separately)

☐ Radio & TV Receiver **CIRCUITRY & OPERATION** (Price $6.75 separately)

☐ **Check here for MONEY-SAVING COMBINATION OFFER . . . Save $1.25.**

Send both of above big books at special price of only $13.00 for the two (Regular price $14.25) . . . you save $1.25. Payable at rate of $4 (plus postage) after 10 days if you decide to keep books and $3 a month thereafter until $13 has been paid.

Name.....

Address.....

City, Zone, State.....

Outside U.S.A.—$8 for TROUBLESHOOTING & REPAIR; $7.25 for CIRCUITRY & OPERATION; $14 for both. Cash with order only, but same 10 return privilege.

NOW.. FOR THE FIRST TIME.. *Ortho-Linearization*

TAILORS SOUND TO FIT YOUR ROOM

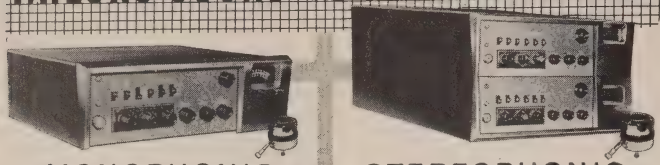

MONOPHONIC STEREOPHONIC

ORPHEON®

FEATURING AAS*

The finest amplifiers are "linear" in the lab, but not in the living room! That's because room acoustics play the most important part in amplifier performance.

Now, for the first time, you can actually tailor the performance of a superb amplifier to suit the acoustics of your room! AAS* — the Acoustical Analyzer System — Precise Development's exclusive new feature accomplishes this amazing feat. And AAS* is found only in the great, new **ORPHEON** amplifier. Using an Acoustical Analyzer Probe, you can actually adjust the low and high frequencies separately to match the mid-range tones, and provide perfect linearity to match the acoustics of your own living room! And once the adjustment is set, the **ORPHEON remains** in balance unless there are major changes of furniture or drapes in the room.

To match the musical tastes of everyone, Precise Developments Inc. provides two versions of the great new **ORPHEON** — one Monophonic, and the other Stereophonic. The **MONOPHONIC ORPHEON** offers 40 watts of undistorted listening pleasure plus every important feature you'd expect to find in a luxury-class amplifier. The **STEREOPHONIC ORPHEON** provides the greatest flexibility ever offered an audiophile. It comprises two systems in a single chassis—each one identical with the monophonic version described above. They may be used together to reproduce brilliant, clean, linear stereophonic sound, or may be used separately to serve two separate areas monophonically with different music . . . or they may be used together as an elaborate mixer for recording.

Before you buy stereo, be sure to hear this great new amplifier concept. It's a revelation of the ultimate in high fidelity engineering!

. . . Just Look At These Amazing Features . . .

- 40 watts monophonic output (peak 80 watts)
- 80 watts stereo output (peak 160 watts)
- Inputs for radio, TV, tape, microphone and magnetic or crystal phono on each system segment
- Tape and monitor outputs on each system segment
- Calibrated Microphonic Acoustical Probe for AAS*, can also be used as public address microphone or for tape recording
- 24 positions of equalization for each system segment
- DC on input filaments
- At least 18 db of bass and treble boost attenuation plus additional 20 db with AAS*
- Volume and Loudness controls on each system segment; 5 mv full output
- Rumble filter • Muting filter
- Output meter reads power output in watts or tape output in volts on each system segment. It is also a Sound-level Meter with AAS*
- Separate tape output level potentiometer on each system segment
- Cathode-follower tape output on each system segment
- Internal grid bias hum control (—80 db for radio, —60 db for phono)

Model STAM80A—40 watt stereo system (160 watt peak, monophonic), with AAS*—factory-wired, complete $289.50
Model STAM40A—20-watt stereo system (80 watt peak, monophonic), with AAS*—factory-wired, complete $249.50

Model ST40—20-watt stereo system (80 watt peak, monaural), without AAS* and Acoustical Probe, factory-wired, complete $189.50
Model AM40A—Monophonic, 40 watts (80 watt peak), with AAS*—factory-wired complete $169.50

*PATENT APPLIED FOR

THE Continental

A superb AM and FM tuner providing matched performance and great beauty. Coupled with variable automatic frequency control and metered output, it brings in the weakest stations and provides razor-sharp selectivity. Rich gold-and-silver trim. Hear the Continental . . . discover how inexpensively you can own one of the finest tuners made today.

FM — 88 to 108 MC; AM — 500 to 1600 KC. Output tuning meter; cathode-follower output; convenience outlet; phono, FM, AM, TV switch and inputs; Foster-Seeley discriminator; flywheel tuning; 2 limiters; Ferri-loop; 3-gang variable condenser; logging scale. 13" x 4¼" x 9¾". Cage at additional cost.

Model TUMK, Kit $49.95
Model TUMW, Factory-wired $69.95

THE Mozart

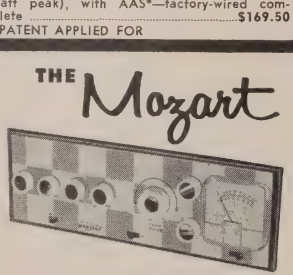

A superb 40-watt amplifier which supports a symphony orchestra with live, crisp, brilliant. distortion-free reproduction.

24 positions of equalization; DC on input tube filaments; Volume or Loudness Control; 5 mv full output; rumble filter; muting switch; convenience outlet; output meter reads power output in watts, tape output in volts; separate and independent tape output level potentiometer; cathode-follower tape output; internal grid bias, grid balance and hum balancing controls (—80 db for radio, —60 db for phono); output selector for different impedance speakers; A-AB-B speaker selector; special patent-pending output transformer; silver-plated, etched-front panel; 10 tubes; fused supply. 13" x 4¼" x 12".

Model AMK, Kit $69.95
Model AMW, Factory-wired $89.95

The Greatest In. TEST INSTRUMENTS

. . . that's the opinion of leading electronic engineers, radio service people and amateur radio enthusiasts. And Precise has achieved this reputation, too, because of its efforts to bring you the best possible equipment at the lowest possible prices. You can depend on Precise for quality — based upon ingenuity, originality, and production "know-how."

Mutual Conductance and Emission

TUBE TESTER

Here is a tester that actually checks a tube for its application, not whether it is just good or bad. GM and emission are checked separately. It is the first and only device that measures 600-mil tubes on a meter. Sweeps from 0 through the normal testing range when making measurements to give an average evaluation of the tube over an extended range of operation. Selected for use by the United States Department of Standards.

MODEL 111K, Kit, $79.95; MODEL 111W, Factory-wired $139.95

Precise Development's

POWER-LAB

A single instrument that takes the place of eleven pieces of equipment. Operates as A BATTERY ELIMINATOR, BATTERY CHARGER, HIGH CURRENT (20-AMP.) LINE VOLTAGE VARIAC, AC LINE VOLTAGE METER, AC LINE AMMETER, AC LINE WATTMETER, AC LINE ISOLATION TRANSFORMER, LOW-VOLTAGE HIGH-CURRENT AC SUPPLY, DC LINE VOLTAGE VARIABLE SUPPLY, DC HIGH CURRENT AMMETER, AGC BIAS BOX. Large, **professional** meter—it's fantastic — and what a value! With 100 watts of isolation: MODEL 711, kit, **$49.95**; MODEL 711W, Factory-wired, **$64.95**. With 300 watts of isolation: MODEL 713K, Kit, **$62.95**; MODEL 713W, Factory-wired $79.95

Printed-Circuit, Voltage-Regulated, Peak-to-Peak

VTVM

With Tilting Meter Movement and Magic Lead Switch

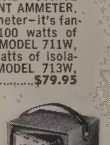

Here's another all-new Precise-engineered instrument, designed with you in mind . . . to make it easier and more convenient as you test. All-new features include voltage regulation, printed circuitry, etched front panel **PLUS** the exclusive Meter Movement Tilt that permits you to turn the meter to face eye-level, no matter where you place the instrument on the bench . . . **AND** the Magic Lead Switch that permits you to short and open leads **automatically** for zero or infinite adjust without removing the leads from the circuit under test! MODEL 904K, Kit, **$34.95**; MODEL 904W, Factory-wired, **$49.95**

Precise Development's

COLOR TV OSCILLOSCOPE

No other oscilloscope at **any** price, high or low, offers so many desired features! Providing a big 7-inch tube, this fabulous instrument is designed to help you solve any color TV problem. It contains low-loss components and has an over-designed fused power supply for additional circuitry. You'll find such special features as a Sweep Magnifier, Triggered Sweep Sync Amplifier, Differential Inputs, Gated and Saw-tooth Outputs, etc. This amazing new scope is the result of over 12,000 hours of engineering. It **shows** more, **tells** more and **gives** more than all other commercial scopes. MODEL 300K, Kit, **$99.95**; MODEL 300W, Factory-wired $199.50

WRITE FOR FREE CATALOG

precise DEVELOPMENT CORPORATION • OCEANSIDE, N. Y.
Cable Address: CHURCHIN

On the Market

RECORDER-HEAD CLEANER, *Kleen-Tape.* Specially impregnated fabric tape on standard recorder reel cleans heads in 2 minutes without tools. When

"played," it dissolves and removes oxide accumulation and picks up dust and other foreign materials. Reusable. — **Walsco Electronics Manufacturing Co.,** 100 W. Green St., Rockford, Ill.

STEREO CONVERSION KITS. *Model CK-2,* complete record-changer replacement, including stereo cartridge with diamond/sapphire styli. *Model SA-2,* speaker–amplifier unit in mahogany-grained table cabinet. *Model SH-3,* amplifier and 3-speaker sound system in console cabinet. *Model SK-2,* modification parts kit including stereo cartridge with diamond/sapphire styli. *Model AK-1,* ac–dc dual-channel amplifier.—**RCA Victor Radio & "Victrola" Div.,** Camden, N.J.

STEREO TAPE DECK, *Telectro series 900.* Records and plays back stereo with 4-track head which accommodates both 2- and 4-channel stereo tapes and 2-track monaural tapes. Pushbutton controls. 3 speeds. Separate record and playback heads for simultaneous monitoring. Flutter and wow less than 0.25%. Signal-to-noise ratio better than 50 db. Response 40–15,000 cycles at 7½ ips, 40–12,000 at 3¾, 40–6,000 at 1⅞. May be mounted vertically or horizontally. Matching record and playback preamps available. — **Telectrosonic Corp.,** 35-18 37 St., Long Island City, N. Y.

STEREO CARTRIDGE, *series RG745.* Magnetic turnover type.

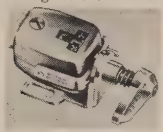

RG745-1SD has 0.7-mil stereo-LP diamond and 1-mil sapphire LP "standby" monophonic stylus. *RG745-3SD* has 0.7-mil diamond and 3-mil sapphire.—**Recoton Corp.,** 52-35 Barnett Ave., Long Island City 4, N. Y.

TURNTABLE KIT, *Model K-33.* 33⅓-rpm crown spindle belt drive; custom-made endless woven fabric belt. Noise level 47

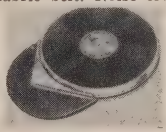

db below average recording level. 4-pole induction motor. Built-in strobe. Assembly time about 30 minutes.—**Rek-O-Kut Co.,** 38-19 108 St., Corona 68, N. Y.

TRANSCRIPTION TURNTABLE, *Collaro model 4TR200.* Weighs 8½ lb for flywheel effect.

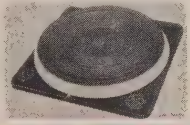

Heavy-duty 4-pole motor; rotor dynamically balanced to zero. Motor mounted on 3 tension springs. Shaft in self-lubricating bearing with steel ball pressed into lower end to take total thrust of turntable. 4-speed. Also new stereo manual player *model TP59* and 3 stereo changers *TSC-640, TSC-740* and *TSC-840.*—**Rockbar Corp.,** 650 Halstead Ave., Mamaroneck, N. Y.

STEREO COMPONENTS, *Premiere* series. Pedestal styling in

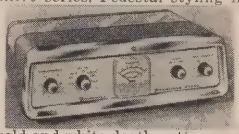

gold and white, leatherette cases. New models include *40PG* stereo amplifier, *209* stereo preamp, *240* basic stereo amplifier, *103GT* AM–FM tuner, *120 GAT* tuner–amplifier.—**Grommes,** Div. of Precision Electronics Inc., 9101 King St., Franklin Park, Ill.

HI-FI CHANGER KIT, *Heathkit RP-3.* Flutter and wow less than 0.18% rms. Turntable

pauses during change cycle; change mechanism disengages during play. Stylus pressure constant within 0.9 gram between first and last record.

Get This Valuable Book FREE

Yes, you get this big, brand new book, "150 Radio-Television Picture Patterns and Diagrams Explained", absolutely FREE! Complete 11x22″ Schematic Diagrams on leading models Radio and TV Sets help cut your servicing time. Easy-to-read, large 8½x11″ pages, with full instructions on how to use the diagrams. A "must" in every repair kit. You get this book as a FREE Gift for asking to see Coyne's new 7-book set, "Applied Practical Radio-Television"!

At Last! Money-Making "Know-How" On Transistors, Color TV and Servicing

Coyne's great 7-volume set gives you all the answers to servicing problems—quickly! For basic "know-how" that's easy to understand you'll find everything you want in Volumes 1 to 5 on over 5000 practical facts and data. Every step from fundamentals to installing, servicing and trouble-shooting all types of radio and TV sets. So up-to-date it includes the latest on COLOR TV and UHF. All this plus Volume 7—TRANSISTOR CIRCUITS—the most complete book ever published on the applications of transistors in electronics. *New!* Set has colorful design, washable covers.

EXTRA! 868-Page TV Cyclopedia Included!

For speedy on-the-job use, you also get Vol. 6—famous Coyne CYCLOPEDIA. Answers problems on servicing, alignment, installation, etc. in easy ABC order. Use this 7-volume TV-RADIO LIBRARY FREE for 7 days; get the Servicing Book FREE!

FREE!
5 Years Of Valuable Supplements

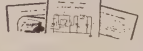

With your set you also get Coyne's annual Supplement Service FREE for 5 years. Keeps your set up-to-date on everything that will be new in radio, television, electronics and electricity.

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL
500 S. Paulina St., Dept. B8-T1, Chicago 12, Ill.

Just For Examining COYNE'S New Set "Applied Practical Radio-Television" on 7 DAY FREE TRIAL!

NOW! 7 BIG BOOKS IN ONE GREAT SET!

SEND NO MONEY! Just mail coupon for 7-volume set on 7 days free trial. We'll include book of 150 TV-Radio Patterns & Diagrams. If you keep the set, pay $3 in 7 days and $3 per month until $27.25 plus postage is paid. (Cash price, only $24.95). Or you can return the library at our expense in 7 days and owe nothing. YOU BE THE JUDGE. *Either way, the book of TV-Radio Patterns is yours FREE to keep!* Offer is limited. Act NOW!

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL, Dept. B8-T1
500 S. Paulina St., Chicago 12, Ill.

YES! Send 7-Volume "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-Radio Patterns & Diagram Book FREE.

Name ..... Age .....

Address .....

City ..... Zone..... State.....

Where Employed .....

☐ Check here if you want library sent C.O.D. You pay postman $24.95 plus C.O.D. postage on delivery. 7-day money-back guarantee.

Automatic speed selector permits intermixing 33⅓- and 45-rpm records. R-C filter prevents pop when turned off; muting switch eliminates noise during change. Supplied with *GE VR-II* cartridge, diamond LP and sapphire 78 styli.—**Heath Co.,** Benton Harbor, Mich.

LOUDSPEAKER STAND, *model SS-4* Telescoping support, for

use with all medium-weight speakers, designed for rental installation. Cast-iron base, full chrome upright. Top adapter permits quick removal of speaker.—**Atlas Sound Corp.,** 1451 39 St., Brooklyn 18, N. Y.

COMMUNICATIONS MICROPHONE, *"Ten-Four."* Extremely rugged. Encased in synthetic resin. Weighs 8½ oz., half as much as die-cast microphone. Won't chip or scratch. No shock hazard. Retains impact strength from —40° to 165°F.—**Shure**

Brothers, Inc., 222 Hartley Ave., Evanston, Ill.

STEREO TUNER, *Masterflex model 28.* Flywheel tuning. Multiplex adapter tap. AM sensitivity 100 μv, delayed agc,

broadband tuning. FM sensitivity 2 μv, afc plus agc; transformer isolation; de-emphasis network; cascode rf stage, 4 if stages; cathode-follower takeoff.—**Tech-Master,** 75 Front St., Brooklyn 1, N.Y.

HI-FI AMPLIFIER, *model 209.* Power 36 watts. Response 19–35,000 cycles ±0.5 db. Peak power rating 72 watts. Harmonic distortion less than 0.5% at full

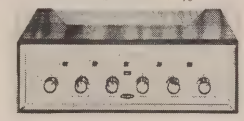

power output. Includes preamp, with provision for operation of 2 amplifiers in tandem using *Stereodapter.* Acoustic level control permits proper operation of loudness control regardless of type of speaker system. Tape recorder facilities for record and playback.—**H. H. Scott Inc.,** 111 Powdermill Rd., Maynard, Mass.

STEREO PREAMP, *Eico model HF 85.* Kit or wired. Separate

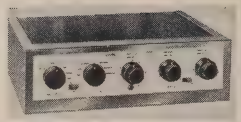

low- and high-level inputs for each channel, including FM multiplex. Independent level, bass and treble controls in each channel may be operated together with built-in clutch. Function selector. Response ±0.3 db 5–200,000 cycles. Sensitivity (input for 2 volts rms output at 1 kc) magnetic phono and microphone 1 mv, tape head 0.5 mv, high-level 0.17 volt. IM distortion maximum 0.17% at 5 volts rms output.—**Electronic Instrument Co.,** 33-00 Northern Blvd., Long Island City 1, N. Y.

STEREO PREAMP KIT, *KT-600.* Dual (input–output) bridge control for balancing channels by audible "null." Third-channel output for middle amplifier–speaker. Tape head equalization for 3¾- and 7½-ips half-track tapes. Clutch type master gain control. Separate turnover and rolloff controls provide 24 positions of equalization on each channel. Response 10–25,000 cycles ±0.5 db. IM distortion less

than .03% at 2.5 volts output, less than 0.1% at 5 volts; harmonic less than 0.1% at 5 volts. —**Lafayette Radio,** 165-08 Liberty Ave., Jamaica 33, N. Y.

STEREO PREAMP, *model SP-210.* Ganged controls. Dc heater supply to all tubes. 12 inputs, 6 on each channel. Outputs for

audio and tape. Response ±1 db, 20-20,000 cycles. Premium-type low-noise triodes used in low-signal-level stages. May be powered from *Pilot* stereo amplifiers or power supply *P-10.*—**Pilot Radio Corp.,** 37-06 36 St., Long Island City, 1, N. Y.

AMP–PREAMP, *model S-1060.* Power output 60 watts at 1.5% IM distortion. Handles peak

powers up to 160 watts. Response ±1 db, 20–30,000 cycles. Sensitivity, radio 0.25 volt, phono 2.5 mv. Maximum hum and noise: radio input 80 db below 20 watts, phono input 60 db below 20 watts. Inputs: phono, tape, 3 high-level, tape monitor. Outputs: 4, 8, 16 ohms and cathode-follower recording. Power consumption 110 watts.—**Sher-**

SR-440 AM-FM Tuner

ASR-433 Stereo Amplifier—Selected for display at the Vienna International Fall Fair.

RF-484 Slimline® 15" Coaxial Transducer

THE NEW STROMBERG-CARLSON COMPONENTS

integrity in music

Integrity in Music, as applied to high fidelity components, means reproduction which adds nothing to, or takes nothing from, the original performance.

Our choice of this slogan is no accident. Just as your purchase of a component system is not a casual investment, our attitude toward the manufacture of components is very serious. Each piece of gear must reflect the highest possible achievement of engineering, production, and musical skill. Yes, musical skill—because the guiding minds of the Stromberg-Carlson component group are those of electronic and acoustic engineers with extensive musical training.

The *musical sound* of our new components was the final critical test before they were made available to you.

We will be glad to submit our specifications to your critical judgment.

See your dealer or write to us for full data on our complete new line of **Amplifiers, Speakers, Speaker Systems, Enclosures and Program Sources.**

"There is nothing finer than a Stromberg-Carlson"

STROMBERG-CARLSON S-C | GD
A DIVISION OF GENERAL DYNAMICS CORPORATION
1478C N. Goodman St. • Rochester 3, N.Y.
Electronic and communications products for home, industry and defense..

wood Electronic Laboratories, 430 N. California Ave., Chicago.

WIRELESS PHONO OSCILLATOR, *Gold Bug SDK-101* for use with stereo cartridge-equipped phono and separate radio, using amplifier and speaker of radio as second channel. No wiring to radio. Self-contained battery, transistor circuit. Adjustable to any unused frequency on standard broadcast band. Available in

kit with stereo cartridge.—**Stereo-Ette Co.,** 4908 N. Lincoln Ave., Chicago 25, Ill.

TV–FM AMPLIFIER, *Uniband* with power supply. For community antenna systems and other multiple installations. High-gain wide-band channel

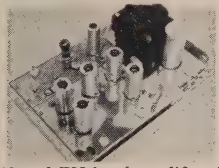

2-13 and FM band amplifier. 75- or 300-ohm single input, 75-ohm single output. Minimum gain 37 db. 6 tubes. New circuit requires no alignment.—**Benco Television Associates,** Ltd., 27 Taber Rd., Rexdale, Ont., Canada.

MULTISET COUPLERS, *Exact-Match. Model A-102* feeds 2 TV or FM receivers from one antenna or mixes 2 antennas into one line; 12–20-db isolation, 3.5-

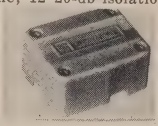

db loss. *A-104* feeds 4 sets; 12–20-db isolation, 7.5-db loss. Weatherproof, nonbreakable cases. *A-100* mounting kit for mounting couplers on antenna mast.—**Blonder-Tongue Laboratories Inc.,** 9 Alling St., Newark 2, N. J.

TV ANTENNA, *Color Royal.* All-channel. *No-Strip* lead-in connector, *Dyna-Coil* phasing fac-

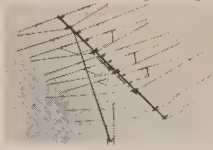

tory assembled. Braced reflectors. *Quik-Lok* clamps eliminate bolts and nuts. No soldering required. Terminal points protected from weather.—**Trio Manufacturing Co.,** Griggsville, Ill.

"FOLD-OVER" TOWER for amateur radio and experimentation. Antenna and rotator may be serviced on ground. Heights up to 70 feet. Tower sections 12½-inch equiangular triangle design with zig-zag steel cross-

bracing, electrically welded. Sections 10 feet long.—**Rohn Manufacturing Co.,** 116 Limestone, Bellevue, Peoria, Ill.

SAFETY - GLASS REMOVER. For removing panels from TV

sets. Suction cups insure safety and speed, prevent fingerprints and damage to glass.—**Walsco Electronics Manufacturing Co.,** 100 W. Green St., Rockford, Ill.

TOOL KIT, *Heathkit TK-1.* All the tools needed for kit building. Two screwdrivers, pliers and sidecutters with insulating rubber handles, *American Beauty* soldering iron with replaceable

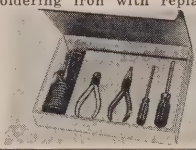

tip.—**Heath Co.,** Benton Harbor, Mich.

BATTERY CHARGER KIT, *Tabkit BCK-1.* Charges 2-, 4-, 6- or 12-volt storage batteries.

Initial current to discharged 12-volt batteries is 4 amps, to 6-volt 3½ amps. Self-regulating. Components premounted in cabinet. — **Technical Apparatus Builders,** 109 Liberty St., New York 6, N. Y.

THERM-O-METER, *model 389-3L.* For measuring temperatures of gases, liquids or solids.

Ranges −50° to 100° and 100° to 250°F. Overall accuracy ±3°F. 7-inch meter. Thermistor lead.—**Simpson Electric Co.,** 5200 W. Kinzie St., Chicago 44, Ill.

VOM-AMMETER SET, *model 100.* Contains *model 310* handsized vom for checking ac and dc volts (dc at 20,000 ohms/volt), ohms, megohms, microamps and milliamps. Adapts instantly into clamp-on ammeter by addition of *model 10* adapter. Line separator to divide 2-conductor cords. Leather carrying

STEREO
THAT MEETS THE REAL TEST

✓ SOUND REALISM at ✓ REALISTIC PRICES!

ST-11 AM-FM STEREO TUNER

Here, for the first time, is an AM-FM STEREO Tuner within the reach of every audiophile. Unmatched by units costing twice the price, the ST-11 is two distinct receivers in one, featuring 4 μV. for 20 db quieting. Variable AFC. Single front panel switch controls AM, FM or STEREO selection.

Wired and tested $74.50
SAVE! Easy-to-build-kit $49.95

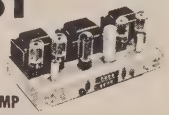

SPA-55 STEREO AMP

Priced for everyone's budget, here at last is a STEREO amp which is a must for every STEREO fan! Housing two identical 27½ watt distortion-free amplifiers the SPA-55 is unsurpassed in quality and performance. This unit may be used as a STEREO amp, a bi-amp, and as a 55 watt Monaural unit.

Wired and tested $79.95
SAVE! Easy-to-build-kit $64.95

SPA-35

Same quality and performance as the SPA-55 - 35 watts.

Wired and tested $62.95
SAVE! Easy-to-build-kit $49.95

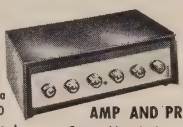

FL-30 AMP AND PRE-AMP

Reasonably priced . . . superlative in quality, the FL-30 now brings to you an amp/pre-amp with fully transistorized front end designed to provide humless & distortion-free reproduction. Freq. response ±db. 10-40,000 cps @ 30 watts–60 watt peak. Inputs for magnetic pickup, tuner, tape and 2 aux.

Wired and tested $74.50
SAVE! Easy-to-build-kit $49.95

Winners of 1958
Fashion Foundation of America
Gold Medal for Distinctive Styling,
& Hi-Fi Music at Home
Commendation Seal for Performance

HFT-7 AM-FM TUNER

World renowned as a standard of excellence, the HFT-7 is a compact self-powered AM-FM tuner of superb engineering and performance. Temperature compensated FM RF circuits and Automatic Frequency Control assures excellent stability and no drift. Foster-Seeley discriminator, Grounded Grid RF amp, flat type construction, AFC with provisions for AFC erase.

Wired and Tested $49.95
SAVE! Easy-to-build-kit $32.00

Prices less cover—for panel mounting

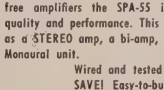

SP-6 STEREO CONTROL CENTER

Prices less cover—for panel mounting

The SP-6 is a completely self powered sensitive dual pre-amp with dual inputs and outputs. Engineered to fit your requirements today, as well as tomorrow, the SP-6 provides unparalleled flexibility. Output of both amps is individually adjusted by one control, reverse position, hi lo filters, etc.

Wired and tested $62.95
SAVE! Easy-to-build-kit $39.95

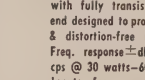

FM-8 Professional FM TUNER

Engineered for the most precise FM reception today, the FM-8 utilizes five I.F. stages and an extremely sensitive tuning meter with unparalleled sensitivity and flexibility of operation. The FM-8 is ideally priced, offers a self-powered AC operated tuner designed for the discriminating audiophile.

Wired and tested $59.95
SAVE! Easy-to-build-kit $39.95

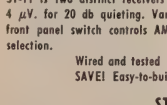

STEREO SA-25 PRE-AMP PLUS ONE 25 WATT AMP

Here is the finest dual channel pre-amp and amp on one precisely engineered and designed chassis. When the SA-25 is attached to your present power amplifier it reproduces two separate channels of sound for STEREO from tape, records, and AM-FM. One easy, inexpensive step brings you the realistic, breathtaking magic of STEREO—with Arkay's SA-25.

Wired and tested $89.95
SAVE! Easy-to-build-kit $59.95

All prices 5% higher west of Mississippi.

FREE! At your dealer or write for complete catalogues of Stereo & Monaural HI-FI, Radio & TV, Kits & Wired.

RADIO KITS, INC. Dept. RE-11
120 Cedar St.
New York 6, N. Y.

Gentlemen:

Please send me your FREE 16 pg. illustrated catalogue without cost or obligation.

NAME_____

ADDRESS_____

CITY_____ STATE_____

arkay 120 CEDAR STREET NEW YORK 6

case included.—**Triplett Electrical Instrument Co.**, Bluffton, Ohio.

TRANSISTOR ANALYZER, *model 850.* Accuracy limited only by indicating meters, within ±2% of full scale. Wide range

of applied voltages available by substitution for breadboard configurations—common base, common emitter and common collector. Under any circuit use conditions, checks for collector leakage (common base or emitter) beta gain, alpha gain, input or output resistance, power gain, linearity.—**Hickok Electrical Instrument Co.**, 10531 Dupont Ave., Cleveland 3, Ohio.

AUDIO OSCILLATORS. Printed-circuit transistor units furnish audio signals of approximately 1 kc and 400 cycles at 0 and −60-db output levels at 600 ohms impedance for equipment testing. *Model PO-2* (shown) has output phone jacks to fit standard patch plug, turns on automatically when inserted. *CO-2* has clip-lead output for

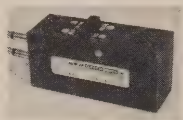

circuit testing. Self-contained battery has 40-hour operating life.—**Dunlap Electronics Inc.**, 764 Ninth St., Des Moines, Ia.

SELENIUM–SILICON TESTER, *Omni-Chex model OC-1.* Checks crystal diodes, power transistors, vibrators and phases speakers.

Direct reading of rectifier quality under load.—**Hallmark Electronics Corp.**, 31-04 Spring Garden St., Philadelphia, Pa.

TRANSISTOR CAPACITORS,

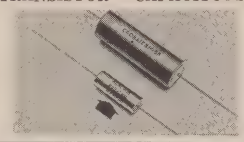

type P1232NNG (arrow). Metallized paper units rated at 50 volts dc. Glass terminal seals. Operate at temperatures from −65° to −85° C at full voltage rating.—**Aerovox Corp.**, Application Engineering Dept. New Bedford, Mass.

CAPACITOR KIT. Contains 76 most-needed *Tobemite* molded-plastic tubular capacitors for use by technicians, in transparent

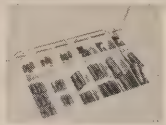

plastic box. Capacitors are 50% smaller than conventional units at equal ratings.—**Tobe Deutschmann Corp.**, Service Div., 2900 Columbia Ave., Indianapolis, Ind.

PRINTED-CIRCUIT ELECTROLYTICS for all printed-circuit requirements. Offset index lug permits insertion right way only. Long- and short-pin and

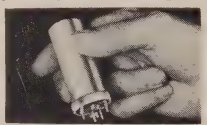

snap-in types.—**Cornell-Dubilier Electric Corp.**, South Plainfield, N. J.

FLYBACK TRANSFORMER, *Stancor HO-288.* Exact replacement for G-E and Hotpoint

RTO-196 used in T series chassis in 6 models.—**Chicago Standard Transformer Corp.**, 3501 W. Addison St., Chicago, Ill.

PREASSEMBLED COMPONENTS *(PAC)* with wire leads for universal wiring. Leads mechanically crimped and soldered to individual component clips. Capacitor – resistor networks with capacitance of 10 μμf–.01

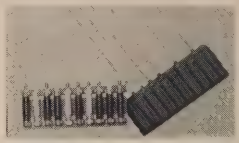

μf (ceramic), .01–.1 μf (mylar), resistance 10 ohms – 50 megs.—**Erie Resistor Corp.**, 644 W. 12 St., Erie, Pa.

PRECISION RESISTORS, *series 77* metal-film units. Smaller, but with higher resistance than previous models. Tubular and flat-side shapes. 25 ohms to 400K. Tolerance ±1% (can be furnished as low as 0.1%). Rated at ¼ watt to 150°C.—**Ohmite Manufacturing Co.**, 3695 Howard St., Skokie, Ill. END

All specifications on these pages are from manufacturers' data.

NEW IMPROVED SENCORE LC3 Leakage Checker

Another Sencore Time-Saver

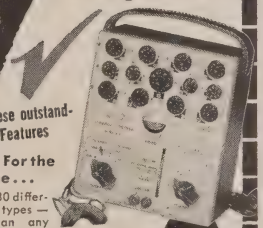

Check these outstanding New Features

Now — For the first time...

Checks 130 different tube types — more than any other "grid circuit" type checker. Includes UHF and latest type tubes.

Checks picture tubes without removing tube from cabinet or chassis.

New Roll Chart prevents obsolescence — just dial the tube type and save time. Chart is easily replaced at no extra cost.

Dynamic Filament checks including heater to cathode leakage & shorts — no need for a second filament tester.

Two spare preheating sockets to cut down testing time.

Capacitor checks simplified.

$28.95 DEALER NET

Really Whips Tough Dogs

The LC3 provides all these new improved features in addition to those employed in earlier leakage or "grid circuit" testers. A must for any TV service technician.

SERVICE INSTRUMENTS CORP.
171 Official Rd • Addison, Ill.

In stock at your local parts distributor

Cut out this ad now for further information

Grommes Little Genie HIGH FIDELITY KITS

• LAYER BUILT • COLOR GUIDE

Before you build another kit, see this new method of kit assembly. Each kit complete with all parts and instructions.

"So simple . . . it's like magic"

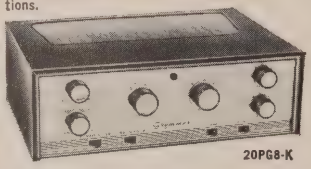

20PG8-K

20PG8-K 20 Watt Amplifier with built-in preamplifier and all controls. Net **59.50**

LJ-6K 10 Watt Amplifier (Little Jewel). Has built-in preamplifier and record compensator on phono channel. Net **24.95**

207A-K Hi-Fi Preamplifier (Self-Powered). Feedback circuit with 10 controls. Net **44.50**

250-K 60 Watt Basic Hi-Fi Amplifier. For use with a preamplifier (such as 207A-K). Net **79.50**

Grommes—Div. of Precision Electronics, Inc.
Dept. RE-10, 9101 King St., Franklin Park, Ill.

Name of Dealer_____

☐ Send complete Kit details.

Name_____

Address_____

City_____ Zone_____ State_____

Dave Rice's OFFICIAL ORDER BOOK for every TV-Radio service call

Triplicate forms serve as order form, invoice and office record with spaces for complete information on every job. Separate listings for receiving tubes, pix tube, parts, serial numbers, labor and tax charges, signatures, etc. 75c a book, $6.50 for dust-proof box of 10.

. . . and for customer's prices on every replacement part, plus flat rate and hourly service charge data, regional and national, Dave Rice's

OFFICIAL PRICING DIGEST

listing over 63,000 items. $2.50

In stock at your distributor, or write

ELECTRONIC PUBLISHING CO. INC.
180 North Wacker Drive Chicago 6, Illinois

BUILD 16 RADIO CIRCUITS AT HOME

with the New Deluxe 1959
PROGRESSIVE RADIO "EDU-KIT"®

only **$22.95**

A COMPLETE RADIO COURSE

Now Also Includes

- ★ TRANSMITTER
- ★ SIGNAL TRACER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools Needed
- ★ EXCELLENT BACKGROUND FOR TV
- ★ School Inquiries Invited
- ★ Attractively Gift Packed

NO NEED TO SPEND HUNDREDS OF DOLLARS FOR A RADIO COURSE

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing.

You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis.

You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester and the accompanying instructional material.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build 16 Receiver, Transmitter, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for Television.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a basic education in Electronics and Radio, worth many times the complete price of $22.95. The Signal Tracer alone is worth more than the price of the entire Kit.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment.

Many thousands of individuals of all ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble-shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio.

You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are sixteen Receiver, Transmitter, Code Oscillator, Signal Tracer, and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

A COMPLETE RADIO COURSE—NOTHING ELSE TO BUY

You will receive all parts and instructions necessary to build 16 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, wire, solder, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book. You receive all parts, tools, instructions, etc. There is nothing else to buy. Everything is yours to keep.

FREE EXTRAS

- SET OF TOOLS
- SOLDERING IRON
- ELECTRONICS TESTER
- TESTER INSTRUCTION MANUAL • HIGH FIDELITY GUIDE • QUIZZES • TELEVISION BOOK • RADIO TROUBLE-SHOOTING BOOK • MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE • FCC AMATEUR LICENSE TRAINING • PRINTED CIRCUITRY • PLIERS-CUTTERS • ALIGNMENT TOOL • CERTIFICATE OF MERIT • VALUABLE DISCOUNT CARD • WRENCH SET

SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of troubles in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

J. Stataitis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend $240 for a Course, but I found your ad and sent for your Kit."

FROM OUR MAIL BAG

Ben Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kits are wonderful. Here I am sending you the questions and also the answers for them. I have been in Radio for the last seven years, but like to work with Radio Kits, and like to build Radio Testing Equipment. I enjoyed every minute I worked with the different kits; the Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

Robert L. Shuff, 1534 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The Troubleshooting Tester that comes with the Kit is really swell, and finds the trouble, if there is any to be found."

Unconditional Money-Back Guarantee

The Progressive Radio "Edu-Kit" has been sold to many thousands of individuals, schools and organizations, public and private, throughout the world. It is recognized internationally as the ideal radio course.

By popular demand, the Progressive Radio "Edu-Kit" is now available in Spanish as well as English.

It is understood and agreed that should the Progressive Radio "Edu-Kit" be returned to Progressive "Edu-Kit" Inc. for any reason whatever, the purchase price will be refunded in full, without quibble or question, and without delay.

The high recognition which Progressive "Edu-Kits" Inc. has earned through its many years of service to the public is due to its unconditional insistence upon the maintenance of perfect engineering, the highest instructional standards, and 100% adherence to its Unconditional Money-Back Guarantee. As a result, we do not have a single dissatisfied customer throughout the entire world.

☐ Send "Edu-Kit" Postpaid. I enclose full payment of $22.95.
☐ Send "Edu-Kit" C.O.D. I will pay $22.95 plus postage.
☐ Send me FREE additional information describing "Edu-Kit."

Name .....

Address .....

.....

PROGRESSIVE "EDU-KITS" INC.
1186 Broadway, Dept. 146G, Hewlett, N.Y.

TRANSFORMER NEWS FROM TRIAD

Solve majority of deflection problems

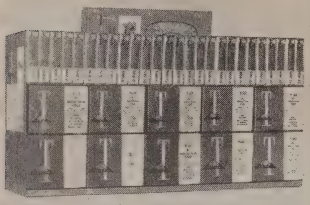

- 8 POPULAR YOKES
- 25 NETWORK KITS
- 2 ACCESSORIES
- PACKAGED IN ALL STEEL CABINET

Most of your deflection problems as well as your yoke stocking problems are solved with the new Triad Yoke Pack. With this equipment, the solutions to more than 4000 yoke testing and replacement problems will be available to the professional service man. The Yoke Pack comes attractively arranged in a handsome steel cabinet—and attractively priced, too. For further information on Triad's Yoke Pack as well as the latest information on yoke servicing, request a copy of the Professional Television Man's Service Aid #3 from your distributor or write direct to:

TRIAD

TRIAD TRANSFORMER CORPORATION
4055 REDWOOD AVE. | 812 E. STATE STREET
VENICE, CALIFORNIA | HUNTINGTON, INDIANA

A SUBSIDIARY OF LITTON INDUSTRIES

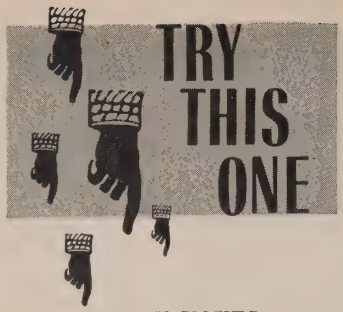

STICKY YOKES

Occasionally a yoke will stick to the neck of a picture tube so tightly that it seems nothing will dislodge it. Rather than resort to a hammer or pipe wrench, I pour a liberal quantity of rubber cement thinner or benzine along the neck of the tube from the socket end. This usually does the job without affecting the insulation or enamel on the wire. Caution: rubber cement thinner and benzine are extremely inflammable.—*Thomas A. Dunn*

TRANSISTOR MOUNTING CLIPS

Many transistors have pigtail leads and are usually soldered into a circuit. However, while this is fine for a 5-cent resistor or 10-cent capacitor, it is hardly recommended for a delicate unit that can cost several dollars, especially in experimental work where circuits are changed often. Not only do the leads become messed up after several solderings and unsolderings, but there is always the chance of heat damage.

To avoid these problems and protect my investment in transitors, I fasten three Fahnestock clips to the lugs of

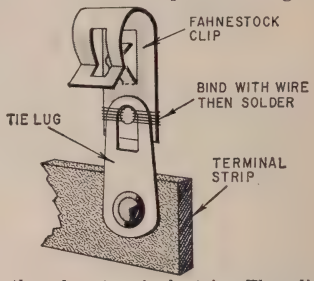

a three-lug terminal strip. The clips are firmly bound to the lugs with short pieces of wire and soldered together. Circuit leads are then soldered to the clips and the transistor leads are inserted in them after all soldering is completed.—*Charles Erwin Cohn*

CHECK 'EM HOT

When checking tubes in a TV set with a parallel heater circuit, a lot of time can be saved if the set is left on during the job. This can be done safely by using any *one* of the following methods:

Remove all low-voltage rectifiers.

If the set is a selenium rectifier type, remove the plug-in fuse resistor.

Remove the high-voltage fuse.

help more people . . . .
save more lives . . . .
GIVE THE UNITED WAY

UNITED

Service men all across the country agree . . . there's no other screw driver or nut driver with the built-in comfort of the VACO "comfordome" handle. Makes service work easy! Enjoy the luxury grip of a VACO... the driver that gives plenty of power, yet is always kind to hands. Next time choose a VACO and *feel the difference!*

Manufactured and Unconditionally Guaranteed by
VACO PRODUCTS CO., 317 E. Ontario Street, Chicago 11, Illinois
In Canada: ATLAS RADIO CORP., Toronto 19, Ont.

Remove the high-voltage rectifier or rectifiers.

The rest of the procedure consists of setting up the tube checker, removing a tube and plugging it immediately into the checker. You can then check the tube without waiting for it to warm up.—*Carleton A. Phillips.*

COIL INSULATION

Sometimes the experimenter, constructor or ham operator winding a coil or small transformer finds himself up against it for a suitable cambric, paper or cloth to insulate the windings. This problem can often be solved by resorting to the common plastic bag, found in the cupboard, tucked away in a corner of the refrigerator or wrapped around the shirts you just had dry-cleaned.

The average plastic bag is thin, resilient, lightweight, moisture-resistant and tough. When this plastic is used in low-wattage units, it provides very satisfactory insulation. At the same time, readily available as it is, it costs you nothing.—*George D. Philpott*

KIT-BUILDING KINK

When building electronic devices from kits, you can save yourself considerable time and get more enjoyment out of the hobby if you sort out all the small components (resistors, capacitors,

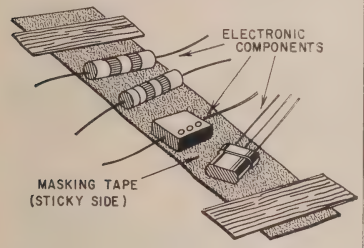

etc.), and lay them out in an orderly manner on a strip of masking tape taped sticky-side up to the bench top. Small easily lost hardware can be safely held in the same manner for easy selection.—*John A. Comstock*

MAT ON THE BENCH

I use a rubber utility mat on the bench in my shop for a number of odd jobs. It makes a handy pix-tube pad when I have to lay a chassis on its side and a catch-all for screws, nuts and other small parts removed from a set. When I have to empty a box of parts to find one of the value I need, I pour them out on the mat. After I get the right one, the mat is folded and the parts easily poured back into their container. Can't you think of some other uses for one of these mats on your bench?—*Scot Mock*

PHILLIPS SCREWDRIVERS

Occasionally use a triangular file on the head of your Phillips screwdrivers to remove nicks and burrs. This lets them get a tight grip and prevents stripping the screw heads.—*Wm. M. Atkinson*

END

For limited budget stereo...

QUAM

"Best Buy"

HIGH FIDELITY SPEAKERS

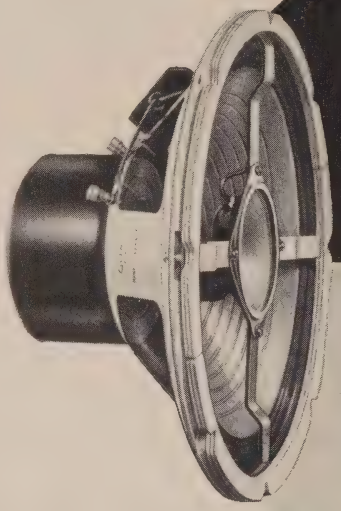

Quam Hi-Fi Speakers perform as well as or better than hi-fi speakers costing up to twice as much ... because their design emphasizes performance rather than non-functional decorative features.

Quam Hi-Fi Speakers offer you the perfect way to keep within your customer's budget without compromising the quality of the system. Quam Hi-Fi Speakers represent the accumulated skill and experience of thirty years of fine speaker manufacturing.

See your Quam distributor or write us directly for complete information on the full line of Quam Hi-Fi Speakers— extended range, tweeters, woofers, coaxials.

QUAM-NICHOLS CO.
236 EAST MARQUETTE ROAD
CHICAGO 37, ILLINOIS

SUPER POWERED SINGLE CHANNEL AMPLIFIER

Minimum 20 V—5 Watts on All Channels

This all new super powered unit has the highest output of any TV channel amplifier with sufficient power to cover large communities with ample signal voltage and deliver a strong signal thru many miles of cable. The unit was designed specifically for community television and is the only unit of its kind that does not produce power in fractions of a watt. For full rated output a high-powered commercial transmitting tube is used.

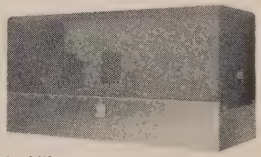

- C. C. S. Service
- 26 db min. gain
- 6-8 mcs. band width
- Channels 2-13 as specified
- Requires only 1 V input
- Co-axial input and output connectors for 75 OHM Line
- Linear class A operation
- Low Power Drain (1 Amp.)

MODEL SPA
$350

Write for details today

SEG Electronics • 1778 Flatbush Ave., Brooklyn 10, New York

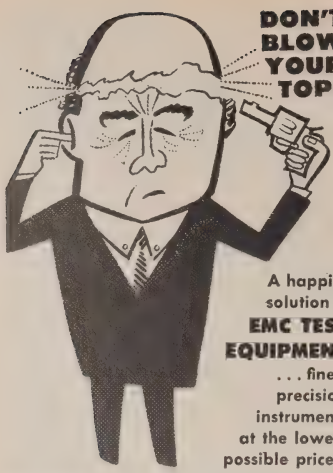

A happier solution is **EMC TEST EQUIPMENT** . . . finest precision instruments at the lowest possible prices!

Model 102 Volometer
Features a 3½", 2% accurate—800 microamperes D'arsonval-type plastic front meter with 3 AC current ranges; and the same zero adjustment for both resistance ranges. Specifications . . . AC Voltage—5 Ranges: 0 to 12-120-600-1200-3000 volts. DC Voltage—5 Ranges: 0 to 6-60-300-600-3000 volts. AC Current—3 Ranges: 0 to 30-150-600 ma. DC Current—4 Ranges: 0 to 6-30-130 ma. 0 to 1.2 amps. Two Resistance Ranges: 0 to 1000 ohms, 0 to 1 megohms. **Model 102**, Wt. 1 lb. 5 oz. Size: 3¾" x 6¼" x 2", **$14.90**; Kit, **$12.50**.

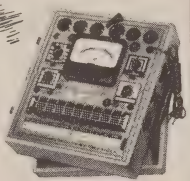

Model 204 Tube-Battery-Ohm Capacity Tester
Emission tube tester. Completely flexible switching arrangement. Checks batteries under rated load on "reject-good" scale. Checks condenser leakage to 1 meg. Checks resistance up to 4 megs. Checks capacity from .01 to 1 mfd. **Model 204P**, illustrated. **$55.90**. **Model CRA**, Cathode ray tube adaptor, **$4.50**.

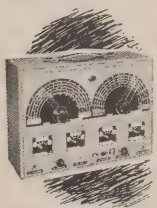

Model 700 RF-AF Crystal Marker TV Bar-Generator
Complete coverage from 18 cycles to 108 megacycles on fundamentals. Bar generator for TV adjustment with a variable number of bars available for horizontal or vertical alignment. Square wave generator to 20 kilocycles. Wien Bridge A. oscillator with sine wave output from 18 cycles to 300 kilocycles. Crystal marker and amplitude control. Individually tuned coils. Constant RF output impedance. Stepped RF attenuator. Variable percentage of modulation. **Model 700** ——— **$55.90**

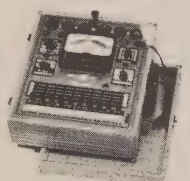

Model 205 Tube Tester
Uses standard emission test. Tests all tubes including Noval and subminiatures. Completely flexible switching arrangement. Checks for shorts, leakages and opens. **Model 205P**, Hand rubbed oak carrying case, **$47.50** (illustrated); Kit, **$36.20**. **Model CRA**, Cathode ray tube adaptor, **$4.50**.

Model 104 Volometer
Features a 4½", 50 microampere meter, with 3 AC current ranges and 3 resistance ranges to 20 megohms. Specifications . . . DC Voltage: 5 ranges (20,000 ohms per volt): 0 to 6-60-300-600-3000 volts. AC Voltage: 5 ranges (1,000 ohms per volt): 0 to 6-60-300-600-3000 volts. DC Current—3 Ranges: 0 to 6-60-600 ma. AC Current—3 Ranges: 0 to 30-300 ma. 0 to 3 amps. 3 Resistance Ranges. 0 to 20K, 0 to 200K, 0 to 20 megs. 5 DB Ranges: —4 to +67 DB. **Model 104**, with carrying strap. **Wt. 7 lbs. 5 oz. Size: 5¼" x 6¾" x 2¼", $26.85**; Kit, **$19.95**. **Model HVT**, 30,000 volt probe for Model 104, **$7.95**.

Yes, tell me more, send me **FREE—a detailed catalog of the complete EMC line. RE-118**

NAME .....

STREET .....

CITY ..... STATE .....

EMC Electronic Measurements Corp.
625 B'way, New York 12, N. Y.
Ex. Dept., 431 Greenwich St., New York 13, N. Y.

NOTEWORTHY CIRCUITS

HUM SQUELCHER AND TONE CONTROL

In these days of negative feedback phase shift has an evil sound, yet like most things it has its good points too. For instance, many equalizer circuits use phase shift. If you notice a reduction in hum at some settings of your equalizer switch, you are probably using an out-of-phase voltage that bucks the hum. An old, but still used, circuit uses an amplified ac voltage (ripple from the B-plus filter) passed through a cathode follower, to cancel hum on low-level grids.

Now, suppose we use the ac signal voltage from our radio tuner or record player for out-of-phase hum bucking? We can put this circuit at the end of our preamp (a standard cathode follower is easily modified for this purpose) or even in the main amplifier and cancel out (or greatly reduce) all the accumulated hum of the preceding stages. Best of all, it will also reduce turntable rumble. Even the rumble from a cheap two-pole motor can be reduced to near inaudibility. With better motors, the noise disappears entirely.

When used as a noise reducer, the circuit can be tucked away anywhere. Hum reduction is regulated by the 200,000-ohm pot, and once set it need not be changed. The setting for best sound may not coincide with greatest

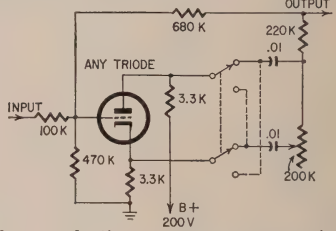

hum reduction, so some compromise may be necessary. However, the noise-reducing potential is so great at any bearable listening level that this point is seldom of much consequence.

This circuit also makes an effective tone control, with some sound variations no other circuit I know of can produce. It gives either high- or low-frequency boost, but not both at the same setting, so it is best used with the regular bass and treble controls. However, very pleasing sound can be obtained with this control alone.

For tone control use it is best to

Popular and Fast Moving . . .

"ILLINI ELECTROMITE CONDENSERS"

Time Tested Quality

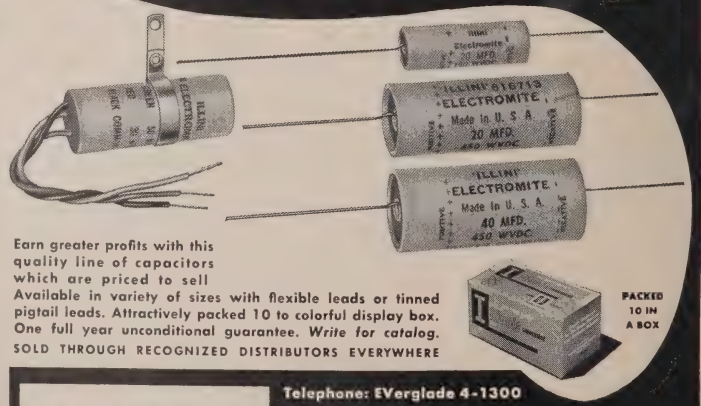

Earn greater profits with this quality line of capacitors which are priced to sell

Available in variety of sizes with flexible leads or tinned pigtail leads. Attractively packed 10 to colorful display box. One full year unconditional guarantee. *Write for catalog.*

SOLD THROUGH RECOGNIZED DISTRIBUTORS EVERYWHERE

PACKED 10 IN A BOX

Telephone: EVerglade 4-1300

ILLINOIS CONDENSER COMPANY

1616 N. Throop Street · Chicago 22, Illinois

wire in a dpdt reversing switch, as shown by the dotted lines, for wider sound variation. Also, when using a straight noise control, try reversing these two leads, and use the one which works best in your particular amplifier.

There is one drawback to this circuit. It has considerable insertion loss—the amount depending on the setting of the variable resistor and the reversing switch, if one is used. If you now operate your volume control in the first half of its arc, you will have enough reserve volume for this circuit. If not, perhaps you can use higher-gain tubes in some other part of the circuit, or install a dual triode, using one half as the hum squelcher and the other half as a straight voltage amplifier (being sure to decouple the B-plus). The new stage should follow the noise control stage (first half of the twin triode) and use a grid resistor of at least 250,000 ohms. The cathode follower does not work very well with low-impedance inputs.

However you manage, you will find your trouble well worth while. The low-frequency noise reduction of this simple circuit, accomplished with negligible bass loss, is unequaled by practically anything except the low-frequency gate of a many, many times more expensive dynamic noise suppressor.—*R. C. Sandison*

VIDEO SHARPENING CIRCUIT

Some recent German *Blaupunkt* TV receivers have an efficient sharpening circuit (see Fig. 1) for improving picture detail. Its principle is illustrated in Fig. 2. The perfect rectangular transient A appears distorted as B at the receiver's output. By differentiation through a short time constant, signal C is obtained. Amplification then delivers signal D. Signal D is then subtracted (added after phase reversal)

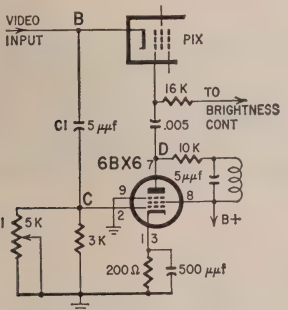

Fig.1

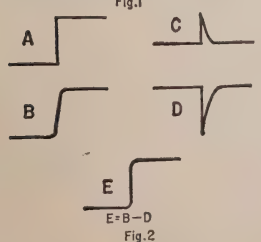

Fig.2

TELEVISION

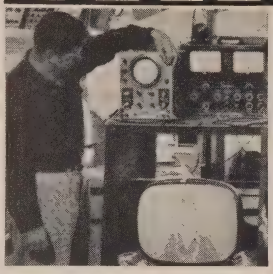

AT HEALDS YOU LEARN BY DOING IN MODERN ELECTRONICS LABORATORIES

HEALD
ENGINEERING COLLEGE
Established 1863
Van Ness at Post, RE
San Francisco, Calif.

Never before in American history has the need been so great for Trained Engineers and Technicians. No other type of training can compare with actual shop practice you get at Healds under expert instructors.

Bachelor of Science Degree, 27 Months

- ☐ Radio-TV Technician including Color TV (12 Months)
- ☐ Electronics Technician (12 Months)
- ☐ Industrial Electronics Technician (12 Months)
- ☐ Electronics Engineering (B.S. Degree)
- ☐ Electrical Engineering (B.S. Degree)
- ☐ Mechanical Engineering (B.S. Degree)
- ☐ Civil Engineering (B.S. Degree)
- ☐ Architecture (B.S. Degree)

Heald College ranks FIRST West of the Mississippi in "Who's Who in America"

Approved for Veterans
DAY AND EVENING CLASSES
Write for Catalog and Registration Application.
New Term Starting Soon.

Your Name .....
Address .....
City .....
State .....

To help you—

MOVE AHEAD in INDUSTRIAL ELECTRONICS

This Library makes plain methods used by today's electronics engineers

HERE'S a Library to help you prepare for a top job in the booming industrial-electronics field . . . help you save time and work in your present job. Experts give you basic theory, practices, and methods. They explain electronic circuits and devices, vacuum tubes, the analysis and use of electron-tube circuits, and provide a vast amount of other data on electronic equipment!

INDUSTRIAL ELECTRONICS ENGINEERING LIBRARY

4 volumes, 1998 pages, 1637 charts, diagrams, and illustrations.

$29.50—payable on EASY TERMS

In this Library are the sort of practical facts that can help you step out in front of the "average" electronics man—they give the kind of help that could very well mean a top-paying job in electronics work. You get practical data on electronic instrumentation, a wealth of facts on vacuum tubes, useful information on electron-tube circuits, and the basic laws of electronic motion. The basic knowledge here can be applied in radar, television, pulse communication, and a wide variety of general electronic control. Use coupon below for free trial—no obligation.

4 Big Volumes

Cage's THEORY AND APPLICATION OF INDUSTRIAL ELECTRONICS
Harman's FUNDAMENTALS OF ELECTRONIC MOTION
Spangenberg's VACUUM TUBES
Seely's ELECTRON-TUBE CIRCUITS

EASY TERMS • 10-DAY FREE TRIAL

McGraw-Hill Book Co., Dept. RE-11
327 W. 41st St., New York 36, N. Y.

Send the *Industrial Electronics Engineering Library* for 10 days' examination on approval. In 10 days, I will send $4.50; then $5.00 monthly until low price of $29.50 is paid. If not wanted, I will return books postpaid.

Name.....
Address.....
City .....Zone....State.....
Employed by .....

For price and terms outside U. S., write McGraw-Hill Int'l, N. Y. C. RE-11

Please Mention

RADIO-ELECTRONICS

when answering advertisements

THIS CAN BE YOU

earning up to $25,000 a year

here is an amazing new BUSINESS OPPORTUNITY for you

Self-service tube testers do all the work for you . . . just collect your profits once a week

A basic principle for making money is to have something work for you, rather than you yourself do the work. As an operator of a FAST-CHECK SELF SERVICE TUBE TESTER route you can be the proud owner of a solid fast-growing business . . . earning money for you while you take life easy. Business can be operated from home and during spare time. All you do is make calls once a week to restock testers and collect profits.

No selling required

Century's self-service tube testers check and sell TV and radio tubes automatically 12 hours a day—7 days a week. Consumers do their own testing and defective tubes are replaced on the spot for highly profitable sales. You place testers and tube stock in stores on consignment . . . and each one can net up to $1000 a year.

Retail stores welcome self-service testers

Drug stores, luncheonettes, supermarkets, candy stores, hobby stores, etc. welcome having a tube tester placed in their store because of the extra traffic it attracts and the commission they earn.

FREE booklet tells all about this booming business

If you are interested in starting a lifetime business, then ACT NOW and send for FREE booklet to convince yourself that this is today's greatest business opportunity.

DON'T DELAY . . . MAIL COUPON TODAY

CENTURY ELECTRONICS CO., INC.
Dept. E-11, 111 Roosevelt Ave., Mineola, N. Y.

Please send me FREE booklet and particulars about setting-up a self-service tube tester route.

Name .....
Address .....
City ..... State.....

From
any Point of View,
more Experts choose

ACROSOUND
ULTRA-LINEAR II
60 watt amplifier

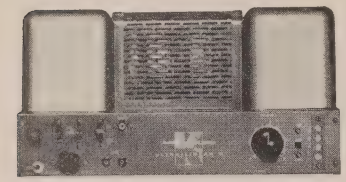

DESIGN The combination of patented ULTRA-LINEAR circuitry—plus new HYBRID FEEDBACK principle—VARIABLE DAMPING control, and ULTRA STABILITY, represents a new high in the art of amplifier design . . . an example of ACROSOUND'S latest achievement in AMERICAN Know-How. This superiority of design now enables anyone with or without any previous knowledge of electronics to assemble for himself or herself . . . (yes! it's that easy!) . . . the finest of amplifiers and at a most reasonable cost, in only two hours!

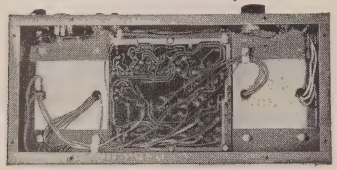

PERFORMANCE By listening test, or by instruments . . . second to none in clarity and frequency response. Normal level distortion is virtually unmeasurable—IM 1% or less at 60 watts, 120 watts peak. Completely stable . . . unaffected by loads, perfect square waves.

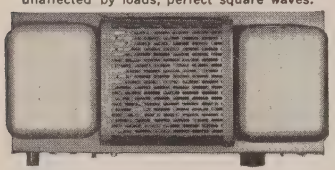

QUALITY Every part going into the assembly of critical and even non-critical circuitry is tested and checked to allow no more than ±½% variation from ACROSOUND'S standards. Specialized test equipment unavailable commercially was designed in ACROSOUND'S laboratories to achieve this result. Every printed circuit board is placed in trial operation on a laboratory amplifier. Output tubes are matched by trial and double checked.

COMPONENTS ACRO'S newest TO-600 output transformer with special hybrid winding—separates functions of output circuit and feedback circuit. Heavy duty, completely assembled, and thoroughly tested, printed circuit board assures uniformity of performance. Low distortion EL34 output tubes are operated well within their ratings ensuring long tube life and optimum performance.

PRICE In preassembled kit form so that you may save money, learn while doing, and have the proud satisfaction you built the best for only **$79.50** net . . . or if you feel you would prefer it laboratory assembled it still represents a bargain at **$109.50** net.

HEAR IT AT YOUR DEALER NOW!

BE READY FOR ACROSOUND DISTORTIONLESS PRE-AMP DESIGNED FOR THE STEREO-PHILE

Experts know why **ACRO** *is best!*
Others . . . Learn why! Write to

ACRO PRODUCTS
369 SHURS LANE
PHILA. 28, PA.

from signal B, and the total result is E, a much better approximation of the ideal A than signal B itself.

In the circuit, video signal B is applied to the cathode of the picture tube. Simultaneously, it is coupled to the grid of the 6BX6 through the short adjustable time-constant circuit R1–C1 to produce the differentiation and create signal C. This signal appears amplified and inverted as D at the 6BX6's plate, and is then applied to the picture tube's control grid.

The resulting total modulating voltage on the picture tube is then the difference between the cathode and control grid voltages, or B − D, or E.

The resulting overamplification of the high video frequencies makes a noticeable improvement in the sharpness of the picture.—*A. V. J. Martin*

HUM SUPPRESSION

There are several effective, but not too well known, ways of suppressing hum. Basically they consist of injecting into the circuit a voltage 180° out of phase with the hum voltage. Fig. 1 shows how some voltage from the power transformer is fed to the grid of one of the tubes—usually a preampli-

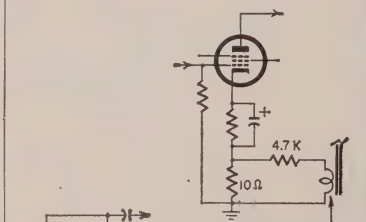

Fig.1

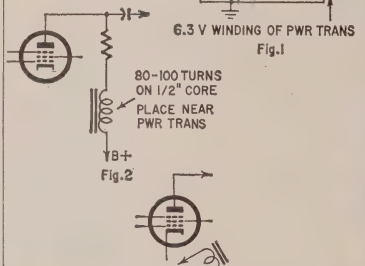

Fig.2

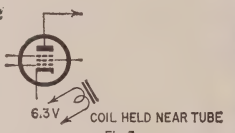

Fig.3

fier. If the hum increases, reverse the connections on the heater winding. The value of the 4,700-ohm resistor can be increased or decreased for fine adjustment.

Fig. 2 shows a small coil of between 80–100 turns wound on a ½-inch core which can be placed in either the plate, grid or cathode circuit and held near the power transformer and rotated until the hum diminishes.

The Fig. 3 arrangement is used for tubes with heavy heater-current drain. The coil is 500 turns of fine wire wound on a ½-inch core. (The coil and core of a 6-volt ac relay should work nicely. —*Editor*) Be sure the core does not touch the metal shell of the tube.—*Carl Hennig*

END

MOSLEY
4-Set Coupler

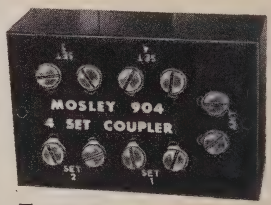

LOW LOSS
EFFECTIVE ISOLATION
EFFICIENT SIGNAL DISTRIBUTION

Owners of Duplex or 4-unit Apartment Buildings will want you to install Mosley 4-Set Couplers!

Here's a Big profit-maker in a Big market!

Mosley 904, 4-Set Coupler
$6.25 List

Another Mosley Premium Quality TV Accessory!

Mosley Electronics, Inc.
8622 ST. CHARLES ROCK ROAD
ST. LOUIS 14, MISSOURI

2 WAY PORTABLE RADIO SET

Sends—Receives up to 10 miles as shown or hundreds of miles with outside antenna! 80 and 40 meter amateur radio bands (novice) also Aircraft and overseas broadcasts (3 to 8 mc.). POWERED WITH SELF-CONTAINED PORTABLE RADIO BATTERIES. NO AC PLUG-INS NEEDED! Take it with you everywhere you go—Keep in contact with home, friends. Has 5 watt crystal controlled transmitter — Sensitive. Regenerative Receiver. Send-receive switch. Wt., only 3 lbs. Size, only 6"x4"x4". TESTED—PROVEN—SIMPLIFIED—PRACTICAL—Full information given on quick easy to get license.

SEND ONLY $3.00 (bill, ck. mo) and pay postman $12.95 COD postage on arrival) or send $15.95 for postpaid delivery. Complete kit includes all parts, tubes, coils, plastoid cabinet, easy instructions. (Set of batteries—$3.49; crystal $1.49). COMPLETELY WIRED AND TESTED POSTPAID $19.95. A regular $49.95 value—Order now before price goes up. GUARANTEED—AVAILABLE ONLY FROM:
WESTERN RADIO, Dept. BNR-11, KEARNEY, NEBR.

OPPORTUNITY ADLETS

Rates—50c per word (including name, address and initials). Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount, 10% for 12 consecutive issues. Misleading or objectionable ads not accepted. Copy for January issue must reach us before November 15, 1958.

RADIO-ELECTRONICS,
154 West 14 St., New York 11, N. Y.

HIGH-FIDELITY SPEAKERS REPAIRED. AMPRITE Speaker Service, 70 Vesey St., New York 7, N.Y. BA 7-2580.

CASH PAID! Sell your surplus electronic tubes. Want unused, clean transmitting, special purpose, receiving, TV types, magnetrons, klystrons, broadcast, etc. Also want military & commercial lab test and communications gear. We swap too, for tubes or choice equipment. Send specific details in first letter. For a fair deal write, wire or telephone: BARRY, 512 Broadway, New York 12, N.Y. WAlker 5-7000.

RECORDERS, Hi-Fi, Tapes. Free Wholesale Catalogue. CARSTON, 215-T East 88th St., New York 28, N.Y.

STEREO TAPE RENTALS. For the very best at lowest prices. Write CALIFORNIA TAPED MUSIC ASSN., 1971 Cordilleras Road, Redwood City, Calif.

DISCOUNTS UP TO 50% on Hi-Fi amplifiers, tuners, speakers, tape recorders, individual quotations only, no catalogs. CLASSIFIED HI-FI EXCHANGE, 2375 East 65th Street Brooklyn 34, N.Y.

LABORATORY QUALITY equipment and Military Surplus Electronics bought, sold. ENGINEERING ASSOCIATES, 434 Patterson Road, Dayton 9, Ohio.

DIAGRAMS FOR REPAIRING RADIOS $1. Television $2. Give make, Model. DIAGRAM SERVICE, Box 672-RE. Hartford 1, Conn.

SAVE MONEY! Get our price list on all types Radio and TV tubes at Mfrs. prices! 100% guaranteed, all brand new and unused, no mechanical or electrical rejects, not washed or rebranded! 24 hour service! Write UNITED RADIO COMPANY, 58 Market St., Newark, N. J.

ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING equipment repaired. HAZELTON INSTRUMENT Co., 128 Liberty Street, New York, N.Y.

TELEVISION Tuner Repairs. DAN'S TELEVISION LABORATORY, 619A Sunrise Highway, Babylon, N.Y.

RUBBER STAMPS—Supplies. Professional. Guaranteed. MODERNS, 924½ Patrick, Jonesboro, Arkansas.

OPERATE profitable mailorder business! Write: BOND, H-1637 West Vernon, Phoenix, Arizona.

DISCOUNTS TO 50%, recorders, tapes, hi-fi components, consoles, photograph equipment. Request specific prices only. LONG ISLAND AUDIO & CAMERA EXCHANGE, 3 Bay 26th St., Brooklyn 14-R, N.Y.

CAMERA Repairmen greatly needed! You can learn manufacturers' service methods at home, in your spare time! Free, big illustrated book tells how! Write today. NATIONAL CAMERA REPAIR SCHOOL, Dept. RE-11, Englewood, Colorado.

JOBS—HIGH PAY; USA, So. America, The Islands. All trades. Many companies pay fare. Write Dept. 71T, NATIONAL EMPLOYMENT INFORMATION, 1020 Broad, Newark, N.J.

PROFESSIONAL Electronic Projects—Organs, Timers, Intercoms, Counters, etc. $1 each. List Free. PARKS, Box 1665, Lake City Station, Seattle 55, Wash.

PLATINUM electronic scrap bought. NOBLE METALS, Box 1113, Santa Monica, Calif.

"HYPNOTIZE . . . One word . . . One fingersnap," on stage. Satisfaction-or refund. $2. HYPNOMASTER, 846-85 Sunnyside, Chicago 40, Ill.

"FAMOUS brand Speaker and Audio manufacturer with national reputation requires alert, progressive sales representatives for several choice territories. Write stating territory now covered and lines carried. P.O. Box 352, Ridgefield, N.J."

POSITION OPEN: Technician as assistant in electronics service shop. Salary range $3600 per year. Apply to Dean Virgil W. Adkisson, Research Coordinator, UNIVERSITY OF ARKANSAS, Fayetteville, Ark.

LEARN WHILE ASLEEP! Exciting details free. RESEARCH ASSOCIATION, Box 24-HH, Olympia, Washington.

Looking For Something?

Chances are you'll find it in the Handy Annual Index of this year's RADIO-ELECTRONICS articles and features. Buy the December issue of RADIO-ELECTRONICS on sale November 25.

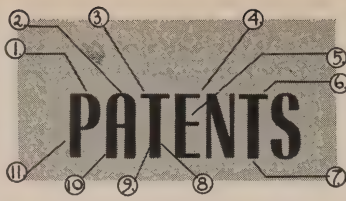

3-PHASE GENERATOR

Patent No. 2,810,843

Carl-Erik Granqvist, Lidingo, Sweden (Assigned to Svenska Aktiebolaget Gasaccumulator, Lidingo, Sweden)

The circuit shown here may be identified as a 3-stage phase-shift oscillator. When each stage is designed to produce a shift of 60° there is an overall difference of 180° between input and output therefore oscillation. This particular circuit has a new twist. Each of the coils forms a stator wind-

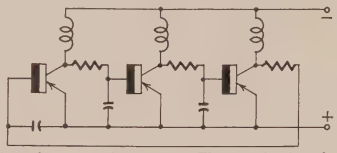

ing of a three-phase motor. This can be done because each coil current is 60° out of phase with that of its neighbors.

A particular application of this circuit deals with a three-phase gyroscope motor. Being quite compact the entire circuit fits easily within the gyroscope itself close to the center of rotation. The oscillator is energized by dc which is commonly available on planes and ships. The output three-phase is commonly 400 cycles.

PRECISE CLOCK

Patent No. 2,820,338

Jacob Rabinow, Takoma Park, Md.

This servo clock is highly precise. The front view (Fig. 1) shows an outer pendulum P1, an inner pendulum P2 and a driving mechanism. While P1 and P2 are coupled indirectly, they tend to swing together. The drive consists of a metal weight M, magnet L1 and its pivoted armature, which normally slants downward against the pin and upward against extension F of weight M.

As P1 swings toward the right, it meets M

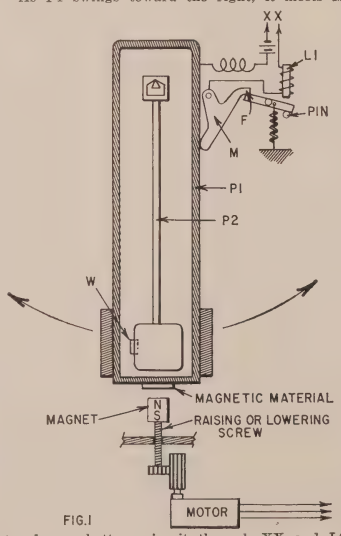

FIG. 1

to close a battery circuit through XX and L2 (Fig. 2). L1 lifts its armature away from extension F. Thus P1 is under the gentle drive of M for a longer period during the swing to the *left* than to the right.

P1 can be retarded by a magnet mounted just below it. The distance between them is controlled by a reversible motor. When P1, P2 are in exact step, the motor is idle since there is no need to speed or slow the outer pendulum. Signal for the motor input is derived from a

4 NEW RIDER BOOKS

For More Electronic Know-How... Increased Income...At Low Cost

BASICS OF DIGITAL COMPUTERS
by John S. Murphy

If you have a knowledge of the fundamentals of electronics, you can master the basics of digital computers and understand the details of any specific digital computer with this new 3 volume 'picture-book' course. #196, 3 vols., soft cover set, $6.95; #196-H, cloth bound, all 3 vols., $7.95.

BASIC PULSES
by Irving Gottlieb

You can learn all about pulses with this thorough, crystal-clear presentation. What they are—how they are produced, measured and used. Pulses are vital in every area of electronics—computers, TV, automation, communication, timing, radar, telemetry and others. This one volume 'picture-book' course is must reading. #216, soft cover, 184 pps., $3.50.

BASIC TELEVISION
by Alexander Schure, Ph.D.

This new 5-volume 'picture-book' training course is the easiest and most economical way of learning all about black and white television—the fundamentals, operation and circuitry. More than 700 understandable, exciting illustrations support the text and make everything from the transmitter to the picture on the receiver screen crystal-clear. #198, soft cover, 5 vol. set, $10.00; #198-H, cloth bound, 5 vols. in one binding, $11.50.

FUNDAMENTALS OF TRANSISTORS
(second edition) by Leonard M. Krugman, P.E.

Published in 1954, the first edition of this book gained an international reputation as an outstanding text devoted to the fundamentals of transistors—their characteristics, performance and application. One of its main features was the lucid presentation of the theory of semi-conductors. This, the second edition (revised and expanded), modernizes the text so as to embrace the latest developments in the transistor art and so bring the book completely up-to-the-minute. The numerical examples contained in this book make every equation both understandable and usable. The tremendous number of transistorized devices—radios, amplifiers, etc.—that require a knowledge of transistors, makes this MUST READING. #160, soft cover, $3.50.

FAMOUS RIDER 'PICTURE BOOK' COURSES

BASIC ELECTRICITY
BASIC ELECTRONICS
by Van Valkenburgh, Nooger & Neville, Inc.

NO OTHER BOOKS LIKE THEM!

The fabulous *illustrated* training course now used by the U. S. Navy.

Here's how this easy, illustrated course works: *every page* covers one complete idea! There's *at least* one big illustration on that *same* page to explain it! What's more, an imaginary instructor stands figuratively at your elbow, doing "demonstrations" that make it even *easier* for you to understand. Then, at the end of every section, you'll find *review pages* that highlight the important topics you've just covered. You build a thorough, step-by-step knowledge at your own pace—*as fast as you yourself want to go!* Sponsored by the Navy to turn out trained technicians in record time, this modern course presents Basic Electricity and Basic Electronics in a simple way that *everyone* can grasp—*regardless of previous education!*

BASIC ELECTRICITY—Volumes 1 and 2 cover DC components and circuits; Volumes 3 and 4 cover AC components and circuits; Volume 5 covers AC and DC motors and machinery.

BASIC ELECTRONICS—Volume 1 covers Diodes and Power Supplies; Vols. 2 and 3 cover Amplifiers and Oscillators; Vols. 4 and 5 cover Transmitters and Receivers.

Basic Electricity, #169, soft cover, 5 vols. 624 pp., per set, $10.00; #169H cloth bound, $11.50. **Basic Electronics,** #170, soft cover, 5 vols., 550 pp., per set $10.00; #170H, cloth bound, $11.50.

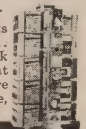

These are just a few of the Rider books that spell greater electronic know-how... career and financial advancement. Look for the familiar Rider book display at your parts distributor or book store today. If these books are not available, order direct: Dept. RE-11

JOHN F. RIDER PUBLISHER, INC.
116 West 14th Street, New York 11, N. Y.
In Canada: Charles W. Pointon, Ltd.
6 Alcina Ave., Toronto, Ontario

These men are getting practical training in...

Electronics

Train in *NEW* Shop-Labs of

COYNE

in Chicago — Electronic Center of the World. Prepare for a better job and a successful future in TOP OPPORTUNITY FIELD. Train on real full size equipment at COYNE where thousands of successful men have trained for 60 years—*largest, oldest, best equipped school of its kind.* Professional and experienced instructors show you how, then do practical jobs yourself on more than a quarter of a million dollars worth of equipment. No previous experience or advanced education needed. Employment Service to Graduates.

Start Now—Pay Later—Liberal Finance and Payment Plans. Pay most of tuition after graduation. Part-time employment help for students. Choose from nine yearly Starting Dates.

Mail Coupon For Free Book—"*Guide to Careers.*" Whether you prefer ELECTRICITY-ELECTRONICS, TELEVISION-RADIO ELECTRONICS or COMBINED ELECTRONICS TRAINING, this book describes all training offered and gives all the facts to Vets and Non-Vets.

Information comes by mail. No obligation and NO SALESMAN WILL CALL.

B. W. Cooke, Jr., Pres. Founded 1899

COYNE ELECTRICAL SCHOOL

Chartered Not For Profit

1501 W. Congress Pkwy., Chicago 7, Ill., Dept. 88-5A

MAIL COUPON FOR BOOK

Coyne Electrical School, Dept. 88-5A
1501 W. Congress Pkwy.
Chicago 7, Ill.

Send FREE book, "Guide to Careers" and details of all training you offer.

Name .....

Address .....

City ..... State .....

(I understand no Salesman will call)

PATENTS *(Continued)*

light beam that shines through W. This window is exposed exactly halfway when P1, P2 are in exact sync. The amount of light through W changes when P2 lags or leads P1.

Fig. 2 shows an edge view of the clock. The lamp shining through W is flashed when L2

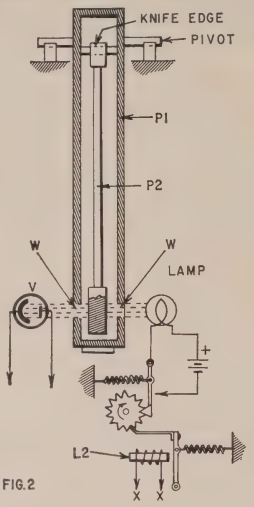

FIG.2

is energized. Note that this magnet is in series with L1 (Fig. 1). Output from the photocell V is amplified (not shown here) then applied to the controlling motor, which rotates in the required direction to correct P1.

By using a separate pendulum P2, unloaded and uncoupled, precision timing results. P2 is mounted on a frictionless knife edge. END

50 Years Ago

In Gernsback Publications

HUGO GERNSBACK, *Founder*

Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some larger libraries still have copies of Modern Electrics on file for interested readers.

In November, 1908, *Modern Electrics*

The Production of Sustained High Frequency Oscillations, by M. A. Deviny.

Iron Pipe Aerial, by Carl Chupp.

Suspension and Insulation of Aerials, by A. C. Austin, Jr.

Wireless in Balloon.

Two New Detectors, by Our Berlin Correspondent.

The Micro-Ceraunograph, by B. Wm. H. Capen.

How to Make an Electrolytic Detector, by C. C. Whittaker.

Antenna Phenomenae, by Sewall Cabot.

Selective Tuner with Weeding Out Circuit, by H. H. Holden.

HELP WANTED!

I hired a new man
He really did goof;
Installed an antenna
But on the *wrong* roof!

By Phyllis Barlow

Save on Essential Tools

DISCOUNTS UP TO 75%

36" FLEXIBLE SHAFT

For Precision Working—Hard to Get At Places!

Reg. $9.95—Now **$4.95** plus 35c pp. & hdlg.

This handy flexible shaft with complete handle increases the utility of your electric drill, electric motor, grinder or drill press where ¼" shank can be attached. Easily attached to do grinding, carving, drilling, sanding, polishing, buffing, slotting, engraving, etching, etc., on wood, metal, glass and plastic. The flexible shaft is tamper-proof, sealed and designed for lifetime service. Can be operated at speeds up to 6000 R.P.M.

Surgical Steel, Hand Ground

SET OF 12 CARVING KNIVES

The sharpest, keenest ground, surgical steel blades we have ever seen—sharp enough to split a human hair in two! 12 different shapes and edges can do every job of wood carving, model making, linoleum cutting, sculpting and whittling imaginable. Each blade has a 4½" long hardwood handle for easy gripping . . . heavy duty blade is firmly attached by means of a brass ferrule to ensure long, continued rugged use. Each surgical steel blade precision hand ground to easily and quickly notch and cut any shape you wish. A sensational all-purpose set, well worth $5.95. **$2.00** ppd.

DRILLS AND SAWS ANY SHAPE!

Supreme DRILLSAW **$1.00** ppd.

Simply insert the amazing Drillsaw into the chuck of your ¼" electric drill and you're ready to cut any shape you desire. Lower portion of Drillsaw acts as regular ¼" drill which easily bore thru wood, plaster, plastics, plywood and similar materials. Then, after penetration, the multiple keen cutting edges of the Drillsaw, cleanly and speedily cut in any direction you move. Cut circles, triangles, zig-zags, any conceivable shape you wish —in seconds!

Windproof, Flameless, Fuel-less

SOLAR CIGARETTE LIGHTER

Pocket-Size—Lights every Cigarette Under the Sun

The most practical outdoor cigarette lighter ever created! A precision instrument that utilizes the power of the sun to light your cigarette. Forget about fuels, matches, wicks, danger of fire. Merely insert a cigarette in scientifically designed parabolic pocket-sized reflector and in just a few seconds your cigarette is lit. NO PUFFING IS REQUIRED! Perfect for all outdoors—camping, fishing, beach and boats. Guaranteed to amaze and amuse you—and your friends! Also works thru sunny windows indoors. **$1.00** ppd. (3 for $2.75 ppd.)

Send check or money order. If COD, fees extra.
Money Back Guarantee

SCOTT MITCHELL HOUSE, Inc.

Dept. P-11, 415 So. Broadway, Yonkers, N.Y.

RESEARCH
EDUCATION
SERVICE

FIGHT CANCER

AMERICAN CANCER SOCIETY

BUSINESS and PEOPLE

Norman L. Harvey (left) is now vice president–engineering of CBS-Hytron, Danvers, Mass. He comes to the company from Sylvania where he was manager of special tube opera-

tions. **Lindsey R. Perry** (right) is now product manager of special-purpose tubes and hi-fi components of CBS-Hytron. He had been manager of the Newburyport, Mass., TV picture-tube plant. **John E. Cunningham,** supervisor of field engineering, New England, was advanced to New England regional manager of equipment tube sales.

Dr. William J. Pietenpol joined Sylvania as vice president and general manager of the Semiconductor Div., Woburn, Mass. He leaves Bell Labs, where he was director of development–semiconductor devices.

Robert Sackman (left) vice president and general manager of Ampex Corp.,

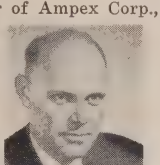

Redwood City, Calif., was elected to board of directors of ORRadio Industries, Opelika, Ala., tape manufacturer. **John M. Leslie, Jr.** of Ampex becomes ORRadio general manager.

Charles D. Manhart (left) was elected vice president, Government relations, for Raytheon Manufacturing Co., Waltham, Mass. He recently resigned as director of military and Government

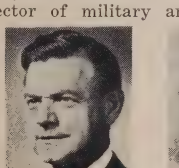

sales at Bendix Aviation Corp. **Fred H. O'Kelley** joined Raytheon as Eastern regional manager for sales of receiving tubes, industrial tubes, and semicon-

VHF or UHF

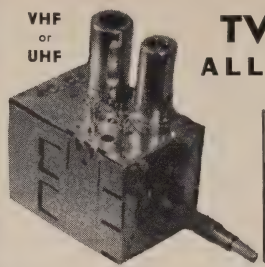

TV TUNERS REBUILT

ALL MAKES & MODELS

THOUSANDS OF TUNERS IN STOCK

EXCHANGED OR OVERHAULED

$9.95 NET

Price includes WORN parts only. Replacement tubes and smashed or missing parts are charged extra.

COMBINATION UHF/VHF UNITS **$19.90**

90 DAYS WARRANTY

ALIGNED TO ORIGINAL STANDARDS USING THE FINEST EQUIPMENT. ALL WORK PERFORMED BY TUNER EXPERTS WITH YEARS OF EXPERIENCE IN THE TUNER FIELD.

SAME DAY SERVICE — EXCHANGE TUNER SHIPPED SAME DAY (OTHERWISE DEFECTIVE TUNER OVERHAULED AND RETURNED: WITHIN 48 HOURS IN MOST CASES.)

Forward Tuner with All Smashed Parts: Quote Make and Model

F.O.B. Chicago or Toronto We will ship C.O.D.

Castle Television Tuner Service

1723 W. LUNT AVE., CHICAGO 26, ILL. **U.S.A.** ● 152 MAIN ST., TORONTO 13, ONT. **CANADA**

Suppliers of rebuilt TV Tuners to leading manufacturers, technicians & service dealers, coast to coast. Original and Only Complete TV Tuner Service covering the North American Continent.

MAIL ORDER HI-FI

You can now purchase all your Hi-Fi from one reliable source and be assured of perfect delivery. Carston makes delivery from NY stock on most Hi-Fi, Recorders and Tape within 24 hours. *SEND US A LIST OF YOUR HI-FI REQUIREMENTS FOR OUR QUOTATION.*

CARSTON STUDIOS 215-RD E. 88 St. New York 28, N. Y.

MAKE OVER 150 SMALL COMPUTING AND REASONING MACHINES WITH

BRAINIAC®

A BETTER ELECTRIC BRAIN CONSTRUCTION KIT

Only $17.95 . . . Why Pay More?

EQUALS OUR ORIGINAL GENIAC® electric brain construction kit (Dec. 1955) **PLUS** many improvements and additions—over 600 parts including 116 patented wipers so that all switches work well. Instead of covering only 33 machines, BRAINIAC gives full specifications for 151 computing, reasoning, arithmetical, logical, puzzle-solving and game-playing machines . . . all 33 GENIACS (1955) and 118 BRAINIACS (1956-58). Each machine works on a single flashlight battery—all connections with nuts and bolts—no soldering required . . . is FUN to make—FUN to use and play with—and TEACHES you something new about computing and reasoning circuits.

ORIGINATED AND PRODUCED EXCLUSIVELY by Berkeley Enterprises, BRAINIAC is the result of 8 years' design and development work with miniature mechanical brains including: Geniac (see "Geniacs: Small Electric Brain Machines and How to Make Them" by E. C. Berkeley, 64 pp., published 1955 by Geniac Project, a partnership with Oliver Garfield discontinued September 1955); Relay Moe (automatic machine playing tit-tat-toe pictured in Life Magazine, March 1956); etc. Berkeley is Author of "Giant Brains or Machines that Think" (Wiley, 1949), and other books & papers; Editor of the magazine "Computers and Automation"; Designer of all the Brainiacs and more than half of the 33 Geniacs (1955); etc.

WHAT CAN YOU MAKE WITH BRAINIAC KIT K 17? LOGIC MACHINES: Syllogism Prover, Intelligence Test, Boolean Algebra Circuits, etc. GAME-PLAYING MACHINES: Tit-tat-Toe, Nim, Black Match, Wheeled Bandit, etc. COMPUTERS: To add, subtract, divide, multiply using decimal or binary numbers; Forty Year Calendar, etc. CRYPTOGRAPHIC MACHINES: Coders and Decoders, Lock with 15,000,000 Combinations, etc. PUZZLE-SOLVING MACHINES: The Missionaries and the Cannibals, Submarine Rescue Chamber, The Uranium Rocket Ship and the Space Pirates,etc. QUIZ MACHINES: History, geography, mathematics, etc. . . . AND MANY MORE!

WHAT COMES WITH YOUR BRAINIAC KIT? Complete descriptions of 151 experiments ● Manual of explanation/instruction by E. C. Berkeley ● Over 600 pieces including control panel, multiple switch discs, jumpers, improved wipers, bulbs, sockets, wire, etc. ● Over 160 circuit diagrams including 46 exact wiring templates ● "How to Go from Brainiacs and Geniacs to Automatic Computers" by E. C. Berkeley ● Claude Shannon's historic 1938 paper "A Symbolic Analysis of Relay & Switching Circuits" ● List of references to computer literature ● Etc.

BRAINIAC KIT (1958 Model K 17) . . . the kit with limitless possibilities backed by an organization of 10 years' standing in the computer field. **$17.95**

(For shipment west of Mississippi, add 80c; outside USA, add $1.80)

7-DAY FULL REFUND GUARANTEE IF NOT SATISFACTORY

—MAIL THIS COUPON—

BERKELEY ENTERPRISES, Inc.
815 Washington St., R166, Newtonville 60, Mass.

Please send me Brainiac Kit K 17. (Returnable in 7 days for full refund if not satisfactory—if in good condition.) I enclose $..... in full payment.
My Name and Address are attached.

TAPE RECORDERS

HI-FI COMPONENTS
Tapes ● Accessories

MERITAPE — Low cost, high quality recording tape, in boxes or cans.

UNUSUAL VALUES — Send for Free Catalog

DRESSNER, 69-02RE 174 St., Flushing 65, N.Y.

NEW *SPEED* TV SERVICING SYSTEM

FIND TUBE—CURE TROUBLE
with **TROUBLE INDICATING**

TUBE LOCATION GUIDES

Each guide shows location and type of all tubes. Also by copyr.ghted method indicates exact location of tubes needing replacement.

Following Books are Available:

☐ **TV TUBE LOCATOR, Vol. 1**—Guides for over 3000—'47 to '54 models—$1 postpaid.

☐ **TV TUBE LOCATOR, Vol. 2**—Guides for over 5000—'55, '56, '57 models—$1.50 postpaid.

☐ **RCA TV GUIDES**—Complete compilation of RCA tube guides—'47-'56 models—$1 postpaid.

☐ **ADMIRAL TV GUIDES**—1500 Admiral models, '47-'56—$1 postpaid.

TV TROUBLE TRACERS

Seven volumes, different guides in ea. Hundreds of TV models. Over 70 illustr. in ea. vol. 40 most common TV Tube troubles Illustr.—50¢ ea.

☐ Vol. 1—Older sets ☐ Vol. 2—'52-'53 sets
☐ Vol. 3—'53-'54 sets ☐ Vol. 4—'54-'55 sets
☐ Vol. 5—'55-'56 sets ☐ Vol. 6—'56-'57 sets
☐ Vol. 7—**JUST OFF PRESS! NEW 1958 Models**

Regular price of all books listed above is $8. If all are ordered same time price is **Only $7.** Check desired books—Clip ad—Print name and address clearly—enclose with remittance.

MAIL NOW TO:

H. G. CISIN, CONSULTING ENGINEER
Amagansett, L.I., N.Y. Dept. E-49

Enclosed Find $.....Rush Books checked above to:

Name.....

Address.....

City.....Zone.....State.....

DYNAKIT

AMPLIFIER KITS

A great amplifier circuit of superb listening quality in money-saving kit form!

MARK III 60 watts **79.95*** net

The New Mark III includes all the sensational attributes of the popular Mark II *plus* these outstanding deluxe features

- ★ 60 watts at less than 1% distortion. Instantaneous peak power of 140 watts. IM less than .05 at average listening levels.
- ★ Choke filtering and low noise circuitry reduce hum and noise to 90 db below 60 watts.
- ★ New rugged KT-88 tubes and other heavy duty parts *used conservatively.*

Mark III also available with added 70 volt output.

Mark III-70 $84.95* net

MARK II 50 watts **69.75*** net

The Mark II is the best buy in high power high fidelity kits

- ★ Ease of assembly due to uniquely simple circuitry and printed circuit construction with factory-mounted parts.
- ★ Highest stability using patented stabilizing networks with minimum number of phase shifting stages. Suitable for all loudspeaker systems including electrostatic.
- ★ Dyna biaset (patent pending) for simplified adjustment and complete freedom from effects of unbalanced components. No balancing adjustments required to meet published specifications.
- ★ Dynaco Super-Fidelity output transformer with patented para-coupled windings. This is the finest available transformer of its type for the most critical audio uses.

COMING SOON!
DYNACO—B & O
PHONO PICKUP
FOR MONOPHONIC AND STEREO DISCS

Available from leading Hi-Fi dealers everywhere. Descriptive brochure available on request.

*Slightly higher in West

DYNACO INC.
Dept. RE, 617 N. 41st St., Phila. 4, Pa.
Export Division: 25 Warren St., New York 7, N. Y.

ductor devices to original equipment manufacturers. His headquarters are in New York. He had been with DuKane Corp. and General Electric.

Walter F. Greenwood (upper left), marketing manager of the General Electric Rectifier Dept., was advanced

to manager of marketing for the Receiving-Tube Dept., Owensboro, Ky. **Stephen J. Welsh** (upper right), New York City district sales manager for the Electronics Components Div., was promoted to manager of marketing for hi-fi components in the Specialty Electronic Components Dept. **Henry B. Nelson, Jr.** (right) is now manager of trade relations and electronic components distributor development in Owensboro. He had been a district sales manager for tubes and components.

B. V. Dale, chief engineer of the former RCA Components Div., was promoted to manager–modules engineering of the Engineering Dept. of the Semiconductor and Materials Div., Somerville, **N. J. Dr. F. E. Vinal** was upped to manager–materials engineering, and **D. H. Wamsley** becomes manager of semiconductor engineering.

Edwin Cornfield, former executive secretary of the Institute of High Fidelity Manufacturers, joined British Industries, Port Washington, N. Y., as sales manager for a number of divisions including Wharfedale loudspeakers, River Edge cabinets and enclosures, Genalex audio tubes and Widney-Dorlec scientific cabinet components.

Gordon E. Parker is the new production manager for the Vermontville, Mich., plant of Michigan Magnetics, Inc. He has been an industrial management-engineer for 16 years. **Jack L. Metz,** an experienced engineer, joined the firm as chief research engineer. **Paul F. Leopold** (above), ex-Pentron and Crescent Industries, joined Michigan Magnetics as sales manager of the new Distributor Div., with headquarters in Chicago.

Harold P. Field, general manager of Stromberg-Carlson's plants in San Diego, assumes additional responsibili-

FULL RANGE FM RECEPTION!
G-C-TELCO
GOLDEN TURNSTILE ANTENNA
Completely Preassembled
Non-rusting gold anodized aluminum elements snap into place. Everything is furnished; there is nothing else to buy. You get perfect reception up to 50 miles from transmitters.
COMPLETE KIT NO. A-125 (shown above).....List $18.95
TURNSTILE KIT NO. A-124 standard aluminum elements....List $15.95
FM Golden Dipole Kit No. A-267..List $17.25
Dipole Kit No. A-261 standard aluminum elements.....List $14.95
AT YOUR DEALER OR WRITE DIRECT
TELCO ELECTRONICS MFG. CO.
Division of G-C Textron Inc.
Los Angeles—Rockford, Illinois

tes as director of marketing of the Electronics Div.

Alfred P. Wertz joined Weller Electric Corp. as European sales manager. He will maintain headquarters in Easton, Pa., and Düsseldorf, Germany. He comes to Weller from Messinger Manufacturing Co., where he was sales and export manager.

Wen Products Inc. Chicago, launched a king-size advertising campaign for the fall and Christmas seasons. Here Nick Anton (seated), president of Wen, discusses the program with Jim Cody,

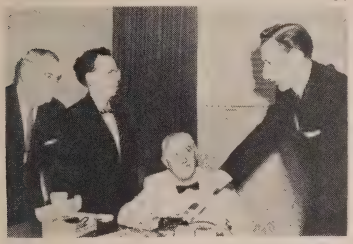

Burton Browne Advertising Agency vice president (right), as Wen sales manager, Miles Blunt (left) and agency manager Bob Abbott look on.

CBS-Hytron, Danvers, Mass., is offering service technicians a new junior

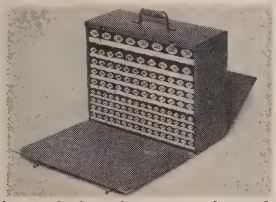

version of its famous tube-and-tool caddy.

Ralph Bellamy (left), stage, screen and TV actor is shown with Stan Neufeld, sales manager of **Rockbar Corp.,**

Mamaroneck, N. Y. with the new Collaro stereo changer. The actor will be featured in the fall advertising campaign for Collaro in advertisements in trade and consumer publications.

JFD Electronics Corp., Brooklyn, N. Y., kicked off a Harvest of Profits advertising campaign, the heaviest in its history, to push sales of its Satellite-Helix antennas. END

FREE

GIANT ALL NEW 1959

B-A CATALOG

WITH THE BIGGEST SAVINGS ANYWHERE

A COMPLETE BUYING GUIDE FOR EVERYTHING IN

RADIO TV ELECTRONICS

B/A 1959 ANNUAL CATALOG 591

SINCE 1927

Guarantee

We guarantee everything in our Catalog to be of the quality and value represented ... to conform exactly to the illustration and description ... to perform in the manner and give the service intended for such apparatus.

180 KING-SIZED PAGES

EVERYTHING IN RADIO TV AND ELECTRONICS

100'S OF NEW ITEMS LISTED HERE FOR 1ST TIME

21 PAGES OF BARGAINS NOT IN ANY OTHER CATALOG

RUSH COUPON TODAY!

BURSTEIN-APPLEBEE

BURSTEIN-APPLEBEE CO. Dept. S,
1012-14 McGee St., Kansas City 6, Mo.

☐ Send Free 1959 B-A Catalog No. 591.

NAME_____

ADDRESS_____

CITY_____ STATE_____

LOOK

no further . . . if you're searching for hi-fi savings. Write us your requirements now.

Key Electronics Company
120-A Liberty St, N.Y. 6, N.Y.
EV 4-6071

BOOK MANUSCRIPTS
CONSIDERED

by cooperative publisher who offers authors early publication, higher royalty, national distribution, and beautifully designed books. All subjects welcomed. Write, or send your MS directly.

GREENWICH BOOK PUBLISHERS, INC,
Atten. MR. IMMS 489 FIFTH AVE.
NEW YORK 17, N. Y.

ENGINEERING

B. S. DEGREE IN 27 MONTHS

Prepare for unlimited opportunities of the Electronic Age! Earn your B.S. DEGREE IN 27 MONTHS in Aeronautical, Chemical, Civil, Electrical or Mechanical Engineering; in 36 MONTHS in Mathematics, Chemistry, Physics. Intensive, specialized courses. Comprehensive training in electronics, television, advanced radio theory and design, math, nuclear physics and elec. eng. Engineering Science preparatory courses. Low rate. Graduates in demand. Spacious campus; 20 bldgs., dorms, gym, playing field. Earn part of your expenses in Fort Wayne. G.I. approved. Enter Dec., March, June, Sept. Catalog.

INDIANA TECHNICAL COLLEGE
1711 E. Washington Blvd., Fort Wayne 2, Indiana

Please send me free information on B.S. ENGINEERING DEGREE IN 27 MONTHS as checked.

☐ Electronics ☐ Chemical ☐ Aeronautical
☐ Civil ☐ Mechanical ☐ Electrical
B.S. DEGREE IN 36 MO. in: Math.☐ Chem.☐ Physics☐

Name_____

Address_____

TRUE HI-FI
for PUBLIC ADDRESS
VOICE and MUSIC

WT-6 LIST $57.50
support stand only,
SS-4 LIST $21.00
Subject to full trade discounts.

new ATLAS
COAX-PROJECTOR WT-6

for wherever HI-FI is a MUST, indoors or out . . entertainment places: theatres, auditoria . . . industrial music & paging systems . . outdoors: carnivals, pools, boat clubs . . home patios, gardens . . permanent or portable installations.

ALL-WEATHER
— install it, forget it! —
HIGH-EFFICIENCY . . COMPACT . .

True HIGH FIDELITY TWO-WAY system — not just a "compromise" of two horns coupled to a single diaphragm. The WT-6 comprises a weather-proof cone type driver (with 6-inch throat) coupled to its individual woofer horn; a separate pressure-type driver loaded to its separate tweeter horn. The built-in crossover electronic filter supplements the electro-mechanical frequency-limiting characteristics of the 2 individual reproducers — providing for smooth frequency division as each speaker functions within its engineered range of frequencies.

Universally adjustable "U"-type rugged steel mounting . . . finished in high temperature baked modern beige enamel.

Power Rating	15 watts continuous
Freq. Resp.	140-15,000 cps
Impedance	8 ohms
Dispersion	120°
Dimensions	Bell opening 15", overall depth 12"

See the WT-6 at your local distributor.
Send for complete catalog R-11.

ATLAS SOUND
ATLAS SOUND CORP.
1443-39 St., Brooklyn 18, N. Y.
Atlas Radio Ltd., Toronto, Canada

LITERATURE

Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears. UNLESS OTHERWISE STATED, ALL ITEMS ARE GRATIS. ALL LITERATURE OFFERS ARE VOID AFTER SIX MONTHS.

RESISTANCE DECADE BOXES of 9 different types are pictured in 8-page *Catalog 20D*, which also contains a decade-box selection chart and listing of performance characteristics.—**Cinema Engineering Div.**, Aerovox Corp., Sales Promotion Dept., 1100 Chestnut St., Burbank, Calif.

ELECTRONIC ITEMS by the hundred, from capacitors and tubes to closed-circuit TV cameras and microwave components, are offered in 28-page *Green Sheet*, listing both new and surplus equipment.—**Barry Electronics Corp.**, 512 Broadway, New York 12, N. Y.

METAL FILM RESISTORS for precision applications, in the new Riteohm 77 series are detailed in *Bulletin 155*.—**Ohmite Manufacturing Co.**, 3696 W. Howard St., Skokie, Ill.

ELECTRONICS CATALOG, *No. 590*. This 260-page book lists stereo and hi-fi equipment of major manufacturers as well as Lafayette's own products—also TV and radio parts, transistor kits and miniaturized components, antennas and installation accessories, amateur gear and tools, as well as sections on industrial equipment, precision scientific instruments and public-address systems.—**Lafayette Radio**, 165-08 Liberty Ave., Jamaica 33, N. Y.

SOLDERLESS TERMINALS and crimping tools are completely illustrated and described in 12-page *Catalog No. T-70*. Also shown are merchandising displays and special-purpose plastic service kits.—**Vaco Products Co.**, 317 E. Ontario St., Chicago 11, Ill.

HI-FI CATALOG *No. 101* contains photographs and specifications of a complete line of amplifiers, tape transports and tuners, together with questions and answers about hi fi and stereo.—**Bell Sound Systems Inc.**, 555 Marion Rd., Columbus, Ohio.

TRANSISTOR CIRCUITS for hams and hobbyists are described in a how-to-build-it brochure, with schematics of transistor audio power amplifier, power

ENGINEERING
Home Study Courses

COURSES written by world authorities in all branches of engineering. Step-by-step instructions using methods proved successful by thousands of our graduates. One hour each day in your spare time will start you off to higher pay, security, prestige. Check the course you are interested in and we will send you a complete outline of the course with a booklet describing the Institute and our advanced methods of teaching. Send to: Canadian Institute of Science and Technology Ltd., 683 Century Bldg., 412, 5th St. N.W., Wash., D.C.

Civil Eng.	Electrical Eng.
Surveying	Radio
Architecture	Electronics
Forestry	Television
Mining	Aeronautical Eng.
Structural	Aircraft Engineer
Mechanical Eng.	Navigation
Industrial Eng. & Management	General Education
Refrigeration	Chemical
Heating	Mathematics
Drafting	Journalism
Plastics	Accounting

NAME.....

ADDRESS.....

CITY..... STATE.....

Course Interested In.....

Canadians: Send to Canadian Institute of Science & Technology Limited, 698 Garden Bldg., 263 Adelaide St. West, Toronto, Ont.

"NOISE" BIG 3
Beware Of Cheap Substitutes!

NO-NOISE NEW RUBBER COAT SPRAY
- Insulates where applied
- Protects indefinitely
- Prevents arcing, shorting, corrosion
- Waterproofs thoroughly
- Non-inflammable
- Contains no plastic

6 Oz. Spray Can Net To Servicemen **$3.25**

NO-NOISE VOLUME CONTROL and CONTACT RESTORER
• Cleans • Protects • Lubricates
NOT A CARBON TET SOLUTION

2 Oz. Bottle — Net To Servicemen **$1.00**
6 Oz. Spray Can — Net To Servicemen **$2.25**

NO-NOISE TUNER-TONIC With PERMA-FILM
- Economical—a little does a lot!
- Cleans, lubricates, restores all tuners, including wafer type.
- Non-toxic, non-inflammable.
- Use for TV, radio and FM

6 Oz. Aerosol Can Net To Servicemen **$3.25**

ELECTRONIC CHEMICAL CORP.
813 Communipaw Avenue Jersey City 4, N. J.

control, battery charger, model power supply, regulated power supply, model train control, Geiger counter and dc-to-dc converter. All use type 2N554 power transistors. — **Motorola Inc.,** Semiconductor Products Div., 5005 E. McDowell Rd., Phoenix, Ariz., or Motorola semiconductor distributors.

AUTO RADIO TRANSFORMERS and their exact replacements are listed for more than 400 models of 37 brands, including a special section on transistor radios, in 16-page *Catalog No. 500, Stancor Auto-Radio Transformer Replacement Guide.* Replacement data for vibrator, audio, driver and interstage transformers are given for all models.—**Chicago Standard Transformer Corp.,** 3501 Addison St., Chicago 18, Ill.

STEREO CARTRIDGE DATA, *Bulletin E-289,* gives complete specifications, with outline drawing, frequency response curve and installation instructions, for the Columbia cartridge Model SC-1.—**CBS-Hytron Advertising Service,** Parker St., Newburyport, Mass.

REPLACEMENT CAPACITORS for all TV sets manufactured from 1946 through 1957 are listed in 56-page *TV Replacement Capacitor Manual K-103.* The ninth edition of this popular book lists thousands of sets arranged alphabetically under nearly 100 TV trade names. In the back of the book are complete listings of Sprague capacitors.—**Sprague Products Co.,** 81 Marshall St., North Adams, Mass. **10c. Free** from Sprague distributors.

INDUSTRIAL TUBE CHART, *T-24.* Handy 30-page flip-style chart, printed on heavy-duty coated paper, indexes industrial tubes by class, briefly explains the use of each class and gives technical information for each type.—**Tung-Sol Electric Inc.,** 95 8th Ave., Newark 4, N. J.

TEST INSTRUMENTS are described and illustrated, with schematics, in 8-page 2-color *Sencore Catalog No. 119.*—**Service Instruments Corp.,** 171 Official Rd., Addison, Ill.

IGNITION INTERFERENCE in automobiles and boats and how to suppress it is treated in a 4-page brochure, *Electrical Interference Suppression for Two-Way Radio Installations,* valuable to anyone who has interference problems in mobile or auto radio.—**Electric Auto-Lite Co.,** Toledo 1, Ohio.

TEST EQUIPMENT catalog, 12 pages, describes in detail 3 models of *Kingston Absorption Analyzers* and accessory equipment, featuring electrostatic pick-up for waveform analysis of circuits in 3–240-mc range.—**Kingston Electronic Corp.,** Medfield, Mass.

MOBILE RECEIVERS *M-40* and *M-160,* tunable in the 30–50- and 152–174-mc bands, are the subjects of a spec sheet. —**Monitoradio Div.,** I.D.E.A. Inc., 7900 Pendleton Pike, Indianapolis, Ind. END

COSMOTRON*

- MINIATURE ATOM SMASHER
- PRODUCES 75,000 VOLTS
- ABSOLUTELY SAFE

In no sense of the word a toy or a gadget. The COSMOTRON* is a scientific instrument capable of producing 75,000 volts—makes sparks up to 2" long—yet is absolutely safe because the current is infinitesimal. The science teacher—science lover—or hobbyist can perform experiments to astound students—friends—family. Makes smoke disappear—defy gravity—turns propellers at a distance—transforms atomic energy into light—makes artificial lightning—demonstrates ionic space ship drive—and many other experiments. Constructed of the finest materials. Will do exactly—for instruction purposes—what generators that cost 3 to 10 times more will do. The perfect device to teach the secrets of atomic physics and electricity. Will hold an audience spellbound as it performs trick after amazing trick. Includes an experiment kit and illustrated experiment manual. Manual explains the "how" and "why." You will invent many new experiments of your own. A fine research tool that will give years of beneficial service to the institution or individual who owns one. In kit form or assembled.

*TM Pending

Kit form $14.95
Assembled $19.95

Build 125 Computers At Home

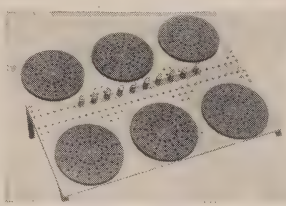

Control Panel of GENIAC® set up to do a problem

You can construct over 125 different machines that compute, reason, solve puzzles and demonstrate a wide variety of basic computed circuits with the GENIAC® electric brain construction kit. Over 30,000 schools, colleges, industrial firms and private individuals have bought GENIACS® since we first brought them on the market.

We have recently added a circuit for composing music, which gives us special pleasure because is was designed by a 16 year old boy who learned about computers from his GENIAC®. Dozens of other youngsters have created their own designs for computing circuits, used GENIACS® in their school projects and established a solid foundation of information on compueters with GENIACS®.

Each kit comes complete with Beginners Manual, Study Guide, instructions for building all the machines and circuits (exclusive with our GENIAC®, parts tray, and our complete question answering service. When you buy a GENIAC® you are buying a first course in computer operation.

Each kit comes with a one week money back guarantee if you are not satified.

Price of Kit complete with parts tray, rack, all components, manuals and texts $19.95 (postpaid in U.S., add 80c west of Mississippi). **($21.95 outside United States.)**

MAIL THIS COUPON

(Please be sure to include your name & address)
OLIVER GARFIELD CO., Inc., Dept. RE-118
108 E. 16th St., New York 3, N.Y.

Please send me:
1 COSMOTRON Atom Smasher and Manual.
$19.95 (Complete assembled) .....
$14.95 (In kit form) .....
Add 80¢ for postage and handling in U. S.; $1.00 abroad.
1 GENIAC® Electric Brain Construction Kit and Manual. .....
Add 44¢ for postage in U.S.; $1.00 abroad.

Do you recognize these scope patterns?

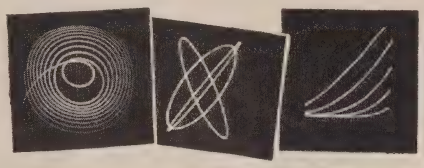

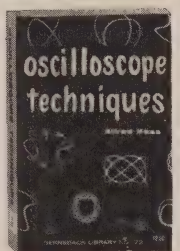

Here are only a few of the hundreds of unusual waveforms illustrated in this new handbook on better scope procedure—"Oscilloscope Techniques" by electronics engineer Alfred A. Haas. He shows you how to understand and interpret waveforms. Tells how to master the scope and put it to many new uses. Now increase your efficiency with the scope 50% or more for better servicing, experimenting and lab work.

TEN BIG CHAPTERS

The Cathode-Ray Tube • Oscilloscope Circuitry • Oscilloscope Accessories • Measuring Electrical Magnitudes • Networks and Waveforms • Display of Characteristics • Fundamental Electronic Circuits • Checking Receiver Circuits • Waveforms in Black-and-White and Color Television • Oscilloscope Fault Patterns • plus a complete index

OSCILLOSCOPE TECHNIQUES
Gernsback Library Book
No. 72. 224 pages
Paper cover ed. $2.90
Hard cover ed. $4.60

OTHER POPULAR G/L BOOKS

Paper cover editions

No. 68—TV and Radio Tube Troubles $2.90
No. 60—Rapid TV Repair 2.90
No. 59—Servicing Record Changers 2.90
No. 57—The VTVM 2.50
No. 55—Sweep and Marker Generators for Television and Radio 2.50
No. 54—Probes 2.50
No. 52—The Oscilloscope 2.25

SEE YOUR DISTRIBUTOR OR MAIL THIS COUPON TODAY

Gernsback Library, Inc., Dept. 118
154 West 14th St., New York 11, N. Y.

My remittance of $..... is enclosed. Please send me books checked, postpaid. No. 72—Oscilloscope Techniques

☐ Paper cover ed. $2.90 ☐ Hard cover ed. $4.60
☐ 68 ☐ 60 ☐ 59 ☐ 57 ☐ 55 ☐ 54 ☐ 52

Name_____
please print
Street_____
City_____Zone_____State_____

Giant Pre-Christmas SALE

OF 1958'S BIGGEST-SELLING

$1 POLY-PAKS®

FREE! Your Choice of ANY ITEM IN THIS AD FREE WITH $10 ORDER!

70 TERMINAL STRIPS
☐ Solder-lug & binding; to 20 terminals. $1
2 lbs.

60 ONE-WATTERS
☐ Asstd. value carbon resistors. 5%, too! $1

2 MINIATURE SOLENOIDS
☐ 12 VDC. Needs small battery to actuate plunger. Reg. $6. $1
1 lb.

80 HALF-WATTERS
☐ Asstd. value carbon resistors, incl. 5%. $1
Reg. $12.

0000-9999 COUNTER
☐ Weeder-Root, w / double shafts. $1
Reg. $5.

75 MICA CONDENSERS
☐ .00025 to .01 to 1200 V. Silver, too. 25 $1
values. Reg. $28.

10 ELECTROLYTICS
☐ Radio, TV, 10-500mf to 450 VDC. Wt. 3 $1
lbs. Reg. $12.

SYLVANIA TV MIRROR
☐ 10x12" Stainless steel. Many uses! 2 lbs. $1
Reg. $4.

$25 SURPRISE PACK!
☐ Large & varied asst. radio & TV parts. $1
3 lbs.

40 TUBE SOCKETS
☐ 4 to 9-pin; ceramic, mica, shield-based. $1
incl. 2 lbs. Reg. $10.

70 HI-Q CARBON RESISTORS
☐ IRC, Ohmite, 10%, too! ½, 2W; 10 ohms to $1
10 megs. 2 lbs.
Reg. $13.

125 CERAMIC CONDENSERS
☐ Hi-Q discs, tubulars; to .01 mf. 2 lbs. $1
Reg. $12.50.

60-CONDENSER SPECIAL!
☐ Molded, paper, ceramic, oil, mica, discs, $1
variable. 2 lbs.

75-PC. RESISTOR SPECIAL!
☐ WW, precision, carbon, variable, mini types. $1
3 lbs.
Worth $15.

WORLD'S SMALLEST RADIO
☐ 2x1x1" KIT includes loopstick, jacks, diode, etc. w/instructions. $1
Wt. 1 lb. Reg. $3.

6 SILICON DIODES
☐ Sylvania 1N22, 1N23. Reg. $36. $1

2 PNP TRANSISTORS
☐ Pop. make, for hundreds projects. $1
$5 value.

2 MIKE TRANSFORMERS
☐ Carbon. Imp. 100 to 100K ohms. Leads, encased. 2 lbs. $1
Reg. $10.

70 TUBULAR CONDENSERS
☐ Paper, molded, oil, pore. .0002 to .5mf to 100V. 2 lbs. $1
Reg. $14.

8 GERMANIUM DIODES
☐ w/long leads. Glass sealed. Reg. $5. $1

300-FT. HOOKUP WIRE
☐ Tinned, asstd colors, sizes. 2 lbs. $1
Reg. $5.

POSTAGE STAMP MIKE
☐ Crystal, 100 to 8,000 cps. 1 lb. $1
Reg. $7.

150 CARBON RESISTORS
☐ ⅛ to 2W; 15 ohms to 1 meg. incl. insulated types. 2 lbs. $1

8-PC. NUTDRIVER KIT
☐ 3 value. Plastic handle, 3/16, 7/32, ¼; 5/16, 11/32, 3/8, 7/16" steel socket wrenches $1
in plastic case. 1 lb.

2000 PCS. HARDWARE
☐ Nuts, screws, washers, etc. 2 lbs. $1
Reg. $8.

40 PRINTED CIRCUIT PARTS
☐ Diodes, chokes, resistors, cond., boards. $1
1 lb. Reg. $7.

60 SUB-MINI RESISTORS
☐ ¼" long; 30 values; 1/5W to 10 megs. $1
Reg. $6.

60 KNOBS, RADIO & TV
☐ Asstd. colors, insulation. Some worth $1 ea. Wt. 2 lbs. $1
Reg. $17.

15 VOLUME CONTROLS
☐ incl. duals. To 1 meg; some w/switch. 2 $1
lbs. Reg. $12.

15-PC. TWIST DRILL KIT
☐ 1/16 thru ¼" by 64ths, w/calibrated $1
case. Reg. $3.

MINI-METER
☐ 1¾" diameter. 0-6 amps, AC. 1 lb. $1
Reg. $3.

30 MOLDED CONDENSERS
☐ Black beauties, incl. Finest made! $1
Wt. 2 lbs.

15 ROTARY SWITCHES
☐ Asstd. gangs, 3 $1
lbs. Reg. $12.

40 DISC CONDENSERS
☐ Wafer-thin, to .01 $1
mf. Reg. $5.

12 POLY BOXES
☐ Clear plastic, hinged, w/snap locks. Asstd. sizes. Wt. $1
1 lb.

8 TRANSMITTER SOCKETS
☐ Mica-filled; for sub-mini tubes, too. $1

40 HI-Q CONDENSERS
☐ Finest porcelain; NPO's too! 1 lb. $1
Reg. $6.

35 POWER RESISTORS
☐ WW, 5 to 50 W, to 10,000 ohms; incl. vitreous. 3 lbs. $1
Reg. $15.

40 PRECISION RESISTORS
☐ 1%, ½ & 1W; Carbon & WW. 100 ohms to 1 meg. $1
Reg. $17.

70 COILS, CHOKES
☐ IF, RF, ant. slug-tuned, too. 3 lbs. $1
Reg. $15.

HOW TO ORDER Check items wanted. Return entire ad w/check or M.O. including sufficient postage; excess returned. C.O.D. orders 25% down; rated, net 30 days. Print name, address WITH POSTAL ZONE NO., amount money enclosed, in margin. (Canada postage, 48¢ 1st lb., 28¢ ea. add'l. lb.) EXPORT ORDERS INVITED.

LEKTRON 131 Everett Ave. CHELSEA 50, MASS.

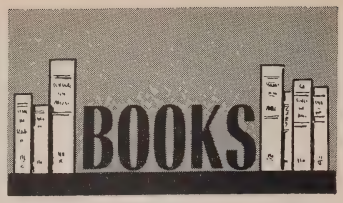

PRINCIPLES OF NOISE, by J. J. Freeman. John Wiley & Sons, Inc., 440 Fourth Ave., N. Y. 16, N. Y. 6 x 9¼ in., 299 pp. $9.25.

A highly mathematical and technical presentation of the principles, facts and techniques used in noise analysis. Definitely for the advanced student, dealing with such topics as probability, power spectra and noise factor of various circuits.—*LS*

ATOMIC RADIATION. RCA Service Co., Camden 8, N. J. 8½ x 11 in., 110 pp. $1.60.

This is a revised reprint of an earlier book. It deals with radiation theory, biological effects and medical treatment. Workers who may expose themselves to radiation must know the safety rules contained here if they are to avoid injury.

The book begins with the theory of charged particles and how they affect various parts of the body. One chapter illustrates and describes counters and dosimeters and tells how to use them. The symptoms of excess radiation and its treatment are given in detail. The all-important matter of permissible levels is given in the final chapter.

Each chapter includes numerous references for further study.

INDUSTRIAL ELECTRONICS HANDBOOK, by R. Kretzmann. Philosophical Library, 15 E. 40 St., N. Y. 16, N. Y. 6 x 9 in., 298 pp. $12.

An enlarged and revised edition of an earlier book, this manual is translated from the Dutch and is part of the Philips' Technical Library. Using European tube designations and circuits, its chapters deal with various types of relays, counting circuits, timers, rectifiers, lamp dimmers, speed and temperature controls, resistance welding, motor control, inductive and capacitive heating and special-purpose apparatus.

ENGINEERING ELECTROMAGNETICS, by William H. Hayt, Jr. McGraw-Hill Book Co., Inc., 330 W. 42 St., N. Y. 36, N. Y. 6 x 9 in., 328 pp. $8.50.

Modern science and engineering would be impractical without the shorthand of math. Certain topics like electric and magnetic fields require a very *concise* shorthand. This is provided by a special branch of math called vector analysis. This author discusses steady and varying fields and shows how to use vectors.

The text is based on Maxwell's laws as derived from early experiments. Gradient, divergence and curl are explained clearly for beginners. Some examples are worked out, others are left for the student. Calculation of capaci-

the indoor TV antenna of the FUTURE!

Channel King®

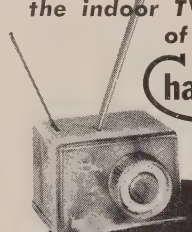

- Hands never touch Antenna Arms - Extends to 42" --- Retracts to 0"!
- Arms COMPLETELY retractable, flexible and indestructible!
- FAST SINGLE dial tuning and adjusting!
- Very COMPACT attractive appearance!
- 5 beautiful decorator colors.....

MAHOGANY BUTTERSCOTCH
IVORY ALABASTER JADE

REGULAR RETAIL PRICE $12.95

FALL SPECIAL PRICE **$7.95**

See your local dealer or distributor, or order direct . . . cash, check or money order to:

(*Money back if not completely satisfied*)

MARJO TECHNICAL PRODUCTS CO.
1148 East Henry Street Linden, New Jersey

The Biggest Ever! New 1959 Catalog of

ELECTRONICS

HIGH FIDELITY, RADIO, TV, AND AMATEUR EQUIPMENT

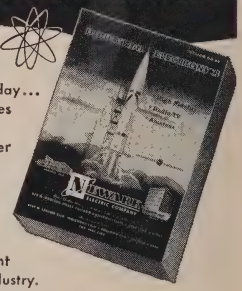

FREE!

Write today... 388 pages packed from cover to cover with the newest and finest equipment in the industry. For prompt, efficient service and low prices, write . . .

Your One Point Source for Electronic Equipment.

NEWARK ELECTRIC COMPANY

Dept.RE-11—223 W. Madison, Chicago 6, Ill.
Dept.RE-11—4747 Century, Inglewood, Calif.

tance, field mapping, radiation, circuit theory and relativistic effects are described. A text for readers who wish to study advanced engineering.—*IQ*

PIN POINT COLOR TV TROUBLES IN 15 MINUTES, edited by Harold P. Manly. Book Publishing Div., Coyne Electrical School, 500 S. Paulina St., Chicago 12, Ill. 5½ x 8¼ in., 548 pp. $5.95.

A practical book on troubleshooting color TV intended for the practicing technician. A thousand faults which cause a total of 150 troubles are listed. Check charts are used to help point out possible trouble spots. Every section of the modern color TV receiver is treated in detail, with oscillograms of important waveforms and partial schematics where needed.—*LS*

REPAIRING PORTABLE AND CLOCK RADIOS, by Ben Crisses and David Gnessin. John F. Rider Publisher, Inc., 116 W. 14 St., N. Y. 11, N. Y. 5½ x 8½ in., 120 pp. $2.75.

The radio repair business is highly competitive. Only skilled and alert technicians can survive. This book is designed to help them to speed up the repair, alignment and improvement of portable and clock radios. It discusses clearly the basic problems: filament circuitry, three-way power supplies, miniature components, printed layouts, as well as more conventional troubles.

The authors have incorporated practical information on transistors, semiconductor rectifiers, batteries and full alignment procedure. They show how to modernize a set by adding a phone jack, installing a selenium rectifier, converting to a ferrite loopstick, etc. The final chapter on clock radios shows how to maintain and service the mechanism. —*IQ*

RADIO ELECTRONICS, by Samuel Seely. McGraw-Hill Book Co., Inc., 330 W. 42 St., N. Y. 36, N. Y. 6 x 9 in., 487 pp. $7.

This excellent text for reference or study discusses electron tubes and the circuits in which they are used. Emphasis is on the methods of analysis, with mathematics used freely. Each chapter ends with practical design problems.

Tubes, amplifiers, oscillators and modulators are covered in detail. There are also chapters on information theory, filters and detectors. A chapter on FM (transmitters and receivers) studies in detail all detectors including the ratio, Bradley, gated-beam, etc.—*IQ*

DAVE RICE'S OFFICIAL PRICING DIGEST, Vol. 3, No. 1. Electronic Publishing Co., 180 N. Wacker Dr., Chicago 6, Ill. 3¾ x 9¾ in., 245 pp. $2.50.

This new edition of the pocket-size handbook for TV–radio technicians lists suggested retail prices of more than 60,000 items, including tubes, batteries, antennas and components. It also contains a special section showing regional and national average service charges for typical television repair jobs.

END

ALL SERVICE DEALERS LOOK TO DeRO

SELECT-O-SWITCH
4-WAY SELECTOR SWITCH
Use as antenna switch or as a hi-fi speaker switch. Permits channeling one input to any one of 4 outputs.
model SS4 LIST $3.25

Switch-in-Base
DUO-JUVENATOR
Parallel and Series TV tube booster. Cures 95% of all CRT failures. One-piece construction.
model RPS2 LIST $2.95

TELE-LINK
2-SET TV & FM COUPLER

Matched transformers for peak performance on 2 TV or FM sets from one antenna.
model TL2 LIST $2.95

DeRO Electronics
134 NASSAU ROAD, ROOSEVELT, N.Y.

SENCORE
Another Sencore Time-Saver
Handy "36" R-C Substitution Unit

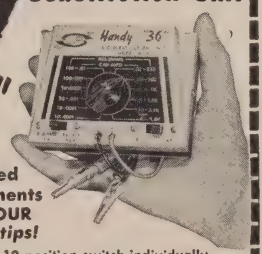

"36" Most Often Needed Components At YOUR Fingertips!

3 pole, 12 position switch individually selects one of the "36" components for direct substitution.

Contains:
★ 12—1 watt 10% resistors from 10 ohms to 5600 ohms
★ 12—½ watt 10% resistors from 10K ohms to 5.6 megohms
★ 10—600 volt capacitors from 100-mmfd. to .5mfd.
★ 1—10mfd., 450V Electrolytic
★ 1—40mfd., 450V Electrolytic
★ For Shop, Lab, or outside service

ONLY $12.75 DEALER NET
Completely isolated

POPULAR SENCORE PRODUCTS
• Transistor Tester
• Leakage Checker
• Filament Tester
• Voltage Regulator
• Bias Supply

AVAILABLE AT ALL PARTS DISTRIBUTORS!
SENCORE SERVICE INSTRUMENTS CORP.
171 OFFICIAL RD., ADDISON, ILL.
Cut out this ad now for further information.

"ONE DOLLAR" buys
As much as $15 worth — Everything Brand New and sold to you with a money back guarantee.

DEDUCT 10% ON ANY ORDER OF $10 OR OVER
Plus a FREE SURPRISE PACKAGE

☐ $15 — "JACKPOT" TELEVISION PARTS....$1
☐ 40 — ASSORTED PRECISION RESISTORS....$1
☐ 4 — ELECTROLYTIC CONDENSERS 10/10-450v..$1
☐ 5 — ELECTROLYTIC CONDENSERS 30-450V...$1
☐ 20 — TUBULAR CONDENSERS .25-600v, 85°...$1
☐ 20 — TUBULAR CONDENSERS .001-1000v....$1
☐ 100 — ASSORTED FUSES popular sizes.....$1
☐ 100 — ASST. ½ WATT RESISTORS some 5%...$1
☐ 70 — ASSORTED 1 WATT RESISTORS " ...$1
☐ 35 — ASSORTED 2 WATT RESISTORS " ...$1
☐ 50 — ASST. TUBULAR CONDENSERS.....$1
☐ 10 — 6' ELECTRIC LINE CORDS with plugs....$1
☐ 5 — TV CHEATER CORDS with both plugs.....$1
☐ 4 — 50' SPOOLS HOOK-UP WIRE 4 colors.....$1
☐ 50 — STRIPS ASST. SPAGHETTI best sizes $1
☐ 100 — ASST. RUBBER GROMMETS best sizes ..$1
☐ 100' — TWIN LEAD-IN WIRE 300Ω heavy duty...$1
☐ 50' — FLAT 4-CONDUCT. WIRE many purposes .$1
☐ 25'—INSULATED SHIELDED WIRE $1
☐ 1 — $7 INDOOR TV ANTENNA hi-gain 3 section .$1
☐ 20 — ASST. TV KNOBS, ESCUTCHEONS, Etc..$1
☐ 3 — ASST. TOGGLE SWITCHES spst, dpdt, etc..$1
☐ 4 — BAKELITE KNIFE SWITCHES dpdt $1
☐ 15 — ASST. ROTARY SWITCHES $15 worth....$1
☐ 100' — FINEST NYLON DIAL CORD best size....$1
☐ 200 — SELF TAPPING SCREWS #8 x ½".....$1
☐ 35 — ASST. RADIO KNOBS screw and push-on...$1
☐ 100 — KNOB SPRINGS standard size ⅜" x ½"..$1
☐ 100 — ASSORTED KNOB SET-SCREWS.....$1
☐ 25 — ASSORTED CLOCK RADIO KNOBS.....$1
☐ 400 — ASST. H'DWARE screws, nuts, rivets, etc..$1
☐ 50 — ASST. SOCKETS octal, noval and miniature..$1
☐ 20 — ASSORTED TUBE SHIELDS best sizes.....$1
☐ 50 — ASST. MICA CONDENSERS some in 5%..$1
☐ 50 — ASST. CERAMIC CONDENSERS " $1
☐ 10 — ASST. VOLUME CONTROLS less switch...$1
☐ 5 — ASST. VOLUME CONTROLS with switch ...$1
☐ 100 — VOLUME CONTROL HEX NUTS.....$1
☐ 20 — ASST. PILOT LIGHTS popular types.....$1
☐ 10 — PILOT LIGHT SKTS. bayonet type, wired...$1
☐ 50 — ASST. TERMINAL STRIPS 1, 2, 3, 4 lug...$1
☐ 10 — ASST. RADIO ELECTRO. CONDENSERS.$1
☐ 5 — ASST. TV ELECTROLYTIC CONDENSERS.$1
☐ 15 — ASST. TV COILS sync. peaking, width, etc. .$1
☐ 25 — ASST. MICA TRIMMER CONDENSERS..$1
☐ 50 — TUBULAR CONDENSERS .001-600v.....$1
☐ 50 — TUBULAR CONDENSERS .01-400v.....$1
☐ 2 — ELECTROLYTIC COND. 40/40-450V.....$1
☐ 2 — ELECTROLYTIC COND. 40/10/10-450v....$1
☐ 30 — FP CONDENSER MOUNTING WAFERS..$1
☐ 3 — ELECTROLYTIC CONDENSERS 80-450v ..$1
☐ 3 — ELECTROLYTIC COND. 50/30-150v. $1
☐ 10 — HV TUBULAR CONDENSERS .001-5000v..$1
☐ 10 — HV TUBULAR CONDENSERS .005-3000V..$1
☐ 35 — MICA COND. 20 - 100 mmf & 15-270 mmf. $1
☐ 35 — MICA COND. 20 - 470 mmf & 15-680 mmf. $1
☐ 35 — MICA COND. 20 - 820 mmf & 15-1000 mmf $1
☐ 35 — CERAMIC COND. 20 - 5 mmf & 15-10 mmf. ...$1
☐ 35 — CERAMIC COND. 20 - 25 mmf & 15-47 mmf. ..$1
☐ 35 — CERAMIC COND. 20 - 56 mmf & 15-82 mmf ...$1
☐ 35 — CERAMIC COND. 20 - 100 mmf & 15-150 mmf ..$1
☐ 35 — CERAMIC COND. 20 - 270 mmf & 15-470 mmf ..$1
☐ 35 — CERAMIC COND. 20 - 1000 mm f & 15-1500 mmf ..$1
☐ 35 — CERAMIC COND. 20 - 2000 mmf & 15-5000 mmf ..$1
☐ 50 — 100Ω ½ WATT RESISTORS 5% $1
☐ 75 — 470KΩ ½ WATT RESISTORS 10%.....$1
☐ 50 — 470KΩ 1 WATT RESISTORS 10%.....$1
☐ 10 — ASST. WIREW'ND RES. 5, 10, 20 watts...$1
☐ 3 — AUDIO OUTPUT TRANS. 50L6 type $1
☐ 3 — AUDIO OUTPUT TRANS. 6K6 or 6V6 type...$1
☐ 3 — I.F. COIL TRANSFORMERS 456 kc $1
☐ 3 — I.F. COIL TRANSFORMERS 10.7 mc FM ...$1
☐ 4 — OVAL LOOP ANTENNAS ass't hi-gain types ..$1
☐ 3 — LOOPSTICK ANT. new ferrite adjustable....$1
☐ 12 — RADIO OSCILLATOR COILS 456 kc.....$1
☐ 3 — ½ MEG VOLUME CONTROLS with switch ..$1
☐ 3 — FOCUS CONTROLS 400, 2K & 5KΩ $1
☐ 10 — SURE GRIP ALLIGATOR CLIPS.....$1
☐ 1 — GOLD GRILLE CLOTH 14"x14" or 12"x18"..$1
☐ 1 — 5" PM SPEAKER alnico ⅝ magnet.....$1
☐ 5 — SETS SPEAKER PLUGS wired $1
☐ 10 — SETS PHONO PLUGS and PIN JACKS..$1
☐ 2 — $2.50 SAPPHIRE NEEDLES 4000 playings...$1
☐ 5 — DIODE CRYSTALS 2-IN21 2-IN22 1-IN64 ..$1
☐ 3 — DIODE CRYSTALS IN34, IN60, IN69.....$1
☐ 2 — SELENIUM RECTIFIERS 1-65 ma & 1-150 ma $1
☐ 5 — ASST. VHF TUNER STRIPS $1
☐ 3 — ASST. UHF TUNER STRIPS.....$1
☐ 5 — TV CRT. SOCKETS with 18" leads.....$1
☐ 5 — HI-VOLT. ANODE LEADS with 18" leads....$1
☐ 1 — LB ROSIN CORE SOLDER 40/60 .....$1
☐ 6 — SPIN TIGHT SOCKET SET 3/16" to 7/16"..$1
☐ 3 — TV ALIGNMENT TOOLS 5", 7", 12".....$1

HANDY WAY TO ORDER—Simply tear out advertisement and pencil mark items wanted (X in square is sufficient); enclose with money order or check. You will receive a new copy of this ad for re-orders.
ON SMALL ORDERS—Include stamps for postage, excess will be refunded. Larger orders shipped express collect.

BROOKS RADIO & TV CORP.
84 Vesey St. Dept. A, New York 7 N.Y.

Are you an audio-hi fi man who's constantly looking for ways to improve your system? Do you want to know more about how to modify circuits, service and maintain hi-fi, switch, test, experiment, and build in your never-ending quest for truer fidelity? If the spirit of the experimenter and perfectionist burns bright within you, here's an unusual opportunity for you to approach your goal.

Now through the **G/L AUDIO-HI FI BOOK CLUB** you can acquire a complete set of beautifully bound books on all the phases of high fidelity you've always yearned to know more about. Look over the titles—and authors—titans like Crowhurst, Hartley, Marshall, Hoefler (see his article elsewhere in this magazine)! These books sell for $5 each—but members get them for only $3.75. A saving of 25%—$1.25 on each book! And you risk nothing. You examine each book before you buy—return it if you don't want it.

THESE BOOKS ALREADY PUBLISHED — select one only

H. A. HARTLEY'S AUDIO DESIGN HANDBOOK —Latest addition to the club. This British expert explains design principles so that the non-engineering hi-fi fan can actually design his own equipment.

ELEMENTS OF TAPE RECORDER CIRCUITS— By Herman Burstein and Henry C. Pollak. Here's a book that answers all your questions about the electronic aspects of a tape recorder. Tells what to look for when you buy—what various types will and will not do.

MAINTAINING HI-FI EQUIPMENT — By Joseph Marshall. Covers the specialized techniques necessary to repair hi-fi equipment. Includes acoustical and mechanical as well as electronic faults.

UNDERSTANDING HI-FI CIRCUITS — By Norman H. Crowhurst. Now you can have the hi-fi system best suited to your tastes—and budget. Crowhurst tells you which phase inverter is best, weighs fixed vs. self bias, triode vs. pentode, answers the questions you ask when looking for hi-fi perfection.

BASIC AUDIO COURSE — By Donald C. Hoefler. Explains everything about audio from the theory of sound to disc and tape recording techniques.

HOW TO JOIN THE G/L AUDIO-HI FI BOOK CLUB

- Select one book from those listed on the coupon.
- SEND NO MONEY—we will send you the book on approval. If you like it send your remittance for the special club price of $3.75.
- New books are released about every four months. You receive these automatically on the same no-risk plan.
- You may cancel any time after you have accepted four books—no time limit.

MAIL THIS COUPON NOW

Gernsback Library, Inc., Dept. 118C
154 West 14th Street, New York 11, N. Y.

Enroll me in the G/L AUDIO-HI FI BOOK CLUB.

Send me the book checked on approval.

(Please check one only)

- ☐ Audio Design Handbook
- ☐ Elements of Tape Recorder Circuits
- ☐ Maintaining Hi-Fi Equipment
- ☐ Understanding Hi-Fi Circuits
- ☐ Basic Audio Course

Name.....
please print
Street.....
City.....Zone.....State.....

headed by Stavid Engineering as captain of a team including some much bigger companies. For the Army, Stavid now is making a missile beacon telemetering system; for the Navy, a submarine command guidance system for the Regulus missile, fire control systems, electronic beachmarking systems, sonar data links; for the Air Force, a radar toss-bombing system and a subminiature radar beacon for the experimental X-15 rocket plane. In addition to such military projects, Stavid is now embarked on a plan to devote 50% of its capacity to civilian work, and has acquired rights to Radio WEB, a French air navigation system, which it hopes to manufacture in this country. One out of every four of the company's employees is a scientist or engineer, and it stresses the hiring of retired persons.

J. RAYMOND POPKIN-CLURMAN, of Amityville, N.Y., was senior engineer for Hazeltine Corp., working on color television research, when it occurred to him that a demand for color TV test equipment would exist long before the FCC even decided on color standards. Accordingly, in 1950, at the age of 34, he founded Telechrome Manufacturing Corp. with a policy based on making whatever anybody wanted, incorporating any standards desired. The policy of Telechrome, which now has 70 employees and annual sales of $1,000,000, hasn't changed: it still strives to manufacture equipment *before* there's a market. It will make "one of anything," will develop it from an idea to complete equipment in 60 to 90 days where some others might take 6 to 9 months. As a result of this flexibility, it is now in the field of broadcast test equipment, telemetering for guided missiles, electro-optical tooling for aviation and industry, spectrophotometers, and its customers include the Government and some of the largest manufacturers in the country. Telechrome claims to be the only firm which ever made a profit on color TV.

—H.G.

"With these top dials, this is the only way I can flip stations!"

SCHOOL DIRECTORY

ENGINEERING DEGREES

E.E.
Option Electronics or Power

Earned through
HOME STUDY
Residence Classes Also Available

PACIFIC INTERNATIONAL UNIVERSITY
Colleges of Engineering, Physics, and Business Administration
5719-M, Santa Monica Blvd., Hollywood 38, Calif.

PACIFIC INTERNATIONAL UNIVERSITY

GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic and advanced courses in theory and laboratory. Assoc. degree in electronics in 29 mos. B.S. in electronic engineering obtainable. ECPD accredited, G.I. approved. Graduates in all branches of electronics with major companies. Start February, September. Dorms, campus. High School graduate or equivalent. Catalog.

VALPARAISO TECHNICAL INSTITUTE
Dept. C Valparaiso, Indiana

ELECTRONICS

PREPARE FOR A GOOD JOB!
BROADCAST ENGINEER
RADIO SERVICING AUTOMATION

TELEVISION SERVICING
BLACK & WHITE—COLOR

APPROVED FOR VETERANS AND SURVIVORS OF VETERANS
BUILDING AIR CONDITIONED
SEND FOR FREE LITERATURE

BALTIMORE TECHNICAL INSTITUTE
1425 EUTAW PLACE, BALTIMORE 17, MD.

college grads get ahead faster!

. . . have higher incomes . . . advance more rapidly. Grasp your chance for a better life. Share rewards awaiting college men. Important firms visit campus regularly to employ Tri-State College graduates. Start any quarter. Approved for Vets.

Bachelor of Science Degree in 27 months

Electrical Engineering with either an Electronics or Power major. Also Mechanical, Civil, Chemical, Aeronautical Engineering. *In 36 months* a B.S. in Business Administration (General Business, Accounting, Motor Transport Management Majors). Superior students faster. More professional class hours. Small classes. Enrollment limited. Beautiful campus. Well-equipped labs. Prep courses. Enter Jan., March, June, Sept. Earnest, capable students (whose time and budget require accelerated courses and modest costs) are invited to *write Jean McCarthy, Director of Admissions, for Catalog and "Your Career in Engineering and Commerce."*

TRI-STATE COLLEGE
24118 College Avenue, Angola, Indiana

ELECTRONICS

Prepare for unlimited opportunities in electronics!

ENGINEERING DEGREE IN 27 MONTHS

B.S. degree in 27 months, mathematics, electrical engineering, TV, advanced radio theory and design. Modern labs. Low tuition, earn board. Also Aero., Chemical, Civil, Electrical, Mech. Engineering. B.S. degree in 36 mo. in Math., Chem., Physics. Also prep courses. G.I. appr. 20 bldgs., dorms, gym. Enter Dec., March, June, Sept. Catalog. Keeping Pace With Progress.

INDIANA TECHNICAL COLLEGE
1511 E. Washington Boulevard, Fort Wayne 2, Indiana

CODE SENDING RECEIVING SPEED

Be a "key" man. Learn how to send and receive messages in International Morse code. Communicate with operators around the globe. Learn at home quickly through famous Candler System. Used by best operators. Qualify for Amateur or Commercial License. Write for FREE BOOK.

CANDLER SYSTEM CO.
Dept.3-M,Box9226,Denver20,Colo.USA

YOUR CAREER IN AVIONICS!

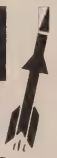

AVIATION - ELECTRONICS
JETS - ROCKETS - MISSILES
SPACE TECHNOLOGY

Jet Airliners; Guidance Systems; Space Studies; Moon Landings — All this means just one thing to a Northrop educated man — OPPORTUNITY!

Graduate in two short years

Thousands of successful Northrop Institute graduates are now employed by leading companies in the fields named above. They hold important, responsible, highly-paid positions, and their Engineering Technology training at Northrop required only 24 months to complete.

EARN A BACHELOR OF SCIENCE DEGREE

If you elect, you may continue your study an additional year and earn a B.S. degree in the fields of Aeronautical Engineering, Electronics Engineering, or Aircraft Maintenance Engineering.

GET COMPLETE FREE INFORMATION

Fill out this coupon and mail today. Check the training which most interests you.

APPROVED FOR VETERANS

NORTHROP AERONAUTICAL INSTITUTE
1181 W. Arbor Vitae Street, Inglewood 1, Calif.

Please send me immediately the Northrop catalog, employment data, and schedule of class starting dates. I am interested in:

- ☐ Electronic Engineering Technology
- ☐ Aeronautical Engineering Technology
- ☐ Aircraft Maintenance Engineering Technology
- ☐ Master Aircraft and Engine Mechanic
- ☐ Jet Engine Overhaul and Maintenance

Name..... Age...
Address .....
City..... Zone... State.....
Veterans: Check here ☐ for Special Veteran Training Information.

Your choice of school is highly important to your career in

INDUSTRIAL ELECTRONICS

RADIO-TELEVISION

ELECTRONICS COMMUNICATIONS

Become an
ELECTRICAL ENGINEER
or an
ENGINEERING TECHNICIAN
at

MSOE *in Milwaukee*

Choose from courses in:

ELECTRICAL ENGINEERING
Bachelor of Science degree in 36 months—
Communications or Electrical Power.

ENGINEERING TECHNOLOGY
Associate in Applied Science degree in 18 months—
Electronics Communications. Electrical Power, or Computers.

MSOE — located in Milwaukee, one of America's largest industrial centers—is a national leader in electronics instruction—with complete facilities, including the latest laboratory equipment, visual aid theater, amateur radio transmitter —offers 93 subjects in electrical engineering, electronics, radio, television, electrical power, and electricity.

Advisory committee of leading industrialists. Courses approved for veterans. Over 50,000 former students. Excellent placement record. Previous educational, military, and practical experience is evaluated for advanced credit.

QUARTERS BEGIN SEPTEMBER, JANUARY, MARCH, JULY

Choose wisely — your future may depend on it. Mail coupon today!

MILWAUKEE SCHOOL OF ENGINEERING

Dept. RE-1158, 1057 N. Milwaukee St.
Milwaukee, Wis.

Please send free illustrated career booklet (please print)

I'm interested in.....
(Course)
Name.....Age.....
Address.....
City.....State.....
☐ I am ☐ I am not eligible for veterans benefits
.....
(discharge date)

HOW TO GET YOUR "TICKET" in a jiffy!

Cash in on radio where the pay is best!

Get one of radio's best paying jobs—as a commercial operator aboard ship, in aviation, in broadcasting or telecasting and the many other places where an FCC license is a "must"!

A practical study guide for **FCC LICENSE EXAMS**

LICENSE MANUAL FOR RADIO OPERATORS by J. R. Johnson is a quick, low cost guide to help you breeze through FCC exams. Written so you can easily understand and remember it.

Covers ALL EIGHT exam elements—not just some of them. Reviews almost 2200 typical questions. Includes the changes in exam elements 1 and 2. Covers all data from electrical and radio fundamentals to navigation and related subjects. Price only $5.00.

JOB OPPORTUNITY NEWS! Under a new ruling, only holders of 1st or 2nd class radio-phone licenses can do any work that affects the broadcasting of a transmitter. This is just one of many good job opportunities open to license holders!

10-DAY FREE EXAMINATION

Dept. RE-118, RINEHART & CO., Inc., 232 Madison Ave., New York 16, N.Y.

Send LICENSE MANUAL FOR RADIO OPERATORS for free examination. In 10 days I will either send $5.00 (plus postage) in full payment or return book and owe nothing. (Save! Send $5.00 with order and we pay postage. Same 10-day return privilege.)

Name.....

Address.....

City, Zone, State.....

OUTSIDE U.S.A.—$5.50 cash with order.

NEW! IMPROVED! SENCORE TRC4 TRANSISTOR CHECKER

Another Sencore Time-Saver

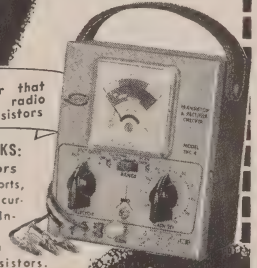

Only tester that checks car radio power transistors

NOW CHECKS:

★ ***Transistors*** for opens, shorts, leakage and current gain. Includes new gain test on power transistors.

★ ***Crystal Diodes*** checks forward to reverse current ratio on all diodes.

★ ***Selenium Rectifiers*** checks forward and reverse currents.

SIMPLE TO OPERATE

ONLY $17.95 Dealer Net

Cannot become obsolete. Approved by leading manufacturers.

Controls are accurately set for each transistor by referring to replaceable set-up chart on rear. Test leads or socket provides for fast hook-up.

See your parts distributor.

SENCORE

Mfg by **SERVICE INSTRUMENTS CORP.** 171 OFFICIAL RD., ADDISON, ILL.

Cut out this ad now for further information

ADVERTISING INDEX

Radio-Electronics does not assume responsibility for any errors appearing in the index below.

Acoustic Research Inc. 102
Acro Products Co. 134
Allied Radio Corp. 17, 26-27
Arkay Radio Kits Inc. 127
Atlas Sound Corp. 140

B & K Manufacturing Co. 89
Barry Electronics Corp. 147
Belden Manufacturing Co. 105
Bell Telephone Labs 24
Benco Television Associates Ltd. 123
Berkeley Enterprises, Inc. 137
Brooks Radio & Television Corp. 143
Burstein-Applebee Co. 139

CBS-Hytron 8
Canadian Institute of Science & Technology 140
Capitol Radio Engineering Institute 93-94
Carston Studios 137
Castle Television Tuner Service 137
Centralab Div. of Globe Union 16
Century Electronics Co., Inc. 117, 133
Chemical Electronic Engineering Inc. 118
Chicago Standard Transformer Corp. 118
Cisin (H. G.) 137
Cleveland Institute of Radio Electronics 11
Columbia Record Club 9
Coyne Electrical School 102, 125, 136

Delco Radio Div. of General Motors 101
DeRO Electronics 143
DeVry Technical Institute 7
Dressner 137
Duotone Co., Inc.....138
Dynaco Inc. 138

Ebex Technical Institute 146
Electro-Voice, Inc. Inside Back Cover
Electronic Chemical Corp. 140
Electronic Instrument Co. (EICO) 29, 30
Electronic Measurement Corp. (EMC) 132
Electronic Publishing Co., Inc. 128
Erie Resistor Corp. 120
E-Z Hook Test Products Co. 100

Garfield (Oliver) Co. 141
Gernsback Library Inc. 141, 144
Grantham School of Electronics.. 15
Greenwich Book Publishers 139
Grommes Div. of Precision Electronics, Inc. 128

Heald Engineering College 133
Heath Co. 62-77
Hickok Electrical Instrument Co. 120-121

Illinois Condenser Co. 132
Indiana Technical College 139
International Correspondence Schools 13

Jensen Manufacturing Co. .....Inside Front Cover

Key Electronics Co. 139

Lafayette Radio 148-150
Lansing (James B.) Sound Inc. 21
Lektron Inc. 142

ORDER by MAIL and SAVE!

TV PICTURE TUBES

10BP4	$ 7.95	17BP4	$10.95	21AMP4	$19.95
12LP4	8.95	17CP4	17.00	21ATP4	20.95
14B/CP4	9.95	17GP4	17.60	21AUP4	20.95
16DP4	14.95	17HP4	13.60	21EP4	14.95
16EP4	15.90	17LP4	13.60	21FP4	15.95
16GP4	15.90	17QP4	11.95	21WP4	17.30
16KP4	10.95	17TP4	19.30	21YP4	15.95
16LP4	10.95	19AP4	19.30	21ZP4	14.95
16RP4	10.95	20CP4	13.90	24CP4	23.95
16WP4	15.20	20HP4	17.95	24DP4	26.95
16TP4	10.95	21AP4	22.10	27EP4	39.95
17AVP4	15.20	21ALP4	20.95	27RP4	39.95

27"—6 month guarantee—all others 1 year. Aluminized Tubes $5.00 more than above prices. These prices are determined to include the return of an acceptable similar tube under vacuum.

ALL PRICES FOB CHICAGO, ILLINOIS. Deposit required, when old tube is not returned, refundable at time of return. 25% required on COD shipments. Old tubes must be returned prepaid. We ship anywhere.

WRITE FOR COMPLETE LIST.

—PICTURE TUBE OUTLET—

3032 Milwaukee Ave., Chicago 18, Ill.

Dickens 2-2048

FIGHT CANCER

AMERICAN CANCER SOCIETY

BUILD YOUR OWN COMPUTER

FANTASTIC? NOT ANY LONGER!

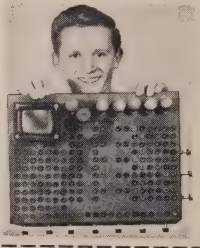

EBEX School courses will not only teach you how to build computers of all types, but also how to design them. 50 computer courses and kits.

EBEX TECHNICAL INSTITUTE

1015 Atkin Ave. SLC 6, Utah

☐ Send book of opportunities in computers
☐ Send free catalog on courses
☐ Send free catalog on kits

Attach Name and Address

EQUIPMENT & COMPONENT SPECIALS

- **General-Radio Variac Type 200 CUH**—The original continuously adjustable autotransformer—Input voltage: 115 volts at output voltage of 0 to 270 volts @ 2 amps. Also will operate from 230 volts and deliver from 0 to 270 volts @ 2 amps. Brand new sealed in original cartons—only $11.95 less knob & dial. With knob and dial.....only $12.95
- **Millen 2" Magnetic Shield** with 2⅝" x 2⅝" Bezel with green-tinted face. For 2" CR tubes. Made of NICOLOI. Brand new—Millen #80042.....$2.50
- **Dolinko & Wilkens** 75 MMFD @ 20 KV. Vacuum capacitors. New—Compact.....$5.50 each
- **Dolinko & Wilkens** 100 MMFD @ 20 KV. Vacuum capacitors. New—Compact.....$7.50 each
- **Choke**—Approx. 6 HY. @ 500 MA.—26 OHMS D.C. Resistance unused.....Price $3.95 2 for $6.00
- **Westinghouse Choke** 10 HY. @ 200 MA.—77 OHMS D.C. resistance—5" x 5" x 3½". Stock No. LI423117.....$1.90

Write For Latest Tube Catalog Free!

Receiving, transmitting, special purpose tubes, diodes, transistors, etc. We have a large diversified stock at sensible prices.

- **SCINTILLATION COUNTER, Grammascint Model 1002.** "Ten times more sensitive than a Geiger counter." Self-contained portable Scintillation type Gamma-Ray Detector designed for prospecting, radiation monitoring, etc. Contains a nine-stage photo multiplier tube coupled to Gamma sensitive plastic phosphor which makes this instrument a real buy. Regular Price $245.00 complete with Trimm headphone, leather case, batteries, ready-to-operate.....Sale Price $49.95
- **Millen 2" Magnetic Shield** with 2⅝" x 2⅝" Bezel with green-tinted face. For 2" C.R. tubes. Made of NICOLOI. Brand new—Millen #80042.....$2.50
- **Marion 2½" Round Hermetically-Sealed 36-Volt D.C. Voltmeter.** Has expanded 18 to 36-volt scale in Half-volt steps. Clean, removed from equipment.....$2.95

2-COLOR TUBE CARTONS

Keeps your tube stock neat. New safety partition prevents tube breakage. Distinctively lithographed in glossy red and black. The most distinctive tube carton available today. Minimum quantity: 100 of any one size. Write for case lot prices. Packed 1000 to case. F.O.B. N.Y.C. No C.O.D.'s on cartons—Send full remittance including postage — Excess refunded.

SIZE	For Tube	Per 100
Miniature	6AU6, etc.	$1.00
GT	6SN7GT, etc.	1.25
Large GT	1B3GT, etc.	1.50
Large G	5U4G, etc.	2.00

WHITE GLOSSY BOXES

Completely blank. No printing or color. Otherwise same as above. Same high quality, same low prices. Specify "WHITE" when ordering. When color is not stated, 2 color cartons will be shipped.

We are factory distributors for Vocaline, Gonset, E. F. Johnson, Eimac, B&W, Hexacon, Adjust-A-Volt, CBS, Hammarlund, etc.

Special Trade-ins on E. F. Johnson and Hammarlund Ham Gear!

- **Johnson Air-System Ceramic Socket,** Metal chimney, sub-mounted shielded (122-275) socket. Used with 4-125A, 4-250A, 4-400A, etc. Type tubes. Clean, removed from equipment. Special $3.50
- **6 and 12 Volt (operates from either) Input Carter Duovolt Dynamotors:** Medium Size Unit Puts out 400 Volts @ 375 Ma.....$15.95 Large Size Unit Puts out 620 Volts @ 280 Ma. $19.95

All Units are brand new, genuine Carter Dynamotors in original packages.

TERMS: 25% deposit with order, balance C.O.D. All merchandise guaranteed for cost of merchandise only. F.O.B. N.Y.C.

We are near Prince St./BMT Station, Spring St./IRT Station. Open Monday thru Saturday. Thousands of unadvertised specials. Come in and browse around.

BARRY ELECTRONICS CORP.
512 Broadway, Dept. RE-11, N.Y. 12, N.Y.
Phone: WAlker 5-7000

Mallory (P. R.) & Co., Inc. 112-113
Marjo Technical Products Co. 142
McGraw-Hill Book Co., Inc. 133
Merit Coil & Transformer Corp. 106
Mosley Electronics Inc. 134
Moss Electronic Distributing Co., Inc. 84-87
National Radio Institute 3, 19-20
National Schools 5
Newark Electric Co. 142
Opportunity Adlets 135
Pentron Corp. 100
Perma-Power Co. 116
Philco Accessory Division 14, 115
Pickering & Co., Inc. 10
Picture Tube Outlet 146
Precise Development Corp. 124
Prentice-Hall, Inc. 109, 121
Progressive Edu-Kits Inc.....129
Pyramid Electric Co. 80
Quam-Nichols Co. 131
Quietrole Co., Inc. 121
RCA Electron Tube Division .....Back Cover
RCA Institutes 119
Radio Shack Corp. 111
Recoton Corp. 114
Rider (John F.) Inc. 135
Rinehart & Co., Inc. 95, 116, 123, 146
Rogers Manufacturing Co. 114
Rohn Manufacturing Co. 28
Sams (Howard W.) & Co. Inc. 10, 25
Schober Organ Co. 122
Scott (H. H.) Inc. 18
Scott-Mitchell House, Inc. 136
Seco Manufacturing Co. 122
Seg Electronics 131
Service Instruments Corp. 128, 143, 146
Sprayberry Academy of Radio Television 23
Stromberg-Carlson 126
Sylvania Electric Products Inc. 22
"TAB" 147
Tarzian (Sarkes) Inc. 109
Telco Electronics Manufacturing Co. 138
Triad Transformer Corp. 130
Trio Manufacturing Co. 97
Tung-Sol Electric Co. 6
University Loudspeakers, Inc.....107
Vaco Products Co. 130
Western Radio 134
Zenith Radio Corp. 12

SCHOOL DIRECTORY PAGE 145

Baltimore Technical Institute
Candler System Co.
Indiana Technical College
Milwaukee School of Engineering
Northrop Aeronautical Institute
Pacific International University
Tri-State College
Valparaiso Technical Institute

BRANCH ADVERTISING OFFICES: Chicago: 600 Waukegan Road, Glenview, Ill., GLenview 4-6900. **Los Angeles:** Ralph W. Harker and Associates, 600 South New Hampshire. Tel. DUnkirk 7-2328. **San Francisco:** Ralph W. Harker and Associates, 444 Market St. Tel. GArfield 1-2481.
FOREIGN AGENTS: Great Britain: Atlas Publishing and Distributing Co., Ltd., 18 Bride Lane, London E.C. 4. **Australia:** McGill's Agency, Melbourne. **France:** Brentano's, Paris 2e. **Belgium:** Agence et Messageries de la Presse, Brussels. **Holland:** Trilectron, Heemstede. **Greece:** International Book & News Agency, Athens. **So. Africa:** Central News Agency, Ltd., Johannesburg, Capetown, Durban, Natal; Universal Book Agency, Johannesburg. **India:** Broadway News Centre, Dadar, Bombay #14. **Pakistan:** Paradise Book Stall, Karachi 3.

Printed in the United States of America

"TAB" Tubes Tested, Inspected, Boxed

New and used Gov't & Mfgrs.

Surplus 6 Mos. Guarantee! No Rejects—

Orders $10 or more, Receiving types only ppd, 48 states

0A2	.80	6BJ6	.72	12AT6	.59	117Z3	.69
0B2	.72	6BK7	.99	12AT7	.89	117Z6	1.10
0C3	.84	6BL7	1.95	12AU6	.63	2C51	2.65
0D3	.80	6BN6	1.08	12AU7	.69	2D21	.68
0Z4	.50	6BQ6	1.19	12AX7	.79	3D23	5.00
1A7	1.00	6BZ7	1.25	12BA6	.65	717A	5/$1
1B3	.78	6C4	.49	12BA7	.99	4-125	29.00
1R5	.78	6C5	.69	12BD6	.59	4-250	35.00
1S4	.78	6CB6	.80	12BE6	.59	4E27	7.00
1T4	.78	6CD6	1.49	12BF6	.59	4PR60	29.50
1U4	4/$1	6H6	.59	12BH7	.99	4X150	19.00
1U5	.89	6J5	.59	12BY7	1.00	4X250	35.00
1X2A	.68	6J6	.59	12BZ7	.99	4X500	38.00
3Q4	.68	6K6	.59	12CU6	1.45	5BP1	3.98
3Q5	.86	6K7	.79	12SA7	.69	5BP4	1.98
3S4	.68	6L6	1.19	12SG7	.89	35T	4.00
3V4	.99	6S4	.49	12SH7	.89	10T	7.00
5R4	1.25	6S8	.99	12SJ7	.75	250T	20.00
5U4	.59	6SA7	.69	12SK7	.75	388A	1.00
5V4	.89	6SB7	1.19	12SQ7	.69	418A	14.00
5Y3	.59	6SC7	.89	19BG6	2.15	450T	43.00
6AB4	.59	6SG7	.79	19T8	1.10	807	1.20
6AC7	.79	6SH7	.69	25BQ6	1.39	808	1.20
6AG7	.89	6SJ7	.69	25L6	.72	809	3.00
6AH6	.99	6SK7	.72	25W4	.77	810	3.00
6AK5	.69	6SL7	.89	25Z5	.72	811	3.00
6AL5	.59	6SN7	2/$1	25Z6	.75	812	3.00
6AQ5	.66	6SQ7	.74	EL34	3.49	813	9.00
6AS7	3.00	6SR7	.79	EL37	2.49	814	2.45
6AT6	.49	6T8	.98	35L6	.59	815	3.50
6AU4	1.29	6U8	.98	35W4	.52	829B	8.00
6AU5	1.19	6V6	1.39	35Y4	.69	832A	7.00
6AU6	.59	6W4	.79	35Z5	.89	866A	1.60
6AX4	.79	6W6	.89	50A5	.69	6146	4.00
6BA6	.59	6X4	.39	50B5	.69	5879	1.20
6BA7	1.00	6X5	.49	50C5	.69	5881	2.70
6BD6	.69	6Y6	.89	50L6	.69	6550	3.90
6BE6	.59	7N7	.89	KT66	3.29	5842	11.00
6BG6	1.50	12AL5	.59	75	.89	5654	1.00
6BH6	.79	12AQ5	.75	80	.59	5894	12.00

Write for Complete Tube List! Discounts to Qty. Buyers

TUBES WANTED! WE BUY! SELL & TRADE!

"ERIN" FINEST HI-FI RECORDING TAPE

1200 Ft.—7" Reel **$1.45** ea. *Lots of 3*
Money Back Gtd.

Highest quality controlled plastic base tape made by new "Erin" process. Precision coated & Slit. Gtd. Constant output. Freq. 7½ IPS 40-15KC Oxide Wnd In. singly $1.59. *ADD 16c each P.P.D. 48 States*

New 1st Quality "Mylar" 2400 Ft.—7" Reel Ferro "Erin" Gloss Process Recording tape—$4.49, 3/$12.

NEW GTD RADIO & T.V. RECTIFIERS

35MA 40¢ @, 8 for $2; 65MA 49¢ @, 6 for $2; 75MA 49¢ @, 5 for $2; 100MA 59¢ @, 6 for $3; 150MA 70¢ @, 8 for $5; 250MA 79¢ @, 6 for $4; 300MA 70¢ @, 10 for $6; 350MA 79¢ @, 10 for $6.50; 400MA $1.10 @, 5 for $5; 500MA $1 @; 10 for $9. *Order $10, Postpaid 48 States!*

Infrared Receiver Assembly USN/US/AM-R1400, direct viewing telescopic unit. Changes invisible infrared energy into a visible image on an 1¾" screen, includes infrared filter & radioactive charging system. **Navy cost $216 includes inst case & data. Special $21.**

KITS! "TAB" *THE BEST* KITS!

All Kits Contain Most Popular Values & Sizes

Kit 35 Precision Resistors	Kit 75 Mica Cond's
Kit 3 Chokes	Kit 6 Crystal Diodes
Kit 3 Transistor Transf.	Kit 8x25 ft. Hookup Wire
Kit 150 Carbon Resistors	Kit 100 Fuses
Kit 42 Panel Lamps	Kit 100 Ceramic Cond.
Kit 15 Volume Controls	Kit 5 Mike Trans.
Kit 36 Tube Sockets	Kit 6 Crystals & Holders
Kit 50 Tubular Cond's	Kit 65 Inductors & Coils
Kit 500 Lugs & Eyelets	Kit 5 Microswitches
Kit 10 Xmit Mica Cond's	Kit 10 Wheat Lamps
Kit 5 Lbs. Surprise Kit	Kit 40 Insulators
Kit Encapsulation Fluid	Kit 85 Insulated Resist.
Kit Volume Control	Kit TV nobs
Kit 35 Power Resistors	Kit Glyptal & Varnish
	Kit 10 Ferri Slugs

BUY 10 KITS, GET ONE FREE! **EACH KIT 99c**

NEW TPSK2 DC POWER for TRANSISTORS!

Transistors! Filtered Power Supply Kit used to power transistor circuits, amplifiers, etc. Delivers 12VDC at 2AMPS filtered less than 0.5% ripple or 28VDC at 1A TPSK2 Kit $18; TPS2W assembled & wired $24.

115VAC Inpt Transformer & Full Wave Bridge Rectifier for 12VDC @ 2AMPS, or RECTRAN KIT RTK.....$4.50
RT1W Assembled & Wired.....$8.50
RT2K Kit 12 or 18VDC @ 4AMPS.....$9.50
RT2W Assembled & Wired.....$14.75

BATTERY CHARGER KIT 2 TO 4 AMPS

Charges 2—4—6 & 12 volt batteries. Kit BCK-1 $11, Built $12.75

Collins/L.N. 32V3 $575. 75A3 $350. Both 32V3 & 75A3 $875.

NEW "TEKSEL" SELENIUM FULL WAVE
BRIDGE RECTIFIERS. *ONE YEAR GTD!*

CURR. CONT.	18VAC 14VDC	36VAC 28VDC	72VAC 56VDC	144VAC 112VDC
1AMP	$ 1.30	$ 2.00	$ 4.00	$ 9.45
2AMP	2.15	3.00	6.25	12.30
3AMP	2.90	4.00	8.60	16.75
6AMP	4.15	8.00	18.75	36.15
10AMP	6.10	12.15	26.30	48.90
15AMP	9.90	19.00	40.00	66.60
24AMP	15.00	29.45	57.50	108.45

Order $10 Postpaid 48 states!

New Silicon Radio & TV 500Ma/280VAC/ 400 p.i.v. Rectifier H'mt Sealed. $.50 @, 5 for $6.50 10 for $46

TOROID COMPUTER LOGIC TRANSFORMER & *DATA*

Toroid—Use as gate or counting circuit or logic drive memory device. 3 windings 200ma/2 microseconds switching tape wound core. "IBM" design, fits 9 pin miniature socket.

$1.50 each, 5 for $5; 100 for $75; *postpaid*

DIAMOND PHONO-NEEDLES! *Postpaid 48 States!*
REGISTERED ONE YR. GUARANTEED BY THE MFR!
ALL MAKES LP&78—ONE DIAMOND $6; TWO DIAMONDS $14; DIAMOND & SAPPHIRE $8.
PLEASE SEND CARTRIDGE NAME & NUMBER

"TAB" 127 **TERMS: Money Back Guarantee! Our 14th year. $2 min order F.O.B. N.Y.C. Add shpg charges or for C.O.D. 25% Dep. Prices shown subject to change.**
111-WL LIBERTY ST., N. Y. 6, N. Y.

Send 25c *for Catalog*

PHONE: RECTOR 2-8245

KT-500 IN KIT FORM 74.50

New! Years Ahead!

LAFAYETTE STEREO TUNER KIT

ONLY $7.45 DOWN 7.00 MONTHLY

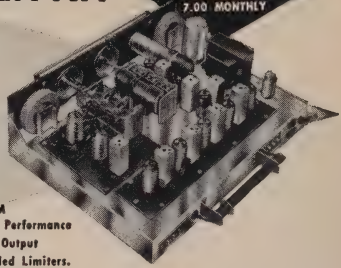

Use it as a Binaural-Stereophonic FM-AM tuner

Use it as a Dual-Monaural FM-AM tuner

Use it as a straight Monaural FM or AM tuner

THE MOST FLEXIBLE TUNER EVER DESIGNED

- Multiflex Output for New Stereo FM
- 10KC Whistle Filter
- Pre-aligned IF's
- Tuned Cascode FM
- 11 Tubes (including 4 dual-purpose) + Tuning Eye + Selenium rectifier Provide 17 Tube Performance
- Separately Tuned FM and AM Sections
- 12 Tuned Circuits
- Dual Cathode Follower Output
- Armstrong Circuit with FM/AFC and AFC Defeat
- Dual Double-Tuned Transformer Coupled Limiters.

More than a year of research, planning and engineering went into the making of the Lafayette Stereo Tuner. Its unique flexibility permits the reception of binaural broadcasting (simultaneous transmission on both FM and AM), the independent operation of both the FM and AM sections at the same time, and the ordinary reception of either FM or AM. The AM and FM sections are separately tuned, each with a separate 3-gang tuning condenser, separate flywheel tuning and separate volume control for proper balancing when used for binaural programs. Simplified accurate knife-edge tuning is provided by magic eye which operates independently on FM and AM. Automatic frequency control "locks in" FM signal permanently. Aside from its unique flexibility, this is, above all else, a quality high-fidelity tuner incorporating features found exclusively in the highest priced tuners.

FM specifications include grounded-grid triode low noise front end with triode mixer, double-tuned dual limiters with Foster-Seeley discriminator, less than 1% harmonic distortion, frequency response 20-20,000 cps ± ½ db, full 200 kc bandwidth and sensitivity of 2 microvolts for 30 db quieting with full limiting at one microvolt. AM specifications include 3 stages of AVC, 10 kc whistle filter, built-in ferrite loop antenna, less than 1% harmonic distortion, sensitivity of 5 microvolts, 8-kc bandwidth and frequency response 20-5000 cps ± 3 db.

The 5 controls of the KT-500 are FM Volume, AM Volume, FM Tuning, AM Tuning and 5-position Function Selector Switch. Tastefully styled with gold-brass escutcheon having dark maroon background plus matching maroon knobs with gold inserts. The Lafayette Stereo Tuner was designed with the builder in mind. Two separate printed circuit boards make construction and wiring simple, even for such a complex unit. Complete kit includes all parts and metal cover, a step-by-step instruction manual, schematic and pictorial diagrams. Size is 13¾" W x 10⅜" D x 4½" H. Shpg. wt., 22 lbs.

The new Lafayette Model KT-500 Stereo FM-AM Tuner is a companion piece to the Models KT-300 Audio Control Center Kit and KT-400 70-watt Basic Amplifier Kit and the "Triumvirate" of these 3 units form the heart of a top quality stereo hi-fi system.

KT-500 .....Net **74.50**

LT-50 Same as above, completely factory wired and tested.....Net **124.50**

KT-600 79.50 IN KIT FORM

ONLY 7.95 DOWN — 8.00 MONTHLY

NEW! LAFAYETTE PROFESSIONAL STEREO MASTER AUDIO CONTROL CENTER

The Lafayette KT-600 Solves Every Stereo/Monaural Control Problem!

- RESPONSE 10-25,000 CPS ± 0.5 DB
- TAPE HEAD PLAYBACK EQUALIZATION FOR NEW 4-TRACK STEREO
- 1.78 MILLIVOLTS SENSITIVITY FOR 1 VOLT OUT
- LESS THAN .03% IM DISTORTION
- 6 CONCENTRIC FRONT PANEL CONTROLS
- 4 CONCENTRIC REAR PANEL INPUT LEVEL CONTROLS
- 180° ELECTRONIC PHASE REVERSAL

- UNIQUE STEREO & MONAURAL CONTROL CENTER FACILITIES!
- OUTSTANDING PERFORMANCE SUPERIORITY!
- AMAZING NEW BRIDGE CIRCUITRY & CONTROL FOR 3d CHANNEL OUTPUT FOR 3-SPEAKER STEREO SYSTEMS!
- VARIABLE CROSS-CHANNEL SIGNAL FEED ELIMINATES "PING-PONG" EFFECTS!
- PRECISE "NULL" BALANCING & CALIBRATING SYSTEM — BETTER THAN METERS!
- 24 EQUALIZATION POSITIONS PER CHANNEL!
- CLUTCH-TYPE DUAL VOLUME-BALANCE CONTROLS!

A REVOLUTIONARY DEVELOPMENT IN STEREO HIGH FIDELITY. Provides such unusual features as a Bridge Control, for variable cross-channel feed for elimination of "ping-pong" (exaggerated channel separation) effects and for control of a 3d-channel output for 3-speaker stereo systems; the 3d-channel output also serves for converting stereo program material to high quality monaural for recording or to play a stereo program monaurally through a separate amplifier and speaker system. The KT-600 also has full input mixing of monaural program sources (such as tape recorder and phonograph, etc.), a special "null" stereo balancing and calibrating system (better than meters), 24 equalization positions per channel, 12 db per octave rumble and scratch filters, and a loudness on-off switch. Has clutch-type dual concentric volume controls which operate independently for balancing or simultaneously as the Master Level Control. Other features include channel reverse, 180° phase reversal, input level controls at all inputs. Sensitivity is 1.78 millivolts for 1 volt out. Dual low impedance outputs ("plate followers," 1300 ohms) are provided. Frequency response is 10-25,000 cps ± 0.5 db; less than .03% IM distortion. Uses 7 new 7025 low-noise dual triodes. Size 14" x 4½" x 10⅝". Shpg. wt., 16 lbs. Complete with printed circuit board, modern-styling metal chassis and cage, profusely illustrated instructions, all necessary parts.

LAFAYETTE KT-600 Stereo Preamplifier Kit .....Net **79.50**

KT-310

ONLY 4.75 DOWN 5.00 MONTHLY

47.50

NEW! LAFAYETTE STEREO/MONAURAL BASIC POWER AMPLIFIER KIT

- 36-WATT STEREO AMPLIFIER - 18-WATTS EACH CHANNEL
- FOR OPTIONAL USE AS 36-WATT MONAURAL AMPLIFIER
- EMPLOYS 4 NEW PREMIUM-TYPE 7189 OUTPUT TUBES
- 2 PRINTED CIRCUIT BOARDS FOR NEAT, SIMPLIFIED WIRING
- RESPONSE BETTER THAN 35-30,000 CPS ± ½ DB AT 18 WATTS
- LESS THAN 1% HARMONIC OR INTERMODULATION DISTORTION

A superbly-performing basic stereo amplifier, in easy-to-build kit form to save you **lots of money** and let you **get into stereo now** at minimum expense! Dual inputs are provided, each with individual volume control, and the unit may be used with a stereo preamplifier, for 2-18 watt stereo channels or, at the flick of a switch, as a fine 36-watt monaural amplifier — or, if desired, it may be used as 2 separate monaural 18-watt amplifiers! **CONTROLS** include 2 input volume controls, channel Reverse switch (AB-BA), Monaural-Stereo switch. **DUAL OUTPUT IMPEDANCES** are: 4, 8, 16 and 32 ohms (permitting parallel (monaural) operation of 2 speaker systems of up to 16 ohms. **INPUT SENSITIVITY** is 0.45 volts per channel for full output. **TUBES** are 2-6AN8, 4-7189; GZ-34 rectifier. **SIZE** 9-3/16"d (10-9/16" with controls) x 5¼"h x 13¼"w. Supplied complete with perforated metal cage, all necessary parts and detailed instructions. Shpg. wt., 22 lbs.

KT-310 Stereo Power Amplifier Kit .....Net **47.50**

LAFAYETTE RADIO DEPT JK

165-08 Liberty Ave. JAMAICA 33; N. Y. Write for FREE Bargain Packed Catalog! PLEASE INCLUDE POSTAGE WITH ORDER

100 SIXTH AVE., NEW YORK, N. Y.
BOSTON, MASS., 110 Federal St.
PLAINFIELD, N. J., 139 West 2nd St.
NEWARK, N. J., 24 Central Ave.
BRONX, N. Y., 542 E. Fordham Rd.

NEW! LAFAYETTE "STEREO" HI-FI PHONO MUSIC SYSTEM

AN IDEAL QUALITY SYSTEM FOR LISTENING TO THE NEW HIGH-REALISM STEREO SOUND!

For Stereo & Monaural Reproduction

LA-90

RC121/11

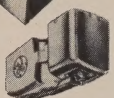

NEW GE GC-7 STEREO COMPATIBLE CARTRIDGE WITH DIAMOND STYLUS

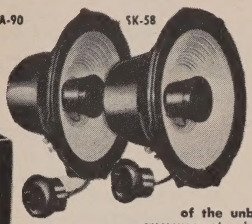

SK-58

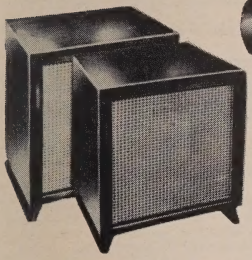

CAB-16

COMPONENTS	
Lafayette LA-90 28-Watt Stereo Amplifier	72.50
Garrard RC121/II Changer	41.65
Lafayette PK-111 Wood Base	3.95
GE GC-7 Stereo Magnetic Cartridge	23.47
2-Lafayette SK-58 Coaxial 12" Speakers	59.00
Total Reg. Price	~~200.57~~

YOU PAY ONLY 167.50 SAVE 33.07!

A complete superb stereo hi-fi phono music system brought to you by Lafayette to bring out the thrilling capabilities of the new stereo recordings. Heart of the system is **the new Lafayette LA-90 with 28 watts per channel** and with all the inputs necessary for a complete stereo control center. Other fine components are the **famous new Garrard RC121/11 4-speed automatic record changer** ready to accept stereo cartridges, the **Lafayette PK-111 wood base** for changer, of fine selected woods; the **new GE GC-7 stereo/monaural variable reluctance cartridge** with 0.7 mil genuine GE diamond stylus; and **2 of the unbeatable, for performance-value, Lafayette SK-58 12" coaxial speakers** with built-in crossover network and brilliance level control. Supplied complete with cables, connectors, and easy-to-install instructions. Shpg. wt., 66 lbs.

HF-374 Stereo Phono System, with mahogany or blonde wood changer base (please specify) ..... Net **167.50**

HF-375 Same as HF-374 but with 2-Lafayette CAB-16 mahogany or walnut or CAB-17 blonde Resonator-type speaker enclosures (specify which) ..... Net **222.50**

ONLY 16.75 DOWN—12.00 MONTHLY

LAFAYETTE STEREO FM/AM-PHONO MUSIC SYSTEM

Same as HF-374 above but with new Lafayette stereo Model LT-99 FM/AM Tuner.

HF-376 Stereo FM/AM-Phono System ..... Net **237.00**

HF-377 Same as HF-376 but with 2-Lafayette CAB-16 mahogany or walnut or CAB-17 blonde speaker enclosures Net **292.00**

LAFAYETTE MASTER AUDIO CONTROL CENTER with BINAURAL CHANNEL AND DUAL VOLUME CONTROL.

• **Self-Powered** • **DC On All Filaments** • **24 Positions of Equalization** • **Tape Head Input, High Impedance** • **Dual Cathode Follower Output Stages**

This is not only the finest hi-fi preamp characterized by unmatched features, but it has been functionally designed to keep pace with the conversion of your present hi-fi system to binaural (Stereophonic) sound. Incorporates an extra channel and dual volume control for binaural reproduction. Features include DC on all tube filaments, negative feedback in every stage, dual cathode follower output stages and latest printed circuit construction. Less than 0.09% IM distortion and less than 0.07 harmonic distortion at 1V. Hum and noise level better than 80 db below 3V. Uniformly flat frequency response over entire audible spectrum. 7 inputs for every type of phono, tuner or tape. Tasteful styling, brilliantly executed. Size 12¾"x 9⅛ x 3¾". Shpg. wt., 10½ lbs.

KT-300—Lafayette Master Audio Control Kit Complete with cage and detailed assembly instructions. ..... Net **39.50**

LT-30—Same as above completely wired and tested with cage and instruction manual. Net **59.50**

DELUXE 70 WATT BASIC AMPLIFIER

• **Conservatively Rated At 70 Watts** • **Inverse Feedback** • **Variable Damping** • **Metered Balance And Bias Adjust Controls** • **Available In Kit and Wired Form**

Here's ultra-stability in a 70 watt basic power amplifier employing highest quality components conservatively rated to insure performance and long life. Features matched pair KT 88's and wire range linear Chicago output transformer, variable damping control, meter for bias and balance and gold finish chassis. Frequency response 10-100,000 cps ± 1db. Hum and noise 90 db below full output. IM distortion less than 1⅓% at 70 watts, less than 0.3% below 30 watts. Harmonic distortion less than 2% at 70 watts from 20 to 20,000 cps ± 1 db. Output impedance 4, 8 and 16 ohms. Handsome decorative cage perforated for proper ventilation. Size 14⅓ x 10 x 7⅜" including cage and knobs. Shpg. wt., 40 lbs.

KT-400—Lafayette 70 watt Deluxe Basic Amplifier Kit complete with cage and detailed assembly instructions. ..... Net **69.50**

LA-70—Same as above completely wired and tested with cage and instruction manual. Net **94.50**

NEW! LAFAYETTE STEREO AMPLIFIER KIT

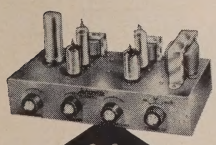

Only 18.95

• **4 WATTS STEREO OUTPUT**

• **COMPLETE STEREO CONTROLS**

Brand new stereo amplifier kit for that extra small stereo hi-fi set, featuring separate volume controls; ganged tone control; stereo, reverse and monaural switch. 40 millivolt sensitivity! Complete kit with tubes, rectifier, all parts and instructions. Only 9½" x 5" x 4½". For 110-120 60 cycle AC. Shpg. wt., 7 lbs.

KT-126 — Complete Kit ..... Net **18.95**

COMBINATION MONEY SAVER

The KT-126 Stereo Amplifier kit and the new **Ronette OV Stereo Turnover Cartridge** with dual sapphire styli.

KT-136 ..... **24.90**

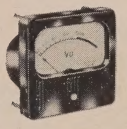

ILLUMINATED SCALE VU METER

• **3⅛" SQUARE**

• **JEWELLED BEARINGS**

• **25-16,000 ±½ db**

• **D'ARSONVAL MOVEMENT**

Standard 7500 ohm (with 3600 ohm external resistor supplied) "B" scale volume indicator calibrated in 0-100% and —20 to +3 VU. Accurate to ±0.2 VU from 35 to 10,000 cps, ±0.5 VU from 25 to 16,000 cps (0 VU corresponds to 100%). Soft, non-glare illumination supplied by two built-in 6-8 volt bulbs. Dynamic and damping characteristics conform to standard VU meter practice—99% of final reading reached in 0.3 second with suddenly applied sine wave, overshoot of 1 to 1½%. 3⅛" square, 1-11/16" depth, 2-9/16" dia. mtg. hole. Shpg. wt., 1 lb.

TM-80 Volume Unit Meter ..... Net **7.50**

Lafayette Radio

Dept. JK

165-08 LIBERTY AVE.
JAMAICA 33, N. Y.

NEW YORK, N. Y.	BOSTON, MASS.	BRONX, N. Y.	NEWARK, N. J.	PLAINFIELD, N. J.
100 6th Ave.	110 Federal St.	542 E. Fordham Rd.	24 Central Ave.	139 W. 2nd St.
WOrth 6-5300	HUbbard 2-7850	FOrdham 7-8813	MArket 2-1661	PLainfield 6-4718

PLEASE INCLUDE POSTAGE WITH ORDER

LAFAYETTE'S 1959 CATALOG

"Everything in Electronics"

260 GIANT-SIZED PAGES

Our 38th Year

The Complete Catalog Featuring "The Best Buys In The Business"

FOR THE NEWEST AND FINEST IN STEREOPHONIC HI-FI EQUIPMENT AND SYSTEMS

- TAPE RECORDERS
- PUBLIC ADDRESS SYSTEMS
- AMATEUR EQUIPMENT
- INDUSTRIAL SUPPLIES
- MINIATURE COMPONENTS
- RADIO & TV TUBES AND PARTS
- EXCLUSIVE LAFAYETTE TRANSISTOR & HI-FI KITS

Send for Lafayette's 1959 Catalog – the most complete, up-to-the-minute electronic supply catalog crammed full of everything in electronics at our customary down-to-earth money-saving prices.

CONTAINS HUNDREDS OF EXCLUSIVE LAFAYETTE ITEMS NOT AVAILABLE IN ANY OTHER CATALOG OR FROM ANY OTHER SOURCE – SEND FOR YOUR COPY NOW!

A "must" for the economy-minded hi-fi enthusiast, experimenter, hobbyist, engineer, technician, student, serviceman and dealer.

EASY PAY TERMS Available on orders over $45— Only 10% down—Up to 18 months to pay

Leaders in Hi-Fi

The most complete selection and largest stocks of hi-fi components and systems—available for immediate delivery at the lowest possible prices. Save even more on Lafayette endorsed "best-buy" complete systems.

NEW!

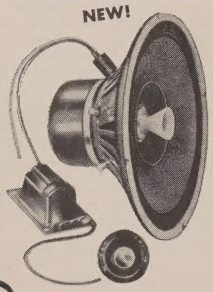

LAFAYETTE-GOODMANS 12" 3-WAY SPEAKER

- 30 WATTS
- FREQUENCY RESPONSE 30-20,000 CPS
- PLUG-IN 12 DB/OCTAVE CROSSOVER NETWORK WITH LEVEL CONTROL

Custom-built by Goodmans of England with 1¾ lb. Alcomax 3 Magnet. Features axially mounted, free-edged wide range woofer, stiff-coned mid-range radiator and compression-driver tweeter.

SK-110 ..... Net **47.50**

Two for Stereo ....Net **89.00**

NEW!

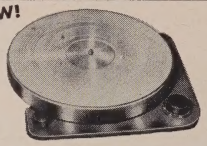

Lafayette TRANSCRIPTION PLAYER WITH 3 LB. 12" ALUMINUM TURNTABLE

Professional 4-speed player ideally suited for stereo. Has magnetic eddy-current brake permitting ± 10% speed variation. Amazingly low priced! Shpg. wt., 14 lbs.

PK-240 .....Net **37.50**

NEW!

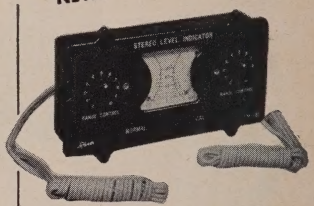

STEREO BALANCE VU METER

Dual audio output level indicator with two meters, for comparing audio levels. Ideal for balancing hi-fi stereo systems.

TM-40 ..... Net **8.95**

NATIONALLY ADVERTISED 4-SPEED AUTOMATIC RECORD CHANGER

NEW GE GC-7 STEREO CARTRIDGE WITH DIAMOND STYLUS

Famous brand latest model with **new GE GC-7 Magnetic Compatible Stereo Cartridge with diamond stylus.** Guaranteed to please or money refunded! Regular 69.50 Value! Shpg. wt., 21 lbs.

PK-251—(less Wood base) Net **39.50**

NEW MINIATURE HIGH SENSITIVITY MULTITESTER

20,000 OHMS PER VOLT DC— 10,000 OHMS PER VOLT AC

20,000 ohms per volt DC and 10,000 ohms per volt AC instrument. Hand-held, weighs only 10 oz! Clear plastic face cover. Has 23 most used ranges selected by single switch. With batteries and leads. Shpg. wt., 1 lb.

AR-660 .....Net **22.50**

FREE

CUT OUT AND PASTE ON POST CARD

LAFAYETTE RADIO, Dept. JK
P.O. Box 511, Jamaica 31, N.Y.

SEND FOR THE WORLD'S LEADING ELECTRONICS, RADIO, T.V., INDUSTRIAL, AND HI-FI GUIDE

☐ Send FREE LAFAYETTE Catalog 590

Name .....

Address .....

City..... *Zone*.... *State*.....

JAMAICA, N.Y. 165-08 Liberty Ave. AXtel 1-7000	NEW YORK, N.Y. 100 6th Ave. WOrth 6-5300	BOSTON, MASS. 110 Federal St. HUbbard 2-7850
BRONX, N.Y. 542 E. Fordham Rd. FOrdham 7-8813	NEWARK, N.J. 24 Central Ave. MArket 2-1661	PLAINFIELD, N.J. 139 W. 2nd St. PLainfield 6-4718

step UP your speaker system with ELECTRO-VOICE BUILDING-BLOCK KITS

Picture your speaker system with E-V Building-Block Kits.* You can start with a single, full-range Electro-Voice Loudspeaker and expand it step-by-step to a multi-way system as your budget permits.

Electro-Voice enclosures are ready for future addition of high-frequency and mid-range speakers. Your E-V enclosure can never be obsolete because there's *always* room to expand your system.

*E-V Building-Block Kits may also be used with some non-E-V quality systems. Ask your high fidelity specialist or write Electro-Voice for details.

Two ways to a Separate Three-Way System

1. Start with an Electro-Voice full-range coaxial speaker. Then, when your budget permits, add-on the correct E-V high-frequency Building-Block Kit to give you a *separate* two-way system; later add-on the E-V mid-range Building Block Kit for a superlative *separate* three-way system.

2. Or, begin your system with an E-V integrated 3-way speaker; merely add-on the E-V mid-range Building-Block Kit to achieve a *separate* three-way system.

Of course, you can purchase a *complete* three-way system composed of low-frequency driver, high-frequency driver BB Kit, and mid-range driver BB Kit.

first, choose an acoustically-perfect Electro-Voice factory-assembled enclosure or a do-it-yourself enclosure kit

E-V Coronet net $35.50

E-V Baronet net $45
E-V Baronet KD7 Kit net $26

E-V Aristocrat net $72
E-V Aristocrat KD6 Kit net $39

or its along-the-wall counterpart the new **E-V Marquis** net $63

E-V Regency net $130
E-V Regency KD4 Kit net $73

E-V Empire net $99
E-V Empire KD5 Kit net $51

second, choose an Electro-Voice full-range coaxial two-way speaker

SP8B net $29.50

SP12B net $35

SP12 net $66

SP15B net $43

SP15 net $89

STEP ONE add-on an Electro-Voice high-frequency Building-Block Kit for a separate two-way system

BB1 BUILDING-BLOCK KIT
includes
T35B Super-Sonax VHF Driver, X36 Crossover, AT37 Level Control, Wiring Harness. net $37

BB2 BUILDING-BLOCK KIT
includes
T35 Super-Sonax VHF Driver, X36 Crossover, AT37 Level Control, Wiring Harness. net $50

BB1 BUILDING-BLOCK KIT net $37

BB2 BUILDING-BLOCK KIT net $50

or start with an Electro-Voice integrated three-way speaker
(equivalent to coaxial plus high-frequency driver)

12TRXB net $66

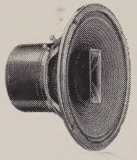

12TRX net $125

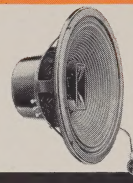

15TRXB net $79

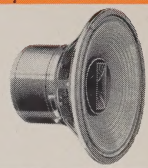

15TRX net $149

STEP TWO add-on an Electro-Voice mid-range Building-Block Kit for a separate three-way system, the ultimate in high fidelity reproduction

STEREO'S STANDARD

BB3 BUILDING-BLOCK KIT
includes
T10A Driver, 8HD Horn, X825 Crossover, AT37 Level Control, Wiring Harness. . . . . net $86

BB4 BUILDING-BLOCK KIT
includes
T25A Driver, 8HD Horn, X8 Crossover, AT37 Level Control, Wiring Harness. . . . . net $114

BB3 BUILDING-BLOCK KIT
includes
T10A Driver, 8HD Horn, X825 Crossover, AT37 Level Control, Wiring Harness. . . . . net $86

BB4 BUILDING-BLOCK KIT
includes
T25A Driver, 8HD Horn, X8 Crossover, AT37 Level Control, Wiring Harness. . . . . net $114

Electro-Voice®

FOREMOST IN ELECTRO-ACOUSTICS—Microphones, Phono-Cartridges, High Fidelity Loudspeakers and Enclosures, Public Address Speakers, Marine Instruments, EVI Professional Electronic Instruments and Military Material.
ELECTRO-VOICE, INC., Buchanan, Michigan

Electro-Voice has the industry's most complete and versatile line of speakers, enclosures, and kits.
Ask your high fidelity dealer or write E-V for complete information on how to step-up your system.

Speed up and Simplify

your color-TV servicing with RCA's new

PICT-O-GUIDE

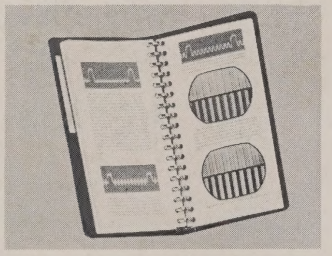

AVAILABLE THROUGH YOUR RCA TUBE DISTRIBUTOR

Or, fill out the coupon below and forward with $4.50 in check or money order payable to Radio Corporation of America for each Color TV PICT-O-GUIDE ordered.

RCA Commercial Engineering
415 South 5th St., Harrison, N. J.
Gentlemen:
Enclosed please find check ☐ or money order ☐ for ..... Color-TV PICT-O-GUIDES. Send to:

Name .....

Address .....

City ..... Zone ..... State .....

It's chock-full-of practical information and illustrations—just what you need for profitable color-TV servicing.

If you are planning to build your share in the business of color-TV servicing, you are sure to find RCA's Color-TV Pict-O-Guide the most useful "bench" friend you have ever had. Whether you are "learning" or are already "doing", the clearly written descriptions, step-by-step instructions, diagrams, and full-color photographs of trouble symptoms make this valuable book a "must"! It was prepared and written by John R. Meagher, RCA's well known authority on TV servicing techniques. Get your copy today!

New Color-TV Pict-O-Guide contains sections on:

Color Mixing · RCA Compatible Color TV System · Purity · Troubleshooting Convergence · Gray-Scale Tracking · Color Operating Controls · Antenna Considerations · RF-IF-Bandpass Alignment · Color-Bar Patterns · Color Test Equipment · Signal Tracing · Interference · "Green Stripe" Test Signals

RADIO CORPORATION OF AMERICA
Electron Tube Division — *Harrison, N. J.*